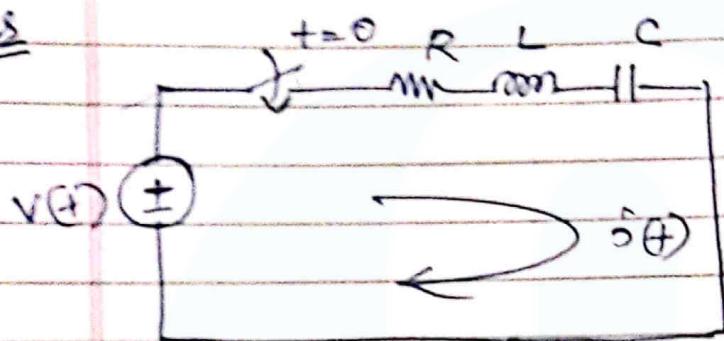


Module 3Transformed circuits in S-domain

- ① A time dependent voltage $v(t)$ is applied to a series RLC circuit. Find S-domain impedance & current. Draw the + domain & S-domain circuits.


AnsApplying KVL at $t=0$

$$v(t) = R i(t) + L \frac{di}{dt} + \frac{1}{C} \int i(t) dt + V_0$$


Taking LT,

$$\begin{aligned} v(s) &= RI(s) + sL I(s) - L i(0^+) \\ &\quad + \frac{1}{C} \frac{1}{s} I(s) + \frac{V(0)}{s} \\ &= I(s) \left[R + sL + \frac{1}{sC} \right] - L i(0^+) + \frac{V(0)}{s} \\ \therefore I(s) &= \frac{v(s) + L i(0^+) - \frac{V(0)}{s}}{R + sL + \frac{1}{sC}} \end{aligned}$$

$$\text{Impedance } Z(s) = \frac{(R + sL + \frac{1}{sC})}{(R + sL + \frac{1}{sC})}$$

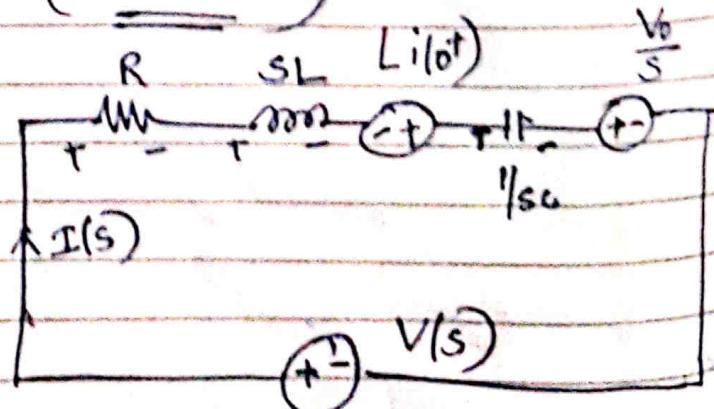S-domain ckt

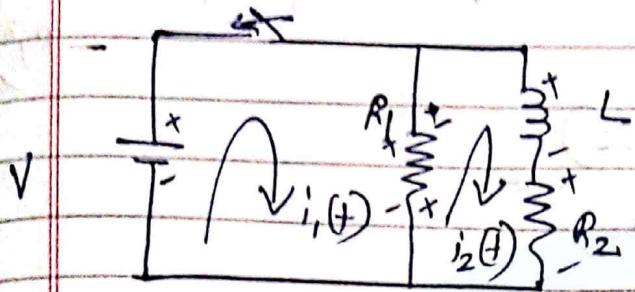- ② A two-mesh network is given. Obtain expression for $\mathbb{I}_1(s) \neq \mathbb{I}_2(s)$, when the switch is closed.



Applying KVL,

$$V - R_1 (i_1(t)) - R_2 (i_2(t)) = 0$$

$$- R_1 (i_2(t)) - L \frac{di_2(t)}{dt} - R_2 i_2(t) = 0$$

Taking LT,

$$\frac{V}{s} = R_1 \mathbb{I}_1(s) + R_2 \mathbb{I}_2(s) \quad \text{--- (1)}$$

$$- R_1 \mathbb{I}_2(s) + R_2 \mathbb{I}_1(s) - (Ls \mathbb{I}_2(s) - L i_2(0^+)) \\ \overline{\rightarrow} R_2 \mathbb{I}_2(s) = 0$$

$$- R_1 \mathbb{I}_1(s) + \mathbb{I}_2(s) \left[\frac{R_1 + sL}{R_2} \right] = + L i_2(0^+) \quad \text{--- (2)}$$

Write these two equations in matrix form,

$$\begin{bmatrix} \frac{V}{s} \\ -L i_2(0^+) \end{bmatrix} = \begin{bmatrix} R_1 & -R_1 \\ R_2 & \frac{R_1 + R_2 + sL}{R_2} \end{bmatrix} \begin{bmatrix} \mathbb{I}_1(s) \\ \mathbb{I}_2(s) \end{bmatrix} \quad i_2(0^+) = 0$$

$$\mathbb{I}_1(s) = \frac{V/s - R_1 \mathbb{I}_2(s)}{R_2 + (R_1 + R_2 + sL)}$$

$$\mathbb{I}_2(s) = \frac{R_1 \mathbb{I}_1(s) - R_1 V/s}{R_2 + (R_1 + R_2 + sL)}$$

$$= + \frac{V}{s} (R_1 + R_2 + SL) = + V (R_1 + R_2 + SL)$$

$$+ R_1 (R_1 + R_2 + SL) - R_1^2 = s (R_1^2 + R_1 R_2 + R_1 SL - R_1^2)$$

$$= + \frac{V (R_1 + R_2 + SL)}{s (R_1 R_2 + R_1 SL)}$$

$$I_2(s) =$$


$$\begin{vmatrix} R_1 & V/s \\ -R_1 & 0 \end{vmatrix}$$


$$\begin{vmatrix} R_1 & -R_1 \\ -R_1 & R_1 + R_2 + SL \end{vmatrix}$$

$$= \frac{R_1 \times 0 - -R_1 V/s}{R_1 (R_1 + R_2 + SL) - R_1^2} = \frac{R_1 V/s}{R_1^2 + R_1 R_2 + R_1 SL - R_1^2}$$

$$= \frac{R_1 V}{s (R_1 R_2 + R_1 SL)} \rightarrow \frac{V}{s (R_2 + SL)}$$

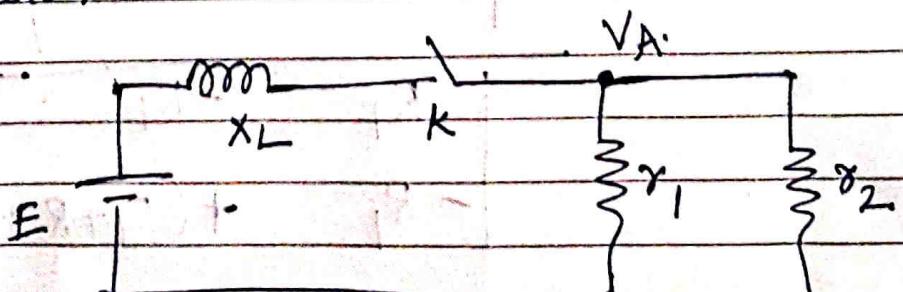3. Apply nodal analysis to find the voltage at node A in the ckt. in S-domain.
 Assume initial current through the inductor as zero.



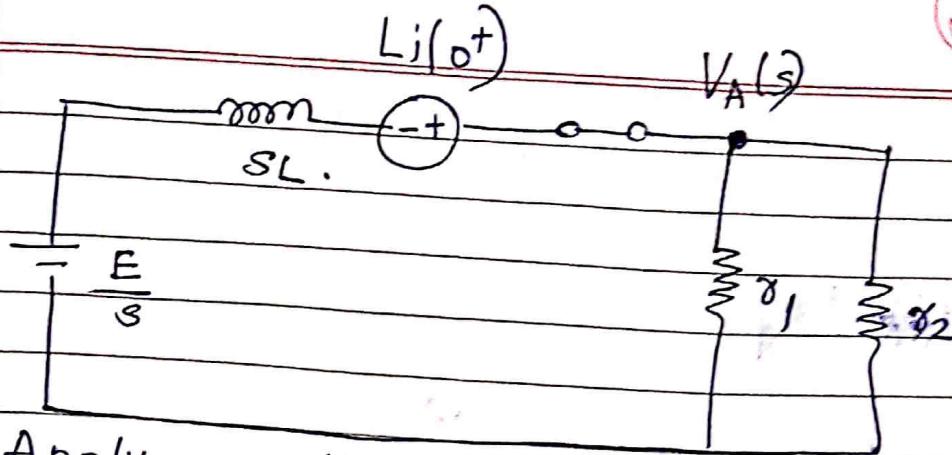

Applying KCL at node A,

$$\frac{V_A(s)}{r_1} + \frac{V_A(s)}{r_2} + V_A(s) - L_i(0+) - \frac{E}{s} = 0.$$

$$V_A(s) \left[\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{sL} \right] - L_i(0+) - \frac{E}{s} = 0.$$

$$V_A(s) = \frac{E}{s}$$

$$sL \left[\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{sL} \right].$$

$$= \frac{E/s}{sL \left[\frac{r_2 sL + r_1 sL + r_1 r_2}{r_1 r_2 sL} \right]} = \frac{E}{s(r_1 sL + r_2 sL + r_1 r_2)}$$

$$M = k\sqrt{L_1 L_2}, \quad k = \frac{M}{\sqrt{L_1 L_2}}$$

Dot Convention


* Self induced Voltages are assigned with +ve sign. Mutually induced voltages may be either +ve/-ve depending upon the direction of the winding of the coil. and can be decided by the presence of dots placed at one end of each of the two coils.

* To determine the relative polarity of the induced voltage in the coupled coil, the coils are marked with dots. This is known as Dot Convention or Dot Rule.



If the currents in two mutually coupled coils enter the dotted ends or leaves the dotted ends, M terms will have the same sign as L terms.

M +ve

M +ve.

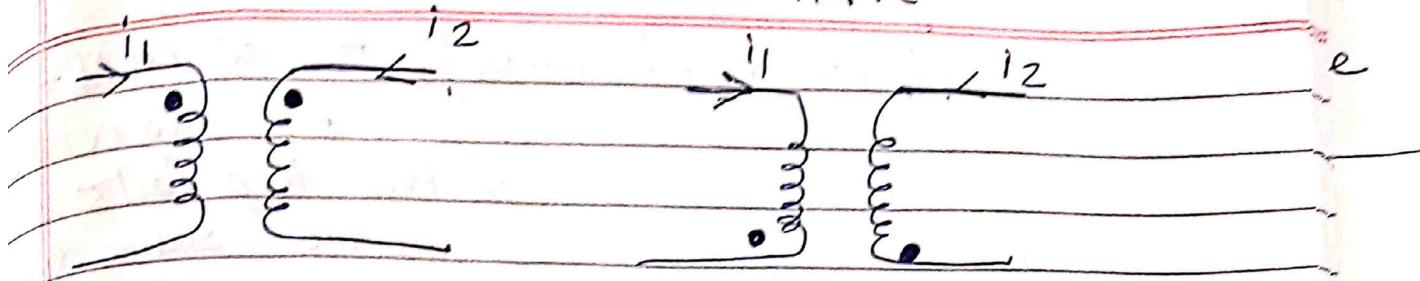

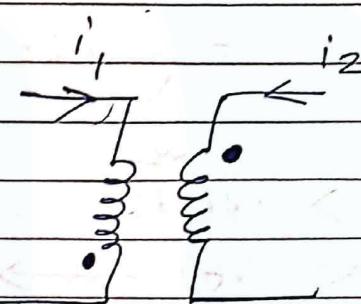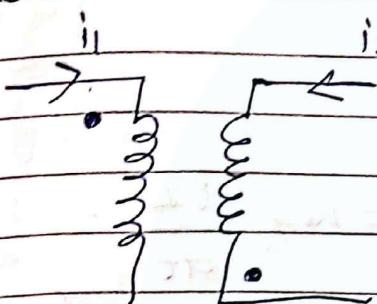
If the current in one coil enters the dotted ends and in the other current leaves the dotted ends, M will have the opposite sign as L terms.



M -ve

M -ve

Coupled circuits in Series.

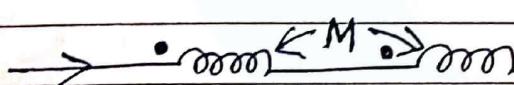

I \rightarrow L_1 and L_2

$\leftarrow V(t) \rightarrow$

$$V(t) = L_1 \frac{dI}{dt} + M \frac{dI}{dt} + L_2 \frac{dI}{dt} + M \frac{dI}{dt}$$

$$= (L_1 + L_2 + 2M) \frac{dI}{dt}$$

I_{heq}


\rightarrow mm

$\leftarrow V(t) \rightarrow$


$$V(t) = \text{heq} \frac{dI}{dt}$$

$$L_{eq} = L_1 + L_2 + 2M$$

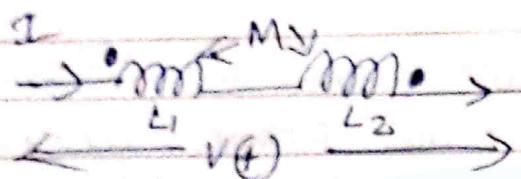- when M +ve
or currents
in the two coils are
in the same direction
or aiding.


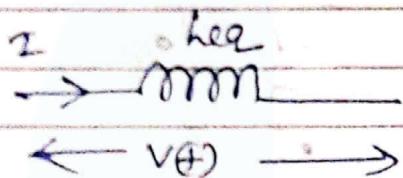
$$\begin{aligned} V(t) &= L_1 \frac{dI}{dt} - M \frac{dI}{dt} + L_2 \frac{dI}{dt} - M \frac{dI}{dt} \\ &= (L_1 + L_2 - 2M) \frac{dI}{dt} \end{aligned}$$



$$V(t) = L_{eq} \frac{dI}{dt}$$


$$\therefore L_{eq} = L_1 + L_2 - 2M$$

when M is -ve.
or the currents

are opposing.

Parallel

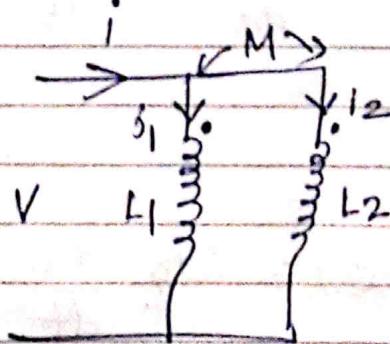Consider two inductors with self inductances L_1 & L_2 connected parallel which are mutually coupled with mutual inductance M .



~~in parallel~~

$$\frac{di}{dt} = \frac{V}{L_1} + \frac{V}{L_2} - M \frac{di_2}{dt}$$

$$V = j\omega L_1 \frac{di_1}{dt} + j\omega M \frac{di_2}{dt}$$

$$\cancel{V = j\omega L_1 I_1 + M I_2}$$

$$\cancel{I_1 = \frac{V - j\omega M I_2}{j\omega L_1}}$$

$$\cancel{I_2 = \frac{V - j\omega L_1 I_1}{j\omega M}}$$

$$V = j\omega L_1 I_1 + j\omega M I_2 \quad (1)$$

Similarly,

$$V = j\omega L_2 I_2 + j\omega M I_1 \quad (2)$$

$$V = j\omega L_2 I_2 + j\omega M I_1 \quad (3)$$

Writing eqns (1) & (3) in matrix form,

$$\begin{bmatrix} V \\ V \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$I_1 = \begin{vmatrix} V & j\omega M \\ V & j\omega L_2 \end{vmatrix} / \begin{vmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{vmatrix}$$

$$= \frac{V j\omega L_2 - V j\omega M}{(j\omega L_1)(j\omega L_2) - (j\omega M)^2}$$

$$= \frac{j\omega V(L_2 - M)}{-\omega^2 L_1 L_2 + \omega^2 M^2} = \frac{j\omega V(L_2 - M)}{\omega^2(M^2 - L_1 L_2)}$$

Similarly, $I_2 = \frac{j\omega V(L_1 - M)}{\omega^2(M^2 - L_1 L_2)}$

$$I = I_1 + I_2$$

$$\frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$I = I_1 + I_2$$

$$= j\omega (L_2 - M) V + \frac{j\omega (L_1 - M) V}{\omega^2 (M^2 - L_1 L_2)}$$

$$\frac{j\omega V (L_2 - M + L_1 - M)}{\omega^2 (M^2 - L_1 L_2)} = \frac{j\omega V (L_1 + L_2 - 2M)}{\omega^2 (M^2 - L_1 L_2)}$$

$$Z = \frac{V}{I} = \frac{j\omega V (L_1 + L_2 - 2M)}{\omega^2 (M^2 - L_1 L_2)}$$

~~$$= j\omega (L_1 + L_2 - 2M)$$~~
$$= j\omega \left(\frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \right)$$


$$Z_{eq} = \frac{L_1 * L_2 - M^2}{L_1 + L_2 - 2M}$$

- parallel aiding

$$Z_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

parallel opposing

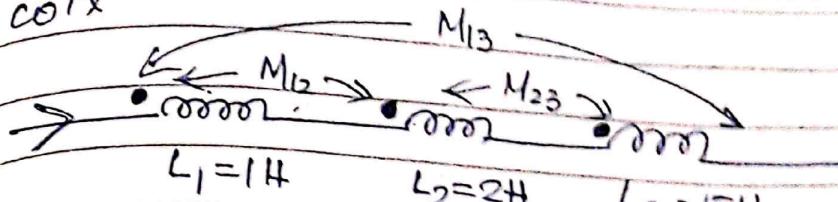1. Find out the equivalent inductance of the coil.



$$L_1 = 1H$$

$$L_2 = 2H$$

$$L_3 = 5H$$

$$M_{12} = 0.5H$$

$$M_{23} = 1H$$


$$M_{13} = 1H$$

$$L' = L_1 + L_2 \pm 2M$$

$$= 1 + 2 + 2 \times 0.5 = 4H$$


$$L'' = 4 + 5 + 2(M_{13} + M_{23}) = 4 + 5 + 2 \times (1+1) \\ = \underline{\underline{13H}}$$

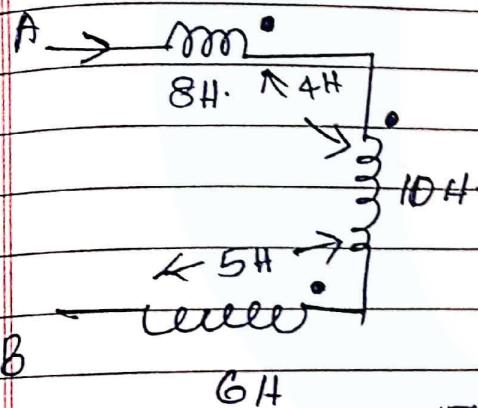2. Calculate the effective inductance of the ckt across AB.



$$L' = 8 + 10 - 4 \times 2 \\ = 18 - 8 = \underline{\underline{10H}}$$
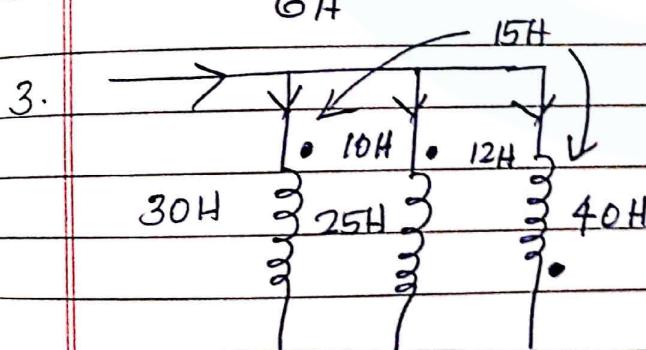
$$L'' = 10 + 2 \times 5 + 6 \\ = 16 + 10 = \underline{\underline{26H}}$$



$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$L_1 = 30 + 10 - 15 = 25H \\ L_2 = 25 + 40 - 12 \\ = \underline{\underline{23H}}$$


$$L_3 = 40 - 15 - 12 = \underline{\underline{13H}}$$

$$L_T = \frac{1}{25} + \frac{1}{23} + \frac{1}{13} = \underline{\underline{6.24H}}$$

Analysis of Coupled CTs

Using Dot Rule


classmate

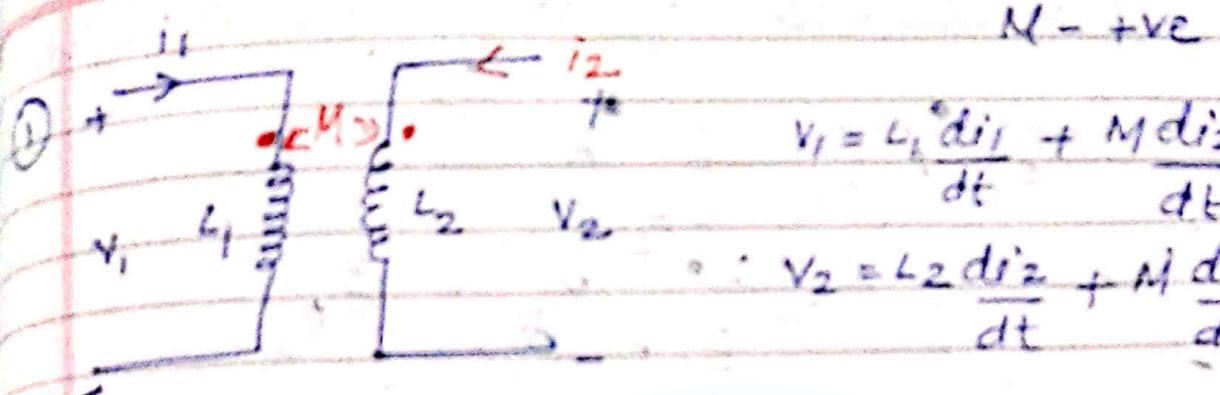Date _____
Page _____ $N = +ve$

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$


$$\therefore v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

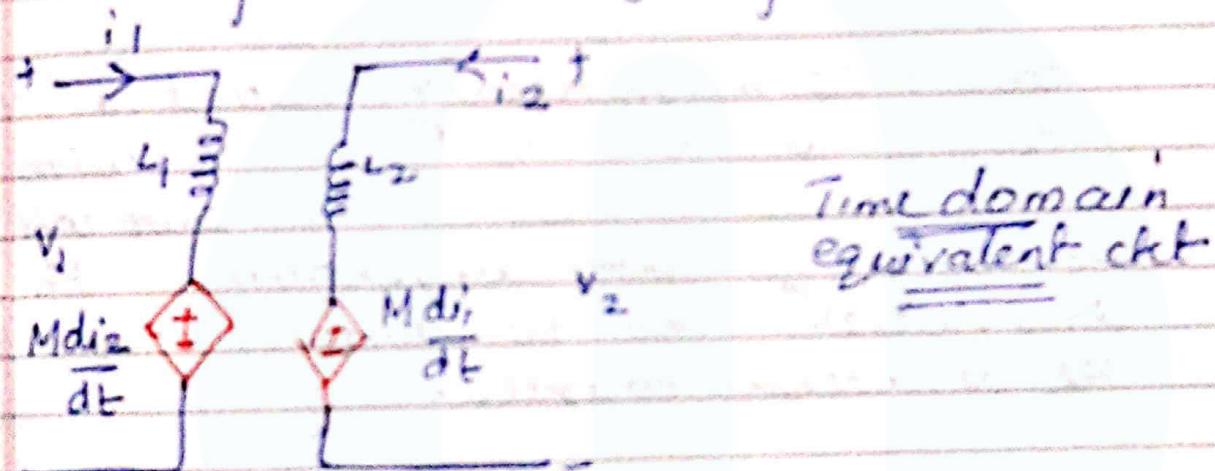We can represent using dependent sources.




Time domain equivalent ckt

Equivalent ckt

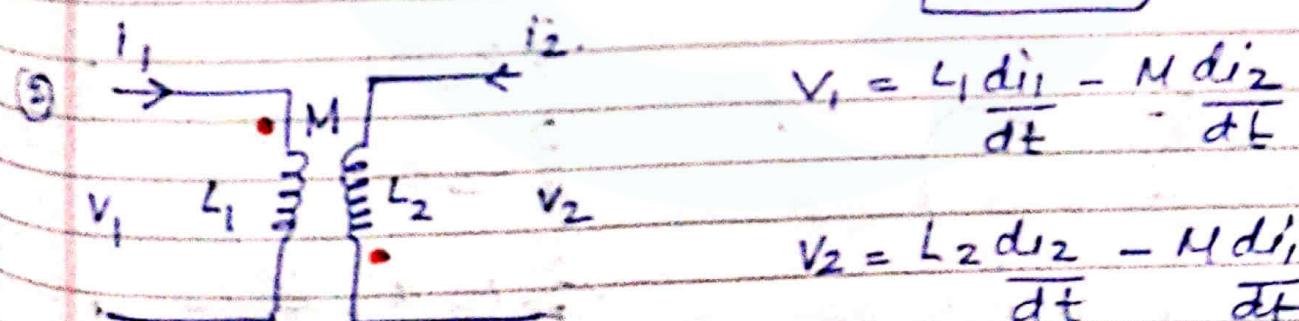
 $M - ve$

$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$
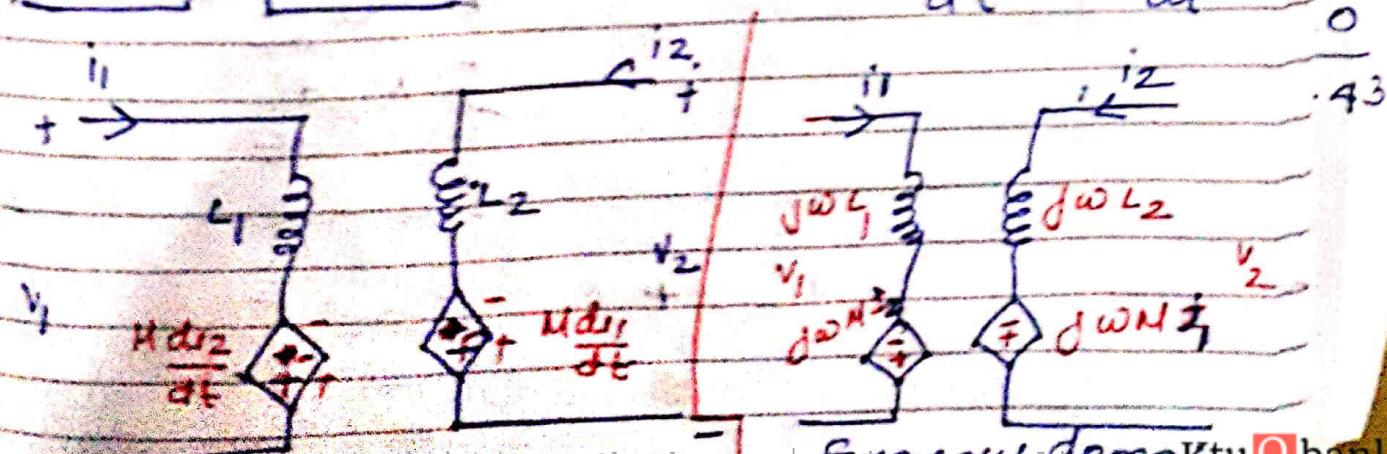
$$v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$




1. Write the mesh equations for the net.

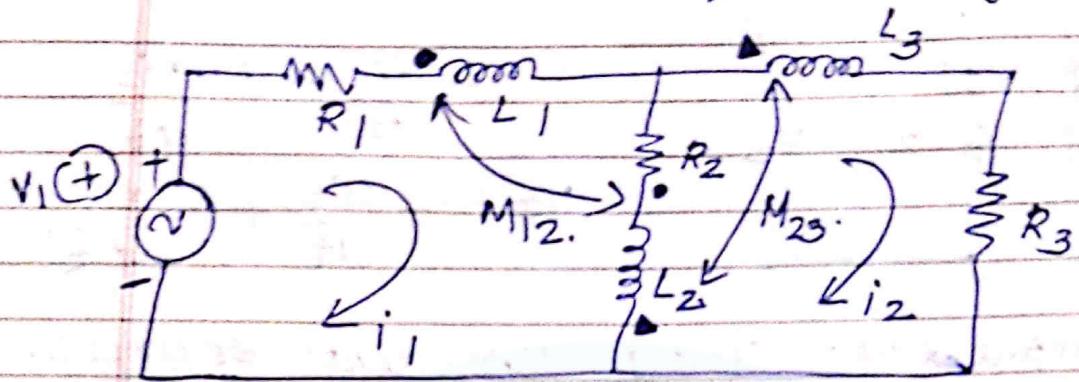

coil 1 is magnetically coupled to coil 2.
coil 2 is " "
with coil 1
and coil 3.

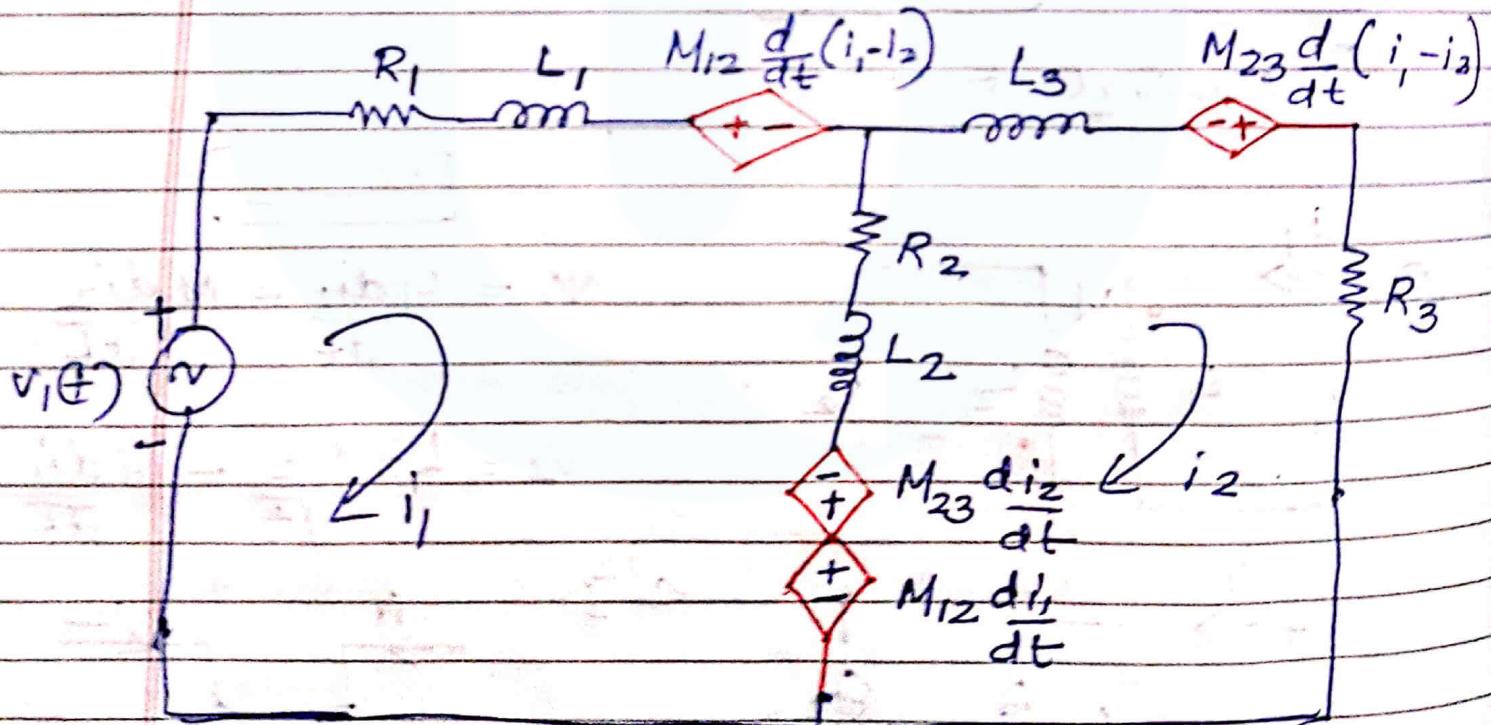By applying dot convention, the equivalent ckt is drawn with the dependent sources.



$$M_{12} = +ve, \quad M_{23} = -ve$$

5.

In coil L₁ - mutually induced emf due to $(i_1 - i_2)$ in coil 2

The polarity of mutually induced emf is the same as that of self produced emf because $i_1 \neq (i_1 - i_2)$ enter in respective coils from the dotted ends.

In coil L₂ - 2 mutually induced emfs. one due to current i_1 in coil 1 & i_2 in coil 3.

The Polarity of mutually induced emf is the same as that of self induced emf.

The polarity of mutually induced emf is due to the current i_2 is opposite to that of self induced emf because current $(i_1 - i_2)$ leaves from the dotted end in coil 2 and the current i_2 enters from the dotted end in coil 3.

In coil L₃ - the polarity of the mutually induced emf is opposite to that of self induced emf because the current $(i_1 - i_2)$ leaves from the dotted end in coil 2 and the current i_2 enters from the dotted end in coil 3.

Applying KVL,


$$V_1(t) = R_1 i_1 - L_1 \frac{di_1}{dt} - M_{12} \frac{d}{dt} (i_1 - i_2)$$

$$- R_2 (i_1 - i_2) - L_2 \frac{d}{dt} (i_1 - i_2) + M_{23} \frac{d}{dt} i_2 - M \frac{di_1}{dt}$$

$$\Rightarrow M_{12} \frac{di_1}{dt} - M_{23} \frac{di_2}{dt} - L_2 \frac{d}{dt} (i_2 - i_1) - R(i_2 - i_1)$$

$$- L_3 \frac{di_2}{dt} + M_{23} \frac{d}{dt} (i_1 - i_2) - R_3 i_2 = 0.$$

2) Write mesh equations for the net.

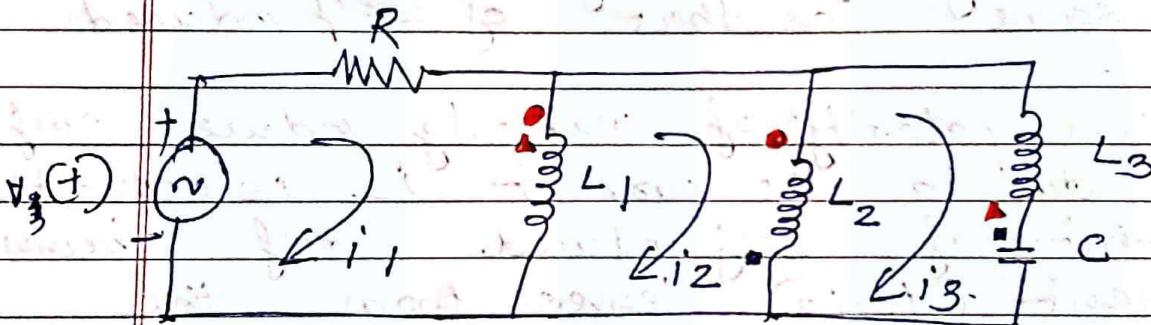


$$B/n \cdot L_1 \# L_2 = +M_{12}$$

$$B/n \cdot L_1 \# L_3 = -M_{13}$$

$$B/n \cdot L_2 \# L_3 = +M_{23}$$

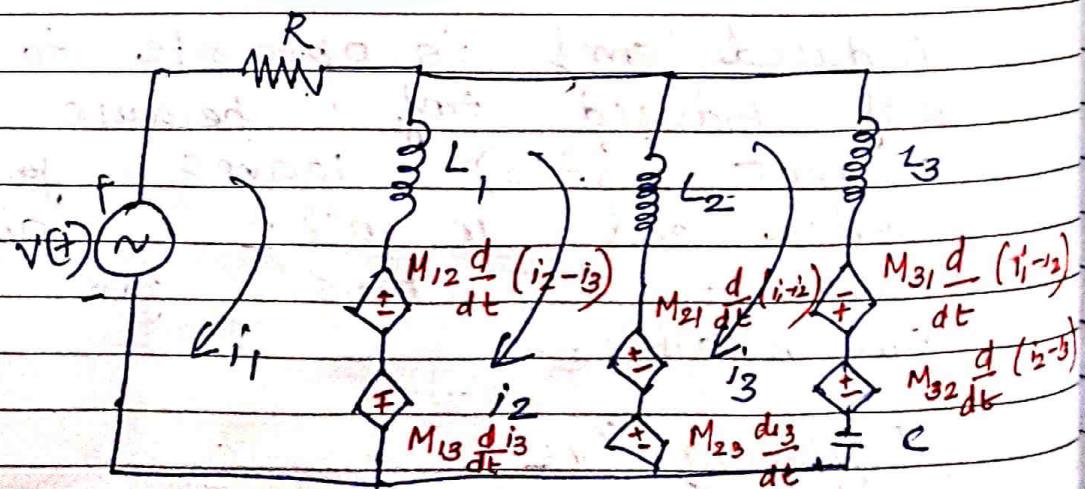The eqt chkt
in terms of
dependent
sources.



$$V(+)-Ri_1-L_1 \frac{d}{dt}(i_1-i_2)-M_{12} \frac{d}{dt}(i_2-i_3)+$$

$$M_{13} \frac{di_3}{dt} = 0.$$

$$-M_{13} \frac{di_3}{dt} + M_{12} \frac{d}{dt}(i_2-i_3) - L_1 \frac{d}{dt}(i_2-i_1) -$$

$$L_2 \frac{d}{dt}(i_2-i_3) - M_{21} \frac{d}{dt}(i_1-i_2)$$


$$-M_{23} \frac{di_3}{dt} = 0$$

$$M_{23} \frac{di_3}{dt} + M_{21} \frac{d}{dt}(i_1-i_2) - L_2 \frac{d}{dt}(i_3-i_2)$$


$$-L_3 \frac{di_3}{dt} + M_{31} \frac{d}{dt}(i_1-i_2) - M_{32} \frac{d}{dt}(i_2-i_3) -$$

$$(i_2-i_3) + \frac{1}{C} \int i_3 dt = 0$$

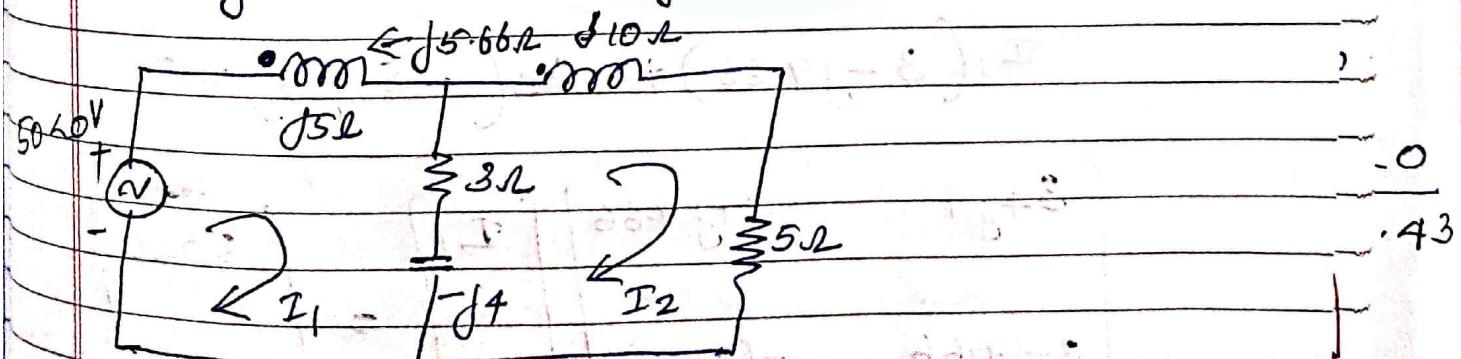Find the voltage across SR resistor using mesh analysis.



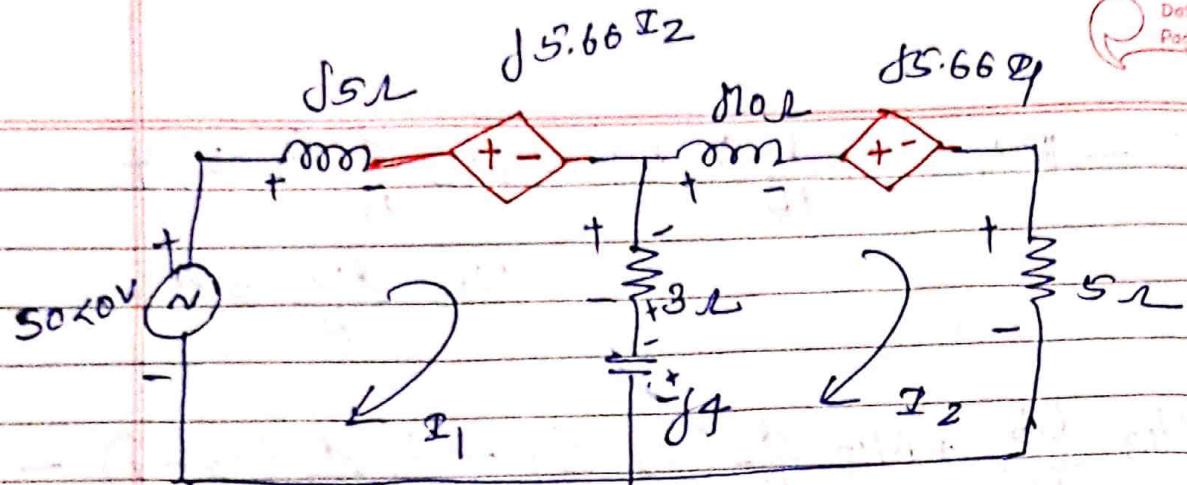Draw the equivalent ckt in terms of dependent sources.



Applying KVL to mesh 1

$$50\angle 0^\circ - j5I_1 - j5.66\angle 12^\circ - 3(I_1 - I_2) + j4(\Phi_1 - \Phi_2) = 0$$

$$50\angle 0^\circ = I_1(j5 + 3 - j4) + I_2(j5.66 - 3 + j4)$$

Applying KVL to mesh 2

$$-j4(I_2 - \Phi_1) - 3(\Phi_2 - \Phi_1) - j10I_2 - j5.66\Phi_1 - 5\frac{I_2}{2} = 0$$

$$I_1(-j4 + 3 - j5.66) + I_2(j4 - 3 - j10) = 0$$

$$I_1(3 - j9.66) + I_2(-8 - j6) = 0$$

$$\begin{bmatrix} 3+j1 & -3+j9.66 \\ 3-j9.66 & -(8+j6) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50\angle 0^\circ \\ 0 \end{bmatrix}$$


$$I_2 = \frac{8+j1 - 50\angle 0^\circ}{3-j9.66}$$

$$\begin{vmatrix} 3+j1 & -3+j9.66 \\ 3-j9.66 & -(8+j6) \end{vmatrix}$$

$$= 3.82 \angle -112.14^\circ$$


$$V_{5\Omega} = -5I_2 = 19.1 \angle -112.14^\circ V$$

4 Find the voltage across 5Ω resistor

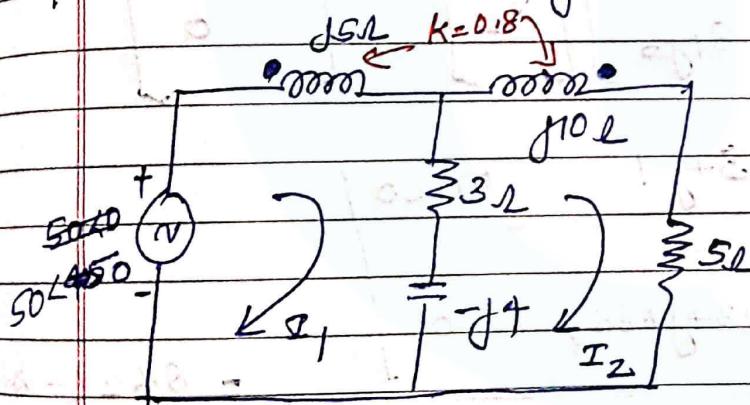

$$M = K\sqrt{L_1 L_2} = j0.8 \sqrt{5 \times 10} = j0.8 \times \sqrt{50}$$

$$= j5.66 \angle 0^\circ$$

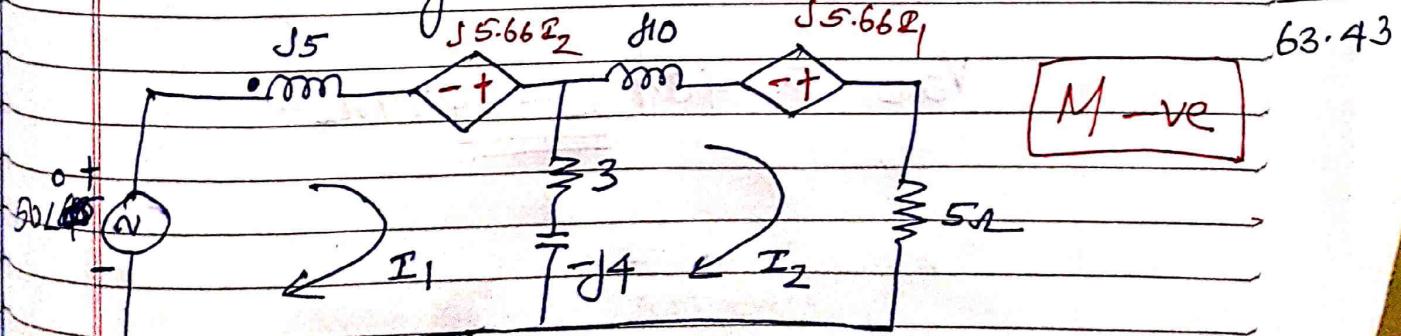

$$\begin{aligned} 50 < 45 - (3+j4) I_1 - (I_1 - I_2) j^3 - j^5 (I_1 - I_2) \\ & \quad - j^3 I_1 = 0 \\ (3+j15) I_1 - j^8 I_2 &= 50 < 45 \end{aligned}$$

Muhi

$$\begin{aligned} 50 < 0 - j^5 I_1 + j^5 \cdot 66 I_2 - (3-j4) (I_1 - I_2) = 0 \\ (3+j1) I_1 - (3+j1 \cdot 66) I_2 &= 50 < 0 \end{aligned}$$

Muha

$$\begin{aligned} -(3-j4) (I_2 - I_1) - j^{10} I_2 + j^5 \cdot 66 I_1 - 5 I_2 &= 0 \\ -(3+j1 \cdot 66) I_1 + (8+j6) I_2 &= 0 \end{aligned}$$

$$\begin{bmatrix} 3+j1 & -(3+j1 \cdot 66) \\ -(3+j1 \cdot 66) & 8+j6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 < 0 \\ 0 \end{bmatrix}$$


$$I_2 = \frac{\begin{vmatrix} 3+j1 & 50 < 0 \\ -(3+j1 \cdot 66) & 0 \end{vmatrix}}{\begin{vmatrix} 3+j1 & -(3+j1 \cdot 66) \\ -(3+j1 \cdot 66) & 8+j6 \end{vmatrix}} = 8.62 L - 0.41 \Omega$$

$$\begin{vmatrix} 3+j1 & -(3+j1 \cdot 66) \\ -(3+j1 \cdot 66) & 8+j6 \end{vmatrix}$$


$$V_{SL} = 43.1 \angle -24.79 \Omega$$

Conductively Coupled Equivalent Ckt's.

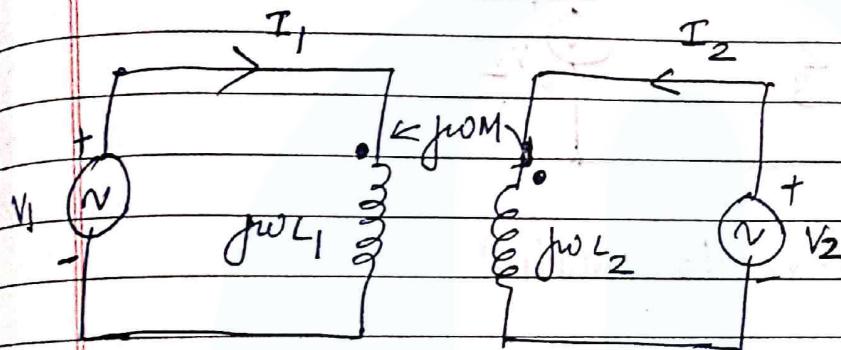- For simplifying circuit analysis, we can replace a magnetically coupled ckt with an equivalent ckt called conductively coupled circuit. In this no magnetic coupling is involved. The dot convention is also not needed.



Equivalent ckt

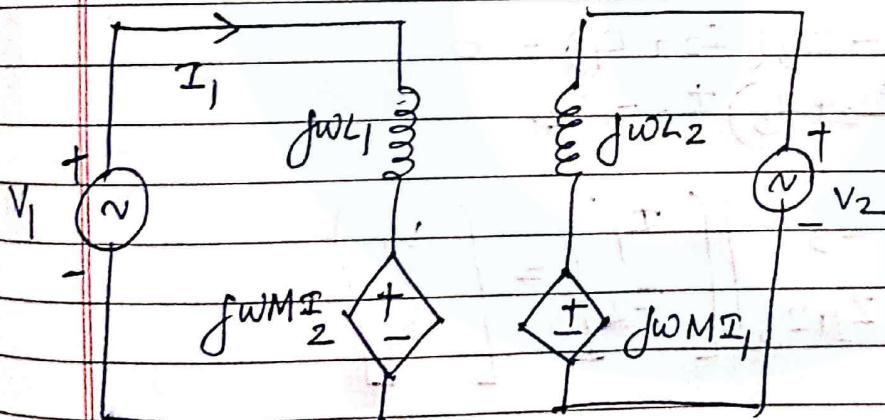

Applying KVL to mesh 1,

$$V_1 - j\omega L_1 I_1 - j\omega M I_2 = 0$$

$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$


Mesh 2

$$V_2 - j\omega L_2 I_2 - j\omega M I_1 = 0$$

$$V_2 = j\omega M I_1 + j\omega L_2 I_2$$

$$\begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Consider a T network

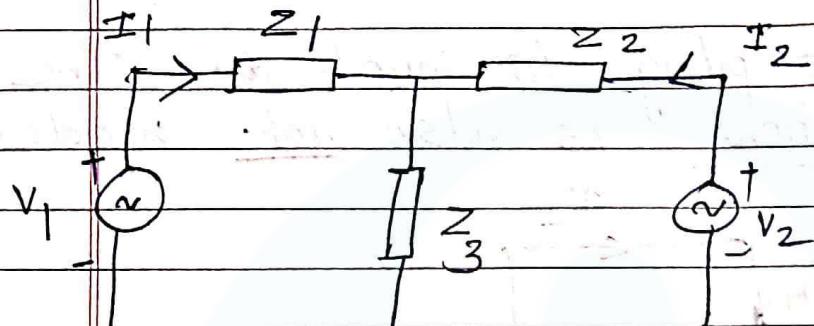

Applying KVL to mesh 1

$$V_1 - I_1 Z_1 - Z_3 (I_1 + I_2) = 0$$

$$(Z_1 + Z_3) I_1 + Z_3 I_2 = 0.$$

Mesh 2

$$V_2 - I_2 Z_2 - Z_3 (I_2 + I_1) = 0$$

$$Z_3 I_1 + (Z_2 + Z_3) I_2 = V_2.$$

$$\begin{bmatrix} Z_1 + Z_3 & -Z_3 \\ Z_3 & Z_2 + Z_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Comparing two matrix eqns.

$$Z_1 + Z_3 = j\omega L_1$$

$$Z_3 = j\omega M$$

$$Z_2 + Z_3 = j\omega L_2$$

Solving


$$Z_1 = j\omega L_1 - j\omega M$$

$$= j\omega (L_1 - M)$$

$$Z_2 = j\omega L_2 - j\omega M = j\omega (L_2 - M)$$

$$Z_3 = j\omega M.$$

Conductively coupled equivalent ckt -

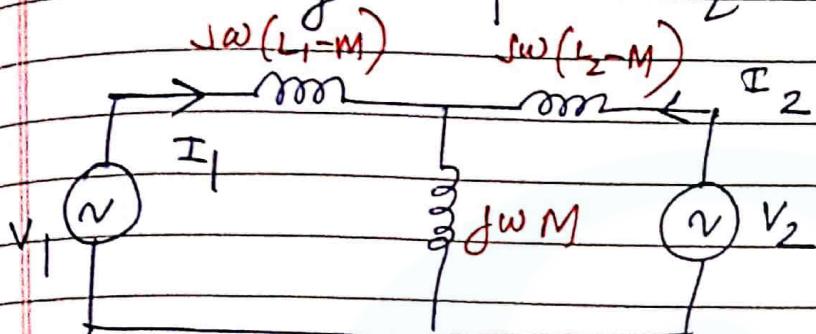


nb

- 40

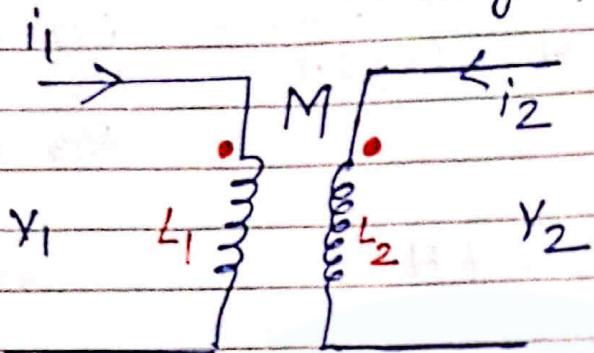63.4


Conductively Coupled Equivalent Circuit

- Energy transfer takes place b/w two circuits through a conductor.



$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
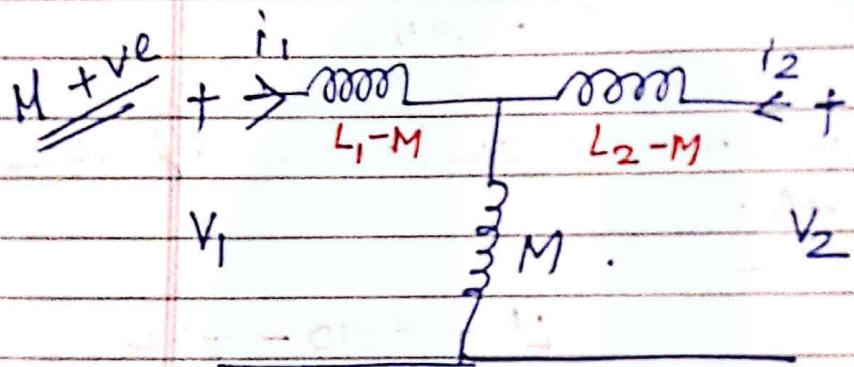
$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$



V₂ ← conductively equivalent of the magnetic ckt

$$V_1 = (L_1 - M) \frac{di_1}{dt} + M \frac{d}{dt} (i_1 + i_2)$$

$$V_2 = (L_2 - M) \frac{di_2}{dt} + M \frac{d}{dt} (i_1 + i_2)$$



If we simplify these 2 eqns, we get eqns ①, ie the two circuits are equivalent.

$$Z_A = L_1 - M, \quad Z_B = L_2 - M, \quad Z_C = M.$$

CASE 2 M is +ve, both the currents are additive.

II If M is -ve, currents in the common branch are opposite to each other.
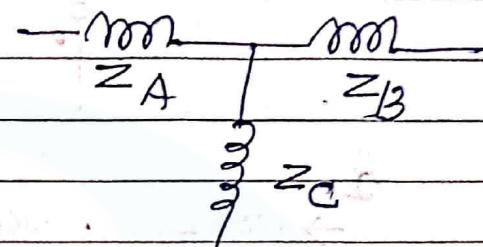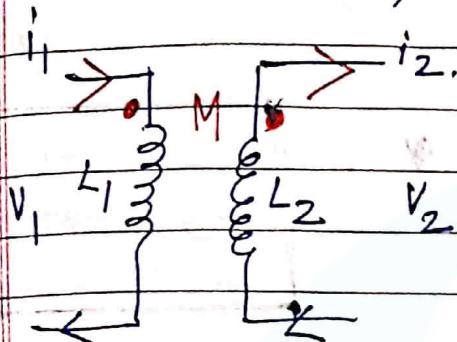
$$Z_A = L_1 - M, Z_B = L_2 - M, Z_C = M$$





$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

III If M is +ve, two currents are opposite to each other.

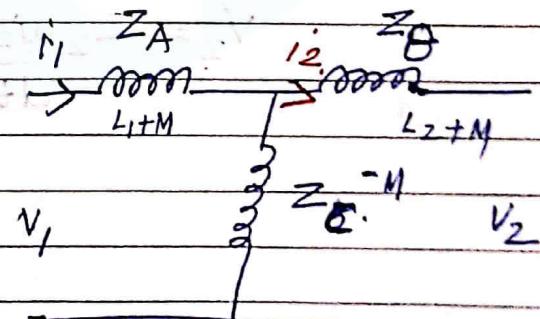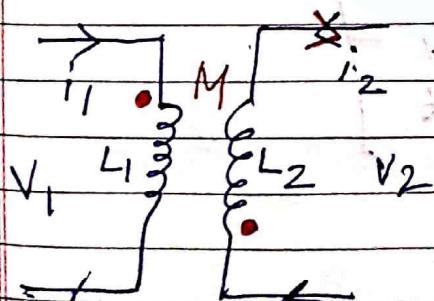
$$Z_A = L_1 + M, Z_B = L_2 + M, Z_C = -M$$



$$V_1 = (L_1 + M) \frac{di_1}{dt} - M \frac{d(i_1 - i_2)}{dt}$$


$$= L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

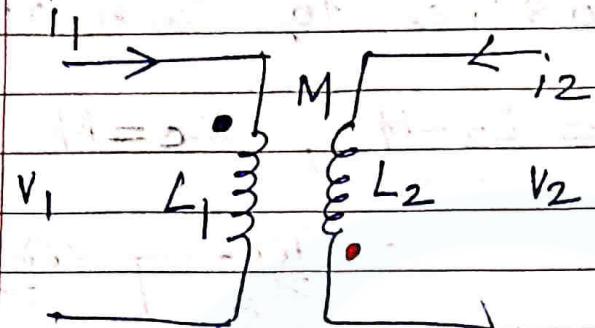IV If M is -ve, two currents are additive.



$$-M$$

i_1, i_2 are same dirn.

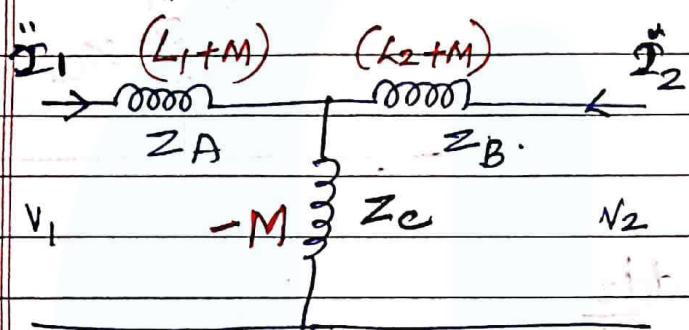

$$\begin{aligned} Z_A &= L_1 + M \\ Z_B &= L_2 + M \\ Z_C &= -M \end{aligned}$$

$$V_1 = (L_1 + M) \frac{di_1}{dt} - M \frac{d}{dt} (i_1 + i_2)$$


$$V_2 = (L_2 + M) \frac{di_2}{dt} - M \frac{d}{dt} (i_1 + i_2)$$

For magnetically coupled circuit,

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

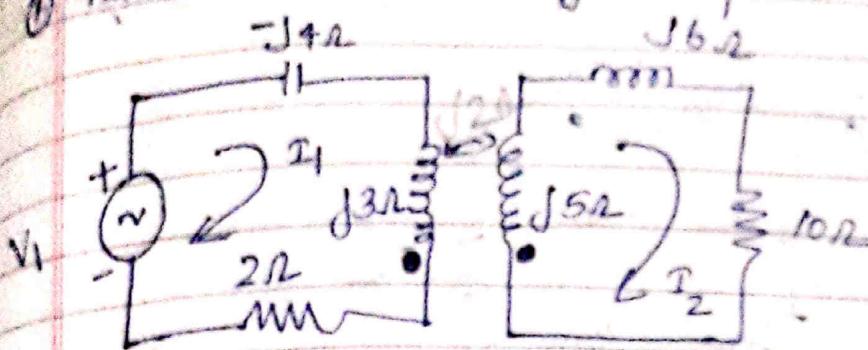① Find the conductively coupled equivalent ckt.



To both
the coils,
currents
leave the
dotted ends.


M is neg

In coil 1, current leaves the dotted end. In second coil, current enters the dotted end. $\therefore M$ is negative.

$$\begin{aligned} Z_A &= j\omega(L_1 - M) = j\omega L_1 - j\omega M \\ &= j^3 - j^2 = j^1 \Omega \end{aligned}$$


$$\begin{aligned} Z_B &= j\omega(L_2 - M) = j\omega L_2 - j\omega M \\ &= j^5 - j^2 = j^3 \Omega \end{aligned}$$

$$Z_C = j\omega M = j^2 \Omega$$

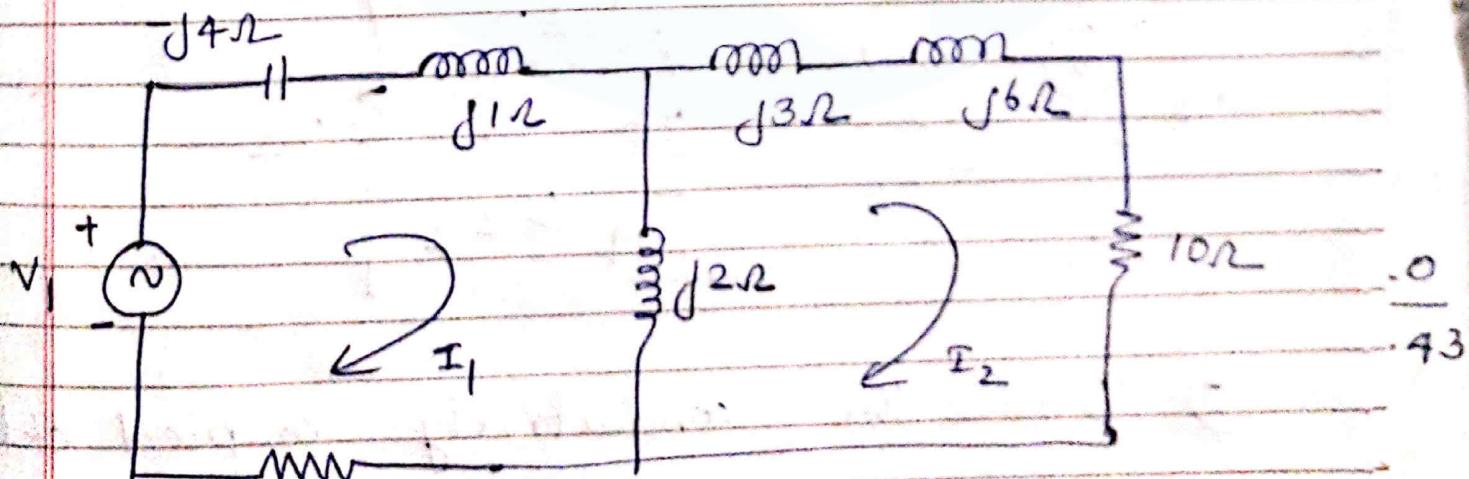

Conductively Coupled equivalent ckt

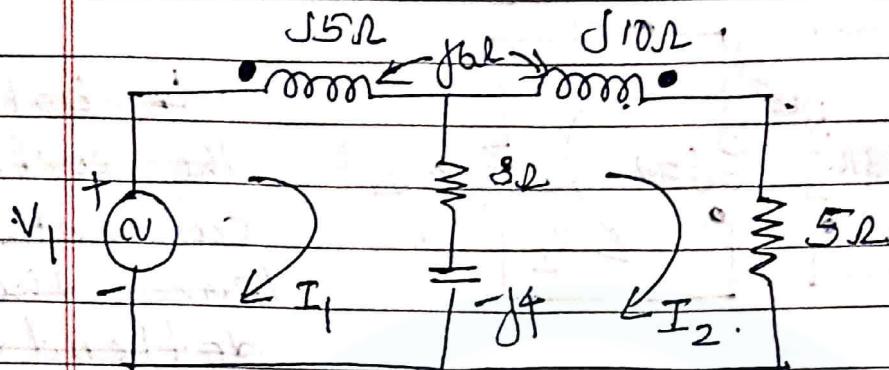- ② Draw the conductively coupled equivalent ckt.



Current I_1 enters at the dotted end.


Current I_2 leaves the dotted end.

Hence, M is negative.


$$Z_A = j\omega(L_1 - M) = j5 - j6 = -j1\Omega$$

$$Z_B = j\omega(L_2 - M) = -j10 - j6 = -j16\Omega$$

$$Z_3 = j\omega M = j6\Omega$$

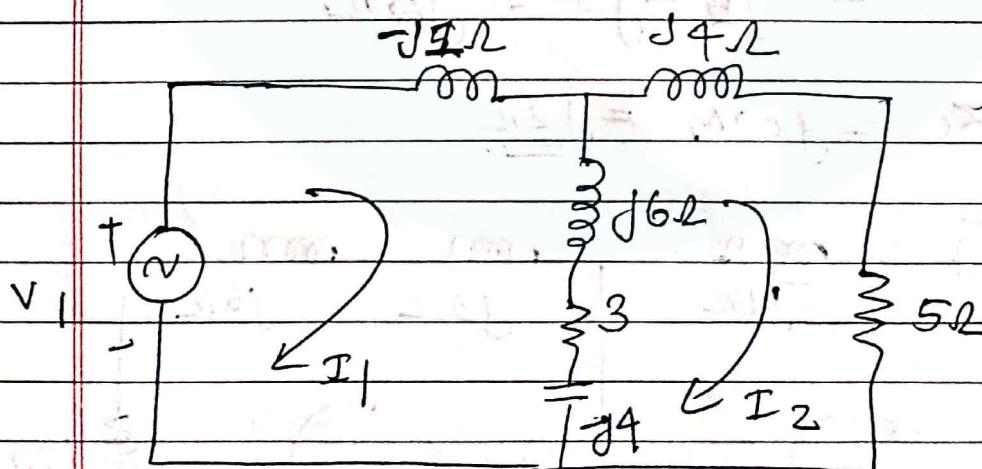

- ③ Draw the conductively coupled ckt.

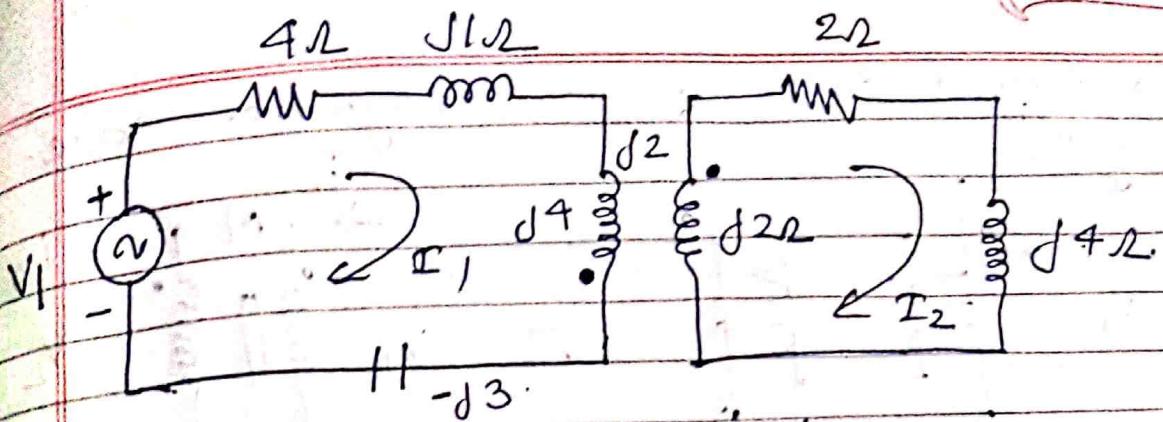


Both currents leave from the dotted ends.
M is +ve.

$$Z_A = j\omega(L_1 + M) = j4 + j2 = j6L$$

$$Z_B = j\omega(L_2 + M) = j2 + j2 = j4L$$

$$Z_C = -j\omega M = -j2L$$

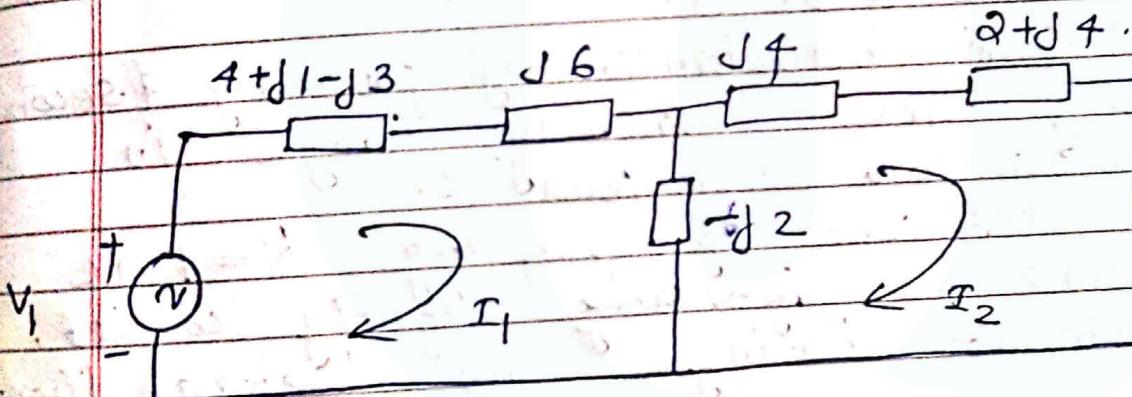


Ideal Transformer

Transfer of energy from one circuit to another circuit through mutual induction is widely utilised in power systems. This purpose is served by transformers.

Transformer is a stationary device having two or more windings.

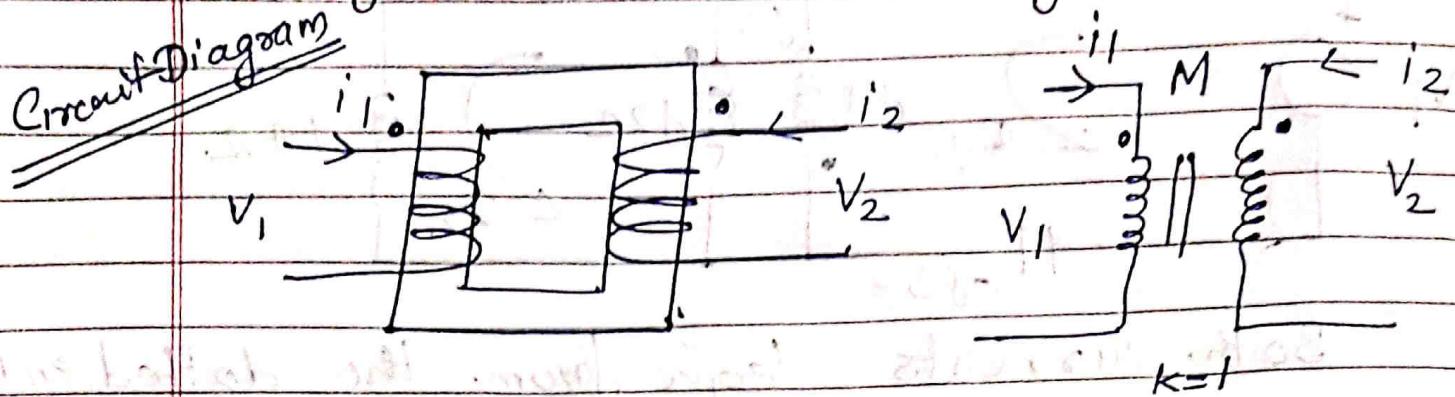Ktu Q bank arranged in a common magnetic core.



The winding to which supply is connected is primary and winding connected to load is secondary.

For an ideal transformer,

- 1) Resistance in both the coils are assumed to be 0.
- 2) Self inductance of primary & secondary are extremely large in comparison with load Z .
- 3) Coefficient of coupling $k=1$ i.e. coils are typically tightly coupled, without having any leakage flux.

The magnitude of self induced emf

$$V = L \frac{di}{dt}$$

Also, $V = N \frac{d\phi}{dt}$; N = no. of turns
 $\frac{N d\phi}{dt}$ = Flux linkage of the coil.

$$L \frac{di}{dt} = N \frac{d\phi}{dt} \Rightarrow L = N \frac{d\phi}{di}$$


$$\text{But } \phi = \frac{m_0 f}{\text{Reluctance}} = \frac{N_s}{s}$$

$$L = N \frac{d\phi}{ds} = N \frac{d}{ds} \left(\frac{N_s}{s} \right)$$

$$L = \frac{N^2}{s} \quad L \propto N^2$$

$$\text{i.e. } \frac{L_2}{L_1} = \frac{N_2^2}{N_1^2} = k^2 \quad k = \text{turns ratio.}$$

Transformer with Sinusoidal Excitations

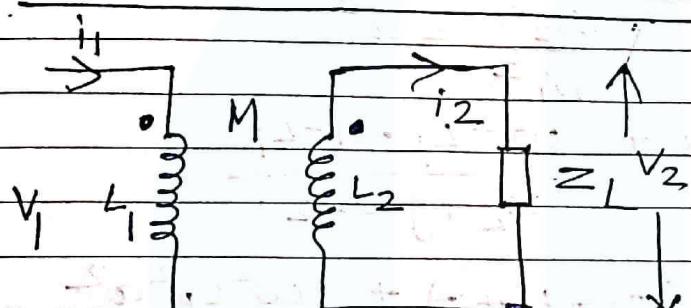

$$V_1 - I_1 j \omega L_1 - j \omega M I_2 = 0$$

$$V_1 = I_1 j \omega L_1 + j \omega M I_2 \quad \dots \quad (1)$$

$$0 = -j \omega M I_1 + (Z_L + j \omega L_2) I_2 \quad \dots \quad (2)$$

$$\therefore \Rightarrow I_2 = \frac{j \omega M I_1}{Z_L + j \omega L_2}$$

$$\begin{aligned} V_1 &= I_1 j \omega L_1 - j \omega M \times \frac{j \omega M I_1}{Z_L + j \omega L_2} \\ &= I_1 j \omega L_1 + \frac{\omega^2 M^2 I_1}{Z_L + j \omega L_2} \end{aligned}$$

$$Z_{in} = \text{Input Impedance} = \frac{V_I}{I_I}$$

$$= j\omega L_1 + \frac{\omega^2 M^2}{Z_L + j\omega L_2}$$

$$\text{When } k=1, \quad M = K \sqrt{L_1 L_2} = \sqrt{L_1 L_2}$$

$$Z_{in} = j\omega L_1 + \frac{\omega^2 L_1 L_2}{Z_L + j\omega L_2}$$

$$\text{Putting } L_2/L_1 = \frac{N_2^2}{N_1^2} = a^2$$

$$\therefore Z_{in} = j\omega L_1 + \frac{\omega^2 L_1 \cdot a^2 L_1}{Z_L + j\omega L_2}$$

$$= j\omega L_1 (Z_L + j\omega L_2) + \frac{\omega^2 L_1^2 a^2}{Z_L + j\omega L_2}$$

$$= Z_L j\omega L_1 - \frac{\omega^2 L_1 L_2 + \omega^2 L_1^2 a^2}{Z_L + j\omega L_2}$$

$$= Z_L j\omega L_1 - \frac{\omega^2 L_1^2 a^2 + \omega^2 L_1^2 a^2}{Z_L + j\omega L_2}$$

$$Z_L j\omega L_1$$

$$\frac{Z_L + j\omega L_2}{Z_L + j\omega L_2}$$

Discard

Date _____

Page _____

As L_2 is assumed to be infinitely large compared to Z_L

$$Z_{in} = \frac{Z_L j\omega L_1}{j\omega a^2 L_1} = \frac{Z_L}{a^2} = \left(\frac{N_1}{N_2}\right)^2 Z_L$$

i.e ideal transformer change the impedance of a load and can be used to match circuits with different impedances in order to achieve maximum power transfer.