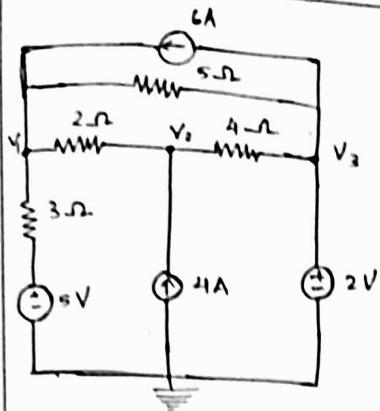


12/11/2021


Module - 1

Qn 1)



Using nodal method, find the current through the resistors in the circuit.

consider 1st node

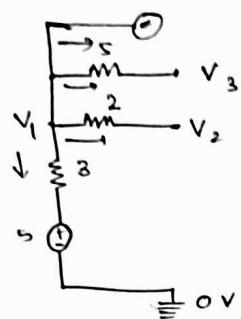

$$V_3 = 2V$$

$$\frac{V_1 - 5}{3} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{5} - 6 = 0$$

$$\frac{V_1 - 5}{3 \times 2} + \frac{V_1 - V_2}{2 \times 3} + \frac{V_1 - 2}{5} = 6$$

$$\frac{2V_1 - 5}{5} + \frac{V_1 - V_2}{2} = 6 \quad \frac{2V_1 - 10 + 3V_1 - 3V_2 + V_1 - 2}{5} = 6$$

$$4V_1 - 10 + 5V_1 - 5V_2 = 60$$

$$9V_1 - 5V_2 = 70$$


$$\frac{5V_1 - 3V_2 - 10}{6} + \frac{V_1 - 2}{5} = 6$$

$$5V_1 - 3V_2$$

$$25V_1 - 15V_2 - 50 + 6V_1 - 12 = 180$$

$$31V_1 - 15V_2 = 242$$


consider 2nd node

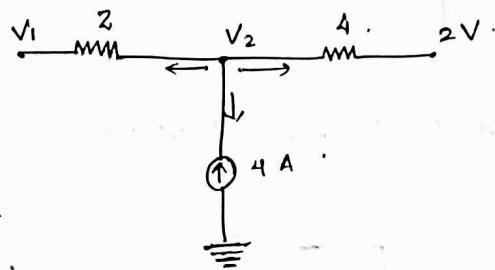


$$\frac{V_2 - V_1}{2} + \frac{V_2 - 2}{4} - 4 = 0$$

$$2V_2 - 2V_1 + V_2 - 2 = 16$$

$$3V_2 - 2V_1 = 18$$

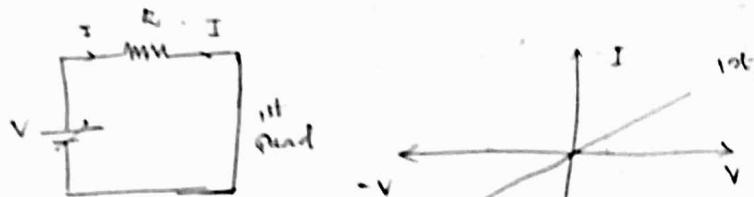

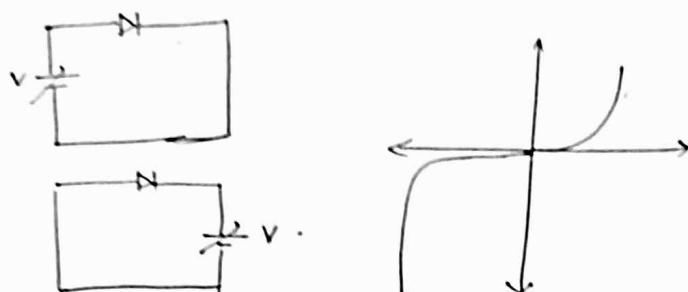The graph on the 1st & 3rd quadrant are the same
 \therefore Bilateral




The graph on the 1st & 3rd quadrant are different.
 \therefore Unilateral


Lateral

Thevenin theorem can be applied only to \rightarrow linear and bilateral.

Ex 3)

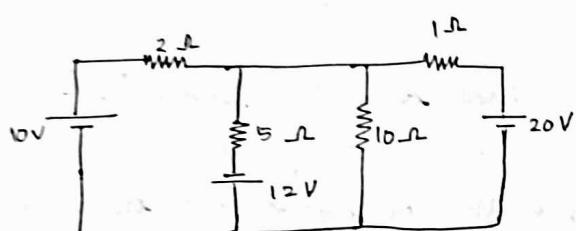

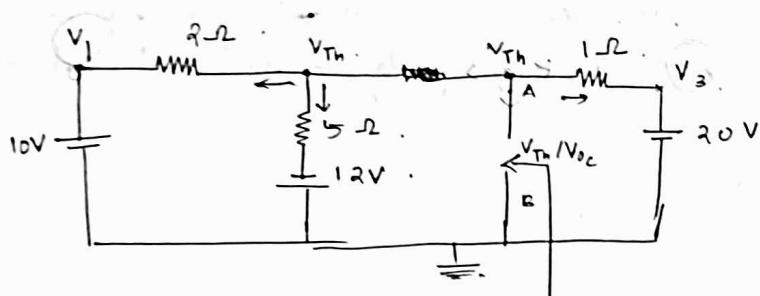Find the current through the 10 ohm resistor, utilizing Thevenins theorem.



$$V_1 = 10V, V_3 = 20V, \text{ wrt the reference.}$$

$$\frac{V_{Th} + 10}{5} + \frac{V_{Th} - 10}{2} + \frac{V_{Th} - 20}{1} = 0$$


$$\frac{2V_{Th} + 24 + 5V_{Th} - 50}{10} + V_{Th} - 20 = 0$$

$$7V_{Th} - 26 + 10V_{Th} - 200 = 0$$

$$17 V_{TH} = 226$$

$$V_{TH} = 13.29 \text{ V}$$

short all the voltages

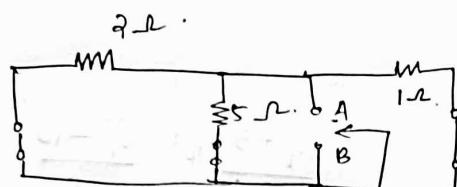


21/5



$\frac{10}{7} \parallel 1$


$$\therefore R_{TH} = 0.588 \Omega$$

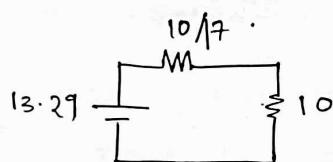

$$R = \frac{10}{17} + 10 = \frac{180}{17} \Omega$$


$$I = \frac{13.29}{180/17} = 1.255 \text{ A}$$

Qn 4)

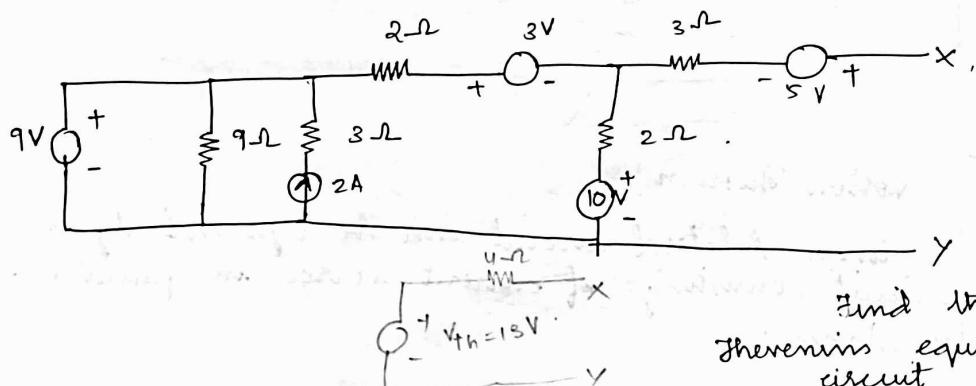

Find the
Thevenin equivalent
circuit


To find R_{TH}

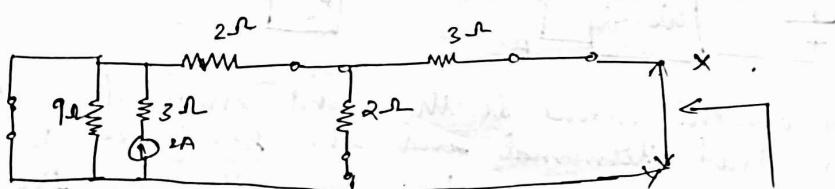

$$2 \parallel 2 = 1$$

$$1 + 3 = 4$$

$$\therefore R_{TH} = 4 \Omega$$

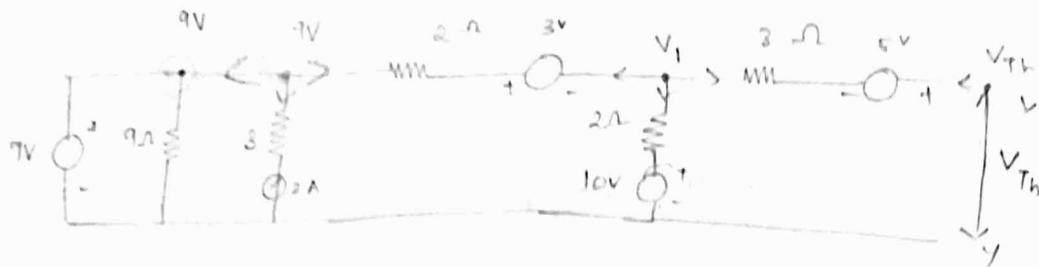

$$\frac{V_{Th} - 5 - V_1}{3} = 0$$

$$V_{Th} - V_1 = 5 \quad \text{--- (1)}$$

$$\frac{V_1 + 5 - V_{Th}}{3} + \frac{V_1 - 10}{2} + \frac{V_1 + 3 - 7}{2} = 0$$

$$\frac{V_1 - V_{Th} + 5}{3} + \frac{2V_1 - 16}{2} = 0$$


$$\frac{V_1 - V_{Th} + 5}{3} + V_1 - 8 = 0$$

$$V_1 - V_{Th} + 5 + 3V_1 - 24 = 0$$

$$-V_{Th} + 4V_1 = 19 \quad \text{--- (2)}$$

$$V_{Th} = 13 \text{ V}$$


$$V_1 = 8 \text{ V}$$

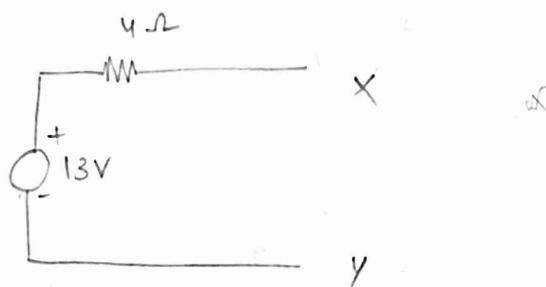

1/12/2021

Norton Theorem


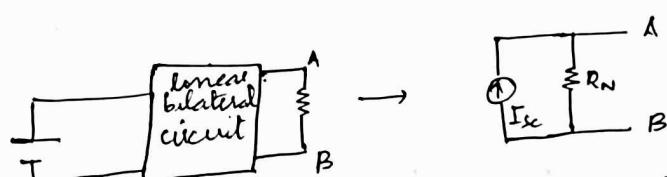
A linear bilateral circuit can be replaced by an equivalent circuit consisting of current source in parallel with a resistance.



The current source be the short circuited current through the load terminal and the resistance be the internal resistance of the source looking through the open circuited load terminal.

$$R_N = R_{Th}$$

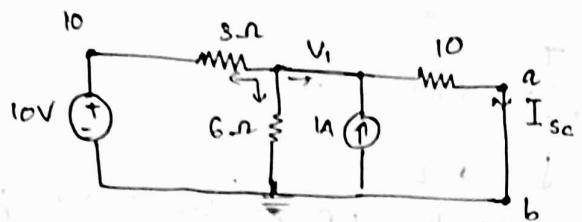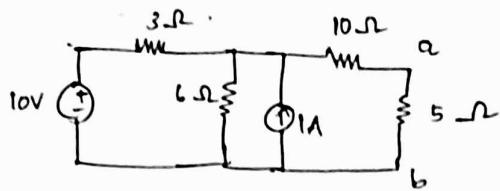- Qn) Find the Norton current in the 5Ω resistance using Norton Theorem



$$\frac{V_1 - 10 \times 2}{3 \times 2} + \frac{V_1}{6} - 1 + I_{sc} = 0 \quad \text{--- (1)}$$

$$\frac{2V_1 - 20 + V_1}{6} - 1 + I_{sc} = 0$$

$$3V_1 - 20 - 6 + 6I_{sc} = 0$$

$$3V_1 + 6I_{sc} - 26 = 0$$

$$3V_1 + 6I_{sc} = 26$$

$$I_{sc} = \frac{V_1}{10} \quad \text{--- (2)}$$


$$3V_1 + \cancel{6} \times \frac{V_1}{10} = 26$$

$$\frac{15V_1 + V_1}{5} = 26$$

$$18V_1 = 130$$


$$V_1 = 7.2 \text{ V}$$
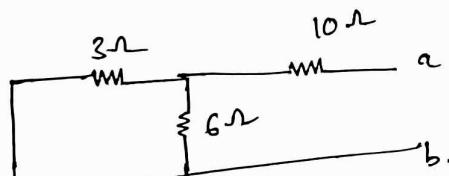
$$I_{sc} = \underline{\underline{0.722 \text{ A}}}$$



$$3I_{sc} \frac{6 \times 3}{9 \times 8} = 2$$


$$2 + 10 = 12 \Omega$$

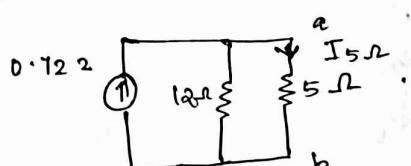




$$g_{s,n} = \frac{0.722 \times 12}{12 + 5}$$

$$= 0.5096 A$$

Qn 2)

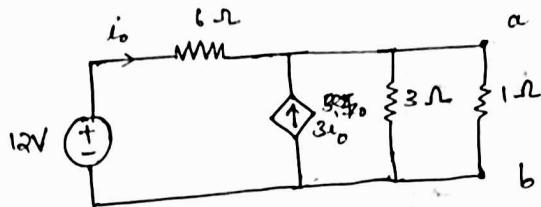

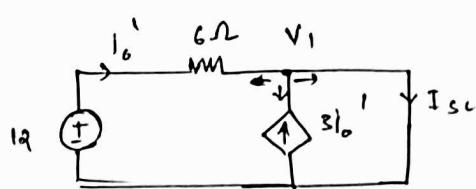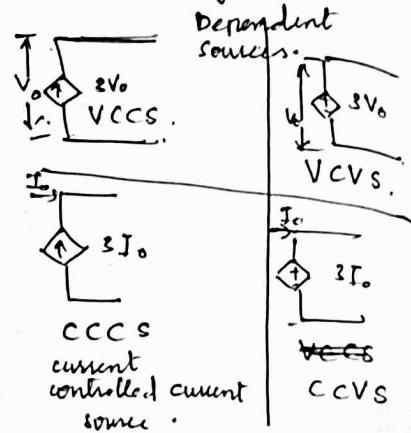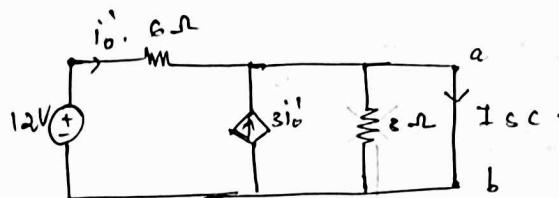Find the current through the 1Ω resistance using Norton Theorem.



$$\frac{V_1 - 12}{6} = -i_o^1$$

$$\frac{V_1 - 12}{6} - 3i_o^1 + I_{sc} = 0$$

$$-i_o^1 - 3i_o^1 + I_{sc} = 0$$

$$-4i_o^1 + I_{cc} = 0$$

$$I_{sc} = 4i_o^1 \quad \text{--- (1)}$$


$$V_1 = 0$$

$$-i_o^1 = \frac{V_1 - 12}{6}$$

$$i_o^1 = \frac{12 - V_1}{6}$$

$$i_o^1 = \frac{12}{6} = 2 A$$

$$I_{cc} = 4 \times 2 = 8 A$$

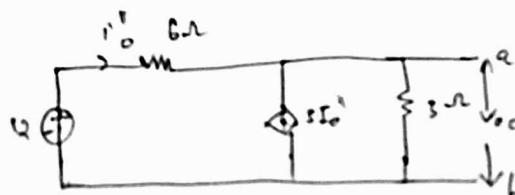

$$R_N = \frac{V_{oc}}{I_{cc}}$$

$$\frac{V_{Th} - 0}{3} + \frac{V_{Th} - 12}{6} - 3i_o = 0$$

$$\frac{V_{Th}}{3} - i'_o - 3i''_o = 0$$

$$\frac{V_{Th}}{3} = 9i''_o$$

$$V_{Th} = 12i''_o$$


$$V_{Th} = 12^2 \left(\frac{12 - V_{Th}}{6} \right)$$

$$V_{Th} = 8V - 2V_{Th}$$

$$3V_{Th} = 24$$

$$\underline{\underline{V_{Th} = 8V}}$$

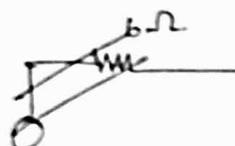
$$R_N = \frac{V_{Th}}{I_{sc}} = \frac{8V}{8A} = \underline{\underline{1\Omega}}$$




$$g_{1\Omega} = \frac{8 \times 3}{14} = \frac{8 \times 1}{2} = \underline{\underline{4A}}$$

current method

Qn 3)

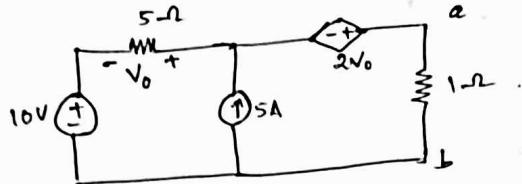

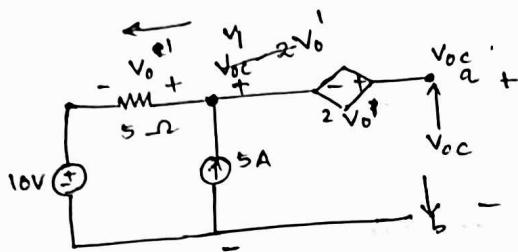Find 'the' current through the 1Ω resistor using Norton theorem.



$$V_{0c} = 2V_0'$$

$$\frac{V_0' - 10}{5} + 5 = 0$$

$$\frac{V_0' - 10}{5} = 5$$

$$V_0' - 10 = 25$$

$$V_0' = 35$$

~~$V_0' \neq 10 \neq 2V_0'$~~

~~$\frac{V_0' - 10}{5} - 5 \neq 0$~~

~~V_0'~~

$$i_{in} = \frac{V_0'}{5}$$

Applying nodal analysis

~~$\frac{V_0'}{5} - 5 = 0$~~

~~$\frac{V_0'}{5} - 5 = 0$~~

$$\frac{V_0'}{5} = 5$$

$$V_0' = 25V$$

$$V_0' = 25V$$

25-10

$$10 + 25 - V_1 = 0$$

$$V_1 = 35$$

$$V_{0c} - 2V_0' = \cancel{V_0' - 10}$$

$$V_{0c} = 50 =$$


$$V_1 = V_{0c} - 2V_0'$$

$$V_{0c} = V_1 + 2V_0'$$

$$= 35 + 2 \times 25$$

$$= 50 + 35$$

$$= 85V$$

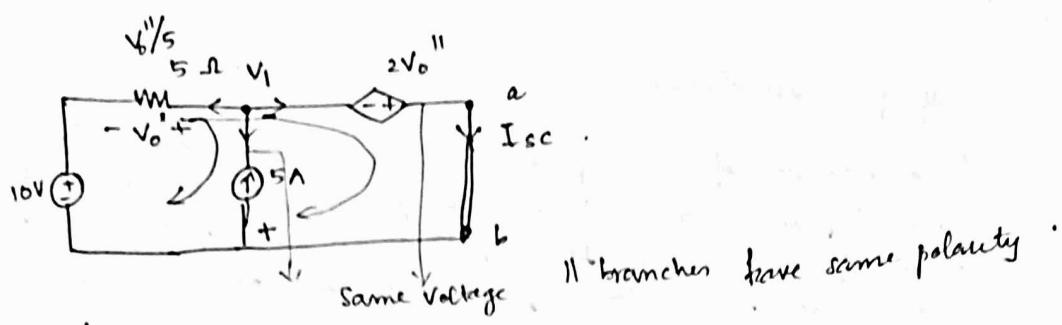

$$\text{KVL} \quad \frac{V_o''}{5} - 5 + I_{sc} = 0$$

$$I_{sc} = 5 - \frac{V_o''}{5} \quad \text{--- (1)}$$

$$10 + \frac{V_o''}{5} + 2V_o'' = 0$$

~~$$10 + V_o'' + 2V_o'' = 0$$~~

$$3V_o'' = -10$$

$$V_o'' = -\frac{10}{3}$$


$$I_{sc} = 5 - \frac{-10}{3 \times 5}$$

$$= 5 + \frac{10}{3 \times 5}$$


$$= \frac{+5+10}{3} = \frac{25}{3} \text{ A} \quad 5.667 \text{ A}$$

$$R_N = \frac{V_{oc}}{I_{sc}} = \frac{85}{17.25/2} = \frac{85 \times 3}{25} \approx \frac{85 \times 3}{17} = 15 \Omega$$

Thevenin

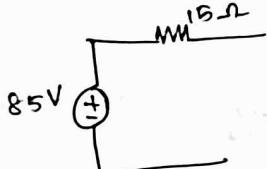

Norton

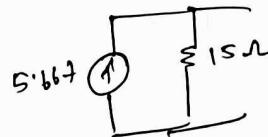


Norton



$$I_{1\Omega} = \frac{5.667 \times 15}{16} = 5.3 \text{ A}$$

Thevenin

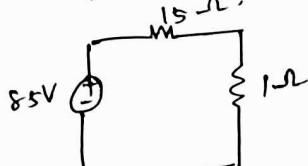

$$R = 15 + 1 = 16 \Omega$$


$$\therefore I = \frac{V}{R} = \frac{85}{16} = 5.3 \text{ A}$$

3/12/2021


Superposition Theorem

If a number of voltage or current sources are active simultaneously, the resultant current in any branch is the algebraic sum of the currents that will be produced in it when each source acts alone replacing all other independent sources by their internal impedance.

Qn 1)

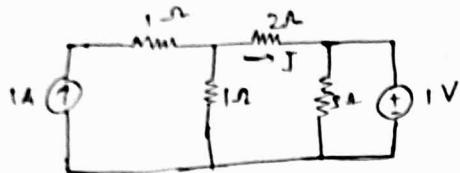

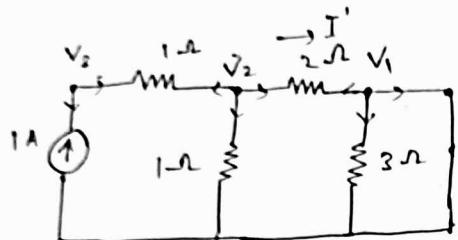Find the current I in the circuit using superposition theorem.



The voltage source is shorted

$$\frac{V_1}{3} + \frac{V_1 - V_2}{2} = 0$$

$$2V_1 + 3V_1 - 5V_2 = 0$$

$$5V_1 - 5V_2 = 0$$

$$\frac{V_2}{1} + \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{1} = 0$$

$$\frac{2V_2 - V_3}{1} + \frac{V_2 - V_1}{2} = 0$$

$$4V_2 - 2V_3 + V_2 - V_1 = 0$$

$$-V_1 + 5V_2 - 2V_3 = 0$$

#8

~~$$\frac{V_3 - V_2}{1} - 1 = 0$$~~


$$V_3 - V_2 = 1$$

$$V_1 = V_2 \quad V_2 = \frac{5}{6}, \quad V_3 = \frac{11}{6}$$

$$I = V_2 = \frac{V_3 - V_1}{2} =$$

$$I = \frac{1 \times 1}{1+2} = \underline{\underline{V_3}}$$

The current source is opened.

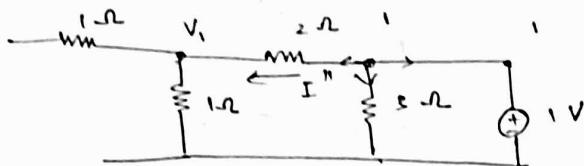

$$\frac{V_1 - 1}{2} + \frac{V_1}{1} = 0$$

$$V_1 - 1 + 2V_1 = 0$$

$$2V_1 = 1$$

$$V_1 = \frac{1}{2}$$

$$I'' = \kappa \frac{1 - V_1}{2}$$

$$\frac{1 - V_1}{2} + \frac{1}{3} = 0$$

$$I'' = -\frac{1}{3} A$$

$$V_1 = 1$$

$$\therefore I'' = \frac{1}{3} A$$

$$I = I' - I''$$


$$\therefore \frac{1}{2} + \frac{1}{2}$$

$$= \frac{1}{3} A$$


$$I = I' - I''$$

$$= 0$$

Qn2)

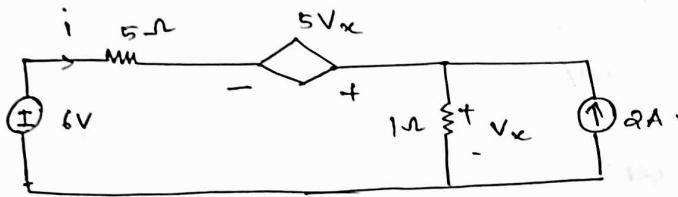

Find current I using superposition.

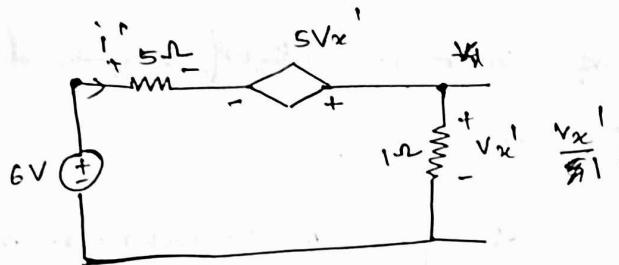

$$6 + 5V_x' - 5i' - V_x' = 0$$

$$4V_x' - 5i' = -6 \quad \textcircled{1}$$

$$V_x' = i'$$

$$\frac{V_1}{1} + V_1 - 5V_x' - 5 = 0$$


$$5V_1 + V_1 - 5V_x' = 6$$

$$6V_1 - 5V_x' = 6$$

$$4i' - 5i' = -6$$

$$-i' = -6$$

$$i' = 6 A$$

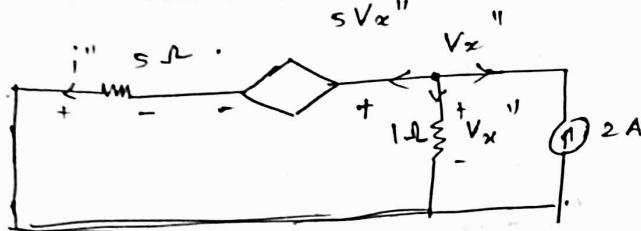

$$-5V_x'' \rightarrow 5i'' \rightarrow -2 + \frac{V_x''}{1} = 0$$

$$-6V_x'' + 5i'' = -2$$

$$-5V_x'' + V_x'' - 5i'' = 0$$

$$-4V_x'' = 5i''$$

$$V_x'' = -\frac{5i''}{4}$$

$$i'' - \frac{5i''}{4} = 2$$

$$(4-5)i'' = 8$$

$$\underline{i'' = -8 \text{ A}}$$

$$i = i' - i''$$

$$= 6 + 8$$

$$\underline{\underline{= 14 \text{ A}}}$$


(*)

7/12/2021

Maximum Power Transfer Theorem (Proof required)

DC Analysis


Imp
for
Exam

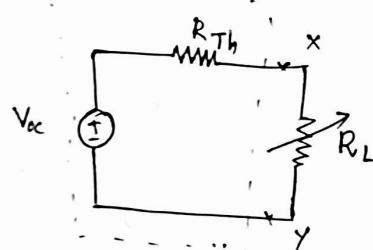

The power is maximum when $R_L = R_{Th}$

$$P_L = I_L^2 R_L$$
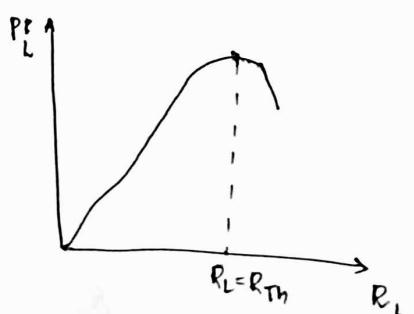
$$\left(\frac{V_o}{R_{Th} + R_L} \right)^2 R_L$$



$$\frac{dP_L}{dR_L} = 0$$

$$P_L = \frac{V_{oc}^2 R_L}{(R_{Th} + R_L)^2}$$

$$\frac{dP_L}{dR_L} = \frac{(R_{Th} + R_L)^2 V_{oc}^2 - 2(R_{Th} + R_L) V_{oc}^2 R_L}{(R_{Th} + R_L)^4} = 0$$

$$(R_{Th} + R_L) V_{oc}^2 (R_{Th} + R_L - 2R_L) = 0$$


$$R_L + R_{Th} = 0$$

$$R_{Th} = R_L$$

at this condition power is maximum


Here A resistance load be connected to a dc network receives maximum power when the load resistance (R_L) is equal to the Thévenin equivalent resistance (R_{Th}). $P_{max} = V_{oc}^2 / 4R_{Th}$

Qn
1)

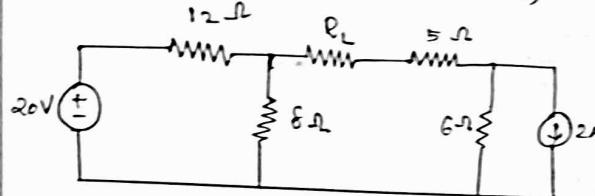

what is the maximum power that would be dissipated in the resistance R_L ?

Using Thévenin's Theorem.

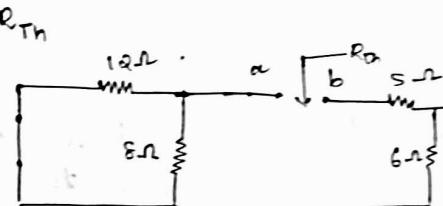


$$R_{Th} = \frac{12 \times 5}{12+5} =$$

$$12||5 = \frac{24}{5} \Omega$$

$$5\&6 = 11 \Omega$$
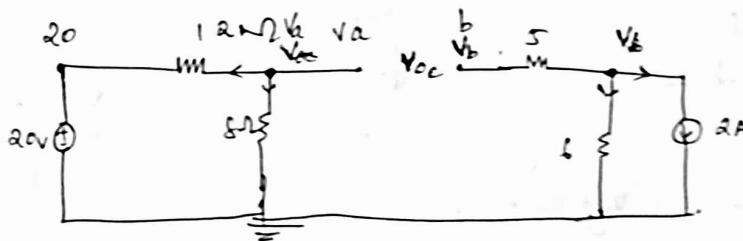
$$\frac{24}{5} + 11 = \underline{\underline{15.8 \Omega}}$$




$$\frac{Va - 20}{12} + \frac{Va}{8} = 0$$

$$8Va - 160 + 12Va = 0$$


$$20Va = 160$$
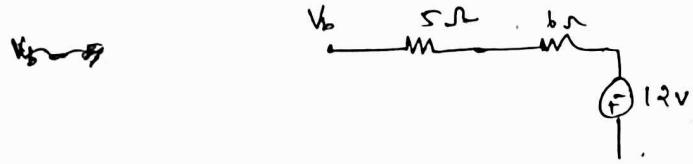
$$Va = \underline{\underline{8 \Omega}}$$



$$\frac{V_b + 12}{11} = 0$$


$$V_b = -12$$

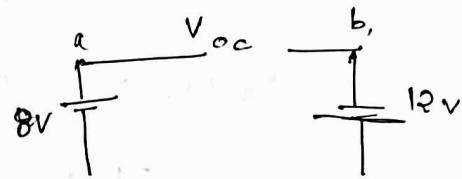

$$V_{oc} = V_a - V_b$$

$$= 8 + 12$$

$$= \underline{\underline{20V}}$$

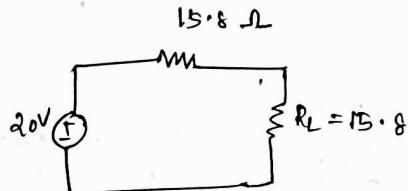


$$P = \frac{V_{oc}^2}{4R_{Th}} = \frac{20^2}{4 \times 15.8}$$

$$= 6.329 W$$


$$= \underline{\underline{6.33W}}$$

Qn
2)

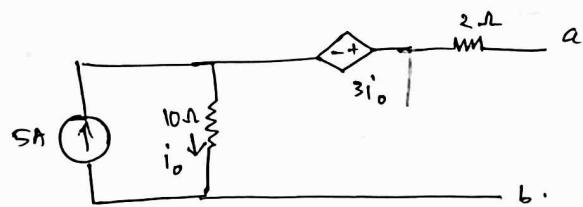

Find the maximum power that can be drawn from the circuit across a & b.

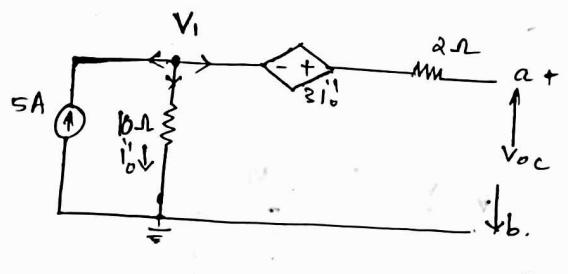Since there is an dependent source, we have to perform both Thévenin and Norton's Theorem.



$$\frac{V_1}{10} = i_o'$$

$$V_1 = 10i_o'$$

$$\frac{V_1 - 0}{10} - 5 + V_1 + \frac{3i_o'}{2} - V_{Th} = 0$$

$$i_o' - 5 + V_1 + \frac{3i_o'}{2} - V_{Th} = 0$$

$$2i_o' - 10 + 10i_o' + 3i_o' - V_{Th} = 0$$

$$15i_o' - V_{Th} = 10$$

$$\frac{V_{Th} - 3i_o' - V_1}{2} = 0$$

$$V_{Th} - 3i_o' - 10i_o'' = 0$$


$$V_{Th} = 13i_o'$$

$$15i_o' - 13i_o' = 10$$

$$2i_o' = 10$$

$$i_o' = 5A$$

$$V_{Th} = 65V$$

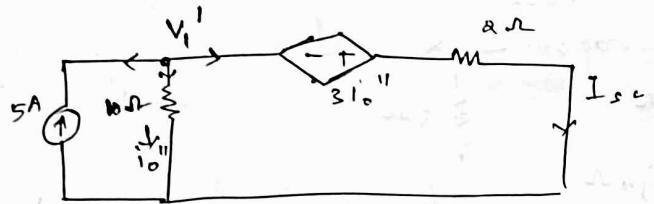

$$\frac{V_1' - 0}{10} = i_o''$$

$$V_1' = 10i_o''$$

$$\frac{V_1' - 0}{10} - 5 \neq I_{sc} = 0$$

$$i_o'' - 5 + I_{sc} = 0$$

$$I_{sc} = 5 - i_o''$$

$$\frac{V_1' - 0}{10} - 5 + I_{sc} = 0$$

$$I_{sc} = 5 - i_o''$$

$$5 - i_o'' = \frac{13i_o'' + 10}{2}$$

$$10 - 2i_o'' = 13i_o'' + 10$$

$$V_1' = 10i_o''$$

$$\frac{5 + V_1' + 3i_o''}{2} - I_{sc} = 0$$

$$10 + V_1' + 3i_o'' = 2I_{sc}$$

$$10 + 10i_o'' + 3i_o'' = 2I_{sc}$$

$$\frac{13i_o'' + 10}{2} = I_{sc}$$

$$5 - i_o''$$

$$V_1' = 10i_o''$$

$$-5 + \frac{V_1' - 0}{10} + \frac{V_1' + 3i_o''}{2} = 0$$

$$-5 + \frac{10i_o''}{10} + \frac{10i_o'' + 3i_o''}{2} = 0$$

$$-5 + i_o'' + \frac{13i_o''}{2} = 0$$

$$-10 + 2i_o'' + 13i_o'' = 0$$

$$15i_o'' = 10$$

$$\frac{V_1' + 3i_o''}{2} = I_{sc}$$

$$I_{sc} = \frac{13 \times \frac{2}{3}}{2}$$

$$= \frac{26}{2 \times 3}$$

$$= \underline{\underline{\frac{13}{3} A}}$$

$$i_o'' = 2/3$$

$$P_{max} = \frac{V_{oc}^2}{4R_{Th}}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{65}{15/3} = \underline{\underline{15\Omega}}$$

$$P_{max} = \frac{65^2}{4 \times 15} = \underline{\underline{70.416 W}}$$

15/12/2021


AC analysis.

$x+jy$ - rectangular

$r\angle\theta$ - polar


$$\begin{aligned} & r \angle \theta \\ & + j1 \angle 90^\circ \\ & - j1 \angle 270^\circ \end{aligned}$$

Qn 1)

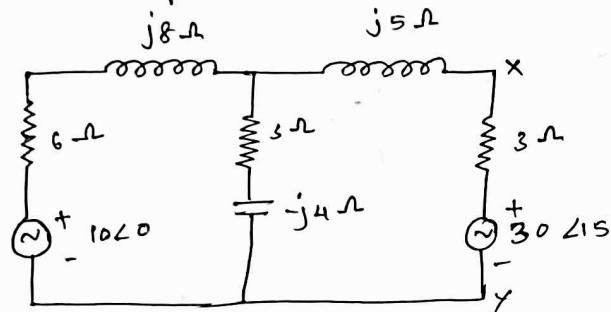

The polarity given is at the an instant

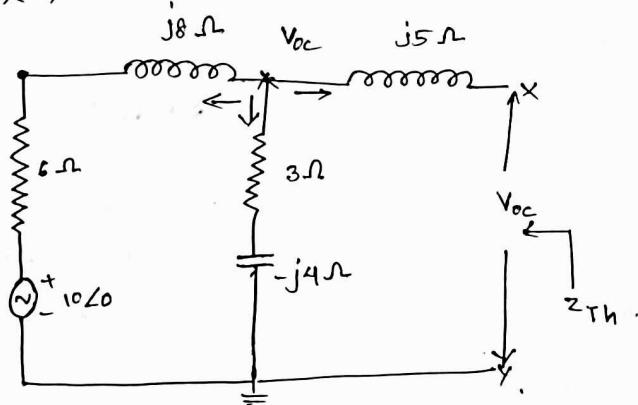Obtain Thvenin equivalent with respect to the terminals X-Y



$$\frac{V_{oc} - 0}{3 - 4j} + \frac{V_{oc} - 10}{6 + 8j} = 0$$

$$\frac{V_{oc}}{3 - 4j} + \frac{V_{oc}}{6 + 8j} - \frac{10}{6 + 8j} = 0$$

$$\frac{V_{oc}}{3 - 4j} + \frac{V_{oc}}{6 + 8j} = \frac{10}{6 + 8j}$$

$$V_{oc} \left[\frac{1}{3 - 4j} + \frac{1}{6 + 8j} \right] = \frac{10}{6 + 8j}$$



$$V_{OC} \left[\frac{6+j8 + 3-j4}{(6+j8)(3-j4)} \right] = \frac{10}{6+j8}$$

$$V_{OC} = \frac{10(3-j4)}{9+j4}$$

$$= 1.13 - 4.94j$$

≈ 50

$$= 5.076 \angle -77.092^\circ V$$

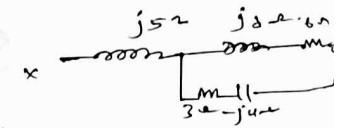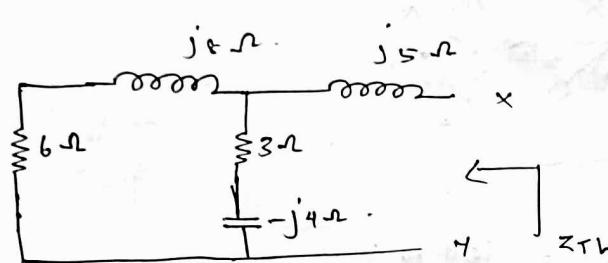

$$\frac{8(6+j8)(3-j4)}{6+j8+3-j4} = \frac{(6+j8)(3-j4)}{9+j4}$$



$$= \frac{450}{9+j4} - \frac{200}{9+j4} j$$

$$z_{Th} = \frac{450}{9+j4} - \frac{200}{9+j4} j$$


$$= \frac{450}{9+j4} + \frac{200}{9+j4} j$$

$$= 5.491 \angle 32.3^\circ$$

Thevenin
Equivalent

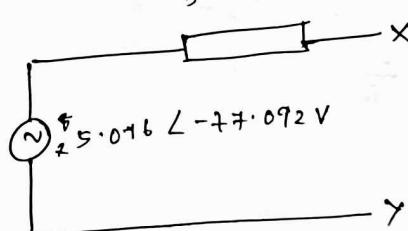
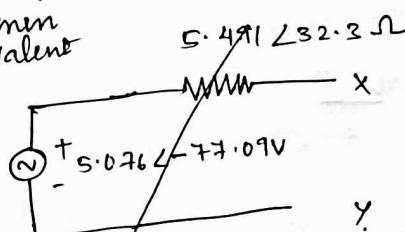


Qn 2)

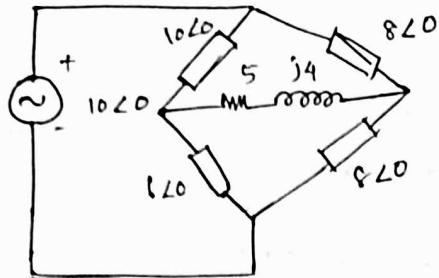

using Thévenin's Theorem
find the current through
the coil $5+j4\ \Omega$ in the
bridge circuit

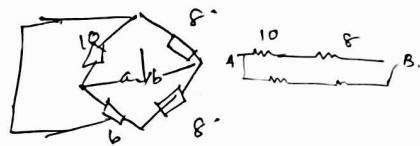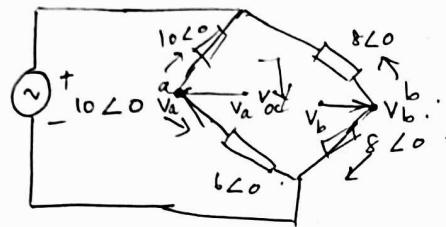Every coil consist
of a resistance in
series with an
inductance



$$\underline{I_1} \quad Z_{th} = 10 \parallel 16 + 8 \parallel 8 \\ = 7.8 \ \Omega$$


$$V_{oc} = V_a - V_b$$

$$\frac{Va}{6} + \frac{Va - 10}{10} = 0$$

$$10V_a + 6V_a - 60 = 0$$

$$16V_a = 60$$

$$V_a = \underline{\underline{3.75V}}$$

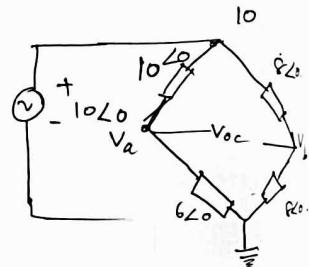

$$\frac{Vb}{8} + \frac{Vb - 10}{8} = 0$$

$$2Vb = 10$$

$$Vb = \underline{\underline{5V}}$$


$$V_{oc} = V_a - V_b$$

$$= 3.75 - 5$$


$$= \underline{\underline{-1.25\angle 0V}}$$

$$I = \frac{1.25}{7.8 + 5 + 4}$$


$$= 2 \cdot 0.0932 \angle -17.35^\circ$$

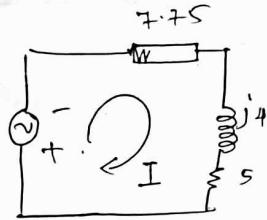

17/12/2021

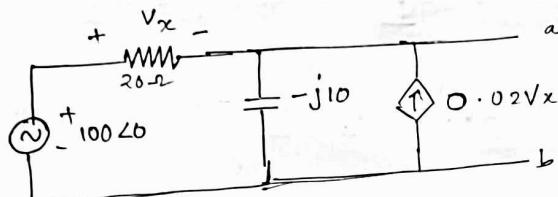

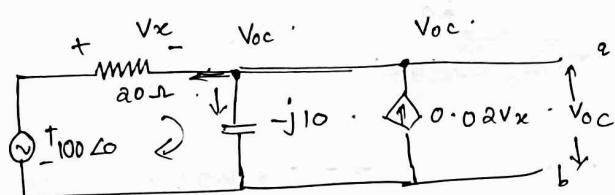Find the Thevenin equivalent of the circuit wrt a & b.



$$-0.02V_x + \frac{V_{oc}}{-j10} + \frac{V_{oc} - 100}{20} = 0$$

$$\frac{V_{oc}}{-j10} + \frac{V_{oc} - 100}{20} = 0.02V_x$$

$$100 - V_x - V_{oc} = 0$$

$$V_x = 100 - V_{oc}$$

$$\frac{V_{oc}}{-j10} + \frac{V_{oc} - 100}{20} = 0.02(100 - V_{oc})$$

$$\frac{V_{oc}}{-j10} + \frac{V_{oc} - 100}{20} = 2 - 0.02V_{oc}$$

$$\frac{V_{oc}}{-j10} + \frac{V_{oc} - 100}{20} + 0.02V_{oc} = 2$$

$$V_{oc} \left[\frac{1}{-j10} + 0.02 \right] + \frac{V_{oc} - 100}{20} = 2$$

$$V_{oc} \left[\frac{1 + 0.02j0}{-j10} \right] + \frac{V_{oc} - 100}{20} = 2$$

1 up 2 down


$$V_{oc} \left[\frac{1}{-j10} + 0.02 + \frac{1}{20} \right] - 5 = 2$$

$$V_{oc} = \left[\frac{1 + 0.02 - j10}{-j10} + \frac{1}{20} \right] = 7$$

$$V_{oc} = \left[\frac{20 + 0.4 - 200j - j10}{20 - j10} \right] = 7$$

$$V_{oc} = [0.122 \angle 55] = 7$$

$$V_{oc} = 57.34 \angle -55.0079$$

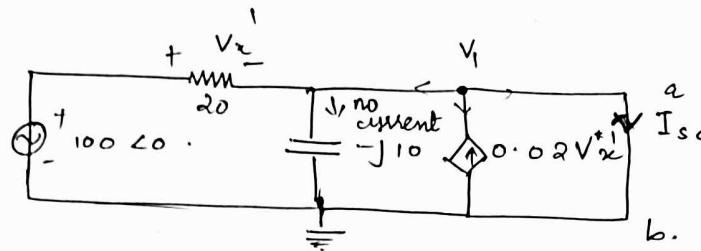

$$V_1 = -0.02V_x' + \frac{V_1 + V_x'}{20} - 100 = 0$$

$$0 = \frac{-100}{20} - 0.02V_x' + I_{sc} = 0$$

$$-5 - 0.02V_x' + I_{sc} = 0$$

$$V_x' = 100 - 0$$


$$V_x' = 100$$

$$-5 - 0.02 \times 100 + I_{sc} = 0$$


$$\cancel{I_{sc}} = 7A$$

$$Z_{Th} = \frac{57.34 \angle -55.0079}{7}$$


$$= 8.191 \angle -55.0079 \Omega$$

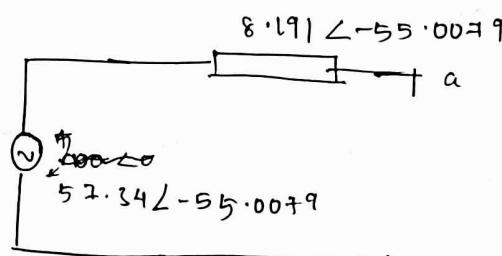

Qn)

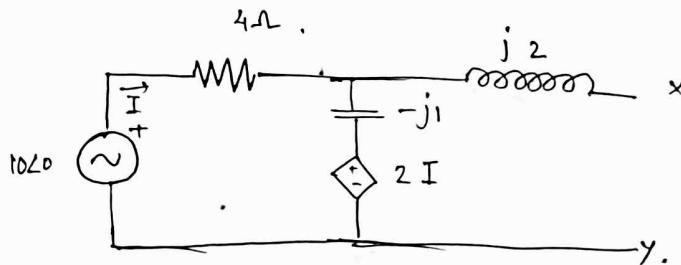

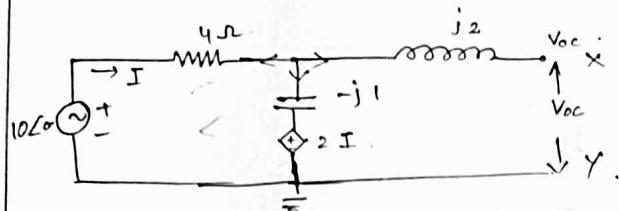obtain the Thevenin & Norton equivalent circuit



$$\frac{V_{oc} - 10}{4} = I .$$

$$\frac{V_{oc} - 2I}{-j1} + \frac{V_{oc} - 10}{4} = 0$$

$$V_{oc} = 10$$

$$\cancel{\frac{V_{oc} - 2I - 2\left(\frac{V_{oc} - 10}{4}\right)}{-j1} + \frac{V_{oc} - 10}{4} = 0}$$

$$\cancel{\frac{2V_{oc} - V_{oc} + 10}{-j2} + \frac{V_{oc} - 10}{4} = 0} .$$


$$\cancel{\frac{V_{oc}}{-j1} + \frac{V_{oc}}{4} + \frac{10}{-j1} - \frac{5}{2} = 0} .$$

$$\cancel{V_{oc} \left[\frac{1}{-j1} + \frac{1}{4} \right] = \frac{5}{2} - \frac{10}{-j1}}$$

$$V_{oc} = \underline{\underline{3.674 \angle -17.1^\circ V}} .$$

$$I_{sc} = 2.71 \angle -102.53^\circ$$
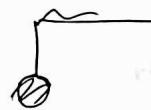
$$Z_{th} = 1.356 \angle 85^\circ \frac{43\Omega}{43\Omega}$$



$$\frac{V_{oc} - 2\left(\frac{10 - V_{oc}}{4}\right) + \frac{V_{oc} - 10}{4}}{-j1} = 0 .$$


$$\cancel{\frac{2V_{oc} - 20 + 2V_{oc}}{-j2} + \frac{V_{oc} - 10}{4} = 0} .$$

$$\cancel{\frac{2V_{oc} - 10 + V_{oc}}{-j2} + \frac{V_{oc} - 10}{4} = 0} .$$

$$\cancel{\frac{3V_{oc}}{-j2} - \frac{10}{-j2} + \frac{V_{oc}}{4} - \frac{10}{4} = 0} .$$

$$V_{oc} \left[\frac{3}{-j2} + \frac{1}{4} \right] = \frac{5}{2} + \frac{10}{-j2} .$$
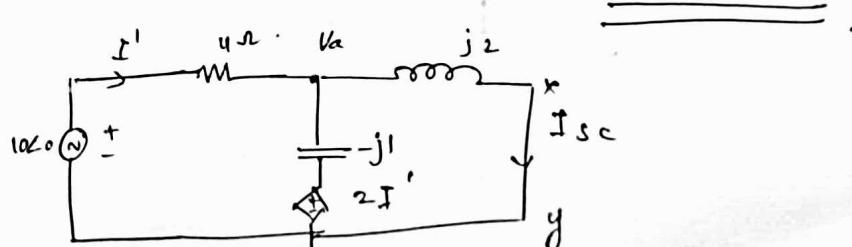
$$\underline{\underline{3.674 \angle -17.1^\circ V}} .$$



$$I_{sc} - J' - \frac{V_a - 2J'}{-j_1} = 0$$

$$\frac{V_a}{j_2} = I_{sc}$$

$$I_{sc} - \left(\frac{10 - V_a}{4} \right) - \left(\frac{V_a - 2(10 - V_a)}{-j} \right) = 0$$

$$I_{sc} - \frac{10}{4} + \frac{V_a}{4} + \frac{V_a}{-j} - \frac{1}{2j}(10 - V_a) = 0$$

$$I_{sc} \left(i + j_2 + \frac{2j_2}{j_2} \right) - \frac{10}{4} + \frac{10}{2j} = 0$$



$$I_{sc} [4 + j_2] = \frac{5}{2} - \frac{10}{2j}$$

$$I_{sc} = \frac{5.59 \angle 63.43}{4 + 2j}$$

$$= 2.71 \angle -102.53$$


$$Z_{Th} = \frac{3.674 \angle -17.1}{2.71 \angle -102.53}$$

$$= 1.355 \angle 85.43 \Omega$$

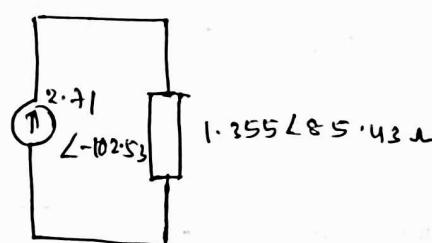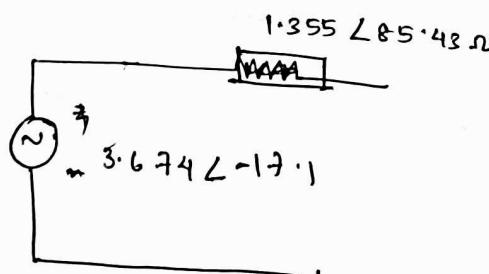


Superposition Theorem

Qn)

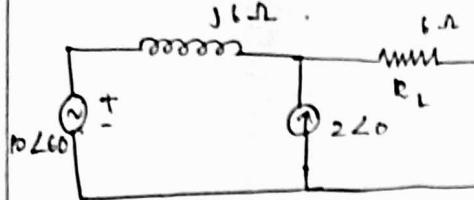


Find the current through the resistor R_L using superposition


$$I = 3.362 \angle 94.48^\circ A$$

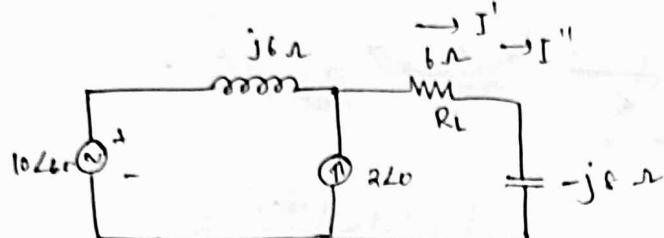

$$I = I' + I''$$

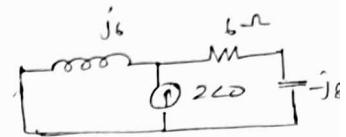
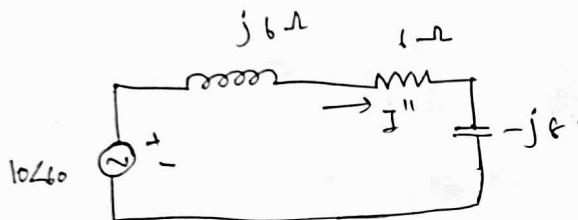
$$I' = \frac{10 \angle 60}{j6 + j6 - j8} = 1.9 \angle 108.43^\circ$$




$$I'' = \frac{10 \angle 60}{j6 + j6 - j8} = \frac{10 \angle 60}{j12} = 1.58 \angle 78.43^\circ A$$

$$I = I' + I''$$

$$= 3.362 \angle 94.48^\circ A$$


Qn)

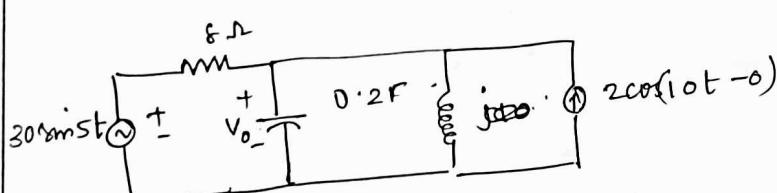

$$\text{Voltage source } 30 \sin 5t \\ = 30 \cos(5t - 90^\circ)$$

$$\therefore 30 \angle -90^\circ$$
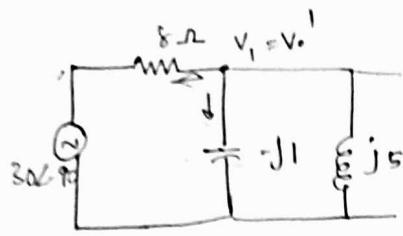
$$\text{Current source } 2 \cos(10t - 90^\circ) \\ 2 \angle 0^\circ$$



$$X_L = \frac{1}{j\omega c}$$


$$= -j$$

$$5 \times 0.2$$

$$= -j1$$

$$\frac{V_o^{'}}{8} + \frac{V_o^{'}}{-j1} + \frac{V_o^{'}}{j5} = 0$$

$$V_o^{' = } 4.681 \angle -171.1^\circ$$

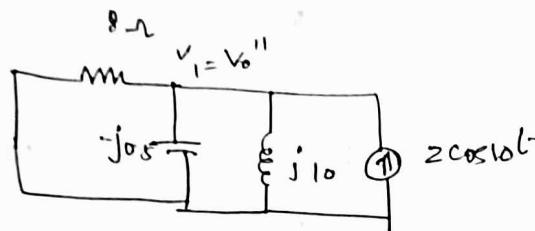

$$X_L = \frac{1}{j\omega c}$$

$$= \frac{1}{j10 \times 0.2}$$

$$= -j0.5$$

$$X_L = j\omega L$$

$$= j \times 10 \times 1$$

$$= j10$$

$$\frac{V_o^{''}}{8} + \frac{V_o^{''} - 0}{-j0.5} + \frac{V_o^{''}}{j10} = 2$$

$$V_o^{''} = 1.05 \angle -86.24^\circ$$


$$V_o = V_o^{' + V_o^{''}}$$

$$= 4.681 \cos(5t - 171.1^\circ) + 1.05$$

$$205(10t - 86.24)$$

,

maximum power transfer theorem (AC).

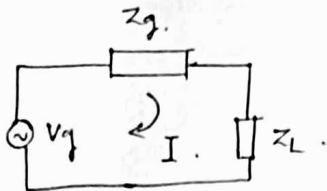

$$I = \frac{V_g}{Z_g + Z_L} = \frac{V_g}{(R_g + jX_g) + (R_L + jX_L)}$$

$$P_L = I^2 R_L = \frac{V_g^2 R_L}{(R_g + R_L)^2 + (X_g + X_L)^2}$$

assume R_L is fixed,

for maximum power transfer $\frac{\partial P_L}{\partial X_L} = 0$

$$\frac{\partial P_L}{\partial X_L} = \frac{0 - V_g^2 R_L \times 2(X_g + X_L)}{\left[(R_g + R_L)^2 + (X_g + X_L)^2 \right]^2} = 0$$

$$X_g = -X_L \quad \text{--- (1)}$$

$$P_L = \frac{V_g^2 R_L}{(R_g + R_L)^2}$$

assume R_L is variable $\frac{\partial P_L}{\partial R_L} = 0$

$$\frac{\partial P_L}{\partial R_L} = \frac{(R_g + R_L)^2 V_g^2 - V_g^2 R_L \cdot 2(R_g + R_L)}{(R_g + R_L)^4} = 0$$

$$R_g + R_L = -2R_L = 0$$

$$R_g = R_L$$

$$Z_L = Z_g$$

$$= R_s + jX_g$$

$$= R_s - jX_g$$

In AC circuits power P_{max} occurs only when



$$R_g = R_L \quad \& \quad X_g = -X_L$$

$$\therefore Z_g = Z_L^*$$

$$P_L = \frac{V_g^2}{4R_L} = \frac{V_g^2}{4R_g}$$

when load impedance is the complex conjugate of source impedance Power max transfer occurs.

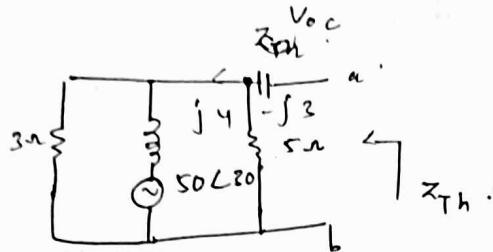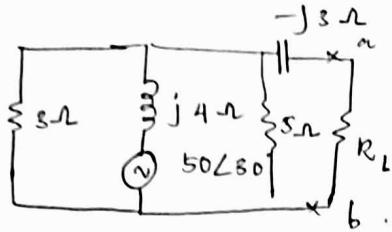Qn) what should be the value of R_L so the max power can be transferred from the source to R_L .




$$\frac{V_{oc}}{3} + \frac{V_{oc}}{j4} - \frac{50 \angle 80}{j4} + \frac{V_{oc}}{3} = 0$$

$$\frac{V_{oc}}{j4} + \frac{V_{oc}}{5} + \frac{V_{oc}}{3} = \frac{50 \angle 80}{j4}$$

$$V_{oc} \left[\frac{1}{j4} + \frac{8}{15} \right] = \frac{50 \angle 80}{j4}$$

$$V_{oc} \left[\frac{1}{j4} + \frac{8}{15} \right] = \frac{25}{2} \angle -60^\circ$$

$$V_{oc} = 21.22 \angle -34.84^\circ$$

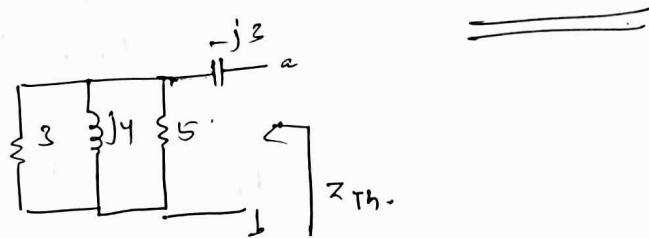

$$Z_{Th} = -j3 + (3||j4||5)$$

$$= -j3 \rightarrow$$

$$= (1.537 - 2.27j) \Omega$$



$$Z_L = Z_g^*$$

$$R_L = R_g$$

$$X_L = -X_g$$

$$P_{max} = \frac{V_{oc}^2}{4R_L} = \frac{(21.22)^2}{4 \times 1.537} = \underline{\underline{73.18W}}$$

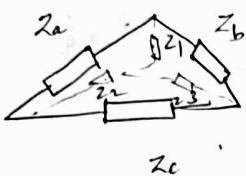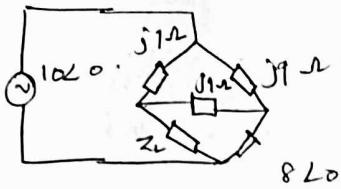Find the value of Z_L to have maximum power transfer from $10\angle 0^\circ$ voltage source. Also determine the amount of maximum power.




Delta to star

$$Z_1 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$
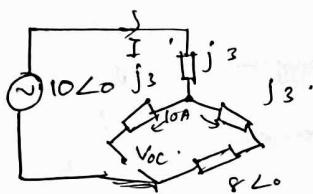
$$Z_3 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$




$$I = \frac{10}{j_3 + j_3 + 8}$$

$$V_{oc} = I (j_3 + 8)$$

$$= \cdot \frac{10}{j_3 + j_3 + 8} (j_3 + 8)$$

$$= 8 \cdot 54 \angle -16.2^\circ$$

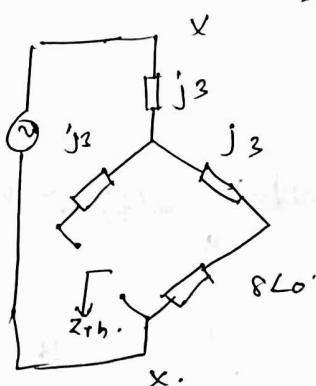

$$Z_{Th} = \frac{j_2 \times (8 + j_2)}{8 + j_3 + j_3} + j_3$$

$$= (0.72 + j 5.46) \angle 0^\circ$$

$$Z_L = 0.72 - j 5.46$$

$$\text{P}_{max} = \frac{V_{oc}^2}{4R_L} = \frac{(8.54)^2}{4 \times 0.72} = \underline{\underline{25.32W}}$$