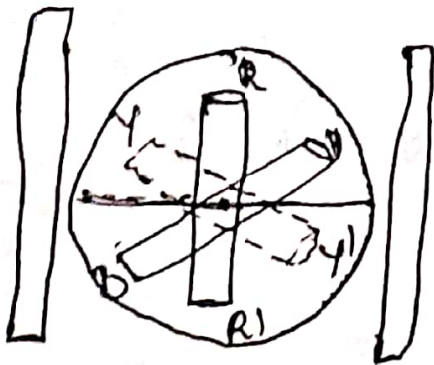


$$\text{Power Factor} = \frac{\text{Active power}}{\text{Apparent power}} = \frac{P}{S}$$


Module

## 3 phase a-c Circuit

- \* \*
- \* Power loss is less
- \* 3 phase motor has a uniform torque
- \* " Generators can work in  $\Delta$  without any difficulties.
- \* Induction motor are self starting, cheaper & more efficient.



120° each

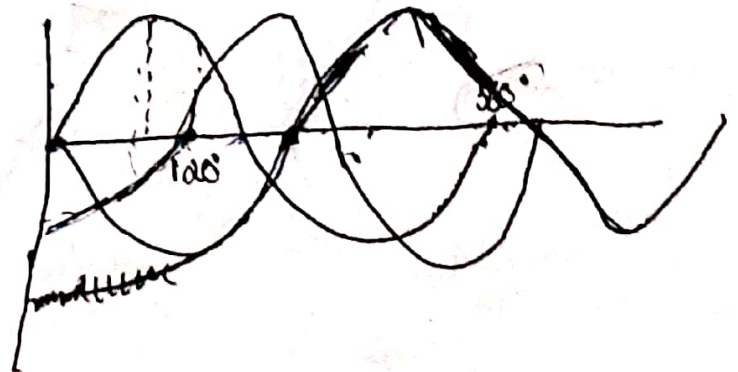


$$V_m \sin \omega t$$

$$V_y = V_m \sin(\omega t - 120^\circ)$$


$$V_b = V_m \sin(\omega t - 240^\circ) = V_m \sin(\omega t + 120^\circ)$$

Phase Sequence - RYB  
RBY

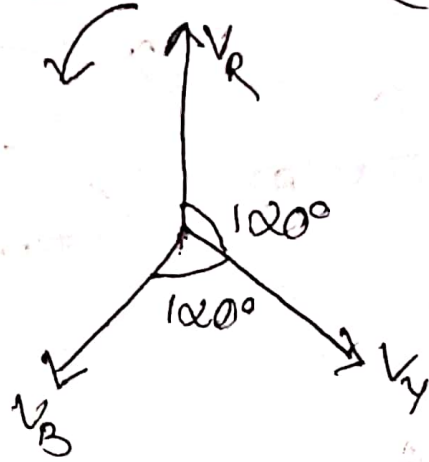

14/11/19


Star connection

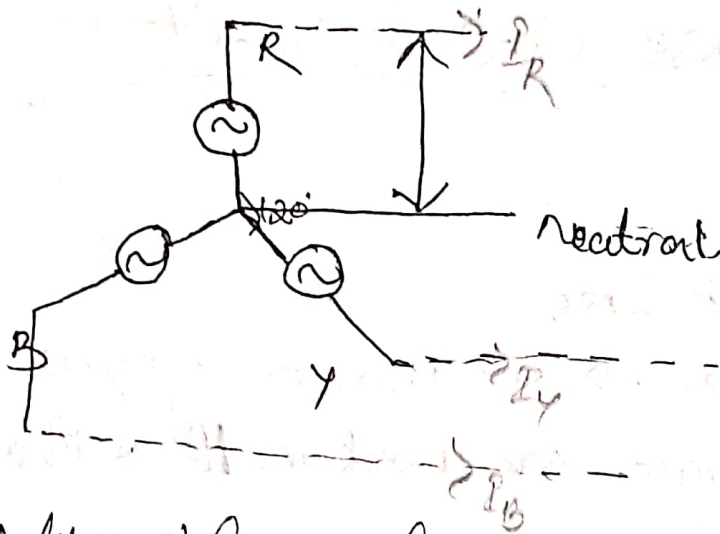

~~Voltage~~  
Voltage b/w  
a line & neutral  
3 phase voltage.

Voltage b/w 2 lines : line voltage.

Balanced 3 phase Systems:  $|V_R| = |V_B| = |V_Y|$

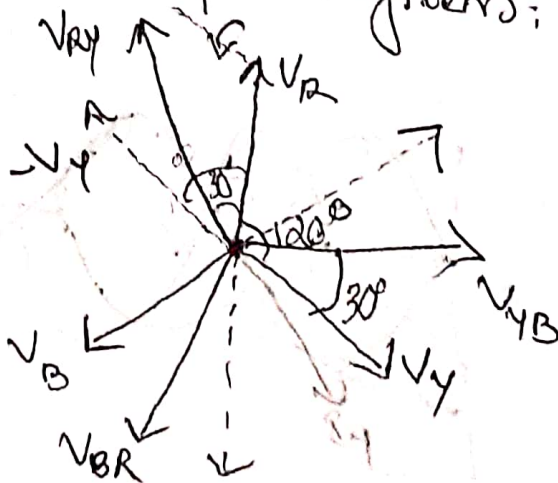

$$V_{RY} = V_R - V_Y$$

$$V_{RY} = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \times \frac{1}{2}} = \sqrt{3} V_L / 2 = \sqrt{3} V_{\text{phase}}$$

$$V_{\text{phase}} = \frac{V_L}{\sqrt{3}}$$

$$I_R = I_m \sin \omega t$$

$$I_m \sin (\omega t - 120^\circ)$$


$$I_B = I_m \sin (\omega t - 240^\circ)$$

Current will be same (star connected) System.

$$V_p = \frac{V_L}{\sqrt{3}}$$

$$I_N = I_R + I_Y + I_B \text{ in unbalanced}$$

$$\text{Balance} \Rightarrow I_N = 0$$

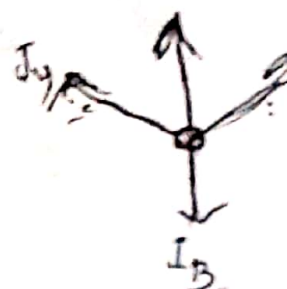

$$\sin(\theta + 120) + \sin(\theta + 240) = 0$$


Power In Balanced, power  $\Rightarrow P = 3 V_L I_L \cos \phi$

$$= 3 V_{ph} I_{ph} \cos \phi = 3 \frac{V_L I_L}{\sqrt{3}} \cos \phi$$

$$= \sqrt{3} V_L I_L \cos \phi$$

$\phi$  - angle b/w phase voltage & phase current

Delta Connection (Mesh connected)

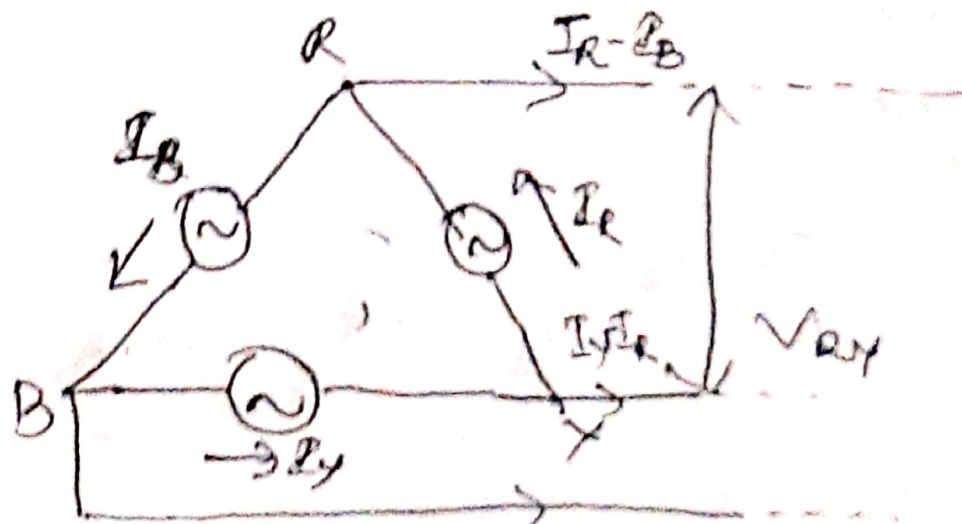

Line voltage or phase voltage are Same.

Current thro a line  $\rightarrow$  line current