

24/09/2020

Module IILaplace Transform.

Time domain analysis is the conventional method of analysing network for higher order differential equation of network variable, frequency domain analysis using Laplace transform is very convenient.

① Solution of differential equation in a systematic procedure.

② Initial conditions are automatically incorporated.

③ It gives the complete solution i.e., both complementary and particular solution in one step.

Laplace transformation :-

$$F(s) = L \{ f(t) \} = \int_0^{\infty} f(t) e^{-st} dt$$

where  $s$  is the complex frequency variable

$$s = \sigma + j\omega$$

The function  $f(t)$  must satisfy following condition.

$$\int_0^{\infty} |f(t)| e^{-\sigma t} dt < \infty \quad \text{where } \sigma \text{ is real & +ve.}$$

Inverse Laplace transform.  $L^{-1} \{ F(s) \}$

$$f(t) = \frac{1}{2\pi j} \int_{\sigma - j\infty}^{\sigma + j\infty} F(s) e^{st} ds$$

$$f(t)$$

$F(s)$  - Laplace form

$$k$$

$$k/s$$

for initial value of  $f(t)$  at  $t=0$  we have  $f(0) = 1/s$

for a function  $t^n$  we have  $\frac{n!}{s^{n+1}}$

$$\text{for } t^2 \quad \frac{2!}{s^{2+1}} = \frac{2!}{s^3}$$

for  $\delta(t)$  we have  $\frac{1}{s^2}$

for  $e^{at}$  we have  $\frac{1}{s-a}$

$$\text{for } \sin \omega t \quad \frac{1}{s^2 + \omega^2}$$

$$\text{for } \cos \omega t \quad \frac{1}{s^2 + \omega^2}$$

for  $\sinh \omega t$  we have  $\frac{\omega}{s^2 - \omega^2}$

for  $\cosh \omega t$  we have  $\frac{\omega}{s^2 - \omega^2}$

for  $e^{-at} \sin \omega t$  we have  $\frac{\omega}{(s+a)^2 + \omega^2}$

for  $e^{-at} \cosh \omega t$  we have  $\frac{s}{(s+a)^2 - \omega^2}$

for  $e^{-at} \sinh \omega t$  we have  $\frac{\omega}{(s+a)^2 - \omega^2}$

$$e^{-at} \cos \omega t \quad \frac{s+a}{(s+a)^2 + \omega^2}$$

$$e^{-at} \sin \omega t \quad \frac{\omega}{(s-a)^2 + \omega^2}$$

$$e^{at} \cos \omega t \quad \frac{s-a}{(s-a)^2 + \omega^2}$$

$$t \cdot e^{at} \quad \frac{1}{(s-a)^2}$$

$$t \cdot e^{-at} \quad \frac{1}{(s+a)^2}$$

Q1 Find the Laplace transform of  $4t^2 + \sin 3t + e^{at}$

$$\begin{aligned} F(s) &= L\left[4t^2 + \frac{3}{s^2+9} + \frac{1}{s-a}\right] \\ &= \frac{8}{s^3} + \frac{3}{s^2+9} + \frac{1}{s-a} \end{aligned}$$

Initial value theorem:  $\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s)$   
 $L[f(t)] = f(s)$  then  $\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s)$

Final value theorem

$$\text{If } L[f(t)] = F(s) \text{ then } \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$$

Q. Find the inverse Laplace transforms of  $\frac{s^2 - 3s + 4}{s^3}$ .

Ans. Results

$$F(s) = \frac{s^2}{s^3} - \frac{3s}{s^3} + \frac{4}{s^3}$$

$$= \frac{1}{s} - \frac{3}{s^2} + \frac{4}{s^3}$$

$$f(t) = 1 - 3t + 4t^2.$$

$$t^2 = \frac{4}{s^3}$$

$$\frac{4}{s^3} = 4 \times \frac{1}{s^3}$$

$$= 4t^2$$

26/9/2020

$$Q. \frac{s+2}{s(s+3)(s+1)} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+1}$$

$$= \frac{A(s+3)(s+1) + B(s+1)s + C(s+3)}{s(s+3)(s+1)}$$

$$s+2$$

$$= A(s^2 + 4s + 3) + B(s^2 + s) + C(s^2 + 3s)$$

$$s+2 = As^2 + 4As + 3A + Bs^2 + Bs + Cs^2 + Cs$$

Equating  
coefficients  $s^2 \rightarrow 0 = A + B + C$ .

$$s \rightarrow 4A + B + 3C = 1$$

$$3A + 2B + 3C = 0$$

$$A = \frac{2}{3} \quad B + C = -\frac{2}{3}$$

Sub: A

$$4 \times \frac{2}{3} + B + 3C = 1$$

$$B + C = -\frac{2}{3}$$

$$\frac{8}{3} + B + 3C = 1$$

$$\Rightarrow B + 3C = -\frac{5}{3}$$

$$B + 3C = 1 - \frac{8}{3}$$

$$\Rightarrow B + 3C = -\frac{5}{3}$$

$$\therefore C = \frac{1}{2}$$

$$\begin{aligned}
 B+C &= -2/3 & A &= 2/3 \\
 B &= -2/3 + 1/2 & B &= -1/6 \\
 \underline{\underline{B = -1/6}} & & \underline{\underline{C = -1/2}}
 \end{aligned}$$

$$\frac{s+2}{s(s+3)(s+1)} = \frac{2/3}{s} + \frac{-1/6}{s+3} + \frac{-1/2}{s+1}$$

$$f(t) = \frac{2}{3} + \left(\frac{-1}{6}\right)e^{-3t} + \left(\frac{-1}{2}\right)e^{-t}$$

Q. Find inverse transform of

$$\frac{s+2}{s^2(s+3)}$$

$$F(s) = \frac{s+2}{s^2(s+3)} \quad (s-2)A = 11 - 2s - s^2$$

$$\frac{s+2}{s^2(s+3)} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s^2} \quad s^2(s+3)$$

$$s+2 = As^2 + 3As + Bs + 3B + Cs^2$$

$$11 - 2s - s^2 = As^2 + 3As + Bs + 3B + Cs^2$$

$$\text{Coefficients of } s^2: A + C = 0 \quad 11 = 3A + B$$

$$3A + B = 1$$

$$3B = 2$$

$$B = 2/3$$

$$A + C = 0$$

$$1/9 + C = 0$$

$$C = -1/9$$

$$\boxed{\begin{array}{l} A = 1/9 \\ B = 2/3 \\ C = -1/9 \end{array}}$$

$$3A = 1 - 2/3$$

$$3A = 1/3$$

$$A = 1/9$$

$$\frac{s+2}{s^2(s+3)} = \frac{1/9}{s} + \frac{2/3}{s^2} + \frac{-1/9}{s+3}$$

$$= \underbrace{\frac{1}{9} + \frac{2}{3}t + \left(-\frac{1}{9}\right)e^{-3t}}_{\text{Ans}}$$

Q3.  $\frac{5s^2 - 15s - 11}{(s+1)(s-2)^2}$

$$\frac{5s^2 - 15s - 11}{(s+1)(s-2)^2} = \frac{A}{s+1} + \frac{B}{s-2} + \frac{C}{(s-2)^2}$$

$$5s^2 - 15s - 11 = A(s-2)^2 + B(s+1) + C(s+1)$$

$$= A(s^2 + 4s + 4) + B(s^2 - s - 2) + Cs + C$$

$$5s^2 - 15s - 11 = As^2 + 4As + 4A + Bs^2 - Bs - 2B + Cs + C$$

$$A + B = 5$$

$$-4A - B + C = -15$$

$$4A - 2B + C = -11$$

$$\underline{\underline{B = 4}}$$

$$-4A - B + C = -15$$

$$\cancel{4A (+) 2B + C = 0} \cancel{11}$$

$$\underline{\underline{B = 4}}$$

$$A + B = 5$$

$$A + 4 = 5$$

$$A = \cancel{4} 1$$

~~$$4 \times \cancel{1} - 4 + C = -15$$~~

~~$$-4 + C = -15$$~~

~~$$-16 + C = -15$$~~

$$\underline{\underline{C = 7}}$$

$$4 - 2 \times 4 + C = 11$$

$$4 - 8 + C = -11$$

$$\underline{\underline{C = 7}}$$

$$\begin{array}{l} A = 1 \\ B = 4 \\ C = -7 \end{array}$$

$$A = 1, B = 4, C = -7.$$

$$\begin{aligned} f(s) &= \frac{1}{s+1} + \frac{4}{s-2} - \frac{7}{(s-2)^2} \\ &= e^{-t} + 4e^{2t} - 7te^{2t} \end{aligned}$$


28/9/2020

### The transformed circuit

1, Resistor

$$V(t) = R i(t)$$

$$V(s) = R I(s)$$

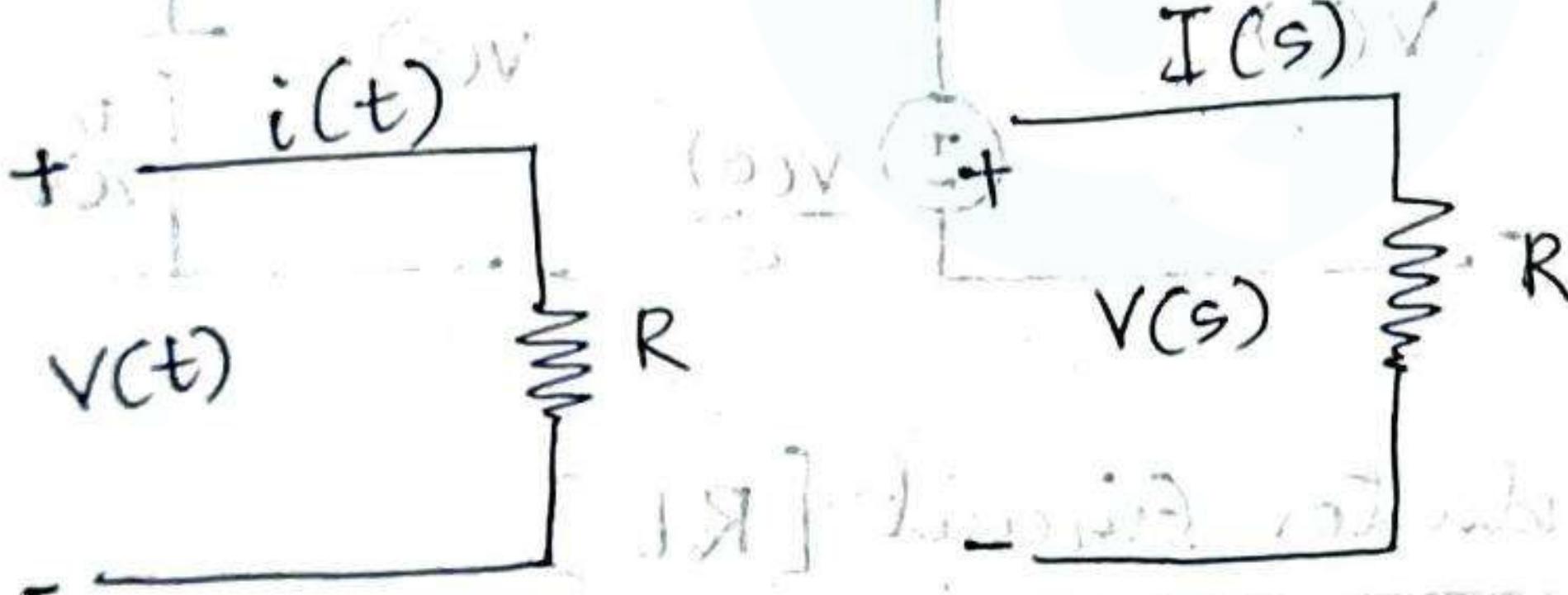


2, Inductor

$$V(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_0^t V(t) dt + i(0)$$

$$V(s) = L(s) \cdot I(s) - L i(0)$$
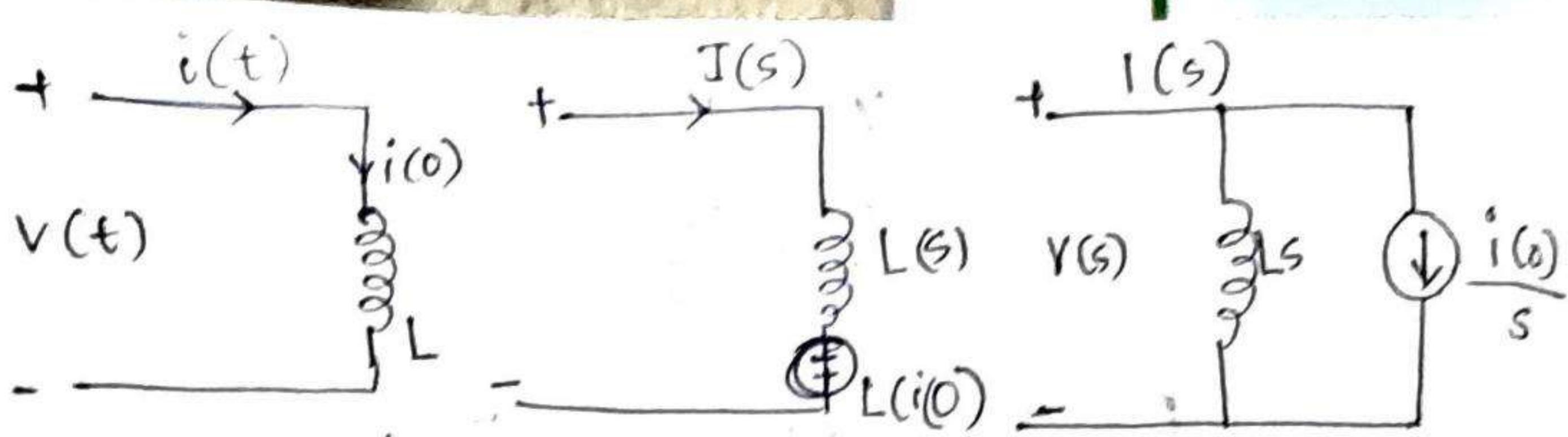
$$I(s) = \frac{1}{Ls} V(s) + \frac{i(0)}{s}$$






### 3. Capacitors

$$V(t) = \frac{1}{C} \int_0^t i(t) dt + V(0)$$

$$i(t) = C \cdot \frac{dV}{dt}$$


$$V(s) = \frac{1}{Cs} I(s) + \frac{V(0)}{s}$$


$$I(s) = (s V(s) - C V(0))$$

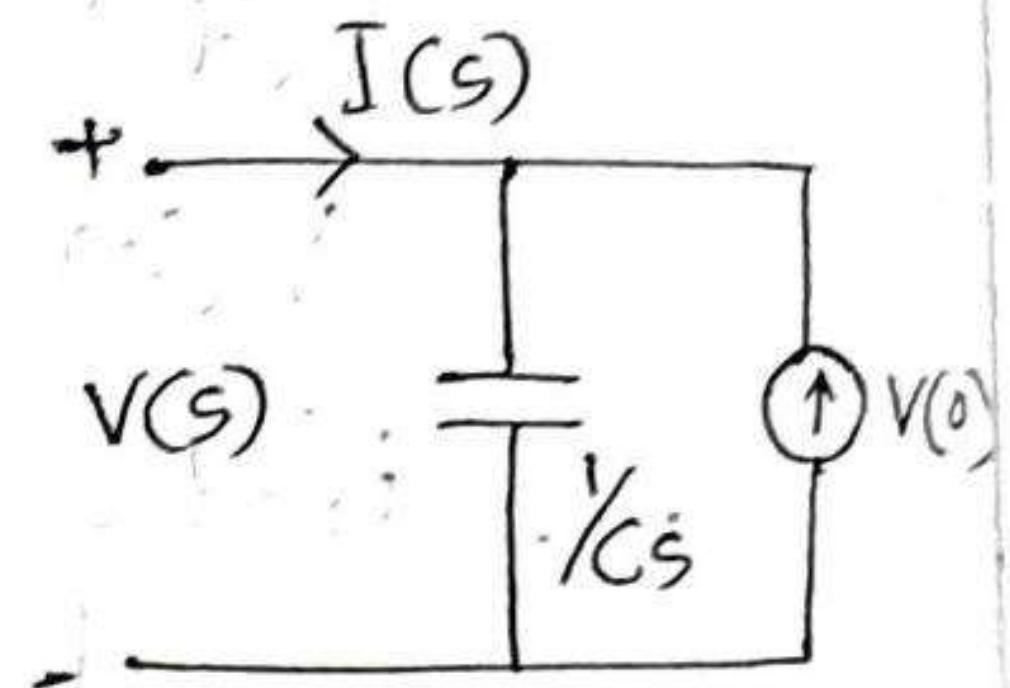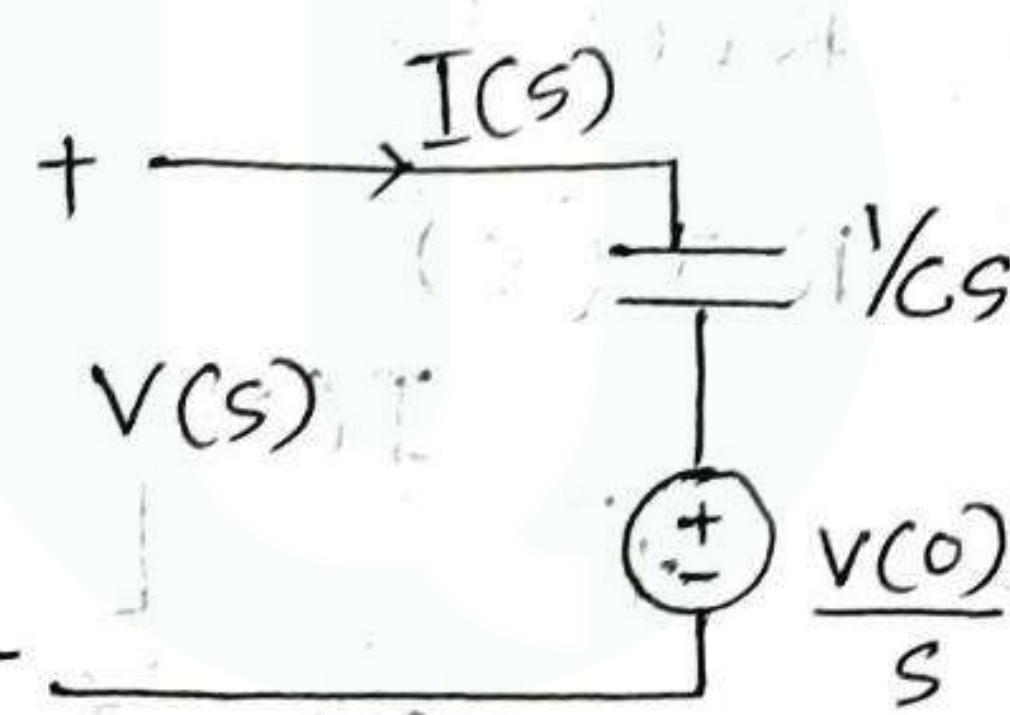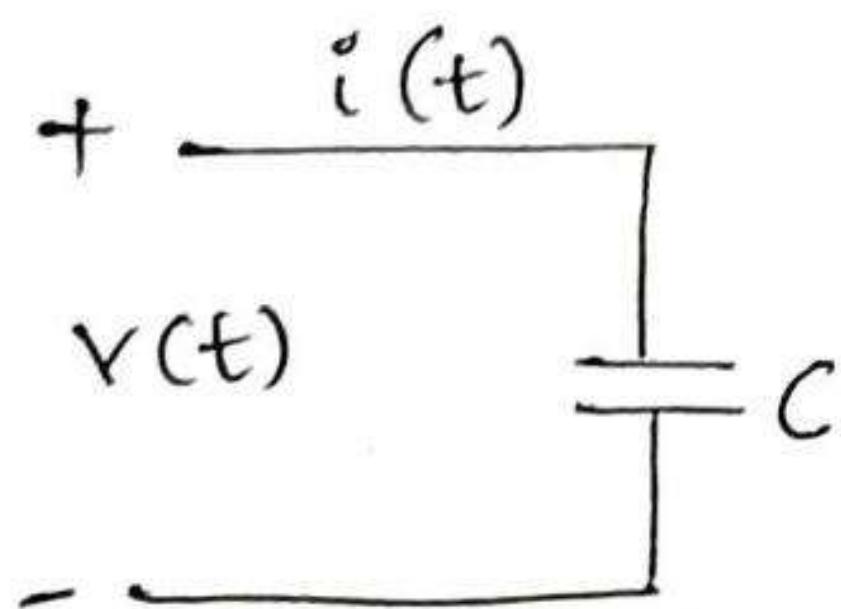
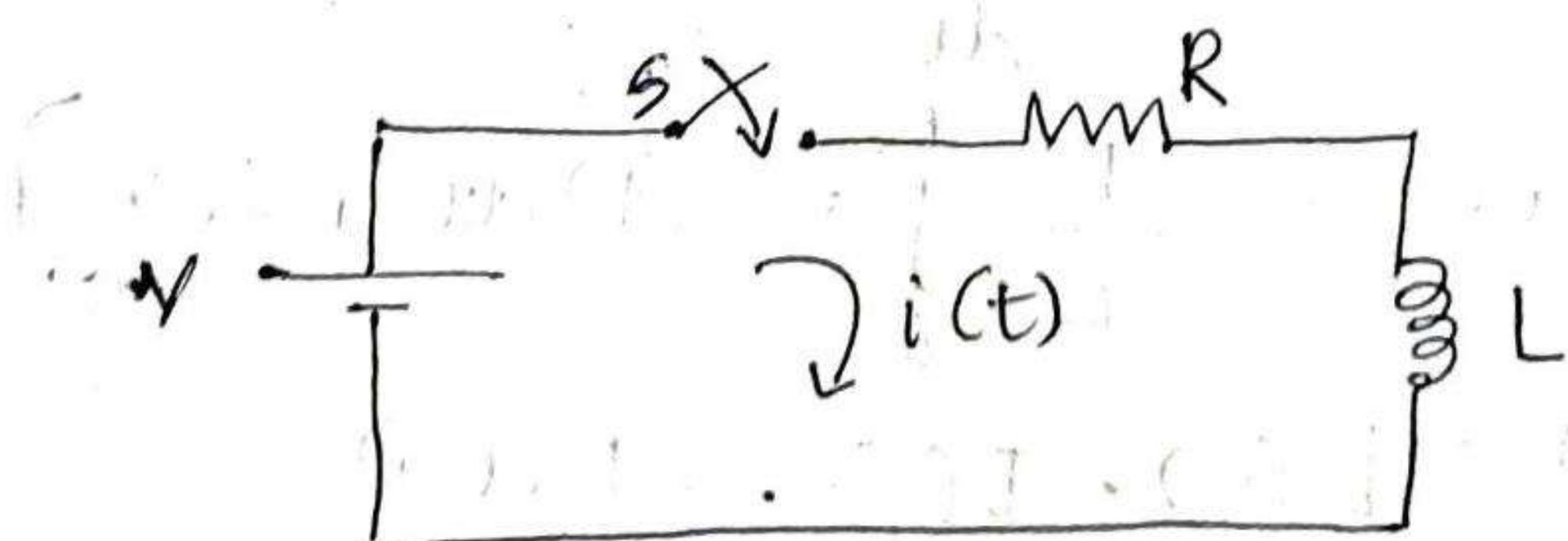
### Resistor - Inductor Circuit [RL]

Consider a series RL circuit as shown in fig. The switch is closed at time  $t=0$ .



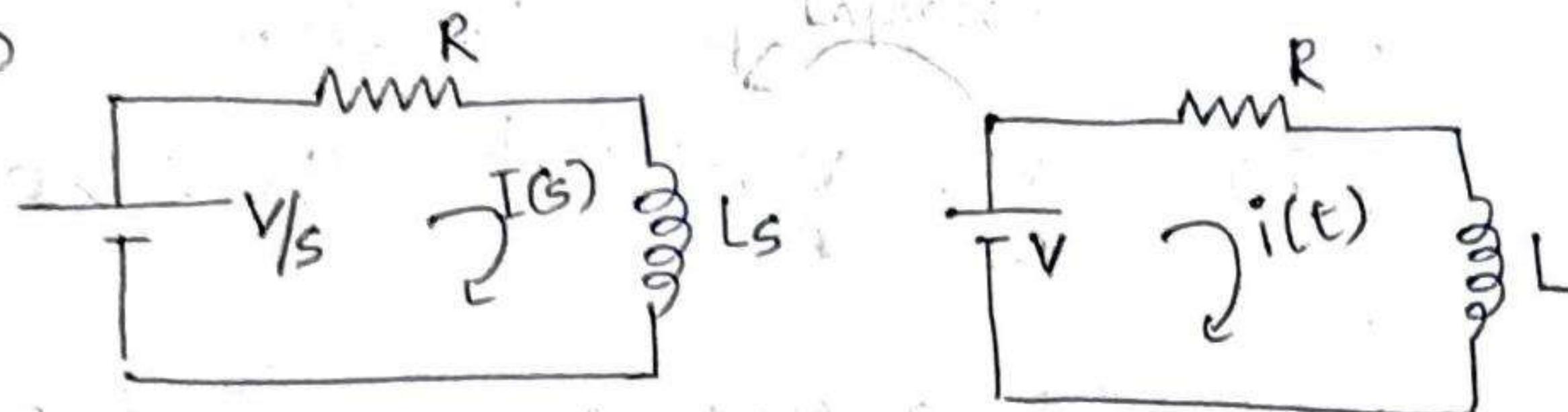For  $t > 0$ 

$$V = R i(t) + L \frac{di(t)}{dt}$$

$$\begin{aligned} \frac{V}{s} &= R I(s) + L \cdot s I(s) \\ &= (R + Ls) I(s). \end{aligned}$$

$$I(s) = \frac{V/s}{R + Ls} = \frac{V}{sL[R/L + s]}$$

$$I(s) = \frac{V/L}{s[s + R/L]}$$

$$I(s) = \frac{A}{s} + \frac{B}{s + R/L}$$

$$A = s_i I(s) \Big|_{s=0}$$

$$= s \times \frac{V/L}{s(s + R/L)} \Big|_{s=0}$$

$$= \frac{V/L}{R/L} = \frac{V}{R} \quad \text{Ans}$$

$$B = (s + R/L) \times \frac{V/L}{s(s + R/L)}$$


$$= \frac{V/L}{-R/L} = -\frac{V}{R}$$

$$I(s) = \frac{V/R}{s} + \frac{-V/R}{s + R/L}$$

Taking inverse Laplace transform

$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-R/L t} \quad \text{for } t > 0.$$

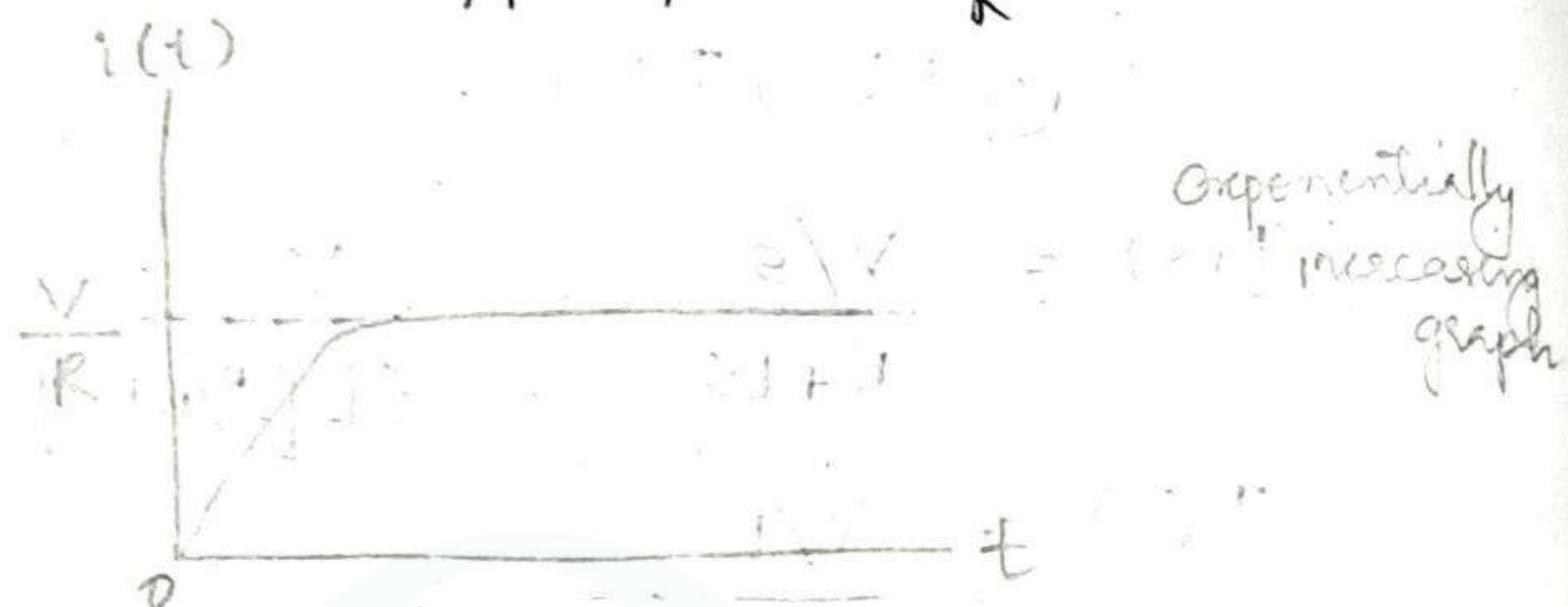The complete response is composed of 2 parts, the steady state response or forced response or zero state response.  $\frac{V}{R}$  and transient response or natural response or zero i/p response  $\frac{V}{R} e^{-R/L t}$ .



current response of R-L circuit

The transient period is defined as the time taken for current to reach its final or steady state value from its initial value.


The term  $\frac{L}{R}$  is called time constant and is denoted by  $\tau$ .  $\tau = L/R$ .

$$\begin{aligned} V_R &= Ri = R \times \frac{V}{R} \left[ 1 - e^{-R/L t} \right] \\ &= V \left[ 1 - e^{-R/L t} \right] \end{aligned}$$

$$V_L = L \frac{di}{dt} = L \frac{V}{R} \frac{d}{dt} \left[ 1 - e^{-R/L t} \right]$$

$$= L \frac{V}{R} \left[ 0 - \left( \frac{-R}{L} \right) e^{-R/L t} \right] \frac{LV}{R} \times \frac{R}{L} e^{-R/L t}$$

$$= V \cdot e^{-R/L t}$$

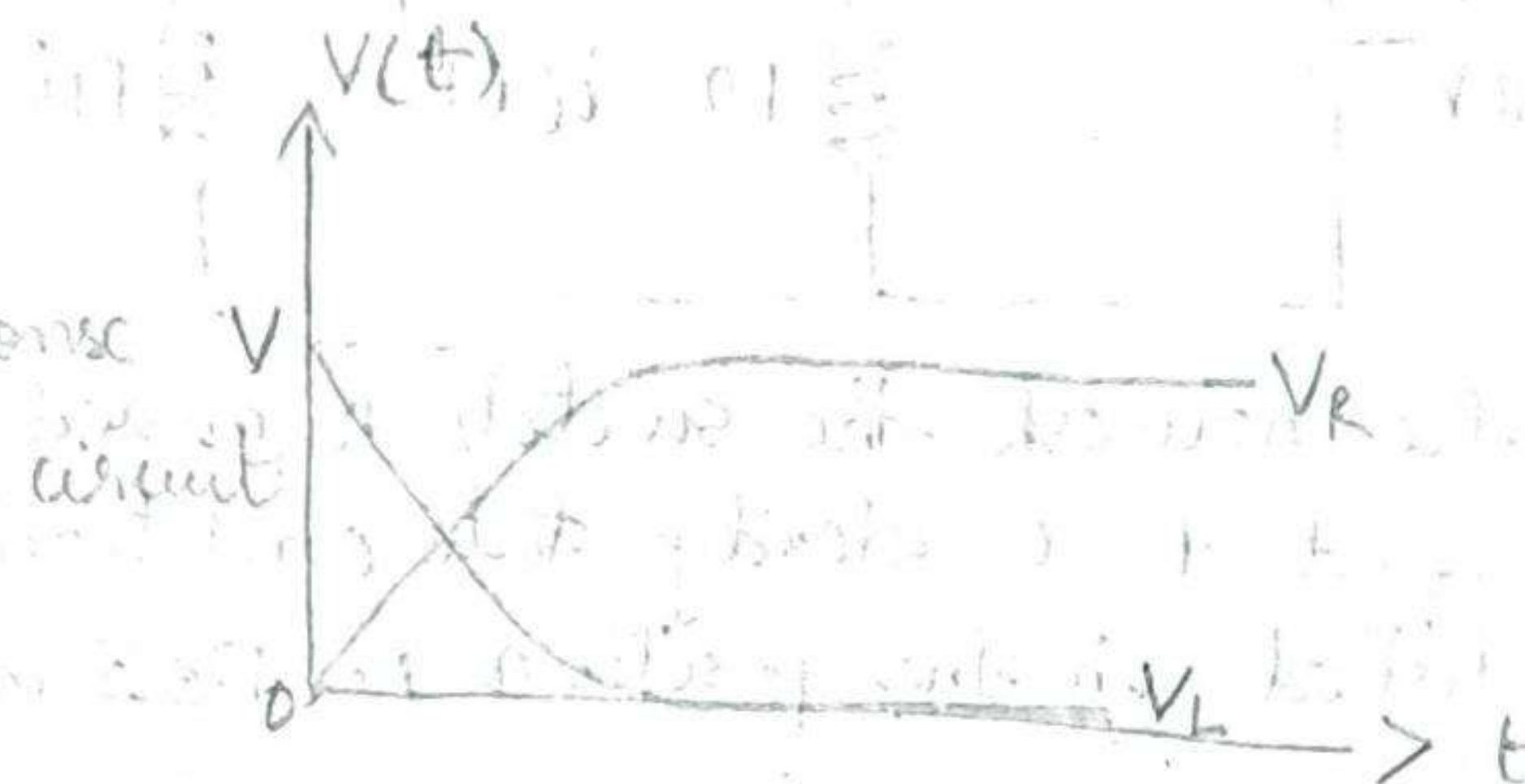

$$Q. \frac{s+2}{s(s+3)(s+1)} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+1}$$

$$\frac{s+2}{s(s+3)(s+1)} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+1}$$

$$A = \left. \frac{s+2}{(s+1)(s+3)} \right|_{s=0} = \frac{2}{3}$$


$$B = \left. \frac{s+2}{s(s+1)} \right|_{s=-3} = \frac{-3+2}{-3 \times -2} = \frac{-1}{6}$$

$$C = \left. \frac{s+2}{s(s+3)} \right|_{s=-1} = \frac{-1+2}{-1(+2)} = -\frac{1}{2}$$

$$\frac{s+2}{s(s+3)(s+1)} = \frac{2/3}{s} + \frac{-1/6}{s+3} + \frac{-1/2}{s+1}$$

$$f(t) = \frac{2}{3} - \frac{1}{6} e^{-3t} - \frac{1}{2} e^{-t}$$

09/09/2020  
Q1,

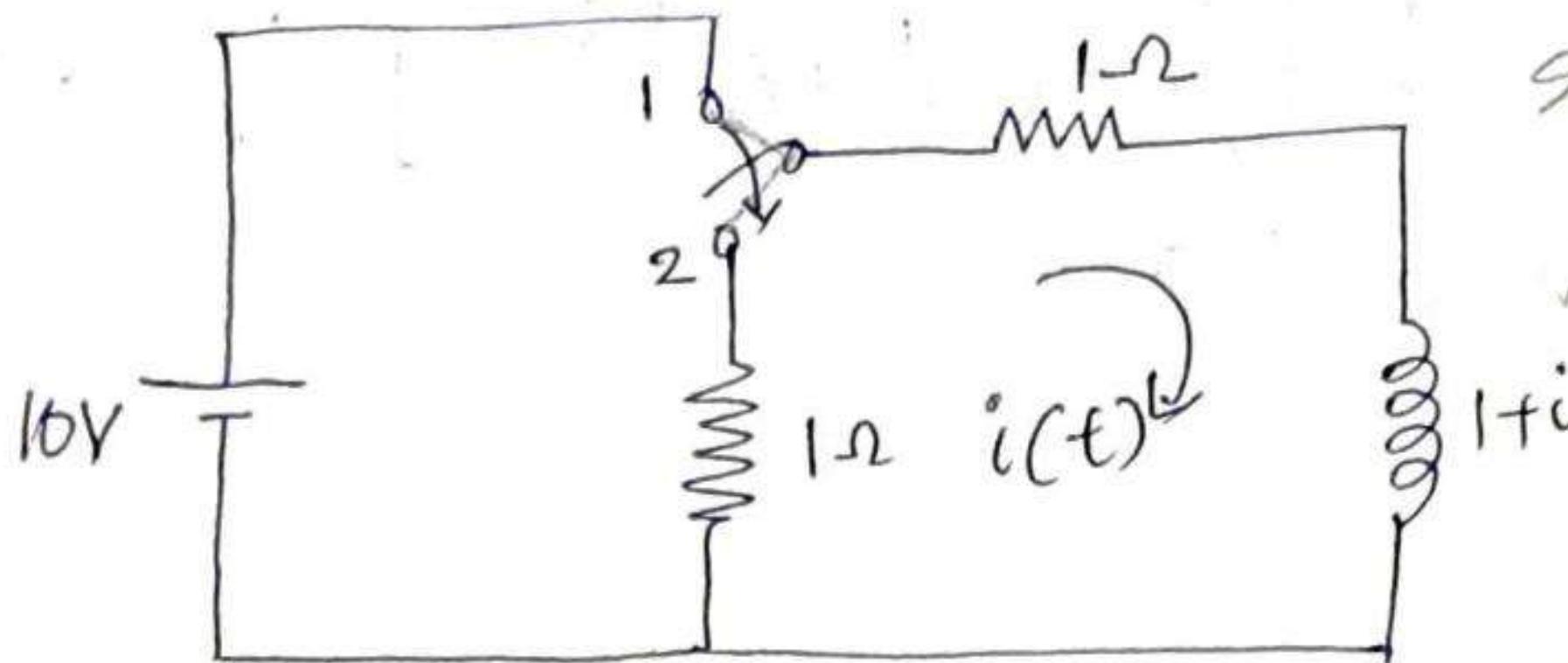

steady state  
→ inductor short


In the network the switch n moved from the position 1 to 2 at  $t = 0$  steady state condition having been established in the position 1. Determine  $i(t)$  for  $t > 0$

Soln: At  $t = 0^-$

the network is shown as below  $\rightarrow$

the network has attained steady state condition,


hence the inductor act as short circuit.

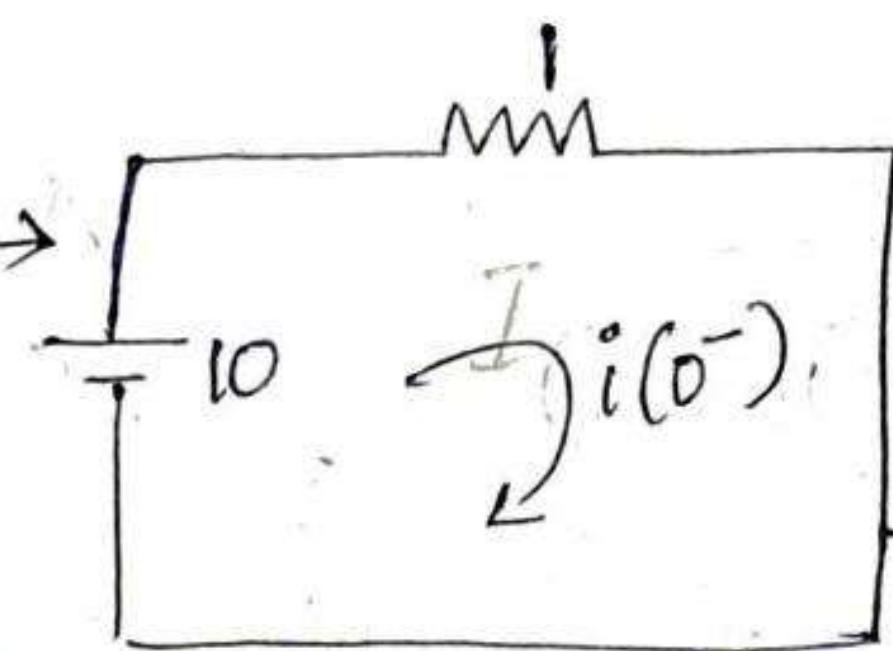

$$i(0^-) = \frac{10}{1} = \underline{10 \text{ A}}$$

Since current in the inductor cannot change simultaneously  $i(0^+) = \underline{10 \text{ A}}$

- for  $t > 0$

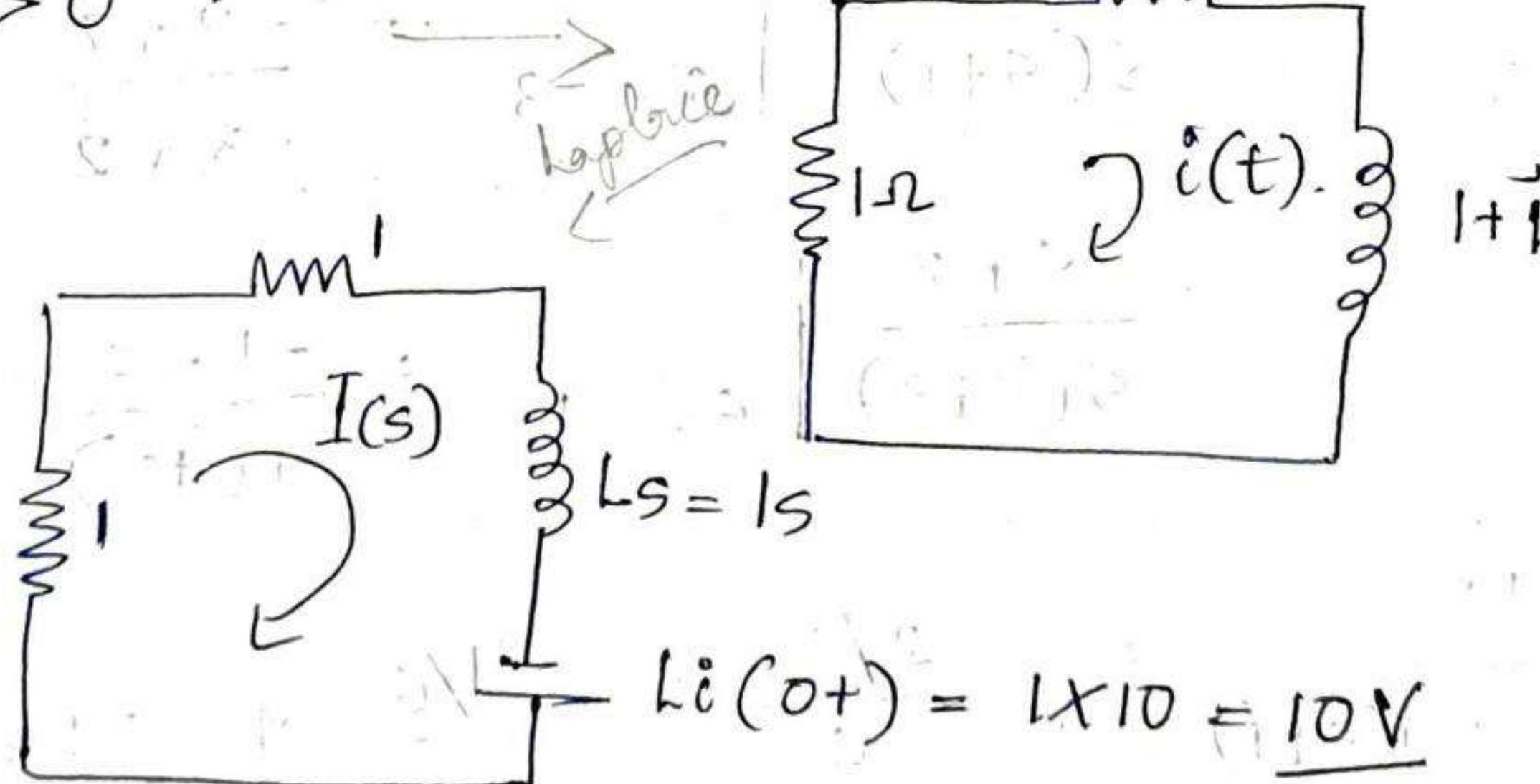

$$+10 = I(s) + J(s) + I_s J(s)$$

$$10 = I(s) (1 + I_s)$$


$$10 = I(s)(s+2)$$

$$I(s) = \frac{10}{s+2}$$

Laplace


$$I(t) = \underline{10 \times e^{-2t}} \quad \text{for } t > 0$$

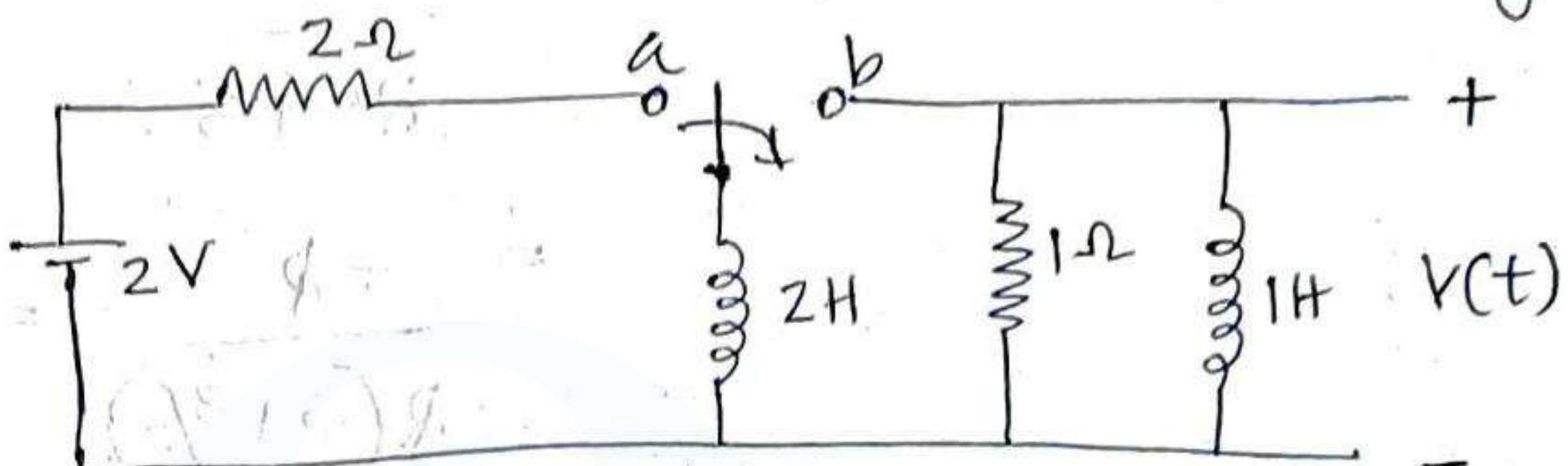Q2, The network was initially in the steady state with the switch in the position a. At  $t=0$ , the switch goes from a to b. Find the expression for voltage  $V(t)$ .





At  $t = 0^-$
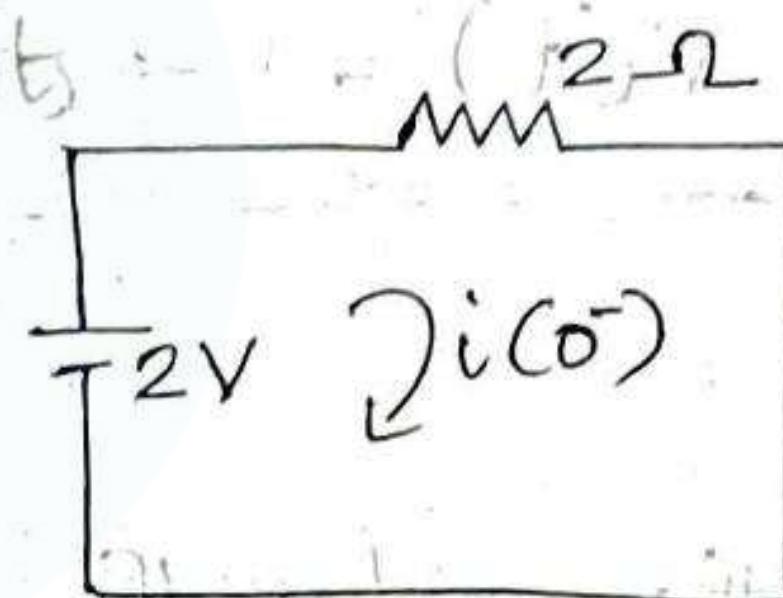
$$i(0^-) = \frac{2}{2} = \underline{1A}$$



so here  $i(0^+) = \underline{1A}$

At  $t = 0^+$

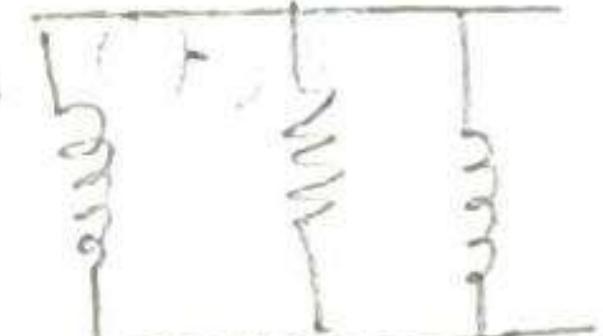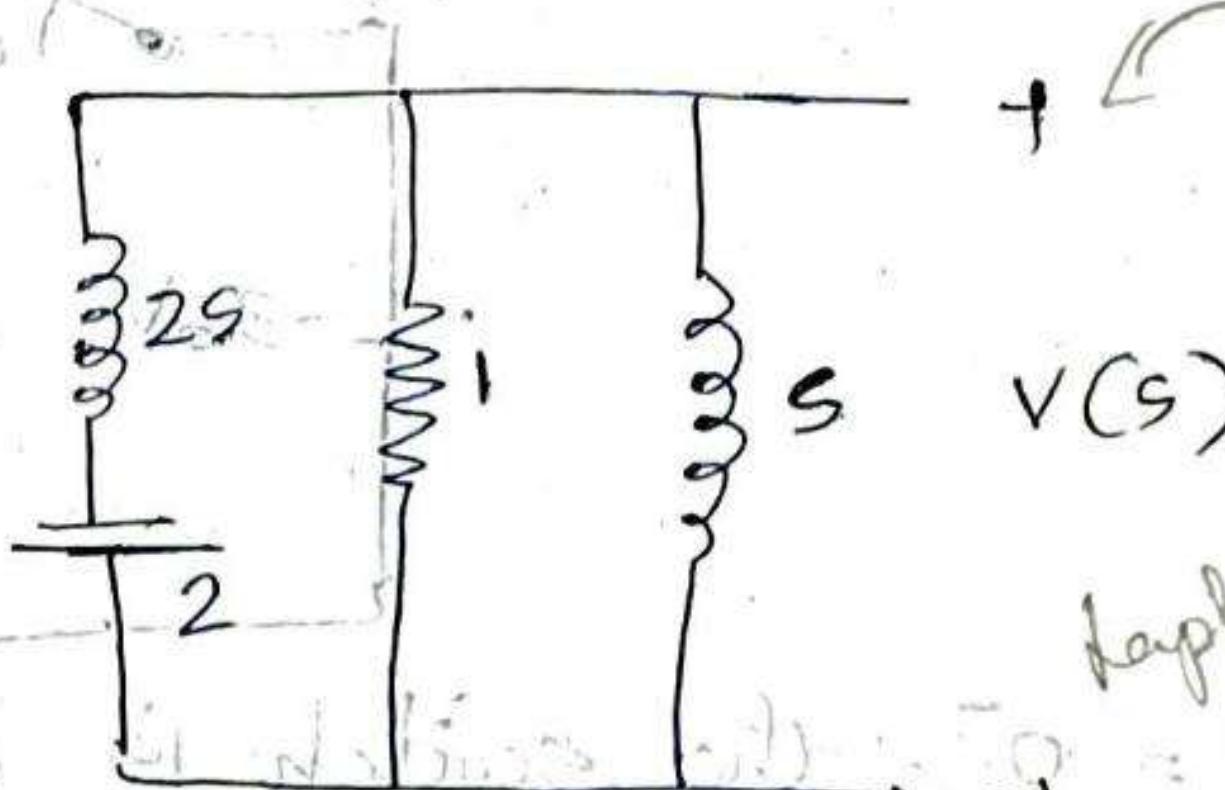

Nodal analysis

$$\frac{V(s)+2}{2s} + \frac{V(s)}{1} + \frac{V(s)}{s} = 0$$

$$\frac{V(s)}{2s} + \frac{2}{2s} + V(s) + \frac{V(s)}{s} = 0$$

$$V(s) \left[ \frac{1}{2s} + 1 + \frac{1}{s} \right] = -\frac{1}{s}$$

$$V(s) \left[ \frac{1}{2s} + \frac{s+1}{s} \right] = -\frac{1}{s}$$

$$V(s) \left[ \frac{s+2s^2+2s}{2s^2} \right] = -\frac{1}{s}$$

$$V(s) \left[ \frac{s(1+2s+2)}{2s^2} \right] = -\frac{1}{s}$$


$$V(s)(1+2s+2) = -\frac{1}{s} \times 2s$$

$$V(s) = \frac{-2}{2s+3}$$


$$= \frac{-2}{2(s+3/2)} = \frac{-1}{s+3/2}$$

$$V(t) = -e^{-3/2 t}$$

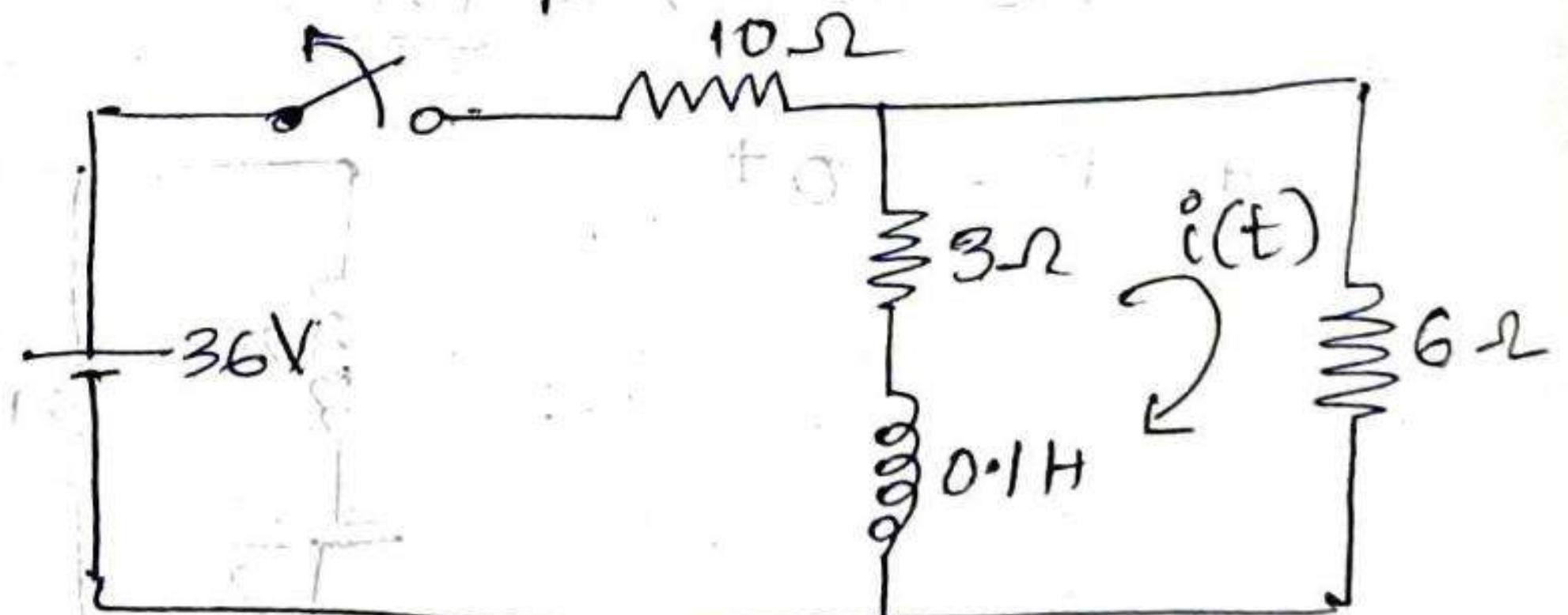30/9/2020  
Q. In the n/w the switch is opened at  $t=0$ , find  $i(t)$



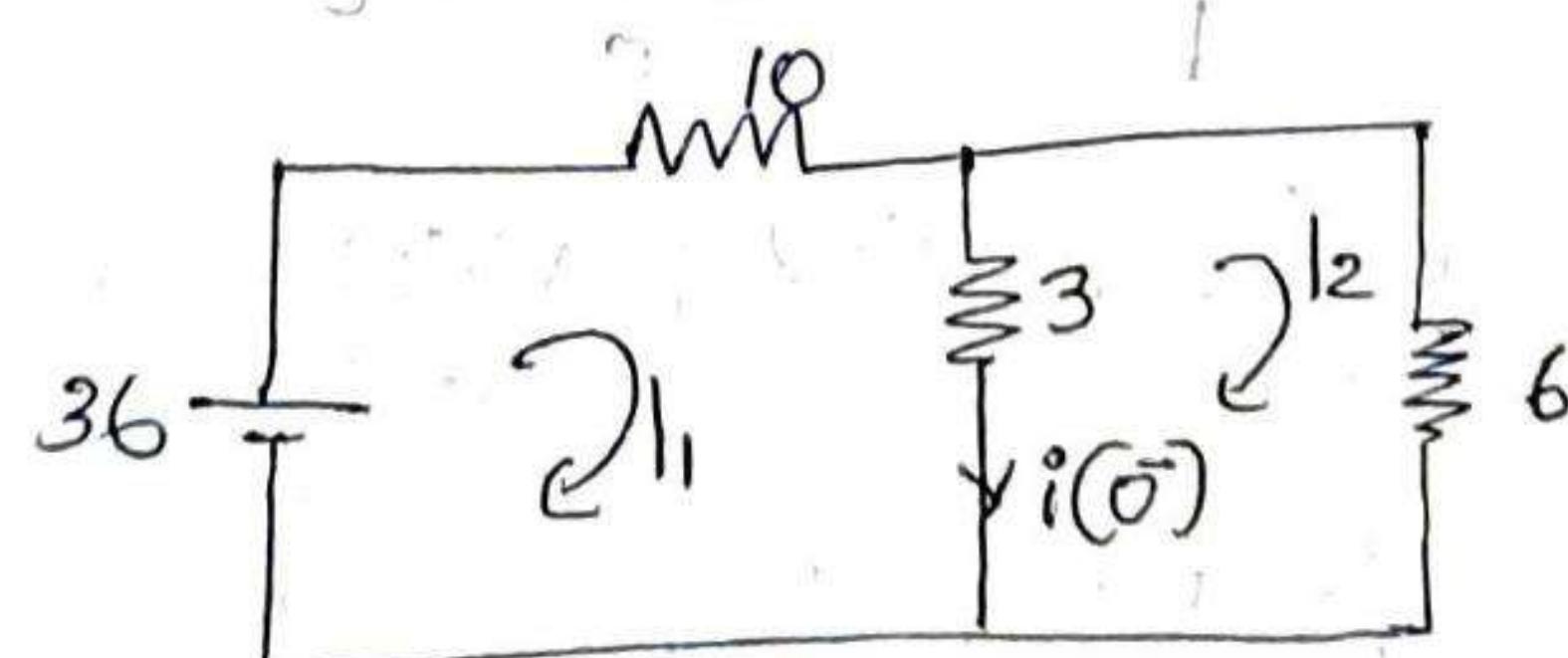At  $t=0^-$ , the switch is closed and steady state is reached, hence inductor will be short.



$$36 = 10 I_1 - 3 I_2$$

$$0 = -3 I_1 + 9 I_2$$


$$\underline{I_1 = 3A}$$

$$\underline{\underline{I_2 = 1A}}$$

$$i_L(s) = I_1 - I_2$$

$$\underline{i(s) = \alpha A}$$

For  $t > 0$  switch open

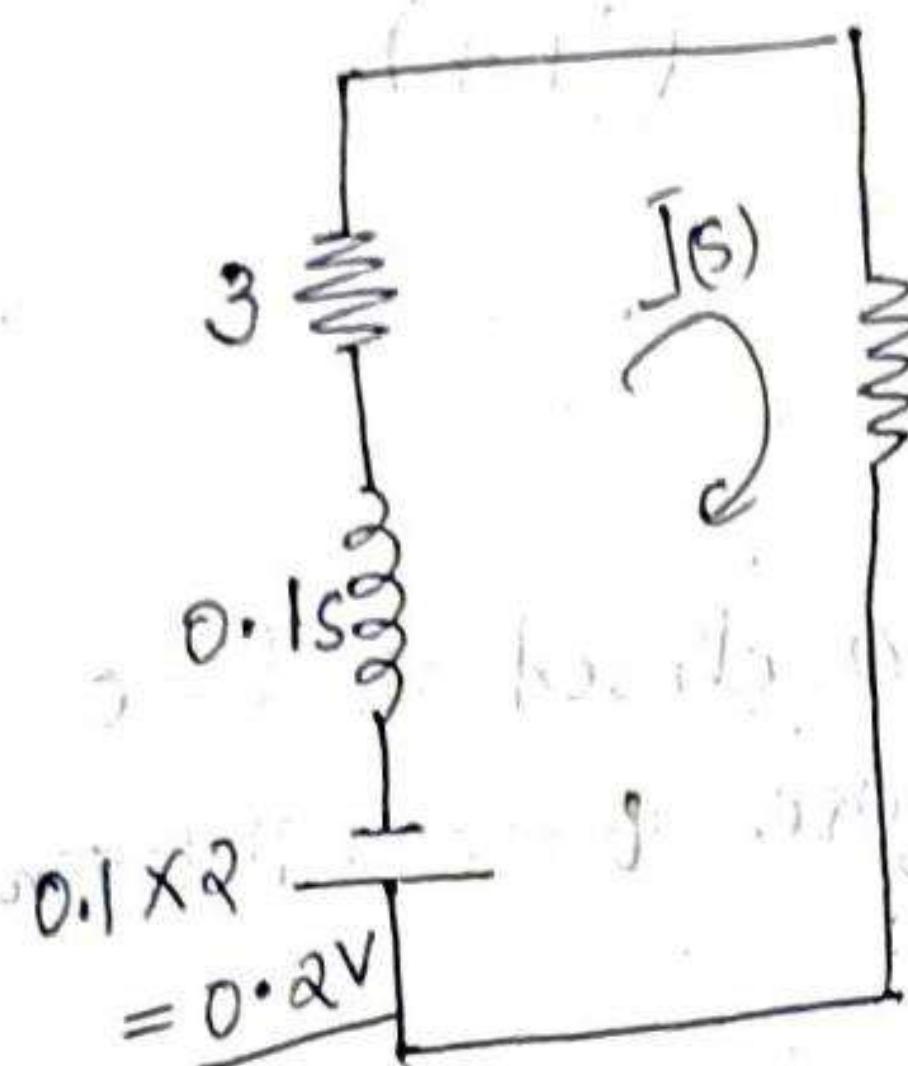

$$-0.2 = q I(s) + 0.1 s I(s)$$


$$-0.2 = I(s) [0.1s + q]$$

$$I(s) = \frac{-0.2}{(0.1s + q)}$$

$$I(s) = \frac{-0.2}{0.1(s + q/0.1)} = \frac{2}{s + 90}$$

$$\underline{\underline{I(t) = 2 \cdot e^{-90t} \text{ for } t > 0}}$$

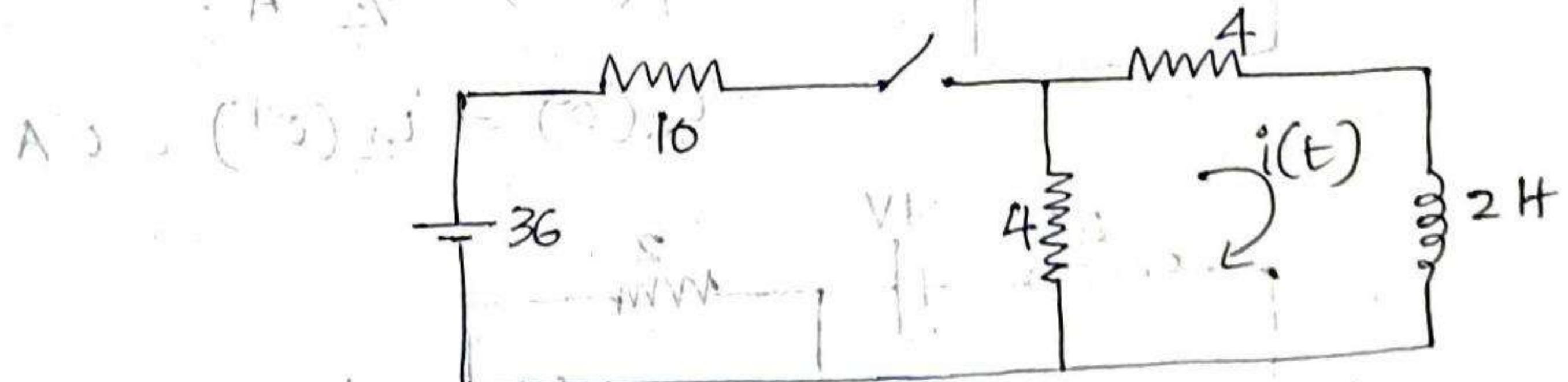- Q. The network shown has acquired steady state with the switch closed for  $t < 0$ . At  $t=0$ , the switch 0 opened. Obtain  $i(t)$  for  $t > 0$ .



At  $t=0^-$


$$36 = 10 I_1 - 4 I_2$$

$$0 = [8 - 4 I_1 + 8 I_2]$$

$$I_1 = \underline{3A}$$

$$I_2 = \underline{3/2 = 1.5A}$$

$$\underline{i(0^-) = 1.5A}$$

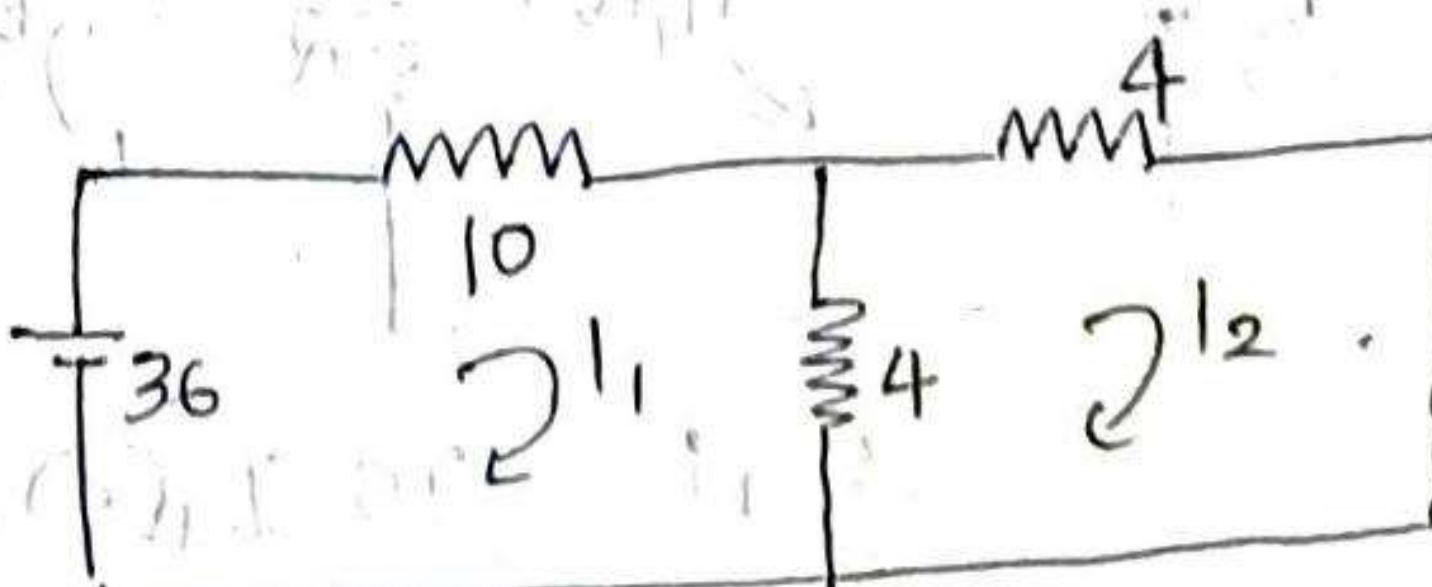


for  $t > 0$ ,

$$+3 = 8I(s) + 2sI(s)$$



$$= I(s)(2s + 8)$$

$$I(s) = \frac{+3}{(2s+8)} = \frac{+3}{2(s+4)} = \frac{+1.5}{(s+4)}$$

$$I(t) = \frac{+1.5 e^{-4t}}{1}$$

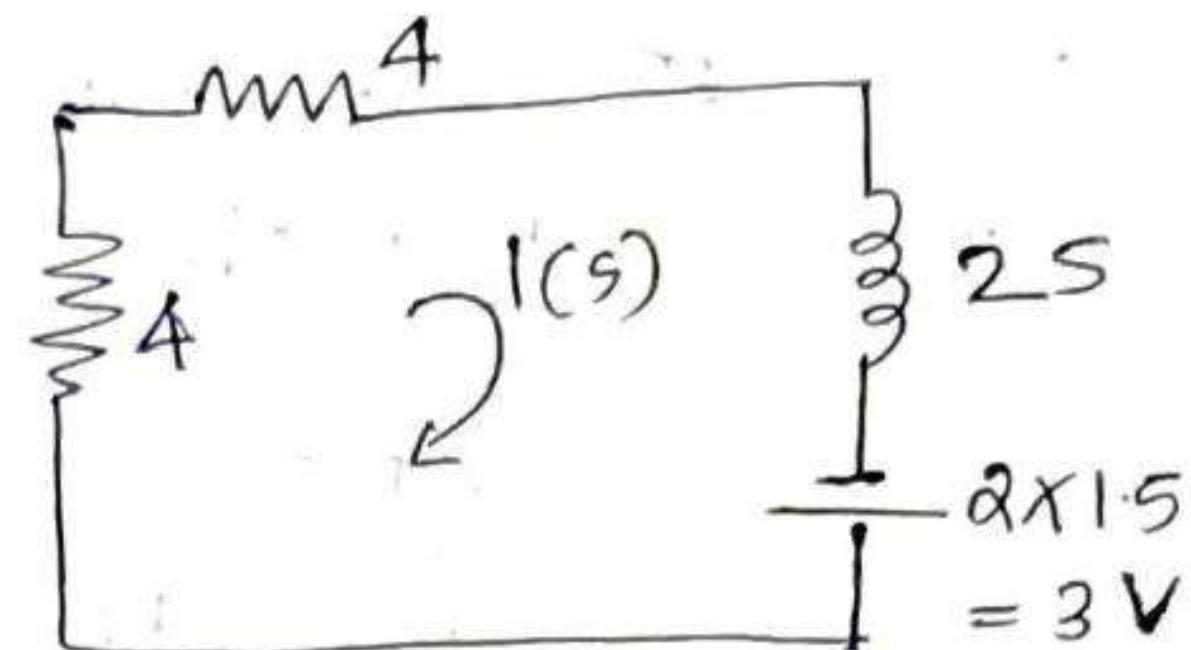

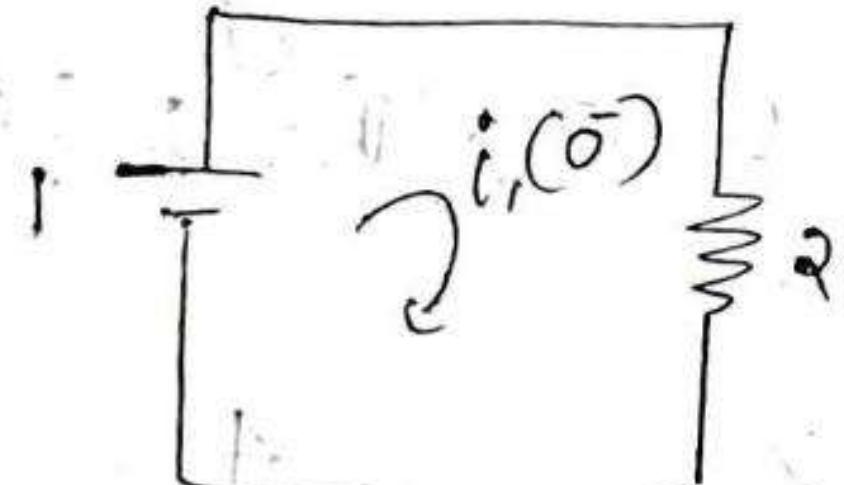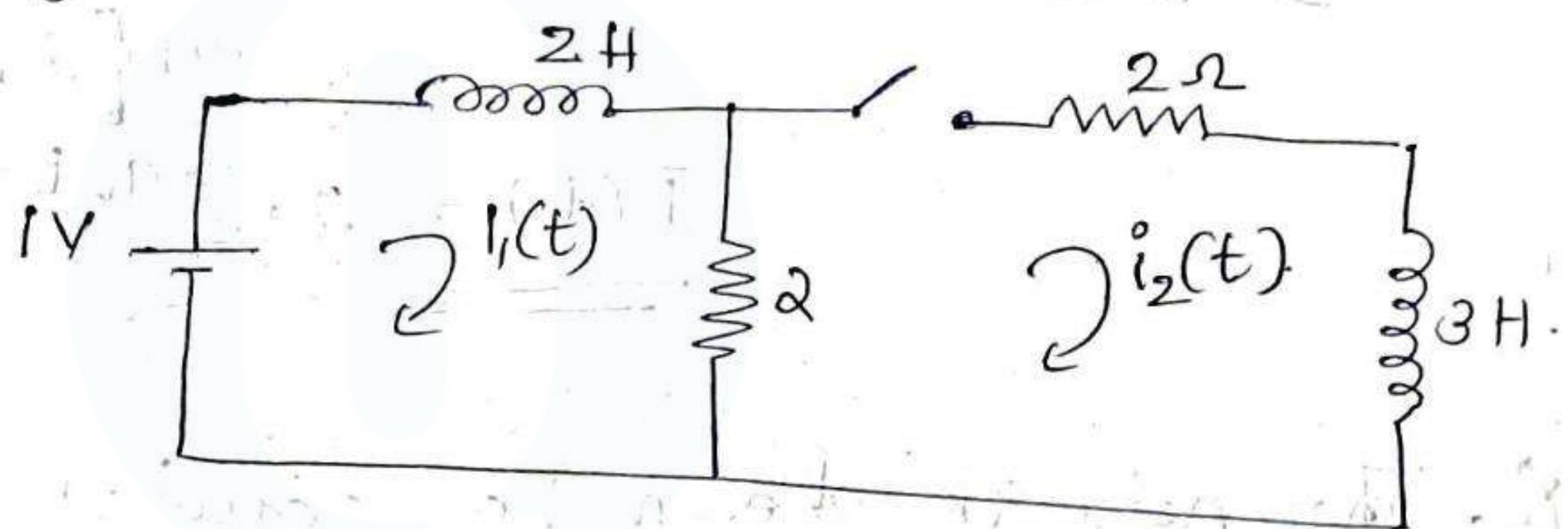
- Q. In the n/w shown, the switch o closed at  $t=0$ , the steady state being reached before  $t=0$ . Determine current through Inductor  $3H$ .



$$i_1(0^-) = \frac{1}{2} A$$

$$i_1(0^+) = \frac{1}{2} A$$

$$i_2(0^-) = i_2(0^+) = 0 A$$

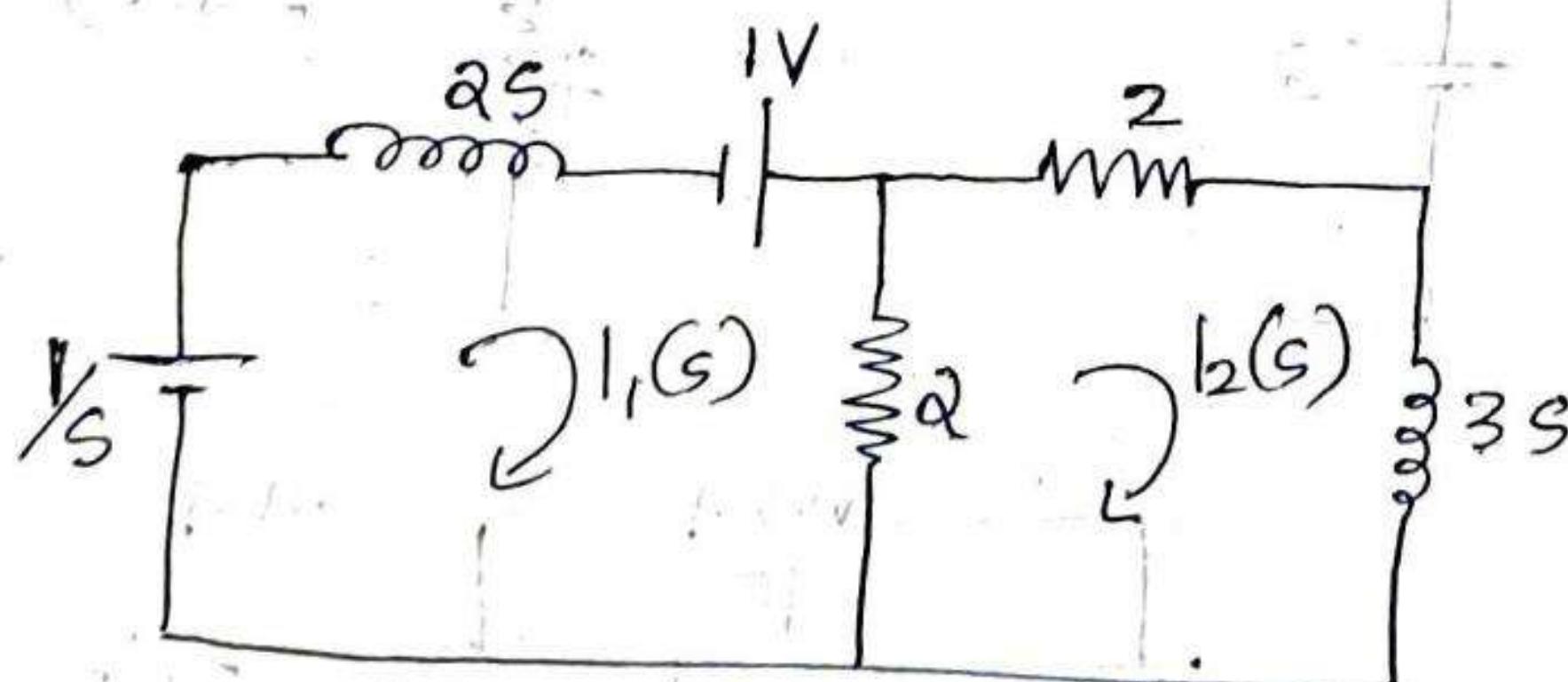

$$\frac{1}{s} + 1 = 2s I_1(s) + 2[I_1(s) - I_2(s)]$$

$$1 + \frac{1}{s} = I_1(s)[2 + 2s] - 2 I_2(s)$$

$$0 = \alpha (I_2(s) - I_1(s)) + \alpha I_2(s) + 3s I_2(s).$$

$$\Rightarrow -\alpha I_1(s) + 4 I_2(s) + 3s I_2(s)$$

$$0 = -\alpha I_1(s) + I_2(s)[4 + 3s]$$

$$\begin{bmatrix} 2s+2 & -\alpha \\ -\alpha & 3s+4 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} 1+s \\ 0 \end{bmatrix}$$

$$T(s) = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 2s+2 & 1+s \\ -\alpha & 0 \end{vmatrix}}{\begin{vmatrix} 2s+2 & -\alpha \\ -\alpha & 3s+4 \end{vmatrix}}$$

$$= \frac{(2s+2) \times 0 - (-\alpha)(1+s)}{(2s+2)(3s+4) - (-\alpha \times -\alpha)}$$

$$= \frac{2s^2 + 2s}{(2s+2)(3s+4) - (\alpha^2)}$$

$$= \frac{2s^2 + 2s}{6s^2 + 8s + 6s + 8 + 4} = \frac{2s^2 + 2s}{6s^2 + 14s + 12}$$

$$= \frac{s+1}{s(3s^2 + 7s + 2)} - \frac{s+1}{3s(s^2 + \frac{7}{3}s + \frac{2}{3})}$$

$$a+b = \frac{1}{3}$$

$$I_2(s) = \frac{s+1}{3s(s+\frac{1}{3})(s+2)} = \frac{\frac{1}{3}(s+1)}{s(s+\frac{1}{3})(s+2)}$$

$$a+b = \frac{2}{3}$$

$$\frac{\frac{1}{3}(s+1)}{s(s+\frac{1}{3})(s+2)} = \frac{A}{s} + \frac{B}{s+\frac{1}{3}} + \frac{C}{s+2}$$

$$A = s I_2(s)|_{s=0}$$

$$= s \times (s+1) = \frac{\frac{1}{3}}{\frac{1}{3} \times 2} = \frac{1}{2}$$

$$B = (s + y_3) I_2(s) \Big|_{s=-y_3}$$

$$= \frac{(s + y_3) \times (s+1)(s+y_3)}{s[s+y_3](s+2)} \Big|_{s=-y_3}$$

$$= \frac{\frac{2}{3} \times \frac{1}{3}}{-\frac{1}{3} \times \frac{5}{3}} = \frac{\frac{2}{9}}{-\frac{5}{9}} = \underline{\underline{-\frac{2}{5}}}$$

$$C = s+2 J(s) \Big|_{s=-2}$$

$$= \frac{(s+2)(y_3(s+1))}{s(s+2)(s+y_3)} \Big|_{s=-2}$$


$$= \frac{\frac{1}{3} \times -1}{-2(-\frac{5}{3})} = \underline{\underline{-\frac{1}{10}}}$$

$$I_2(s) = \frac{1/2}{s} + \frac{-2/5}{s+y_3} + \frac{-1/10}{s+2}$$


$$I_2(s) = \frac{1}{2} e^{-\frac{1}{2}s} - \frac{2}{5} e^{-\frac{1}{5}(s+1)} - \frac{1}{10} e^{-\frac{1}{10}s}$$

1/10 [ao 20]

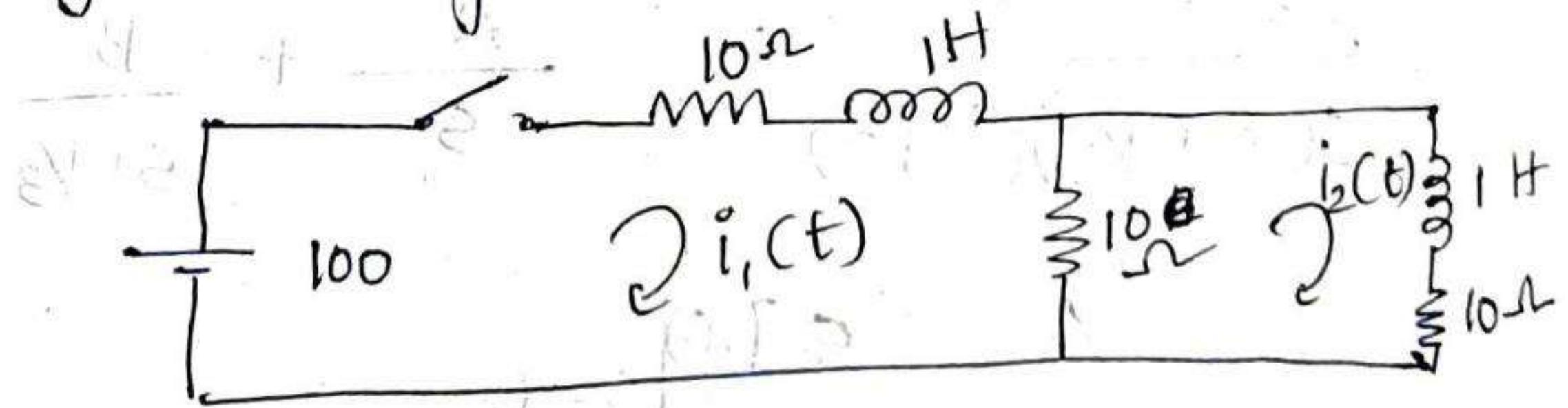Q. In the n/w the switch is closed at  $t=0$ , the n/w is previously unenergised. Determine current  $i_1(t)$ .



For  $t > 0$

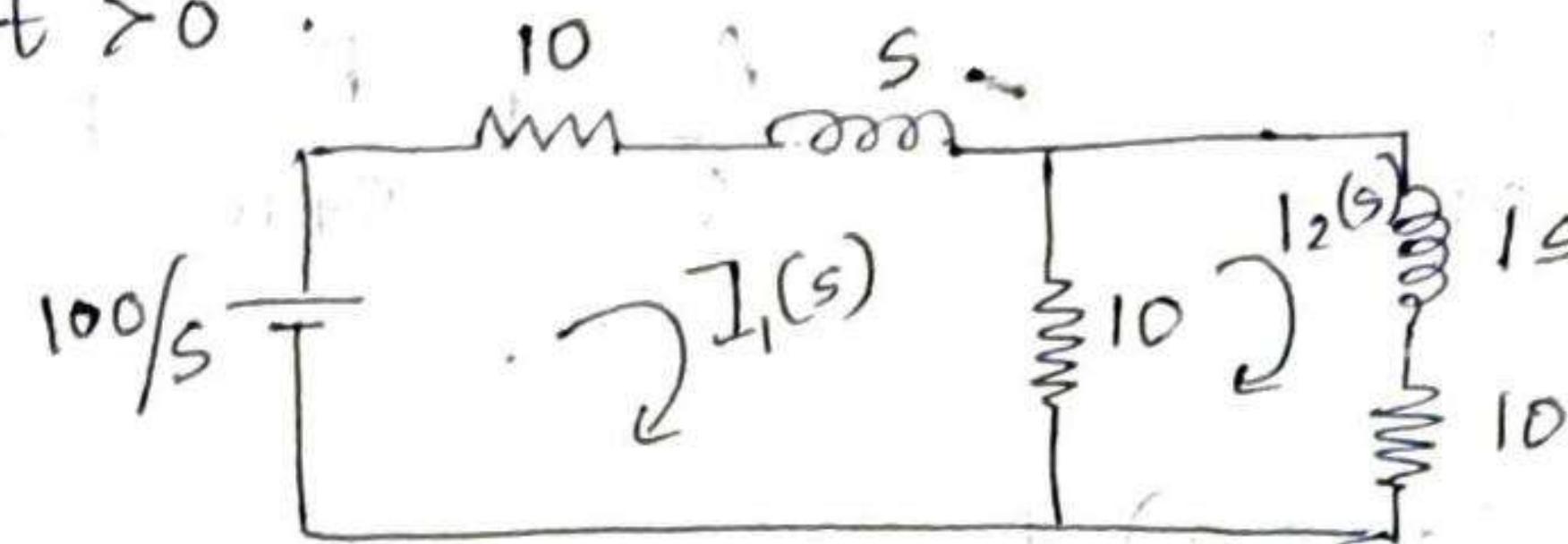

$$\frac{100}{s} = 20 I_1(s) + s I_1(s) - 10 I_2(s)$$

$$\frac{100}{s} = (20+s) I_1(s) - 10 I_2(s) \quad (1)$$

$$0 = 20 I_2(s) + s I_2(s) - 10 I_1(s)$$

$$0 = -10 I_1(s) + (20+s) I_2(s) \quad (2)$$

$$\begin{bmatrix} 20+s & -10 \\ -10 & (20+s) \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} 100/s \\ 0 \end{bmatrix}$$

$$I_1(s) = \frac{\Delta i}{\Delta} = \frac{100/s}{\begin{vmatrix} 20+s & -10 \\ -10 & 20+s \end{vmatrix}} = \frac{100/s}{(20+s)(20+s) - 100}$$

$$I_1(s) = \frac{100/s(20+s)}{(20+s)(20+s) - 100} = (3)$$

$$I_1(s) = \frac{100(20+s)}{s(s^2 + 40s + 400) - 100} = (4)$$

$$= \frac{100(20+s)}{s(s^2 + 40s + 300)}$$

$$I_1(s) = \frac{100(20+s)}{s(s+10)(s+30)}$$

$s = 40$   
 $\rho = 30^\circ$   
10, 10

$$\frac{100(s+20)}{s(s+10)(s+30)} = \frac{A}{s} + \frac{B}{s+10} + \frac{C}{s+30}$$

$$A = \left. \frac{100(s+20)}{(s+10)(s+30)} \right|_{s=0}$$

$$= \frac{10\Phi \times 2\Phi}{1\Phi \times 3\Phi} = \underline{\underline{\frac{20}{3}}}$$

$$B = \left. \frac{100(s+20)}{s(s+30)} \right|_{s=-10}$$

$$= \frac{10\Phi(-10)}{-10\Phi \times 2\Phi} = \underline{\underline{-5}}$$

$$C = \left. \frac{100(s+20)}{s(s+10)} \right|_{s=-30}$$


$$= \frac{10\Phi(-10)}{-3\Phi \times -2\Phi} = \underline{\underline{\frac{-5}{3}}}$$

$$I(s) = \frac{20/3}{s} + \frac{-5}{s+10} + \frac{-5/3}{s+30}$$


$$I(t) = \underline{\underline{\frac{20}{3} + -5e^{-10t} - \frac{5}{3}e^{-30t}}}$$

8/10/2020 RC circuits

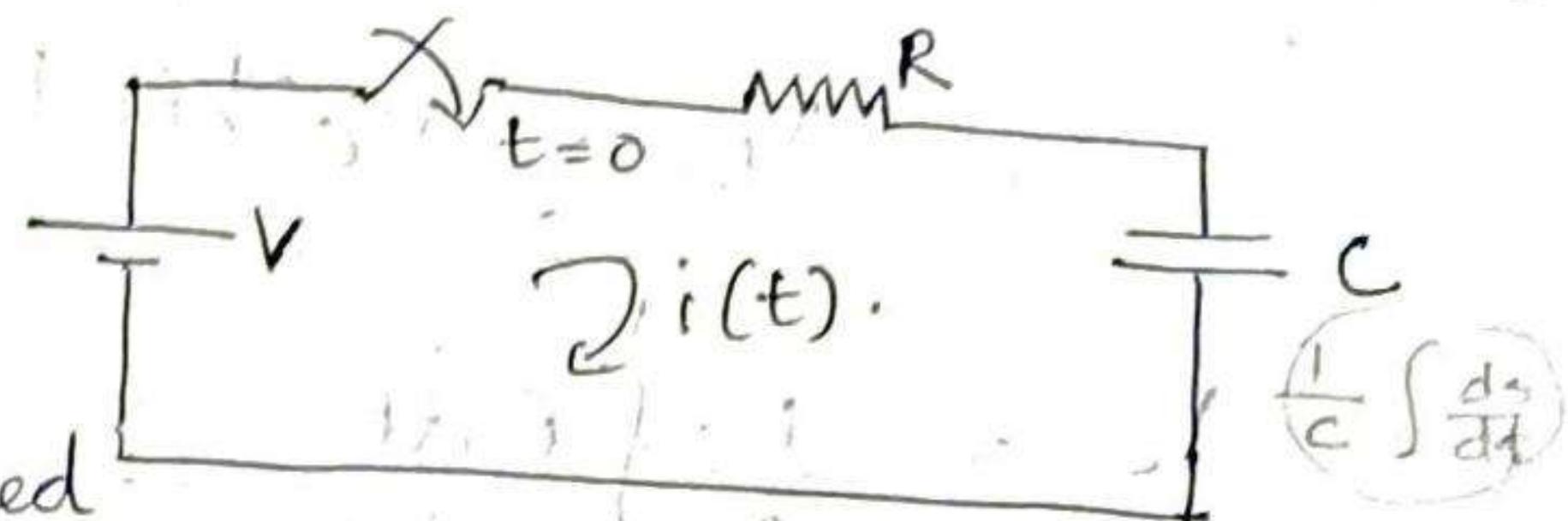consider a series RC circuit. The switch is closed at time  $t = 0$ .



For  $t > 0$  the transformed circuit

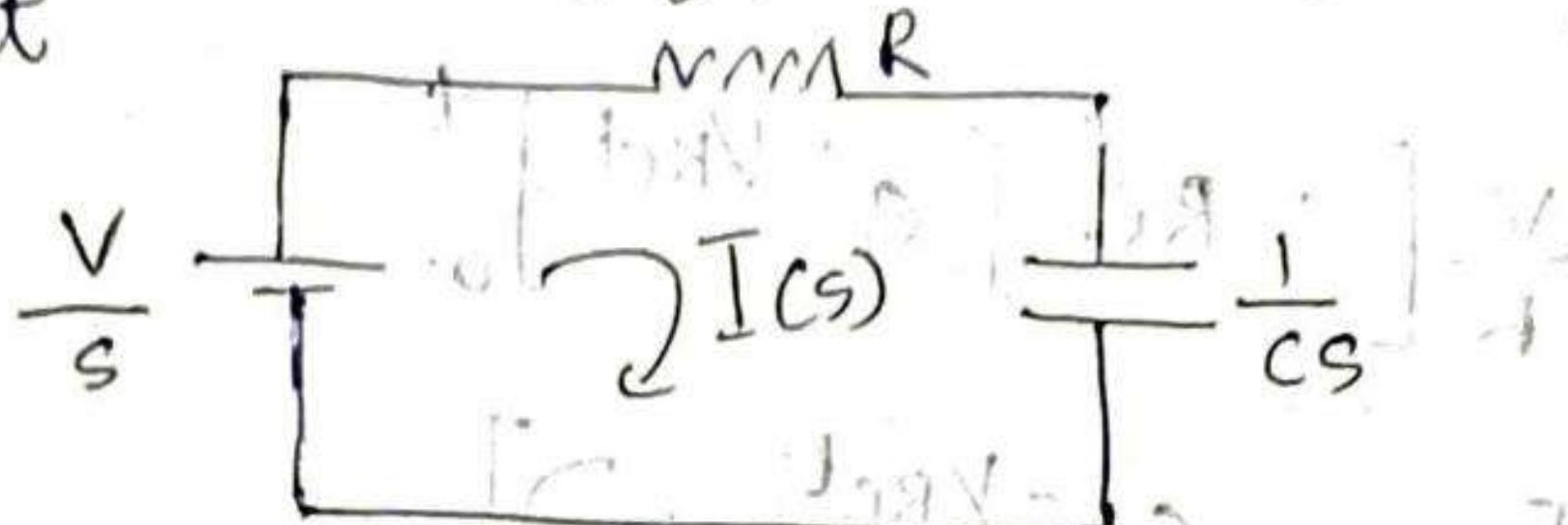

$$R I(s) + \frac{1}{cs} I(s) = \frac{V}{s}$$


$$\left[ R + \frac{1}{cs} \right] I(s) = \frac{V}{s}$$

$$I(s) = \frac{\frac{V}{s}}{\left[ R + \frac{1}{cs} \right]} = \frac{\frac{V}{s}}{\frac{Rcs + 1}{cs}} = \frac{\frac{V}{s} \times cs}{Rcs + 1}$$

$$= \frac{Vc}{Rc[s + \frac{1}{Rc}]} = \frac{V/R}{s + \frac{1}{Rc}}$$


on multiplying both sides with denominator, we get
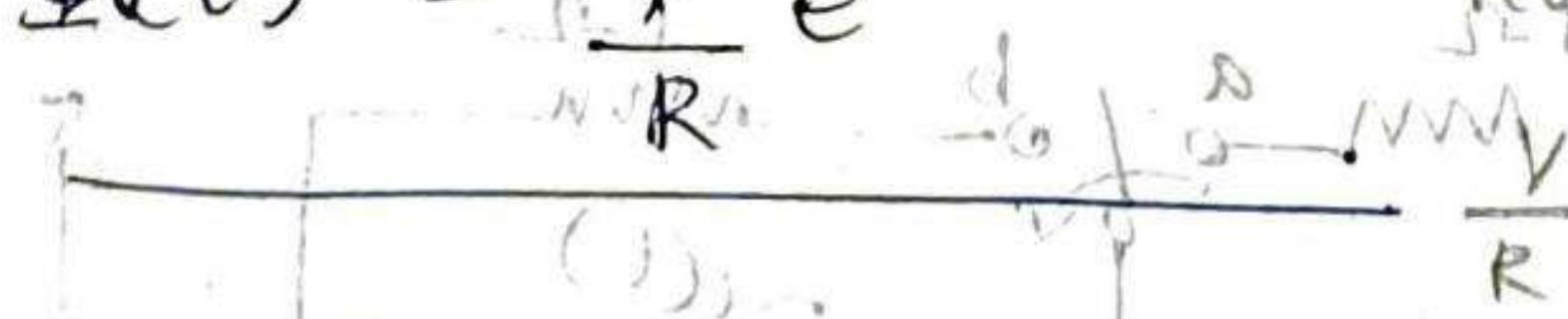
$$i(t) = \frac{V}{R} e^{-\frac{1}{Rc} t} \cdot I(s)$$



The term  $RC$  is the time constant.

$$\underline{T = RC}$$

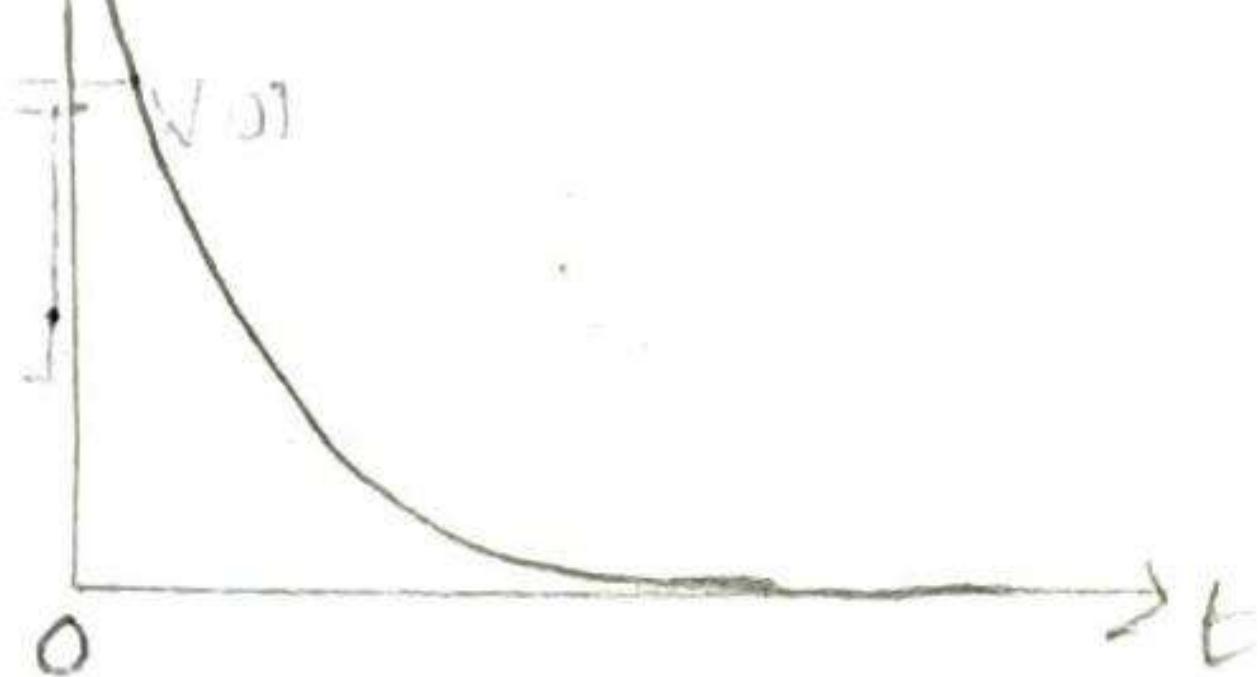


$$\underline{T = RC}$$


$$V_R = R^o = R \times \frac{V}{R} e^{-\frac{1}{RC} t}$$

$$\underline{V_R = V e^{-\frac{1}{RC} t}}$$
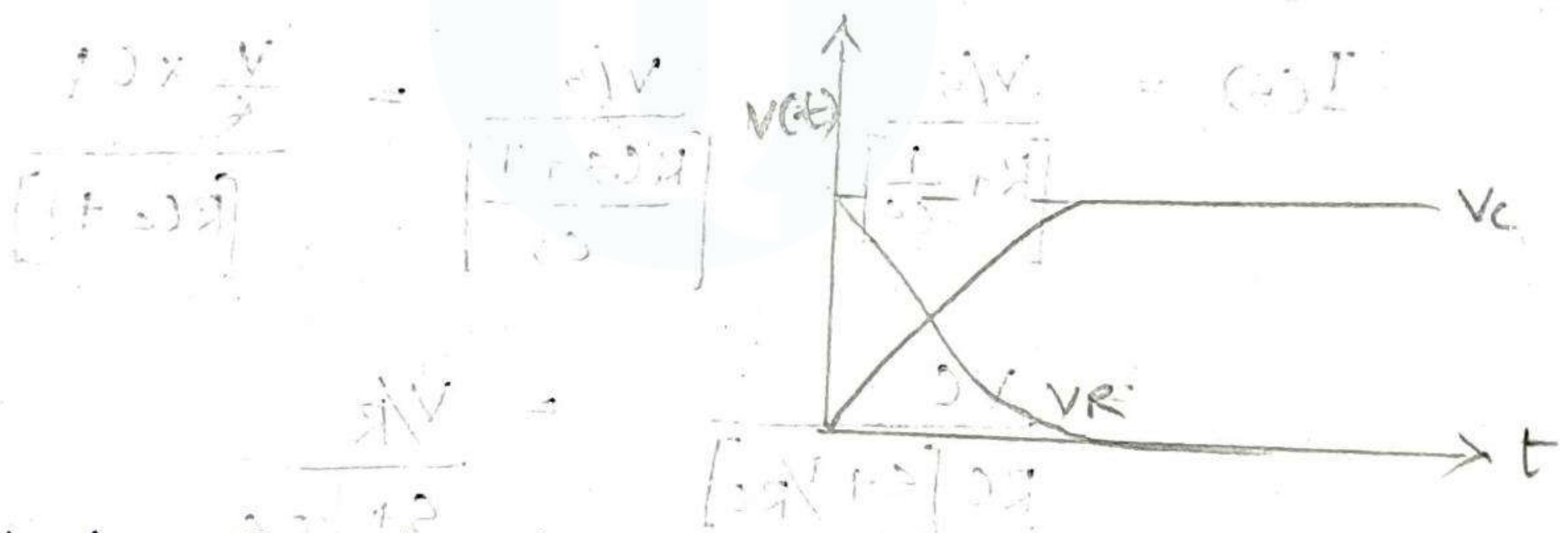
$$\begin{aligned} V_C &= \frac{1}{C} \int_0^t i dt = \frac{1}{C} \int \frac{V}{R} e^{-\frac{1}{RC} t} dt \\ &= \frac{1}{C} \cdot \frac{V}{R} \left[ -RC [e^{-\frac{1}{RC} t}] \right]_0^t \\ &= \frac{V}{CR} \left[ -RC (e^{-\frac{1}{RC} t} - 1) \right] \\ &\approx -V e^{-\frac{1}{RC} t} + V = V [1 - e^{-\frac{1}{RC} t}] \end{aligned}$$



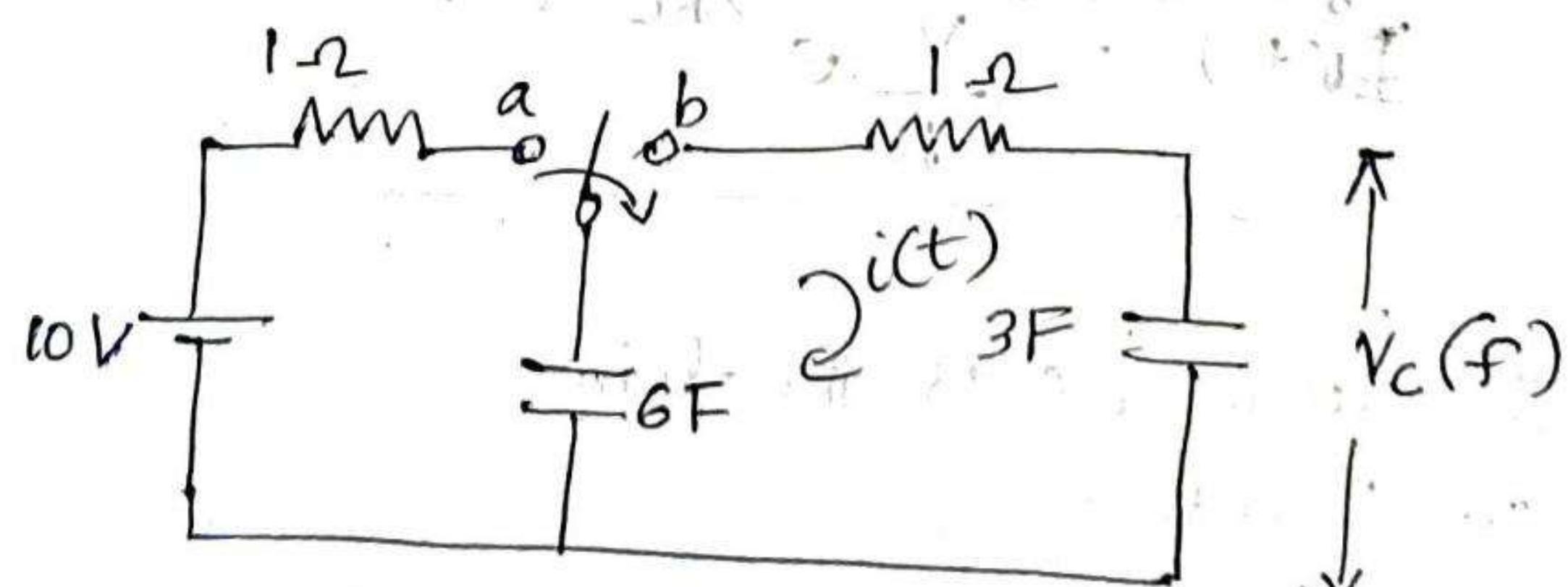Q' In the network, the switch is moved from a to b at  $t=0$ . Determine  $i(t)$  and  $v(t)$ .




At  $t = 0^-$ , the network has attained steady state condition. Hence  $6\text{ F}$  capacitors act as an open circuit.

$$V_{6F}(0^-) = 10\text{ V}$$

$$i(0^-) = 0$$


$$V_{3F}(0^-) = 0$$

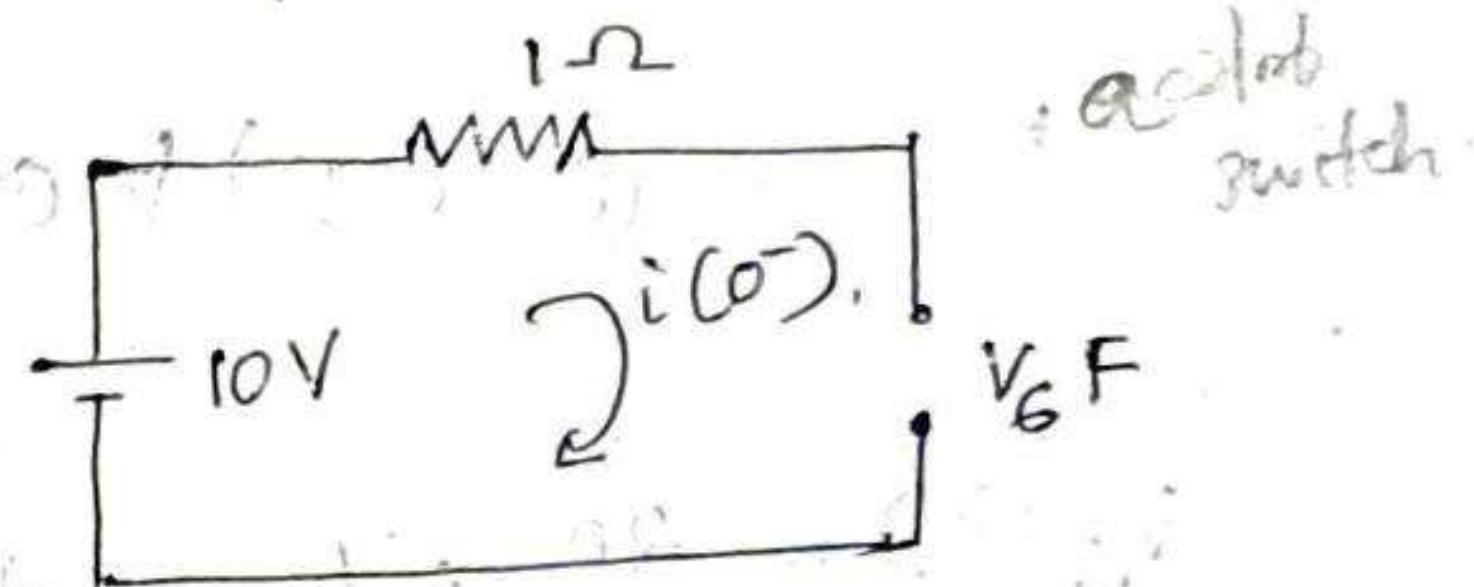

Since voltage across the capacitor cannot change simultaneously  $V_{6F}(0^-) = 10\text{ V}$

$$V_{3F}(0^+) = 10$$

For  $t > 0$

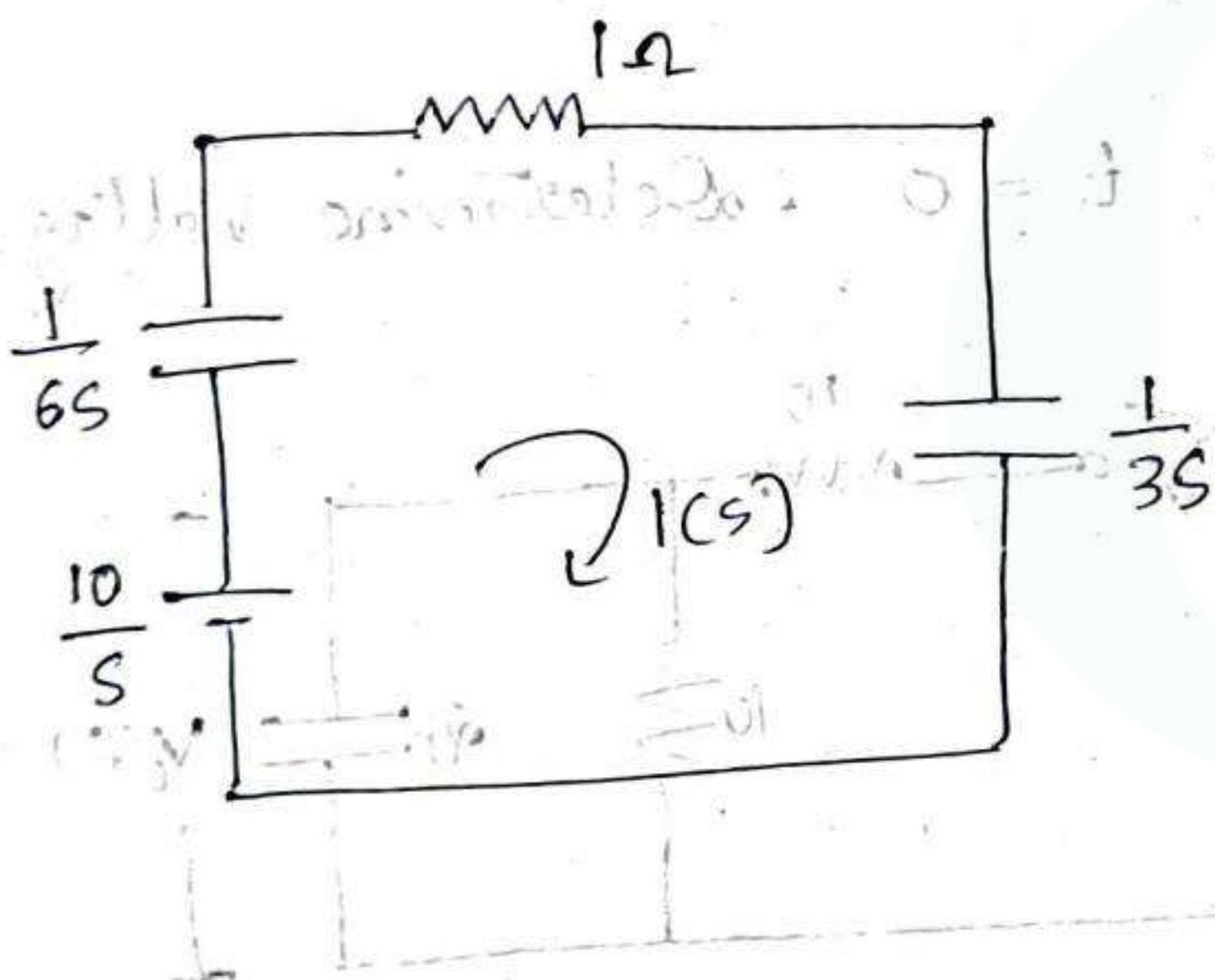

Mesh

$$\frac{10}{s} = \frac{i}{6s} + I(s) + \frac{I}{3s}$$

$$\frac{10}{s} = I(s) \left[ \frac{1}{6s} + 1 + \frac{1}{3s} \right]$$

$$I(s) = \frac{10}{s \left( \frac{1}{6s} + 1 + \frac{1}{3s} \right)}$$

$$I(s) = \frac{10}{s + 0.5} \quad \text{or } 0 = (0)\text{ V} \quad \frac{60}{6s + 3} = \frac{10}{s + 0.5}$$

$$i(t) = 10 e^{-0.5t}$$

Voltage across  $3\text{ F}$ ,

$$V_{3F}(s) = \frac{1}{3s} I(s) = \frac{10}{3s(s+0.5)}$$

$$\frac{10/3}{s(s+0.5)} = \frac{A}{s} + \frac{B}{s+0.5}$$

$$A = 8V_C(s) \Big|_{s=0} = \frac{10/3}{s+0.5} = \frac{20}{3}$$


$$B = (s+0.5)V_C(s) \Big|_{s=0.5} = \frac{10}{3s} \Big|_{s=0.5} = -\frac{20}{3}$$

$$V_C(s) = \frac{20}{3} \times \frac{1}{s} - \frac{20}{3} \times \frac{1}{s+0.5}$$

$$= \frac{20}{3} - \frac{20}{3} e^{-0.5t}$$

$$V_C(s) = \frac{20}{3} (1 - e^{-0.5t})$$

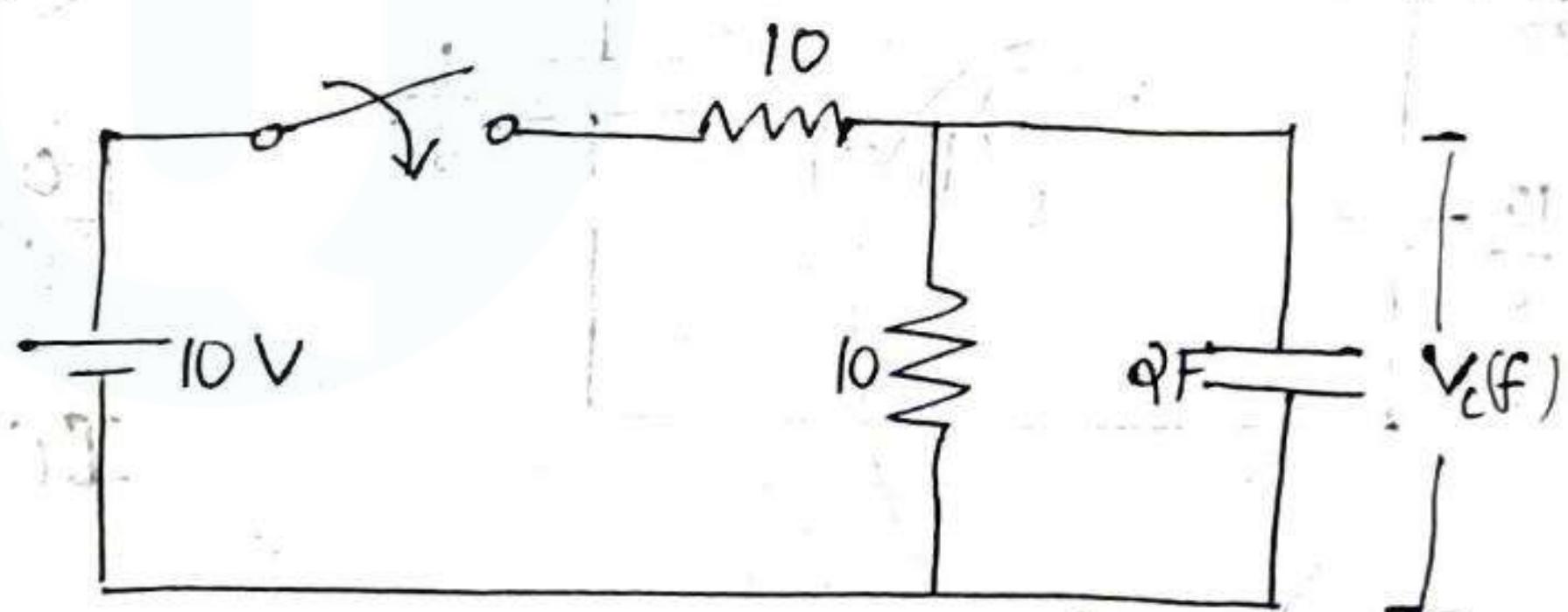Q. The switch is closed at  $t=0$ . Determine voltage across the capacitor.




At  $t=0^-$  capacitor is uncharged.

$$V_C(0^-) = 0$$

$$V_C(0^+) = 0$$

For  $t > 0$

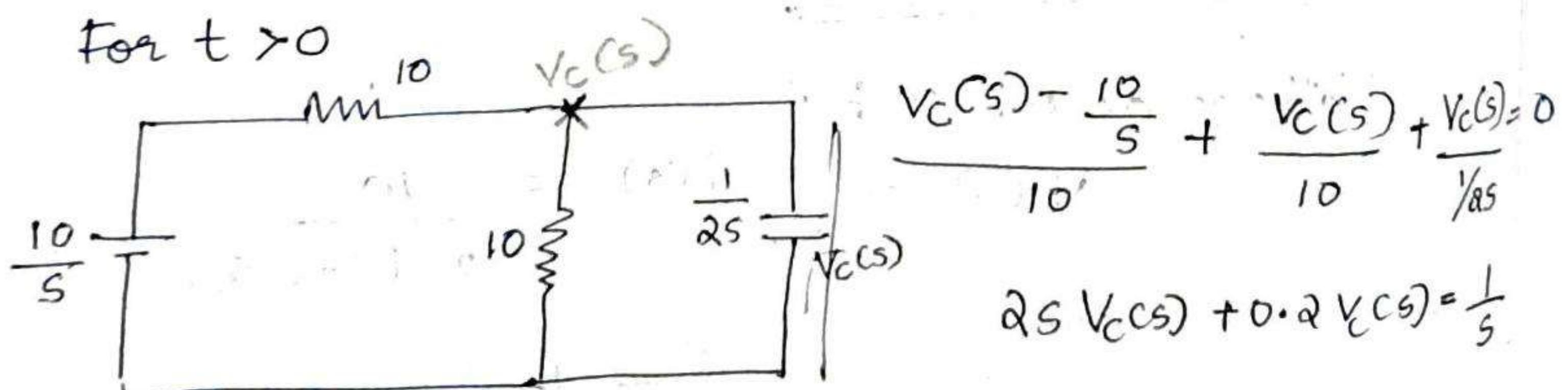

$$V_C(s) = \frac{1}{s(2s+0.2)} = \frac{0.5}{s(s+0.1)}$$

$$\frac{0.5}{s(s+0.1)} = \frac{A}{s} + \frac{B}{s+0.1}$$


$$A = \lim_{s \rightarrow 0} s V_C(s) = \lim_{s \rightarrow 0} \frac{0.5}{s+0.1} = 5$$

$$B = \lim_{s \rightarrow -0.1} (s+0.1) V_C(s) = \lim_{s \rightarrow -0.1} \frac{0.5}{s} = -5$$

$$V_C(s) = \frac{5}{s} - \frac{5}{s+0.1} = 5 - 5e^{-0.1t}$$

$$= 5(1 - e^{-0.1t})$$

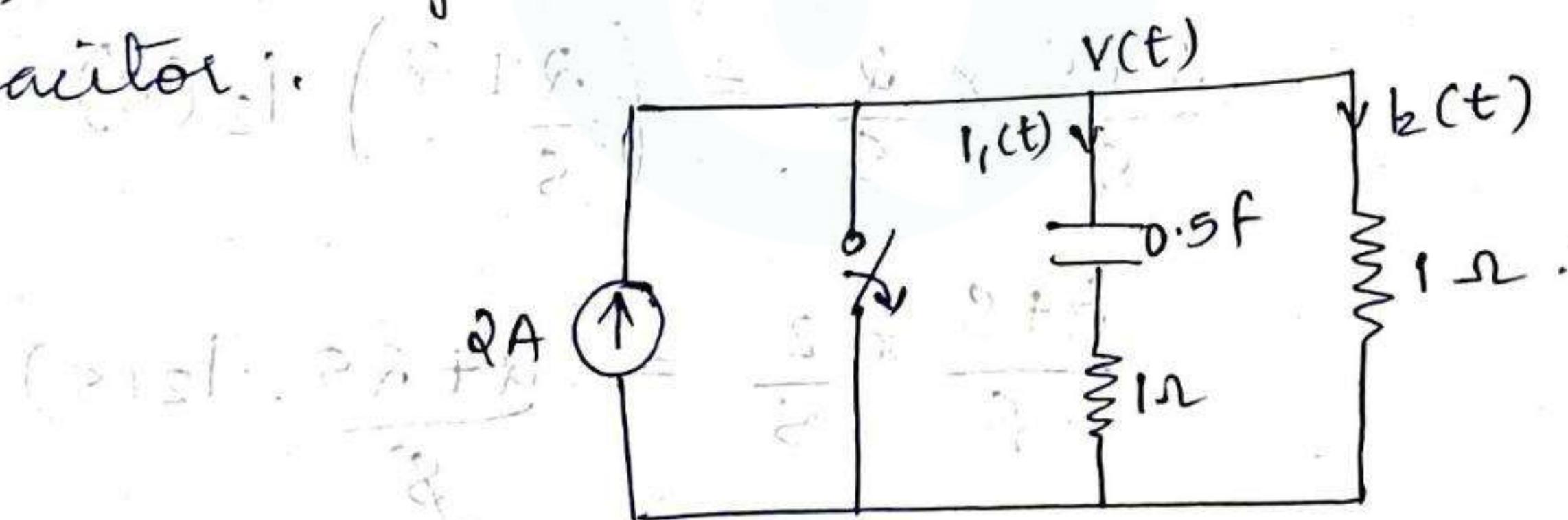
Q. The switch is closed for a long time and at  $t = 0$  the switch is opened. Determine current through capacitor.




at  $t(0^-)$  switch is closed

$$0.5F(0^-) = 2$$

$$i(0^-) = 0$$

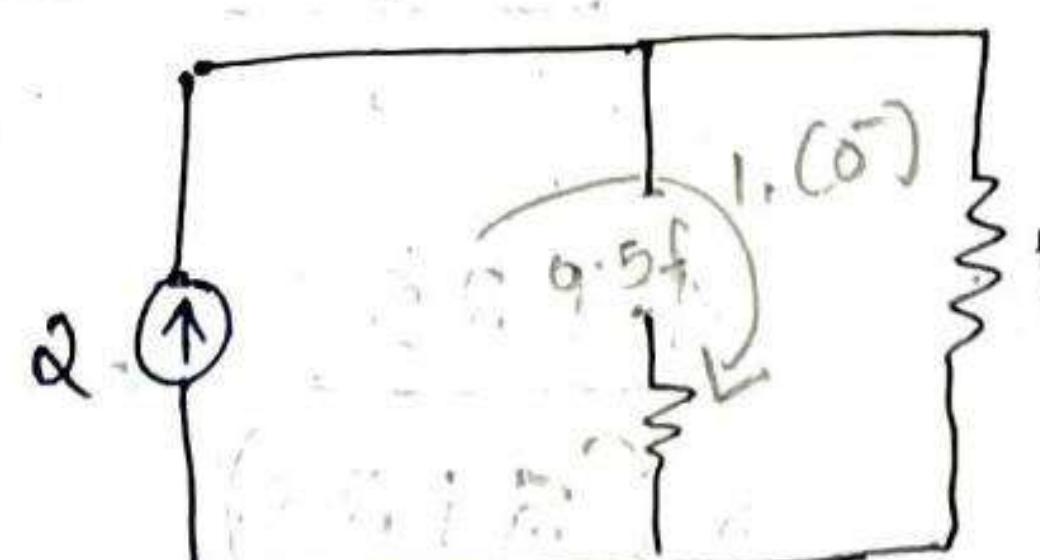

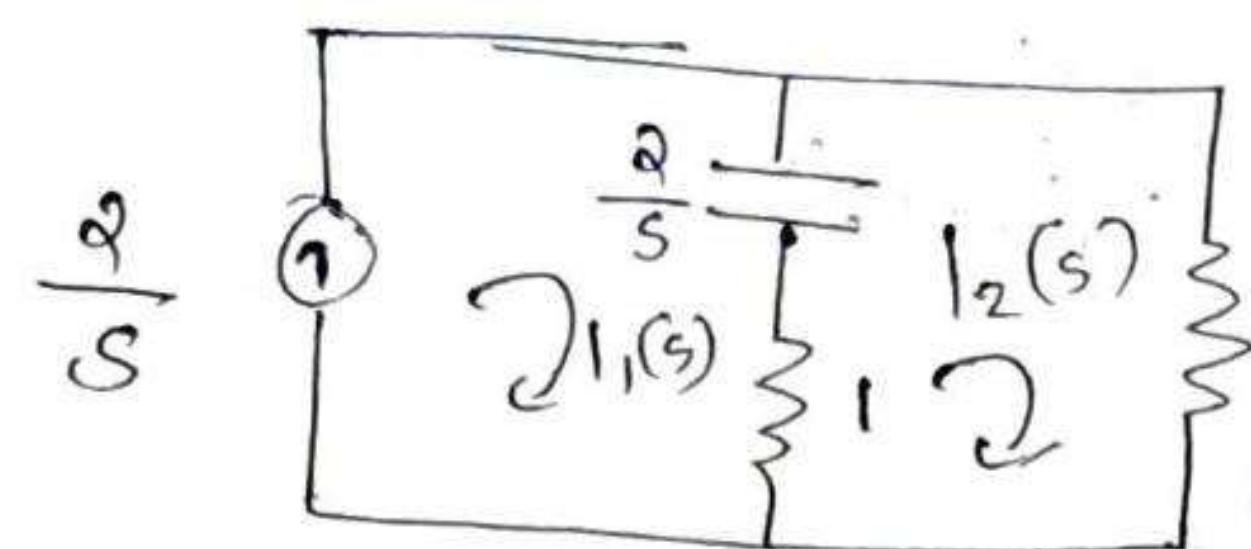

$$\frac{2}{s} = \frac{2}{s} I_1(s) + I_1(s) - \frac{2}{s} I_2(s)$$

$$\frac{2}{s} = \left( \frac{2}{s} + 1 \right) I_1(s) - \left( \frac{2}{s} + 1 \right) I_2(s)$$

$$0 = \frac{2}{s} (I_2(s) - I_1(s)) + \frac{2}{s} I_2(s) - 1 I_1(s)$$

$$= \left( \frac{2}{s} - 1 \right) I_1(s) + \left( \frac{2}{s} + 2 \right) I_2(s)$$

$$\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} \begin{bmatrix} \frac{2}{s} + 1 & 0 \\ 0 & \frac{2}{s} - 1 \end{bmatrix} = \begin{bmatrix} \frac{2}{s} + 2 \\ 0 \end{bmatrix}$$

$$\left( \frac{2}{s} + 1 \right) I_1(s) = \left[ \frac{2}{s} + 2 \right] I_2(s)$$

$$I_1(s) = 2/s$$

$$\frac{2+s}{s} \times \frac{2}{s} = \left( \frac{2+2}{s} \right) I_2(s)$$

$$\frac{2+s}{s} \times \frac{2}{s} = \frac{2+2s}{s} I_2(s)$$

$$\frac{4+2s}{s} = (2+2s) I_2(s)$$

$$I_2(s) = \frac{4+2s}{s(2+2s)} = \frac{2+(2+s)}{2s(1+s)}$$

$$I_2(s) = \frac{2+s}{s(1+s)} = \frac{A}{s} + \frac{B}{s+1}$$

$$A = \left. \frac{qts}{s+1} \right|_{s=0} = \frac{q}{1} = \underline{\underline{q}}$$

$$B = \left. \frac{q+s}{s} \right|_{s=-1} = \frac{1}{-1} = \underline{\underline{-1}}$$

$$I_2(s) = \frac{q}{s} - \frac{1}{s+1}$$

$$I_2(t) = \underline{\underline{2 - e^{-t}}}$$

$$I_1(s) = \frac{q}{s}$$

$$I_1(t) = \underline{\underline{q}}$$

Current through capacitor



$$= I_1(t) + I_2(t)$$

$$= 2 - (2 - e^{-t})$$

$$= e^{-t}$$

12/10/2020

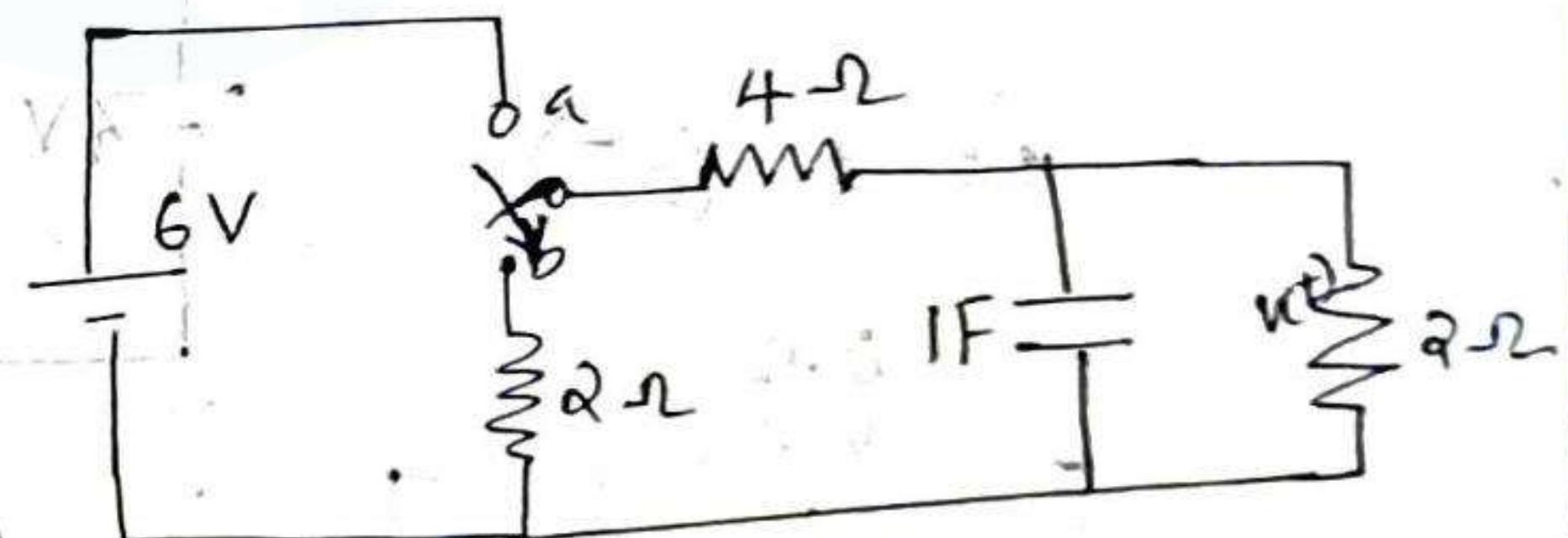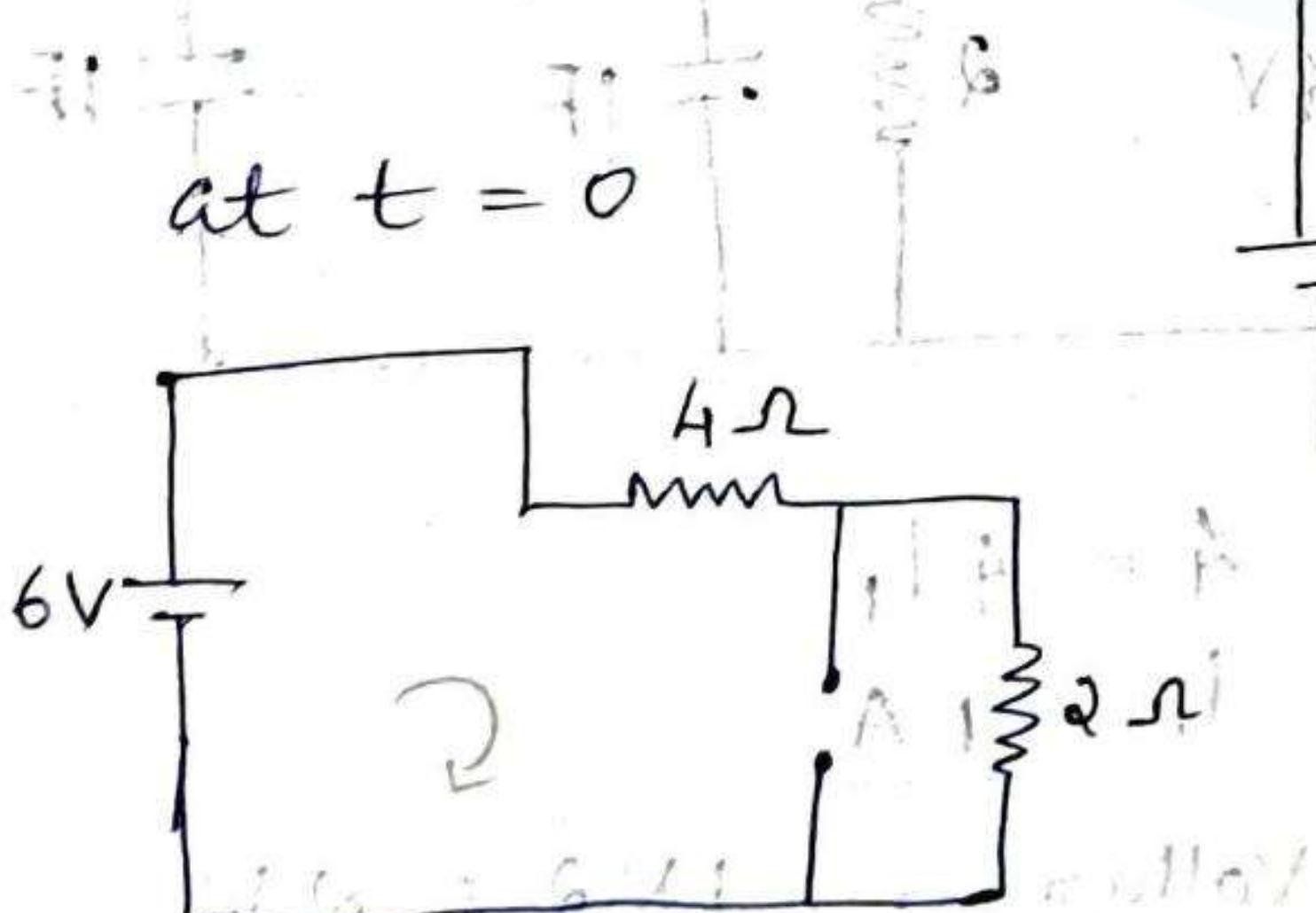Q. In this network, the switch is moved from a to b at  $t = 0$ , find  $v(t)$



$$\text{Voltage} = \frac{\text{Total V} \times \text{Res of branch}}{\text{Sum of resistor}}$$

mesh

$$6 = 6I_1$$

$$= 6 \times \frac{2}{6}$$

$$I_1 = \underline{\underline{1 A}}$$


$$= \underline{\underline{2 V}}$$

V across  $2\Omega$

$$= 2 \times 1 = \underline{\underline{2 V}}$$

Since the voltage across capacitor does not change

$$V(0^+) = \alpha V$$

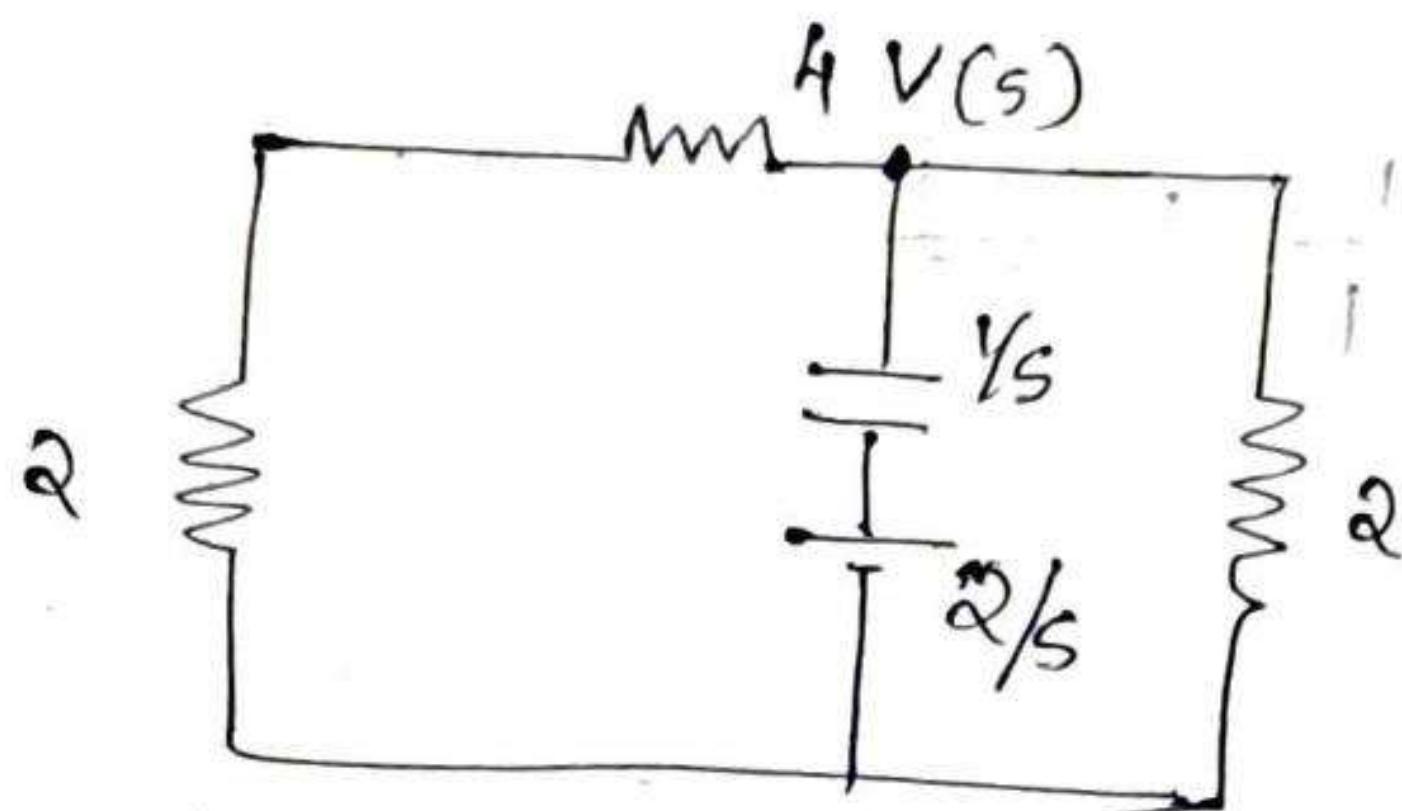

$$\frac{V(s)}{2} + \frac{V(s) - 2/s}{1/s} + \frac{V(s)}{2} =$$


$$V(s) \left[ \frac{1}{6} + \frac{1}{2s} \right] + \cancel{sV(s)} = 0$$

$$V(s) \left[ \frac{2}{3} + s \right] = 2$$


$$V(s) = \frac{2}{\frac{2}{3} + s}$$

$$(+) \quad V(t) = 12 e^{-2/3 t} \text{ (Ans)}$$

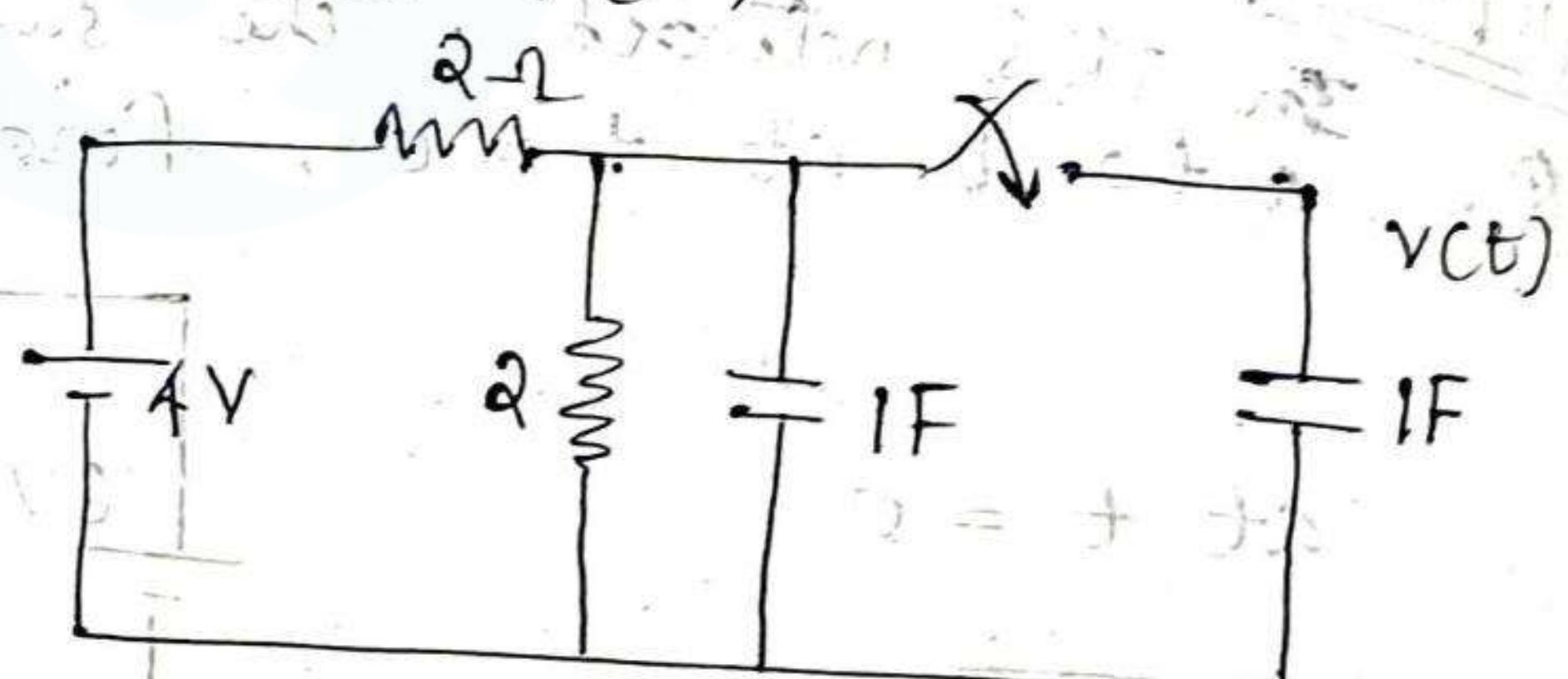- Q. The network shown has acquired steady state at  $t < 0$  with the switch is open. The switch is closed at  $t = 0$ . Determine  $V(t)$



at  $t = (0^-)$

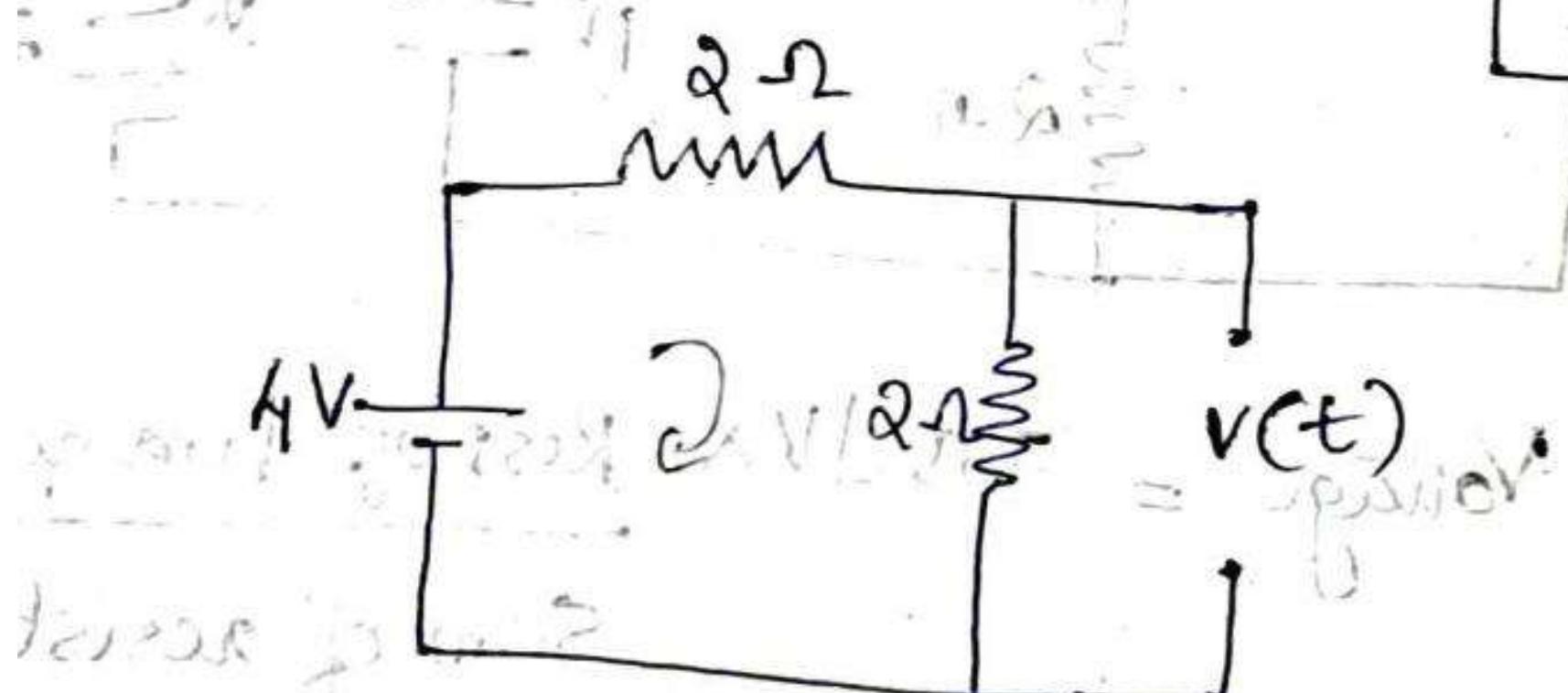

$$I = I_1$$

$$I_1 = 1 \text{ A}$$


$$\text{Voltage} = 1 \times 2 = \underline{\underline{2V}}$$

$$V(0^+) = \underline{\underline{2V}}$$

$$V_p =$$

Ans 1.2 mark question 9 ans  
mark 1.2

at  $t = 0$

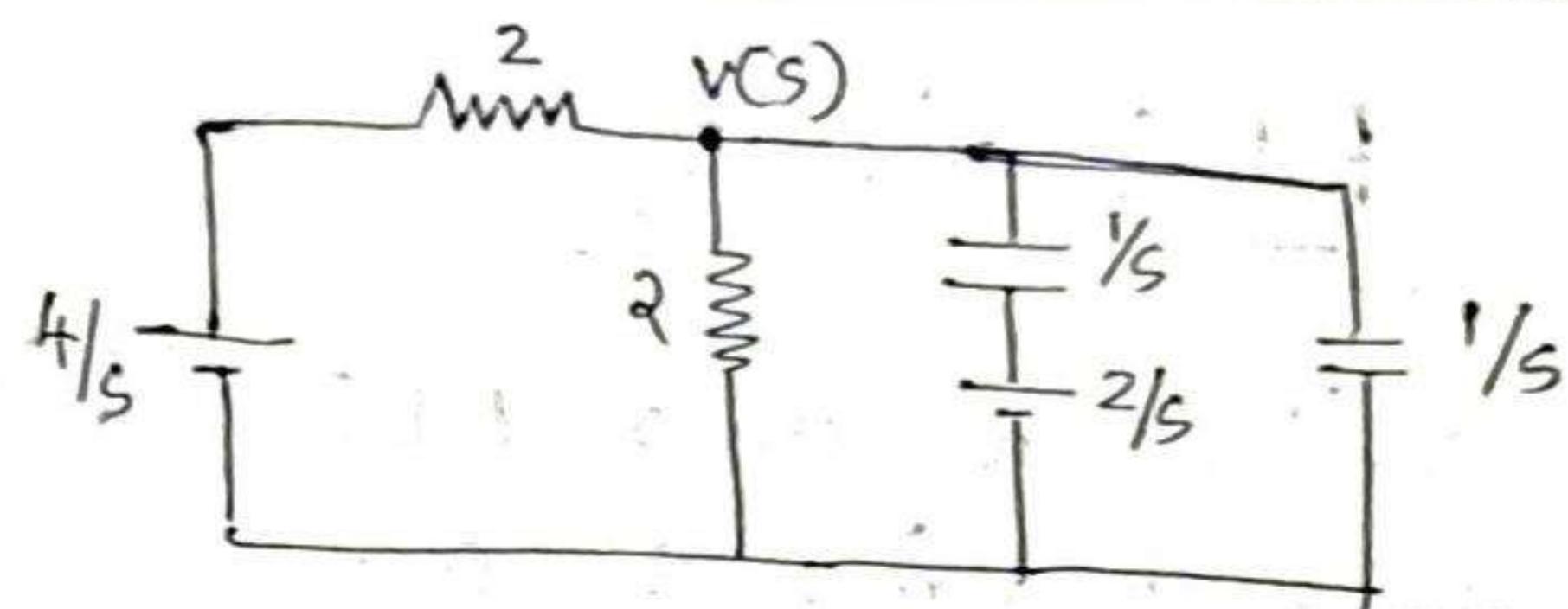

$$\frac{V(s) - 4/s}{2} + \frac{V(s)}{2} + \frac{V(s) - 2/s}{1/s} + \frac{V(s)}{1/s} = 0.$$

$$\frac{V(s)}{2} - \frac{4}{2s} + \frac{V(s)}{2} + sV(s) - 2 + sV(s) = 0.$$

$$\cancel{\frac{V(s)}{2}} - \frac{4}{2s} + 2sV(s) - 2 = 0.$$

$$2sV(s) + V(s) = \cancel{-\frac{2}{s}} + 2.$$

$$V(s)[2s+1] = \frac{2(s+1)}{s} \frac{2+2s}{s(1+s)}$$

$$V(s) = \frac{2(s+1)}{s(2s+1)}$$

$$= \frac{2(s+1)}{2s(s+y_2)}$$

$$V(s) = \frac{s+1}{s(s+y_2)} = \frac{A}{s} + \frac{B}{(s+y_2)}$$

$$A = \left. \frac{s+1}{s+y_2} \right|_{s=0} = \frac{1}{y_2} = \underline{\underline{2}}$$

$$B = \left. \frac{s+1}{s} \right|_{s=-y_2} = \frac{y_2}{-y_2} = \underline{\underline{-1}}$$

$$V(s) = \underline{\underline{\frac{2}{s}}} - \frac{1}{s+y_2}$$



$$V(t) = \underline{\underline{2}} - e^{-\frac{1}{2}t}$$

## RLC circuit

Consider a series RLC circuit. The switch is closed at time  $t = 0$ .

For  $t \geq 0$ , the transform

D/w

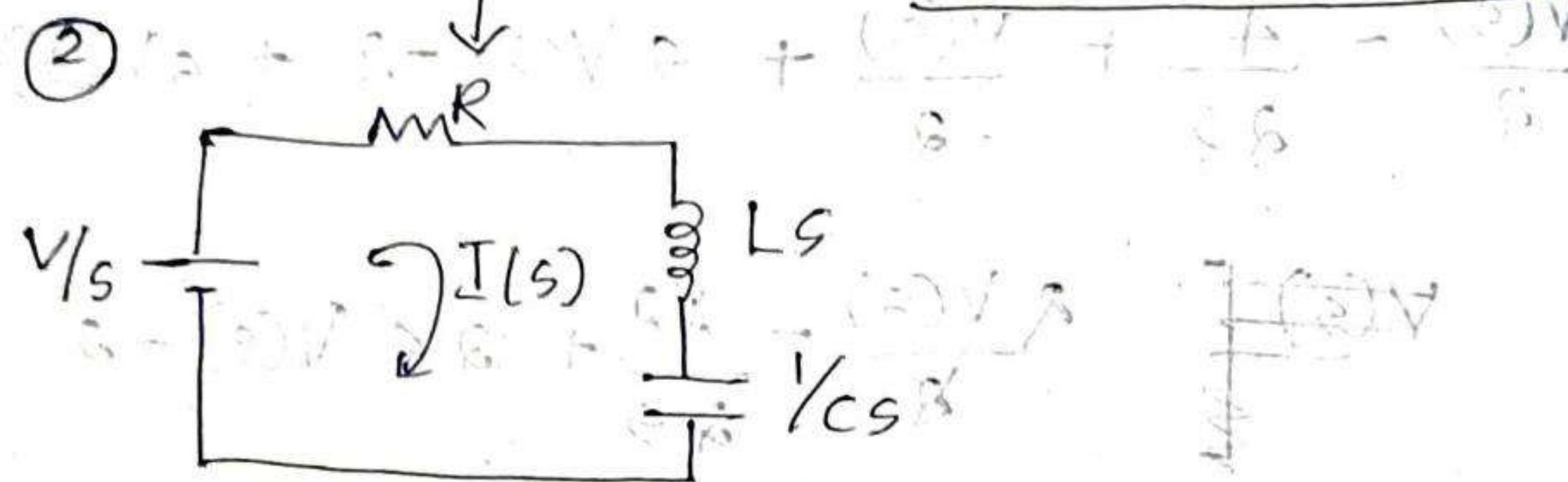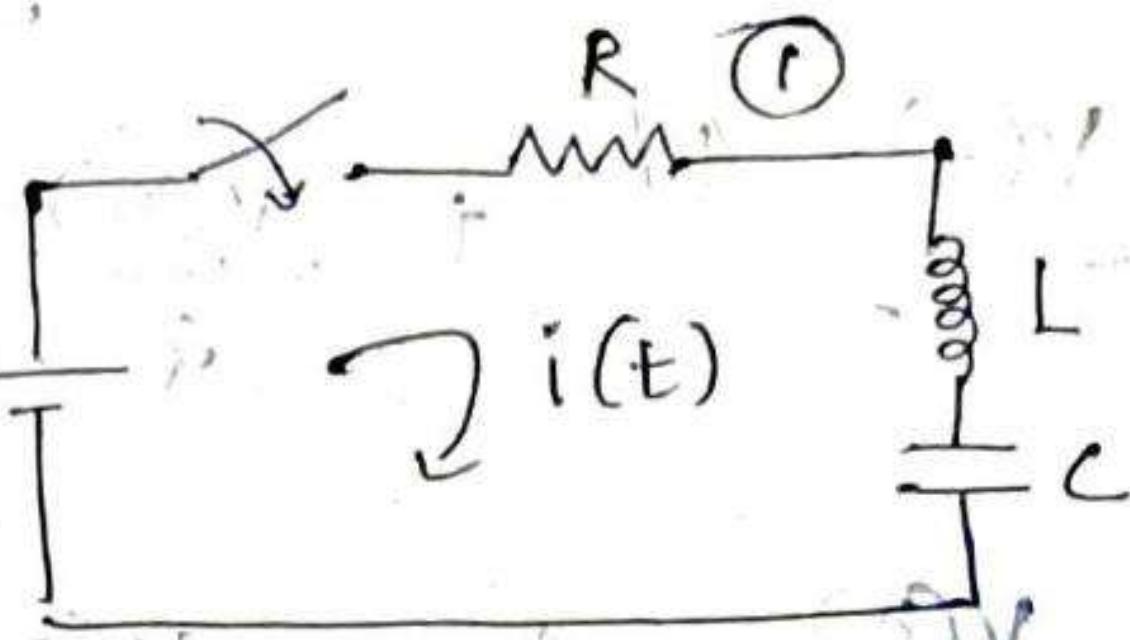

Applying KVL

$$\frac{V}{s} = R I(s) + L s I(s) + \frac{1}{cs} I(s)$$

$$\frac{V}{s} = I(s) \left[ R + Ls + \frac{1}{cs} \right]$$

$$\frac{V}{s} = I(s) \left[ \frac{Rcs + Lcs^2 + 1}{cs} \right]$$

$$I(s) = \frac{VC}{(s^2 + \frac{R}{L}s + \frac{1}{LC})}$$

$$= \frac{VC}{Lcs^2 + Rcs + 1}$$

$$I(s) = \frac{VC}{LC \left[ s^2 + \frac{R}{L}s + \frac{1}{LC} \right]}$$

$$= \frac{V/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$-b \pm \sqrt{b^2 - 4ac}$

$$= \frac{V/L}{(s-a)(s-b)}$$

a and b are roots of  $s^2 + \frac{R}{L}s + \frac{1}{LC}$

$$a, b = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\alpha = -\frac{R}{2L}$$

$$\beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$a = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$= -\alpha + \sqrt{\alpha^2 - \omega_0^2} = \underline{-\alpha + \beta}$$

$$b = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$= -\alpha - \sqrt{\alpha^2 - \omega_0^2} = \underline{-\alpha - \beta}$$

$$\alpha = \frac{R}{2L} \quad \text{and} \quad \beta = \sqrt{\alpha^2 - \omega_0^2}$$

$$I(s) = \frac{A}{s-a} + \frac{B}{s-b}$$

$$\frac{1}{s-a} < \frac{1}{s-b}$$

$$s_a < s_b$$

$$A = (s-a) I(s) \Big|_{s=a} = \frac{V/L}{(s-a)(s-b)} \Big|_{s=a}$$

$$= \frac{V/L}{a-b}$$

$$B = (s-b) I(s) \Big|_{s=b} = \frac{V/L}{(s-a)(s-b)} \Big|_{s=b}$$

$$= \frac{V/L}{b-a}$$

$$= -\frac{V/L}{a-b}$$

$$I(s) = \frac{V/L/a-b}{s-a} - \frac{V/L/a-b}{s-b}$$

$$= \frac{V}{L(a-b)} \left[ \frac{1}{s-a} - \frac{1}{s-b} \right]$$

$$i(t) = \frac{V}{L(a-b)} \left[ e^{at} - e^{bt} \right]$$

$$= \underline{k_1 e^{at} - k_2 e^{bt}}$$


13/10/2020

Now depending upon the values of  $a$  and  $b$ .

Case 1; When the roots are real and unequal, it gives an overdamped response

$$\frac{R}{2L} > \frac{1}{\sqrt{LC}}$$

$$\alpha > \omega_0$$

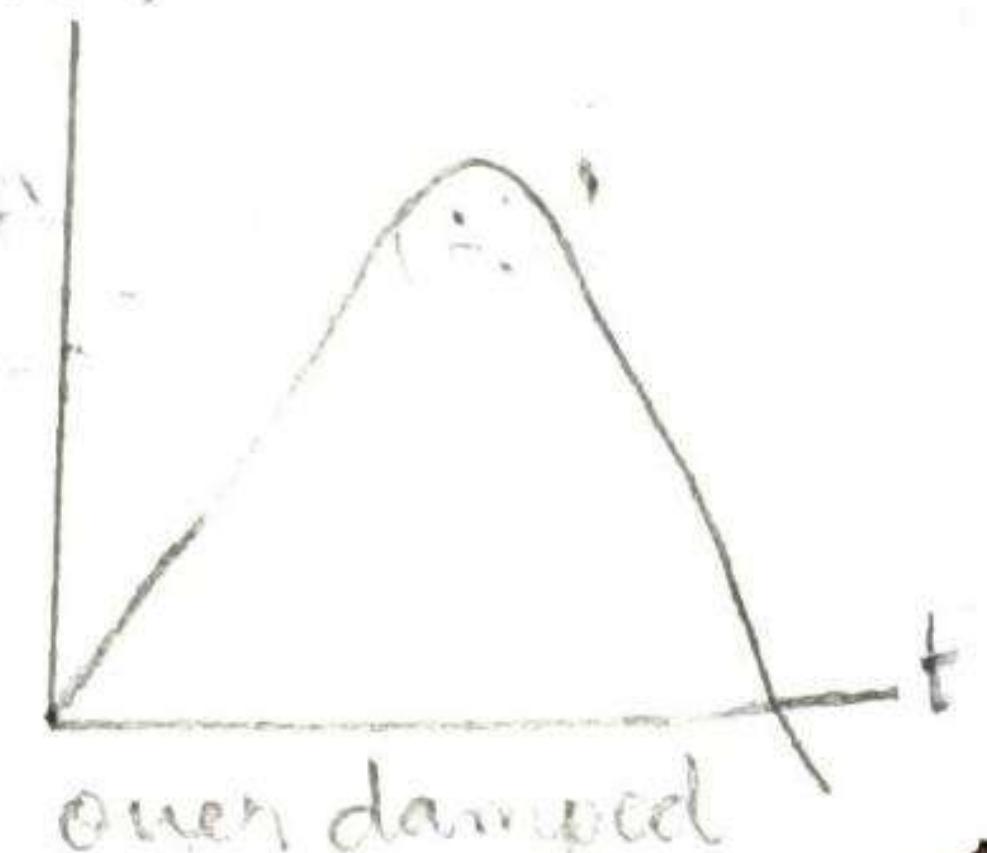


$$i(t) = k_1 e^{at} + k_2 e^{bt}$$

Case II; When the roots are real and equal, it gives a critically damped response  $i(t)$

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}}$$

$$\alpha = \omega_0$$


$$i(t) = e^{-\alpha t} [k_1 + k_2 t]$$

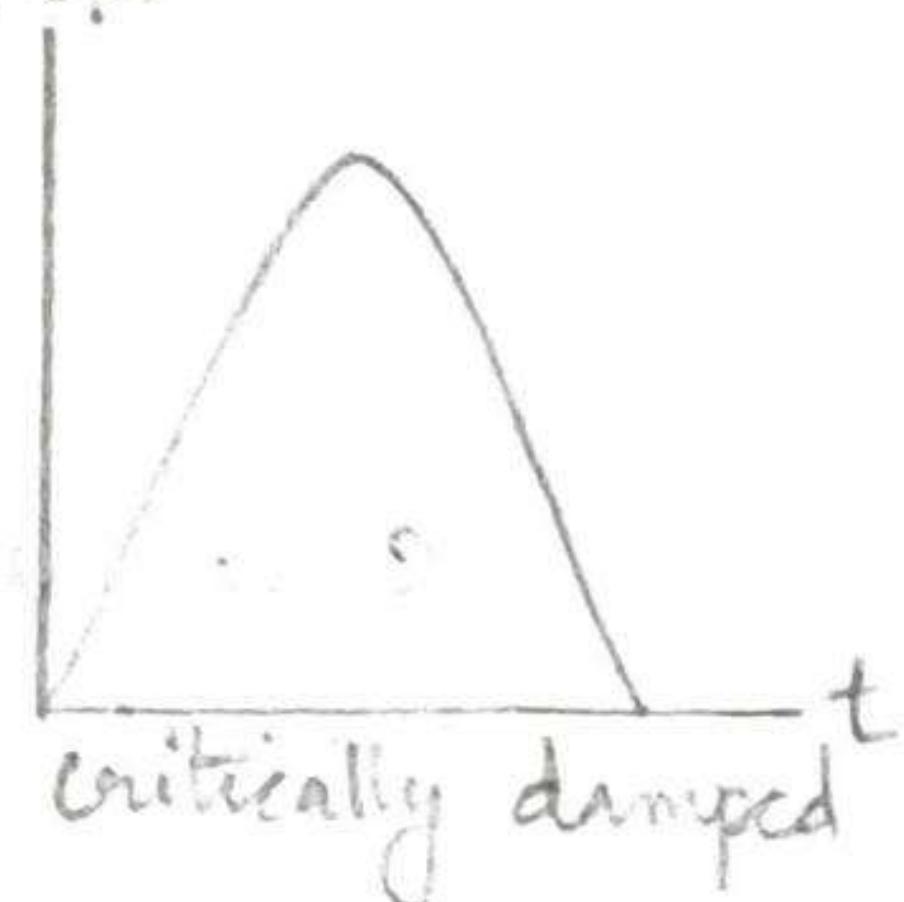

Case III; When the roots are complex conjugate, it gives an under-damped response  $i(t)$

$$\frac{R}{2L} < \frac{1}{\sqrt{LC}}$$

$$i(t) = k_1 e^{at} + k_2 e^{bt}$$

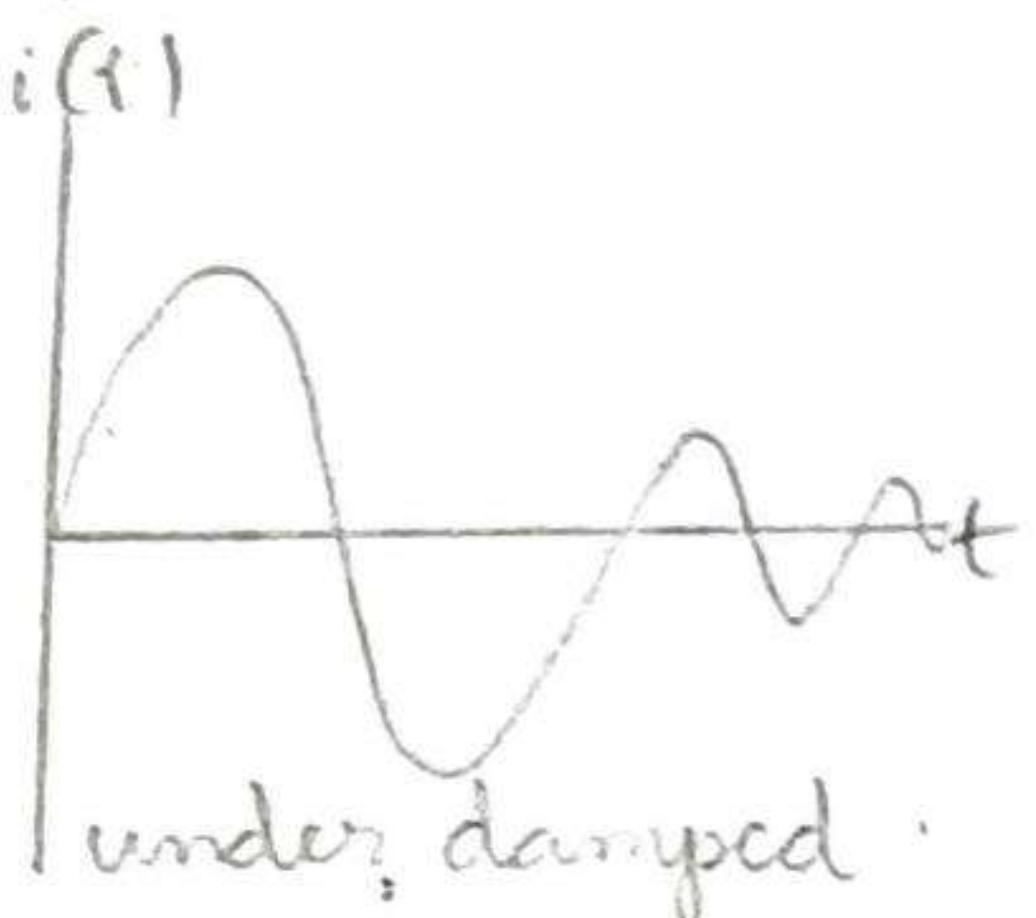


$$a, b = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\sqrt{\alpha^2 - \omega_0^2} = \sqrt{-1} \sqrt{\omega_0^2 - \alpha^2} = j\omega_d$$


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$i(t) = e^{-\alpha t} [k_1 e^{j\omega_d t} + k_2 e^{-j\omega_d t}]$$

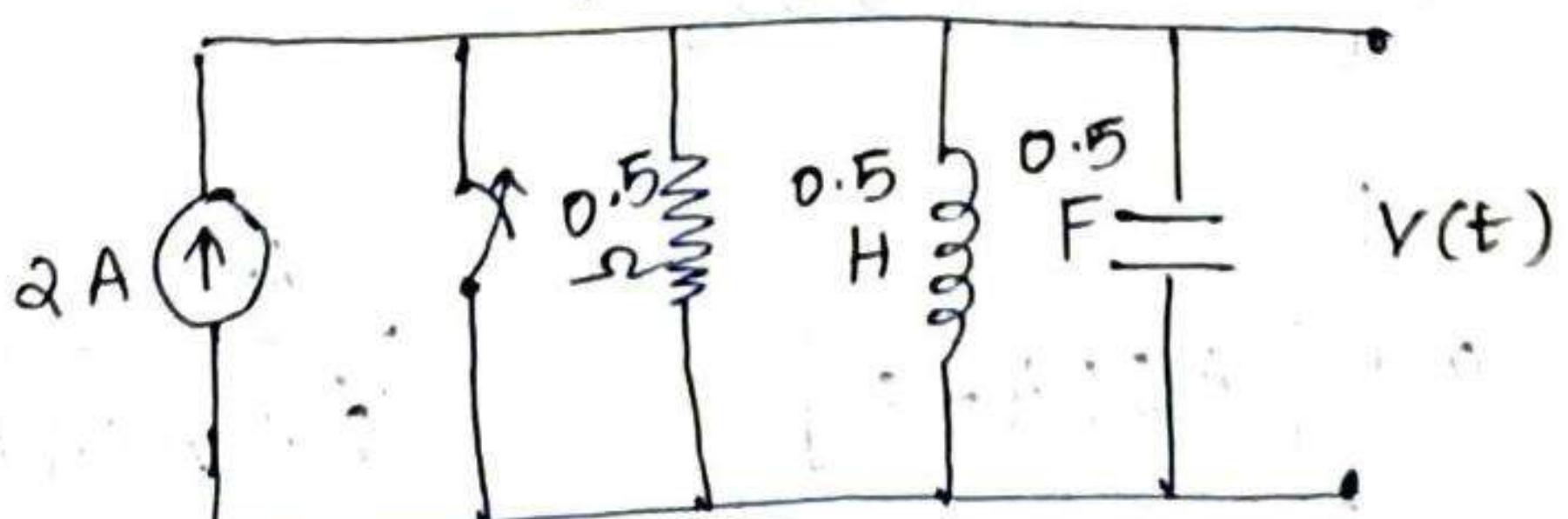Q. The switch is open at  $t=0$ , Determine  $V(t)$



Help n/w

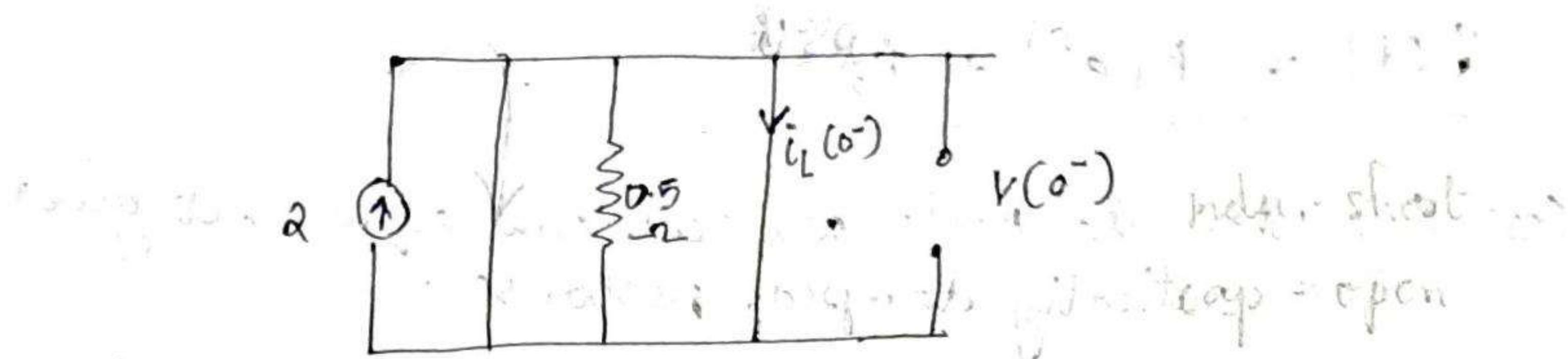

$$i_L(0^-) = 0$$


$$v(0^-) = 0$$

Since the current through inductor and capacitor cannot change instantaneously

$$i_L(0^+) = 0$$

$$v(0^+) = 0 \quad \text{from all nodes}$$

Nodal analysis

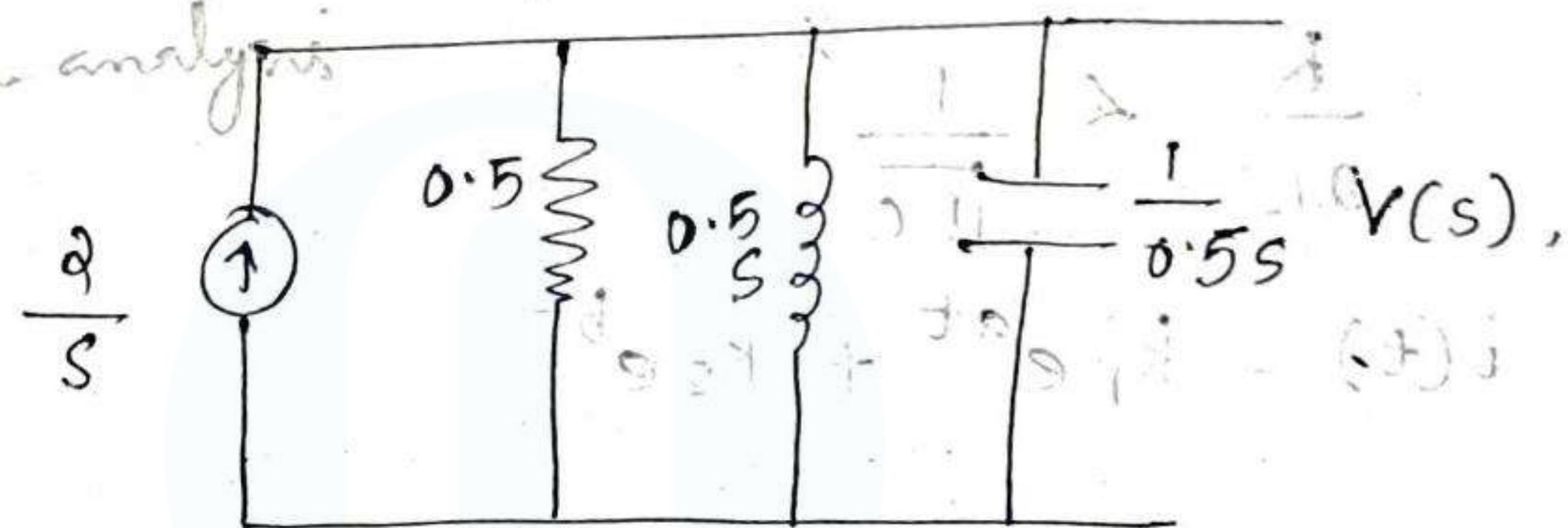

$$\frac{d}{s} = \frac{V(s)}{0.5} + \frac{V(s)}{0.5s} + \frac{V(s)}{0.5s}$$

$$= 2V(s) + \frac{2V(s)}{s} + 0.5sV(s)$$

$$\frac{d}{s} = V(s) \left[ 2 + \frac{2}{s} + 0.5s \right] = (s+2)(s+0.5)$$

$$V(s) = \frac{s}{s \left[ 2 + \frac{2}{s} + 0.5s \right]}$$


$$= \frac{s}{0.5 \left[ 4s + 4 + s^2 \right]} = \frac{4}{s^2 + 4s + 4}$$



$$= \frac{4}{(s+2)^2}$$

$$V(t) = \underline{4t e^{-2t}}$$

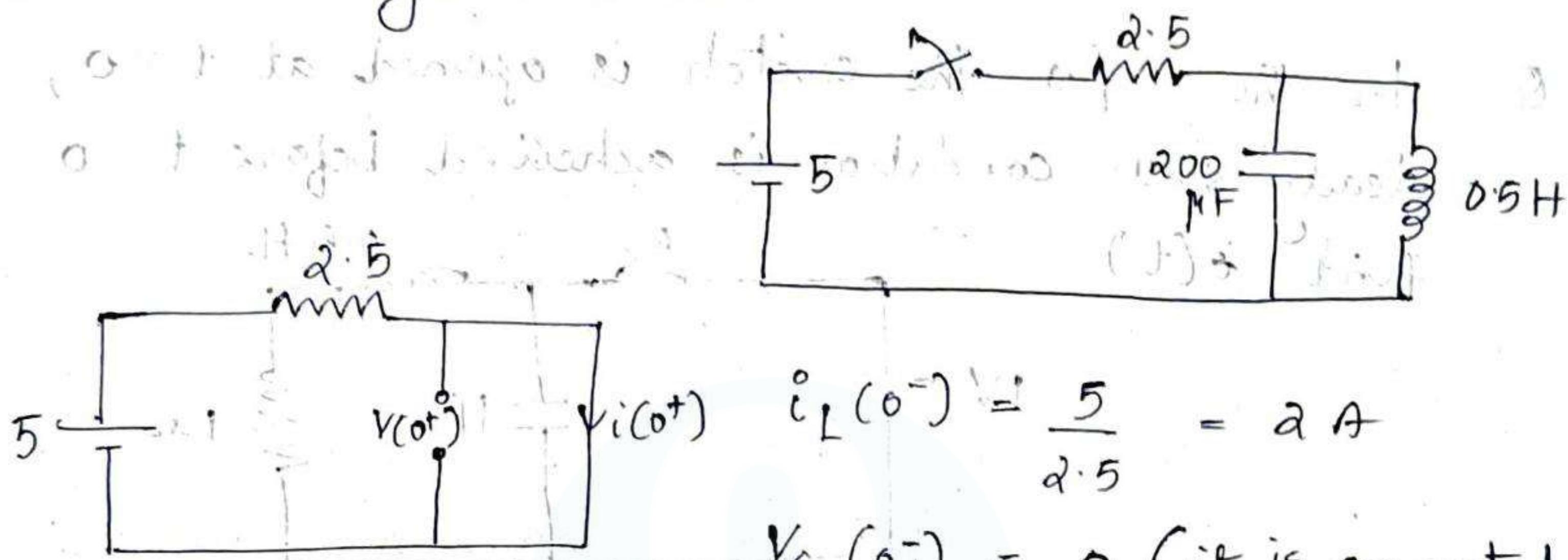- 2) In the network, the switch is closed and steady state 0 is attained. At  $t = 0$ , switch is opened. Determine current through inductor.




$$i_L(0^-) = \frac{5}{2.5} = 2 \text{ A}$$

$V_C(0^-) = 0$  (it is connected || to short)

$$i_L(0^+) = 2 \text{ A}$$

$$V_C(0^+) = 0$$

At  $t > 0$

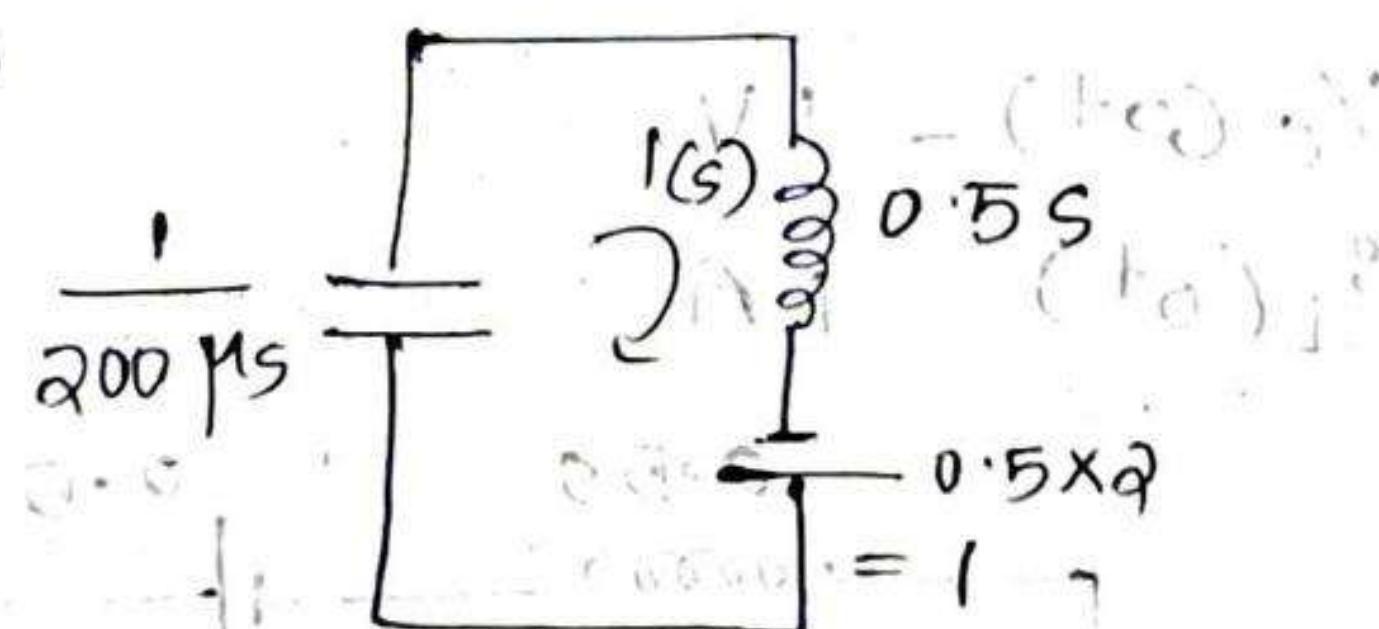

$$I = \frac{1}{200 \mu s} I(s) + 0.5 s J(s)$$

$$= \frac{I(s)}{200 \times 10^{-6}} + \left[ \frac{1}{200 \times 10^{-6}} + 0.5 s \right]$$

$$= I(s) \left[ \frac{5000}{s} + 0.5 s \right]$$

$$I(s) = \frac{1}{\frac{5000 + 0.5s^2}{s}} = \frac{s}{0.5[s^2 + 10000]}$$


$$= \frac{2s}{s^2 + 10000}$$

$$j6s + j1 = (3+j)$$

Q. At  $t=0$ ,  $i(t) = 2 \times \cos 100t$ . Find initial value of  $i_L$  at  $t=0$ . Given  $\omega = 100 \text{ rad/s}$ . Find initial value of  $v_C$  at  $t=0$ .


Q. In the circuit the switch is opened at  $t=0$ , steady state condition is achieved before  $t=0$ .

Find  $i_L(t)$

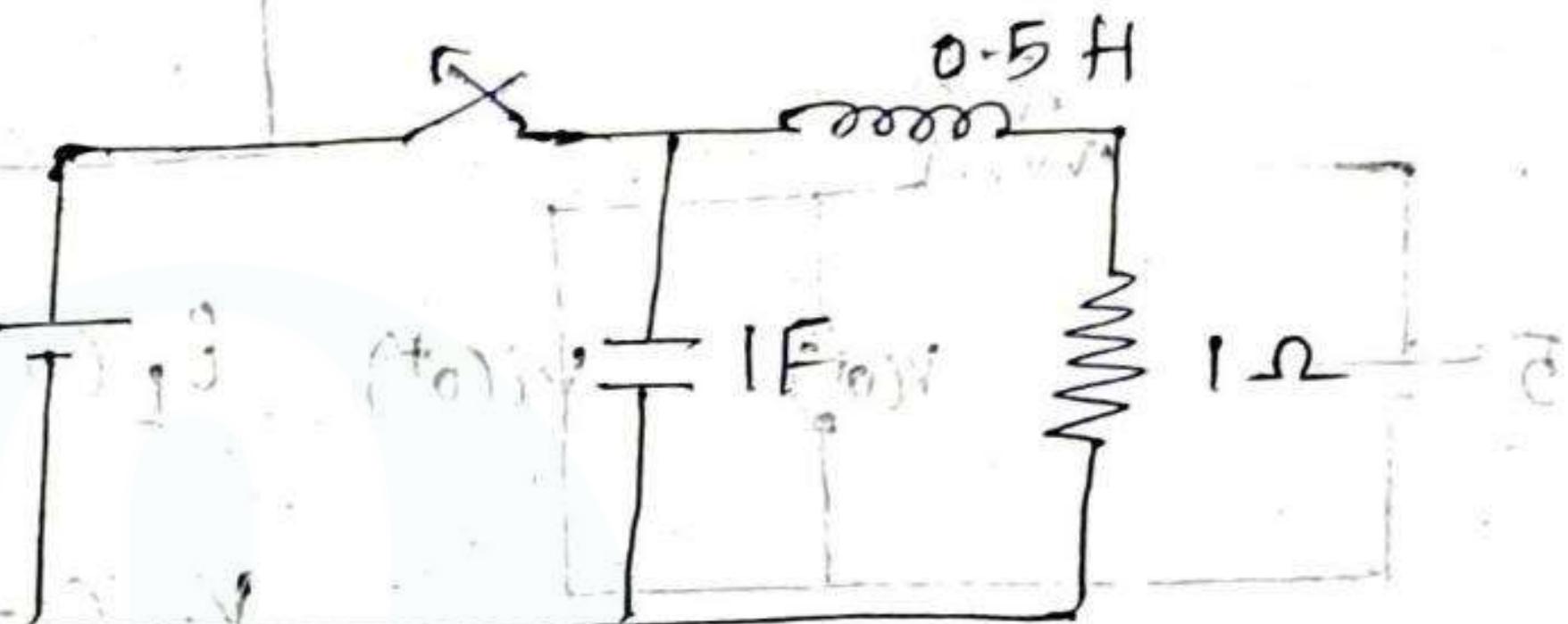

At  $t=0^-$

(Initial values)

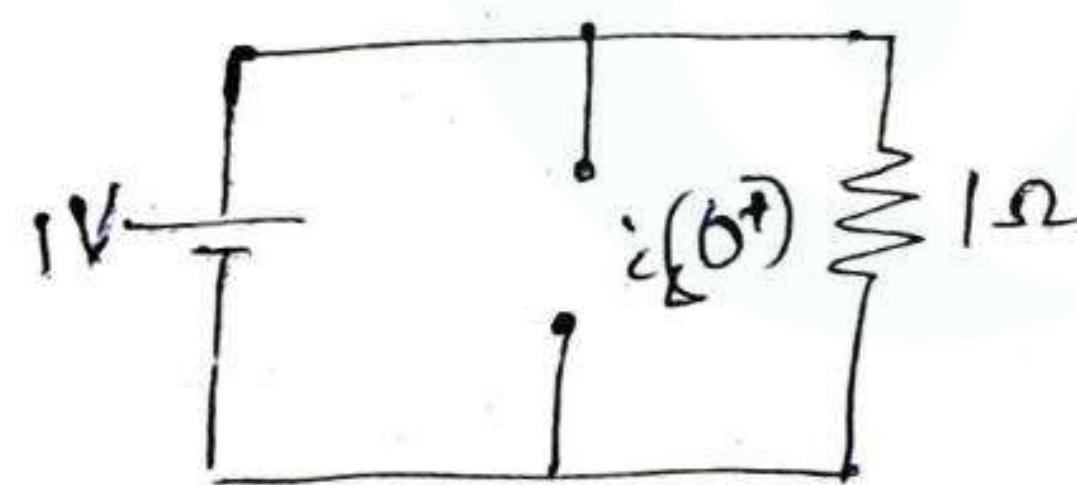


$$v_C(0^-) = 1V$$

$$i_L(0^-) = 1A$$

$$v_C(0^+) = 1V$$

$$i_L(0^+) = 1A$$

At  $t > 0$

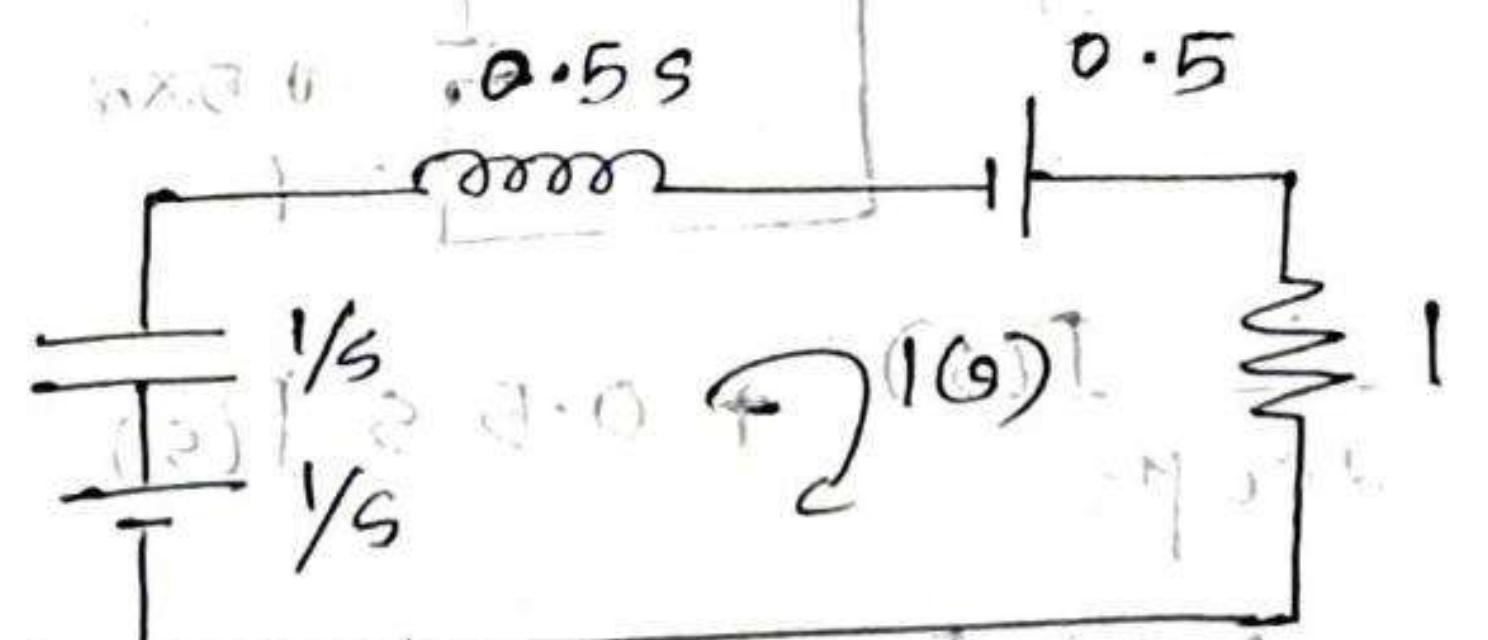

$$\frac{1}{s} + 0.5 = \left[ \frac{1}{s} I(s) + 0.5s \right] (s) + I(s)$$

$$\frac{1+0.5}{s} = I(s) \left[ \frac{1 + 0.5s^2 + s}{s} \right]$$



$$I(s) = \frac{0.5s + 1}{0.5s^2 + s + 1} = \frac{0.5(s+2)}{0.5(s^2 + 2s + 2)}$$

$$= \frac{s+2}{s^2 + 2s + 2} = \frac{s+1+1}{(s+1)^2 + 1}$$

$$I(s) = \frac{s+1}{(s+1)^2 + 1} + \frac{1}{(s+1)^2 + 1}$$

$$I(t) = e^{-t} \cos t + e^{-t} \sin t$$

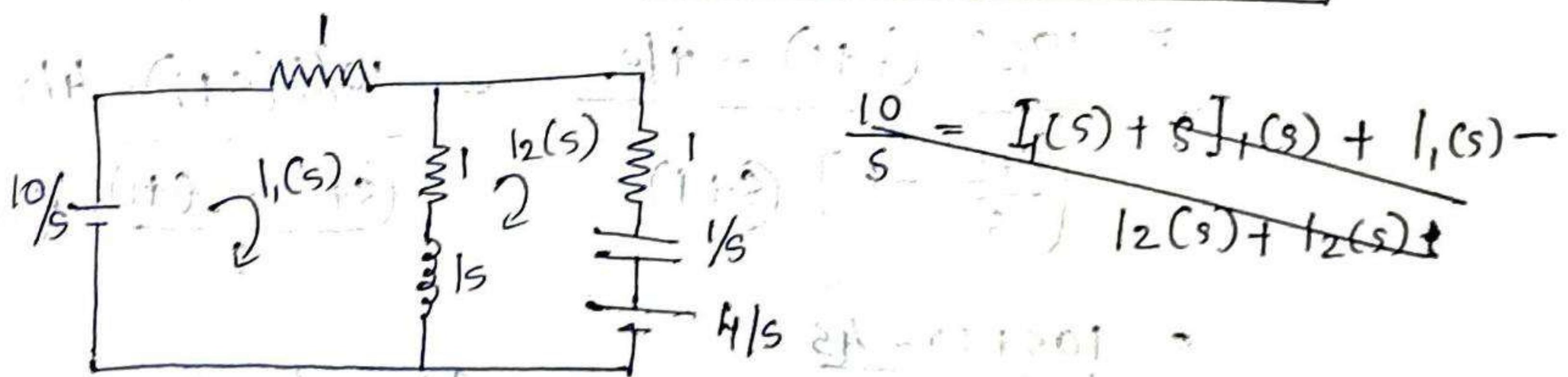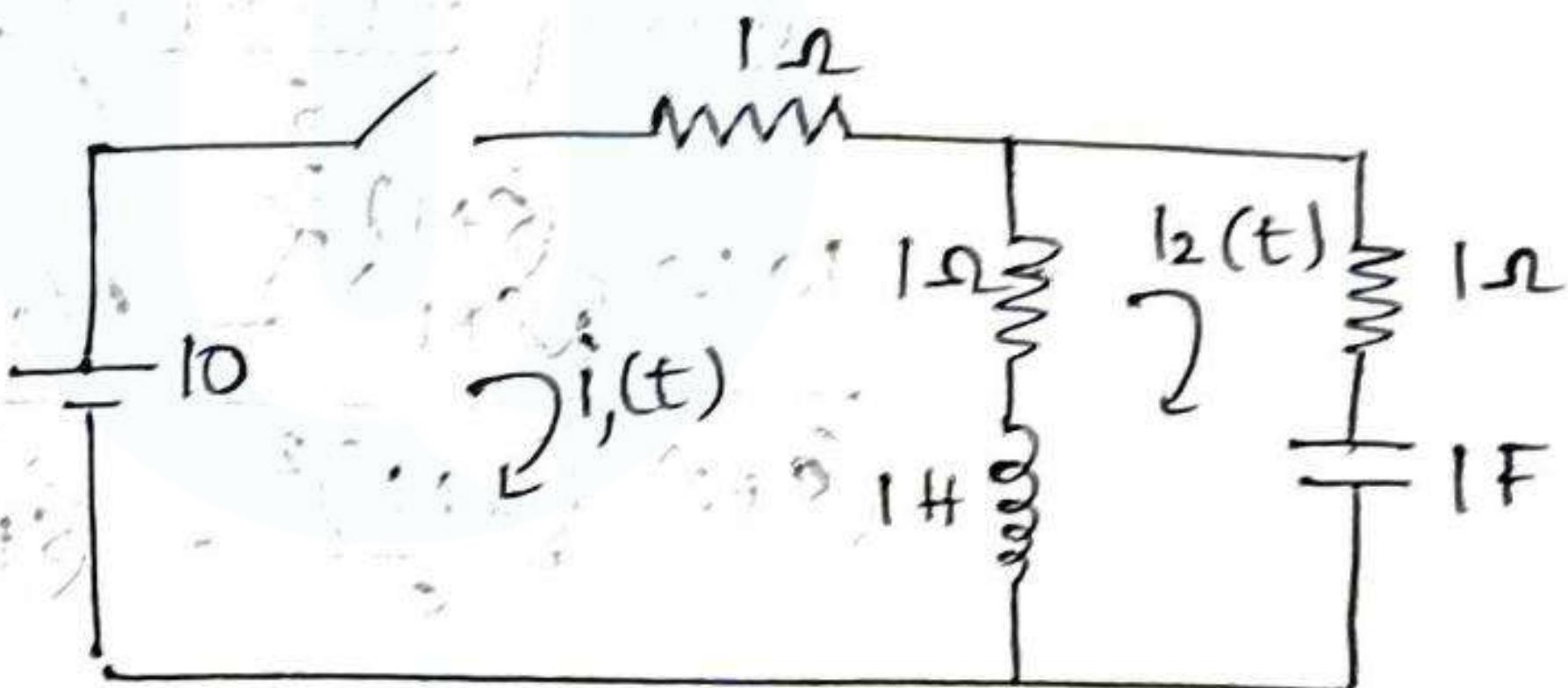Q4, In the a/w the switch is closed at  $t=0$ , Find the current  $i_1(t)$  when the initial current through inductor is 0 and initial voltage on capacitor is 4V.



$$\frac{10}{s} = I_1(s) + sI_1(s) + I_2(s) - I_2(s) - I_2(s)$$

$$\frac{10}{s} = [2+s] I_1(s) - (1-s) I_2(s)$$

$$\frac{-1}{s} = -(1+s) I_1(s) + \left(2+s+\frac{1}{s}\right) I_2(s)$$

$$\begin{bmatrix} s+2 & -(s+1) \\ -(s+1) & (2+s+1/s) \end{bmatrix} \cdot \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} 10/s \\ -4/s \end{bmatrix}$$

$$I_1(s) = \frac{\begin{vmatrix} 10/s & -(s+1) \\ -4/s & s+2+1/s \end{vmatrix}}{\begin{vmatrix} (s+2) & -(s+1) \\ -(s+1) & (s+2+1/s) \end{vmatrix}}$$

$$= \frac{10/s(s+2+1/s) - -(s+1)(-4/s)}{(s+2)(s+2+1/s) - (s+1)(s+1)}$$

$$= \frac{10/s^2 [s^2 + 2s + 1] - \frac{4}{s}(s+1)}{(s+2)(\frac{s^2 + 2s + 1}{s}) - (s+1)^2}$$

$$= \frac{10/s^2 (s+1)^2 - 4/s(s+1)}{(s+2)(\frac{s+1}{s})^2 - (s+1)^2} = (s+1)$$

$$= \frac{10/s^2 (s+1) - 4/s}{(s+2)(s+1)} = \frac{10/s^2 (s+1) - 4/s}{(s+2)(s+1)} = \frac{10/s^2 (s+1) - 4/s}{(s+2)(s+1)}$$

$$= \frac{10s + 10 - 4s}{s^2} = \frac{6s + 10/s^2 \times s}{4s + 2} = \frac{6s + 10/s^2 \times s}{4s + 2}$$

$$(s+1)(1+2+\frac{5}{s}) + (s+1) = \frac{23s+5}{s(s+1)}$$

$$\frac{3s+5}{s(s+1)} = \frac{A}{s} + \frac{B}{s+1}$$

$$A = \left. \frac{3s+5}{s+1} \right|_{s=0} = 5$$

$$B = \left. \frac{3s+5}{s} \right|_{s=-1} = \frac{-3+5}{-1} = -2$$


$$I(s) = \frac{5}{s} + \frac{-2}{s+1}$$

$$i(t) = 5 - 2e^{-t}$$

14/10/2020

Transients in circuits excited by AC source.

RL circuit excited by AC source

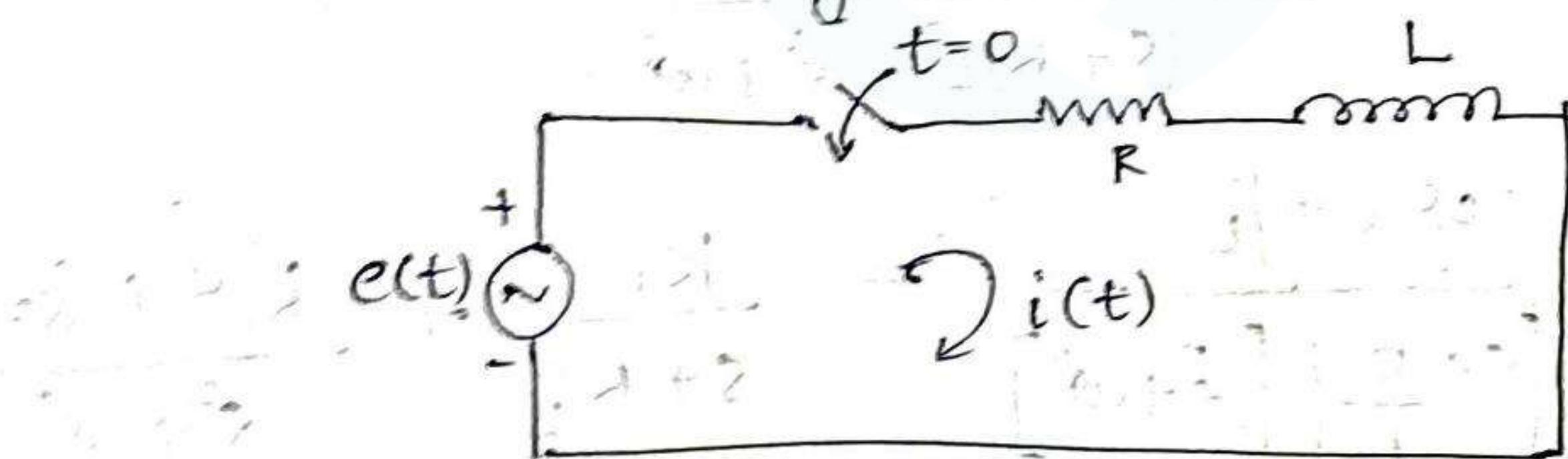


Consider the RL circuit. Let the circuit be excited by sinusoidal source  $e(t) = E_m \sin \omega t$ . When the switch is closed at  $t=0$ , let  $i(t)$  be the current through the circuit. Let us assume that there is no stored energy in the circuit.

$$L[i(t)] = I(s)$$

$$L[e(t)] = E(s)$$

$$E(s) = L[e(t)] = L[E_m \sin \omega t] \\ = E_m \cdot \frac{\omega}{s^2 + \omega^2}$$

The s domain RL circuit is shown below

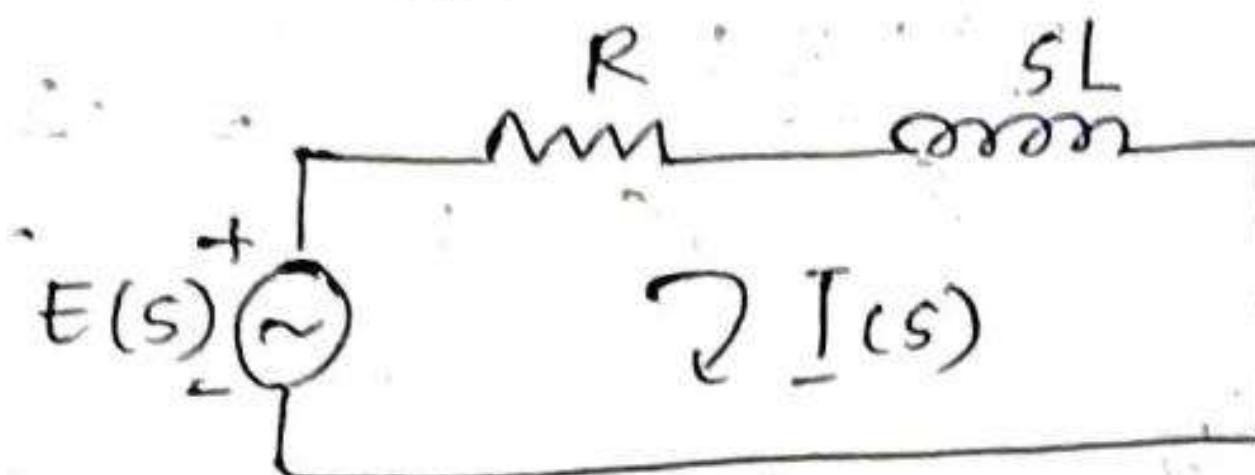

$$[R + LS] I(s) = E(s)$$

$$I(s) = \frac{E(s)}{R + LS} = E(s) \cdot \frac{1}{L[s + R/L]}$$

$$= \frac{\omega E_m}{s^2 + \omega^2} \times \frac{1}{L[s + R/L]}$$

$$= \frac{\omega E_m / L}{(s + R/L)(s^2 + \omega^2)}$$

$$I(s) = \frac{\omega E_m / L}{\left[s + \frac{R}{L}\right] \left[s^2 + \omega^2\right]} = \frac{k_1}{s + R/L} + \frac{k_2 s + k_3}{s^2 + \omega^2}$$

$$k_1 = \frac{\omega E_m / L}{(s + R/L)(s^2 + \omega^2)} \Big|_{s = -R/L}$$

$$\text{we get } k_1 = \frac{\omega E_m / L}{-R^2/L^2 + \omega^2}$$

$$= \frac{\omega E_m / L}{R^2 + \omega^2 L^2}$$

$$= \frac{\omega L E_m}{R^2 + \omega^2 L^2}$$

In frequency domain, magnitude of impedance of RL circuit is given by

$$\pi = R + j X_L$$

$$= \sqrt{R^2 + \omega^2 L^2}$$

$$X_L = \omega L$$

$$\pi^2 = R^2 + \omega^2 L^2$$

$$k_1 = \frac{\omega L E_m}{\pi^2}$$

$$\frac{\omega E_m / L}{(s + \frac{R}{L})(s^2 + \omega^2)} = \frac{k_1}{s + R/L} + \frac{k_2 s + k_3}{s^2 + \omega^2}$$

$$\frac{\omega E_m / L}{(s + R/L)(s^2 + \omega^2)} = \frac{k_1 (s^2 + \omega^2) + (k_2 s + k_3)(s + R/L)}{(s + R/L)(s^2 + \omega^2)}$$

$$\begin{aligned} \frac{\omega E_m}{L} &= k_1 s^2 + k_1 \omega^2 + k_2 s^2 + k_2 s R/L + k_3 s \\ &\quad + k_3 R/L \\ &= (k_1 + k_2) s^2 + [k_2 R/L + k_3] s + k_1 \omega^2 \\ &\quad + k_3 R/L \end{aligned}$$

Coeff: of  $s^2$

$$k_1 + k_2 = 0$$

$$k_2 = -k_1$$

$$k_2 = \frac{-\omega L E_m}{\pi^2}$$

Equating coeff: of  $s$  ..

$$k_2 \cdot \frac{R}{L} + k_3 = 0$$

$$-\frac{\omega L E_m}{\zeta^2} \times \frac{R}{L} = -k_3$$

$$k_3 = \frac{\omega L E_m R}{\zeta^2}$$

$$I(s) = \frac{\frac{\omega L E_m}{\zeta^2}}{s + R/L} + \frac{-\frac{\omega L E_m}{\zeta^2} s + \frac{\omega R E_m}{\zeta^2}}{s^2 + \omega^2}$$

$$= \frac{\omega L E_m}{\zeta^2} \times \frac{1}{s + R/L} - \frac{\omega L E_m}{\zeta^2} \frac{s}{s^2 + \omega^2} + \frac{R E_m}{\zeta^2} \frac{1}{s^2 + \omega^2}$$

$$i(t) = \frac{\omega L E_m}{\zeta^2} e^{-R/L t} - \frac{\omega L E_m}{\zeta^2} \cos \omega t + \frac{R E_m}{\zeta^2} \sin \omega t$$

$$i(t) = \frac{\omega L E_m}{\zeta^2} e^{-R/L t} + \frac{E_m}{\zeta^2} [R \sin \omega t - \omega \cos \omega t]$$


$$\text{Ansatz: } i(t) = A \sin(\omega t + \phi)$$

$$\tan \phi = \frac{\omega L}{R}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

$$\cos \phi = R/\zeta$$

$$R = \zeta \cos \phi$$

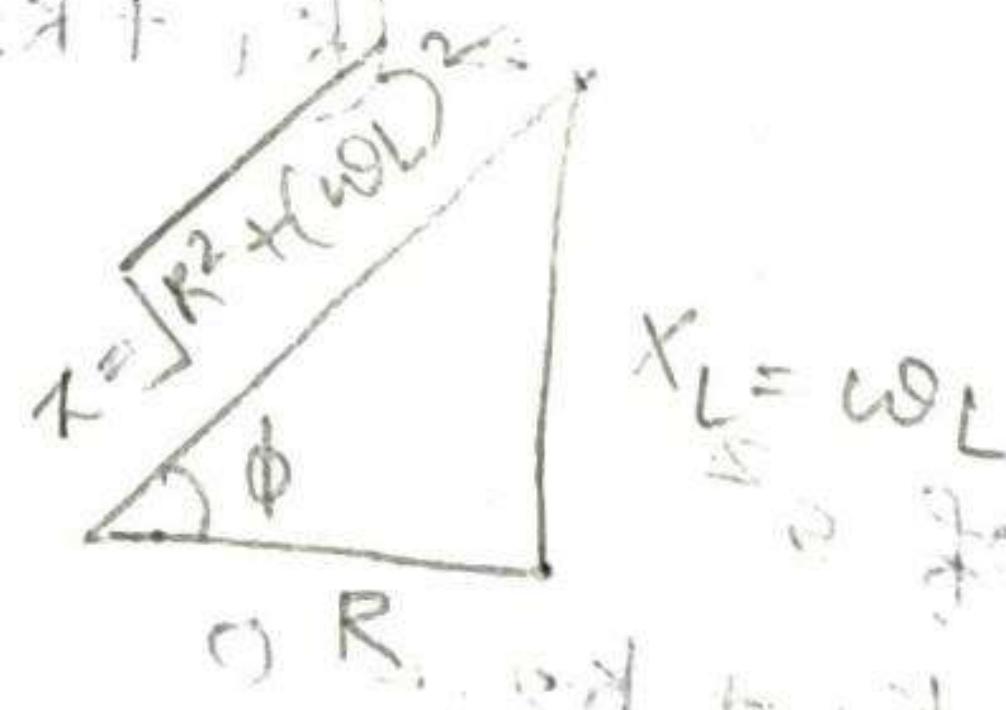


$$\sin \phi = \frac{\omega L}{Z}$$

$$\omega L = \zeta \sin \phi$$

$$\begin{aligned}
 i(t) &= \frac{\omega L E_m}{\pi^2} e^{-R/Lt} + \frac{E_m}{\pi^2} \left[ \sin \omega t \cdot \pi \cos \phi - \right. \\
 &\quad \left. \pi \sin \phi \cdot \cos \omega t \right] \\
 &= \frac{\omega L E_m}{\pi^2} e^{-R/Lt} + \frac{E_m}{\pi^2} \times \cancel{\pi} \left[ \sin \omega t \cos \phi - \sin \phi \right. \\
 &\quad \left. \cos \omega t \right] \\
 i(t) &= \underbrace{\frac{\omega L E_m}{\pi^2} e^{-R/Lt}}_{\text{Transient part}} + \underbrace{\frac{E_m}{\pi} \sin(\omega t - \phi)}_{\text{Steady state part}}
 \end{aligned}$$

15/10/2020

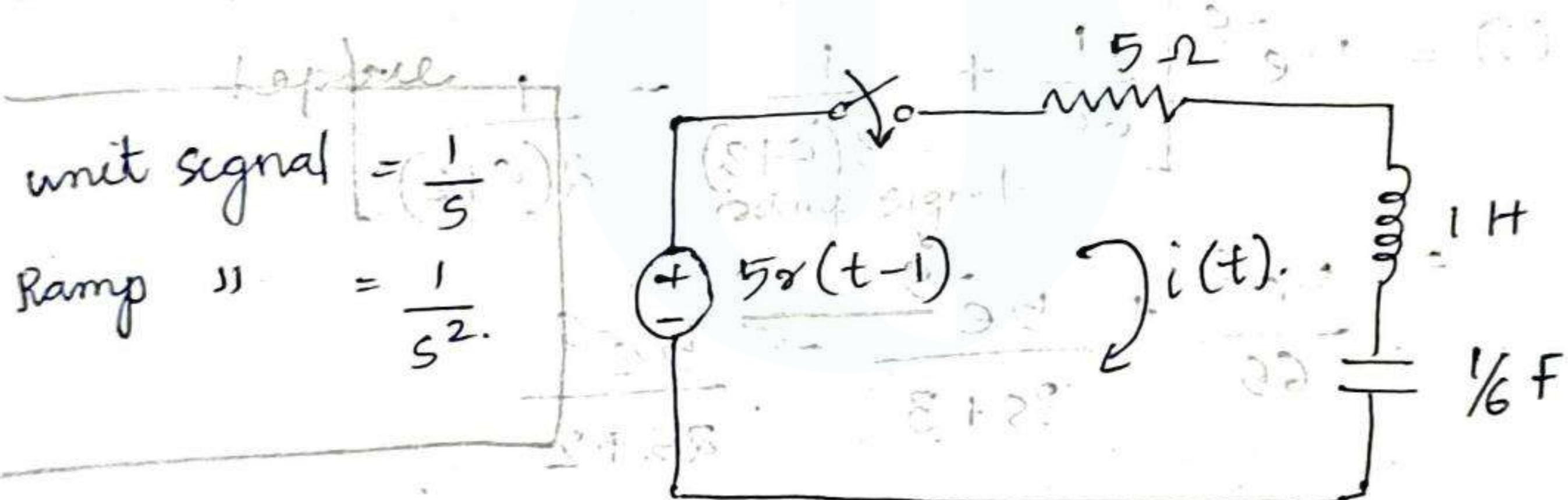
Q. Determine the current  $i(t)$  when the switch is closed at  $t=0$  with zero initial conditions.



At  $t=0$ , KVL applied:

$$\frac{5e^{-s}}{s^2} - 5i(s) - sI(s) - 6/s I(s) = 0$$
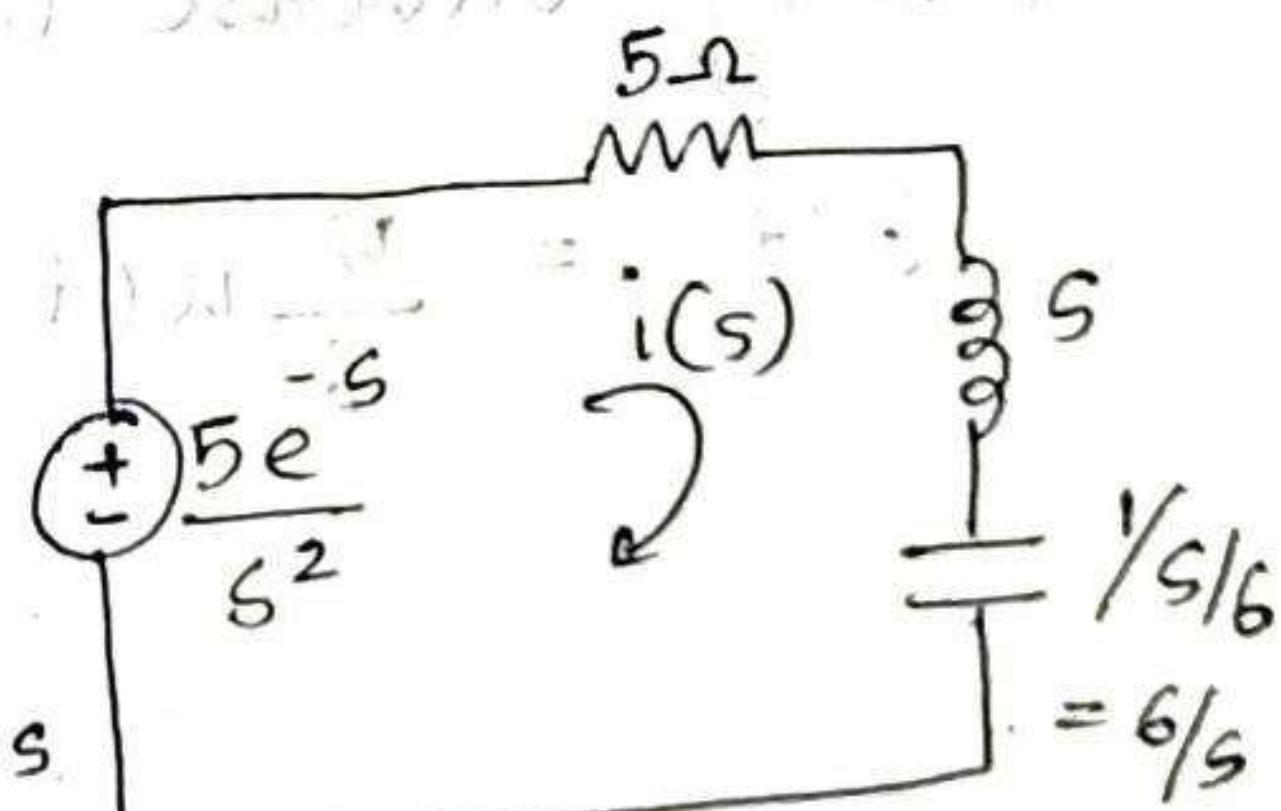
$$5\bar{I}(s) + s\bar{I}(s) + 6/s \bar{I}(s) = \frac{5e^{-s}}{s^2}$$



At  $s=0$

$$\bar{I}(s) = \frac{5e^{-s}}{s(s^2 + 5s + 6)}$$

$$I(s) = \frac{5e^{-s}}{s(s^2 + 5s + 6)} = \frac{5e^{-s}}{s(s+3)(s+2)}$$

By partial fraction expansion:

$$\frac{1}{s(s+3)(s+2)} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{s+2}$$

$$(4 - 1) A = \left. \frac{1}{(s+3)(s+2)} \right|_{s=0} = \frac{1}{6}$$

$$B = \left. \frac{1}{s(s+2)} \right|_{s=-3} = \frac{1}{3}$$

$$C = \left. \frac{1}{s(s+3)} \right|_{s=-2} = \frac{1}{2}$$

$$I(s) = 5e^{-s} \left[ \frac{1}{6s} + \frac{1}{3(s+3)} - \frac{1}{2(s+2)} \right]$$

$$= \frac{5e^{-s}}{6s} + \frac{5e^{-(s+3)}}{3s+3} - \frac{5e^{-(s+2)}}{2s+2}$$


Taking inverse laplace

$$c(t) = \frac{5}{6} u(t-1) + \frac{5}{3} e^{-3(t-1)} u(t-1) - \frac{5}{2} e^{-2(t-1)} u(t-1)$$

$$u(t) = \frac{1}{s^2}$$

$$e^{-st} = u(t-1)$$

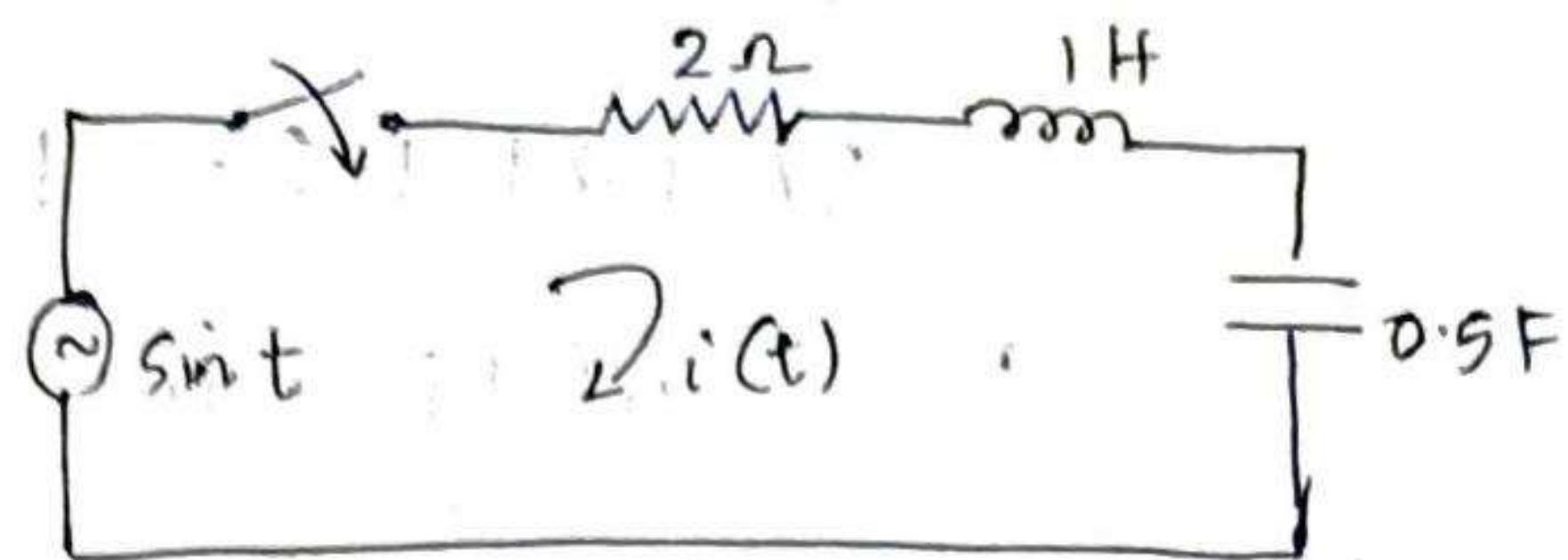Q. Switch is closed at  $t = 0$ . Determine the current  $i(t)$  assuming zero initial condition.



Transformed network

$$\frac{1}{s^2+1} - 2I(s) - sI(s) - \frac{2}{s}I(s) = 0$$

$\sim \frac{1}{s^2+1} \quad 2I(s) \quad \frac{2}{s}$

$$\left(2 + s + \frac{2}{s}\right)I(s) = \frac{1}{s^2+1}$$

$$\frac{s}{(s^2+1)(s^2+2s+2)}$$

$$= \frac{s}{(s^2+1)(s^2+2s+2)}$$

Partial fraction

$$I(s) = \frac{As+B}{s^2+1} + \frac{Cs+D}{s^2+2s+2}$$

$$s = (As+B)(s^2+2s+2) + (Cs+D)(s^2+1)$$

$$As^3 + 2As^2 + As + Bs^2 + 2Bs + 2B + Cs^3 + Cs + Ds^2 + D$$

$$= (A+C)s^3 + (2A+B+D)s^2 + (2A+2B+C)s + 2B+D$$

$$A + C = 0$$

$$2A + B + D = 0$$

$$2A + 2B + C = 1$$

$$2B + D = 0$$

we get  $A = 0.2$ ,  $B = 0.4$ ,  $C = -0.2$ ,  $D = -0.8$ .

$$\begin{aligned} I(s) &= \frac{0.2s + 0.4}{s^2 + 1} - \frac{0.2s + 0.8}{s^2 + 2s + 2} \\ &= \frac{0.2s}{s^2 + 1} + \frac{0.4}{s^2 + 1} - \frac{0.2s + 0.2 + 0.6}{(s+1)^2 + 1^2} \\ &= \frac{0.2s}{s^2 + 1} + \frac{0.4}{s^2 + 1} - \frac{0.2(s+1)}{(s+1)^2 + 1} - \frac{0.6}{(s+1)^2 + 1} \end{aligned}$$


taking inverse laplace

$$\begin{aligned} i(t) &= 0.2 \cos t + 0.4 \sin t - 0.2 e^{-t} \cos t - 0.6 e^{-t} \sin t \\ &\approx 0.2 \cos t + 0.4 \sin t - \overline{e^{-t}} (0.2 \cos t + 0.6 \sin t) \end{aligned}$$

17/10/2020 RC circuit excited by an AC source

Consider the RC circuit. Let the circuit be excited by a sinusoidal source.

$$e(t) = E_m \sin \omega t$$

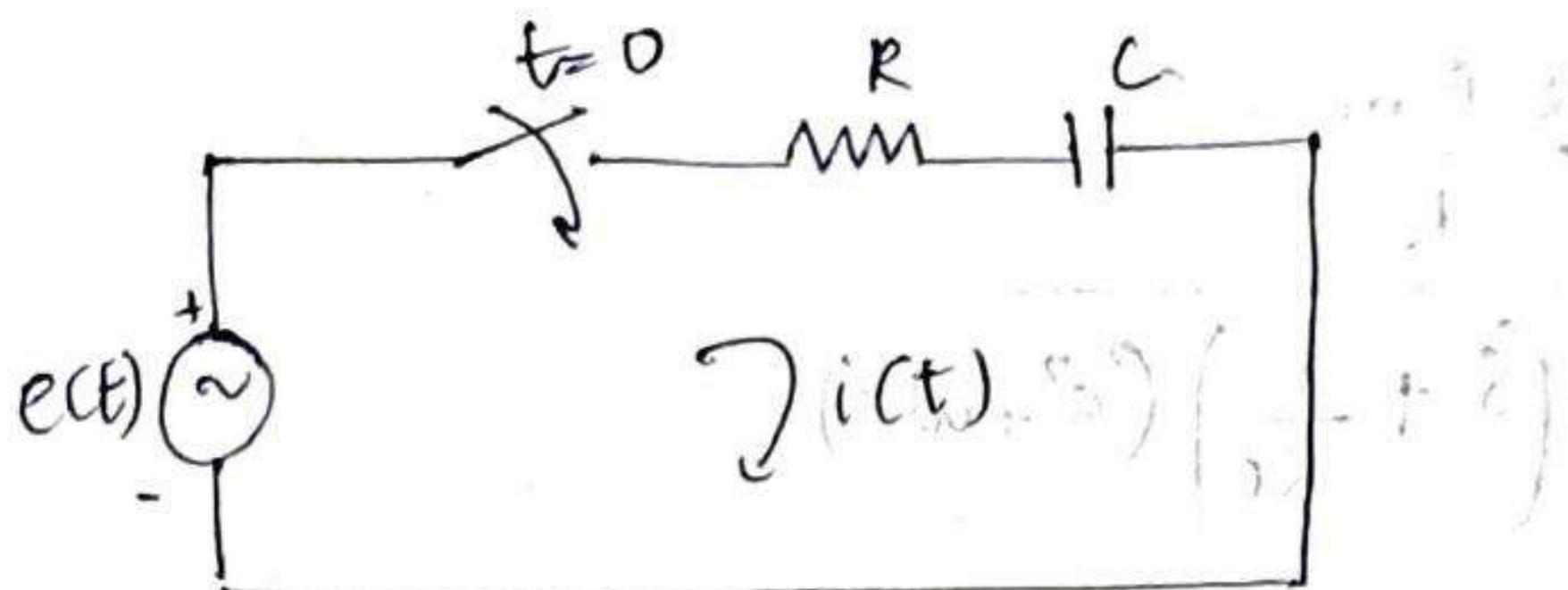


when the switch is closed at  $t=0$ , let  $i(t)$  be the current through the circuit. let us assume that there is no standard energy in the circuit

$$L[i(t)] = I(s)$$

$$L[e(t)] \cdot E(s) = L[E_m \sin \omega t] \\ = E_m \frac{\omega}{s^2 + \omega^2} \left( \frac{1}{s} + j \right)$$

The S domain equivalent of RC circuit.

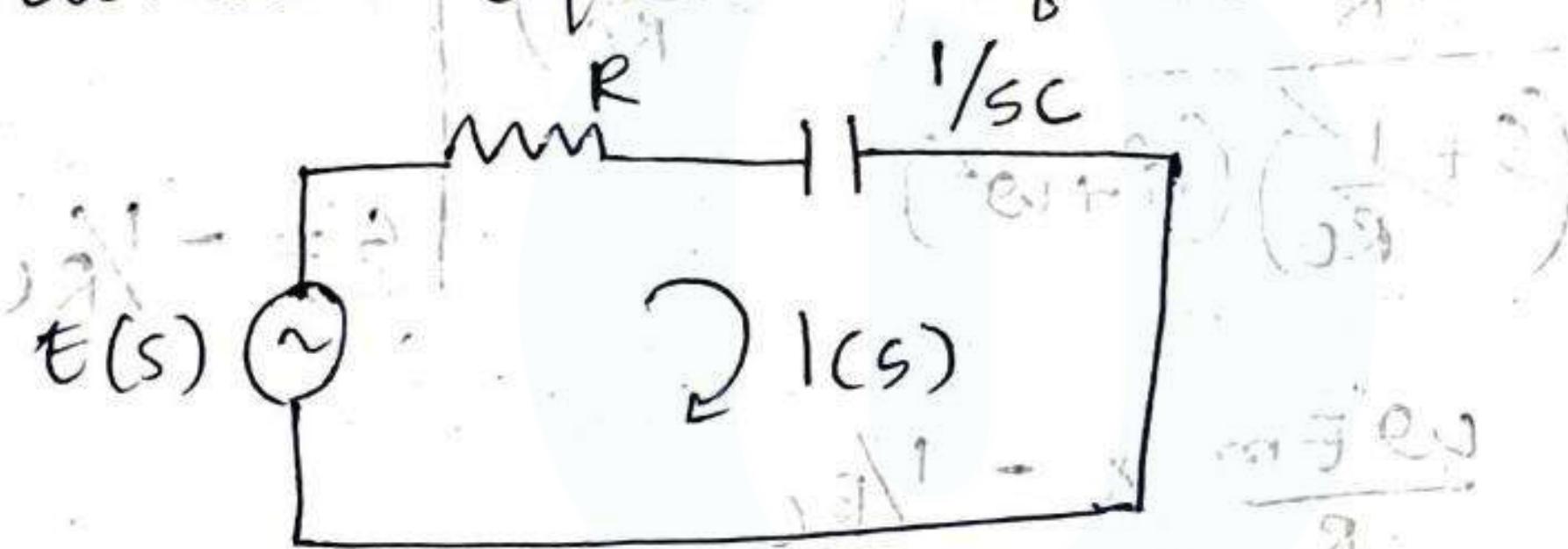

$$I(s) \left[ R + \frac{1}{sC} \right] = E(s) \frac{1}{s^2 + \left( \frac{1}{RC} \right)^2}$$

$$I(s) = \frac{E(s)}{R + \frac{1}{sC}} = \frac{E(s)}{\frac{R \cdot sC + 1}{sC}}$$

$$\therefore \left( \frac{1}{sC} \right) + \frac{R \cdot sC}{sC} \left[ s + \frac{1}{RC} \right]$$

$$= \frac{E(s)}{\frac{R}{s} \left[ s + \frac{1}{RC} \right]}$$

$$= \frac{\omega E_m \cdot s}{R} \cdot \frac{1}{(s + \frac{1}{RC})(s^2 + \omega^2)}$$

$$I(s) = \frac{k_1}{s + \frac{1}{RC}} + \frac{k_2 s + k_3}{s^2 + \omega^2}$$

$$\text{Compare } \frac{\omega E_m \cdot s}{R} \cdot \frac{1}{(s + \frac{1}{RC})(s^2 + \omega^2)} = \frac{k_1}{s + \frac{1}{RC}} + \frac{k_2 s + k_3}{s^2 + \omega^2}$$

$$k_1 = \frac{\omega E_m \cdot s}{R} \Big|_{s = -\frac{1}{RC}}$$

$$= \frac{\omega E_m}{R} \Big|_{s = -\frac{1}{RC}} = \frac{-\omega E_m}{R^2 C}$$

$$= -\frac{\omega E_m}{R^2 C} \Big|_{s = -\frac{1}{RC}}$$

$$= -\frac{\omega E_m}{R^2 C} \times \frac{R^2}{\omega^2} \Big|_{s = -\frac{1}{RC}}$$

$$k_1 = -\frac{E_m / \omega C}{R^2 + (\frac{1}{\omega C})^2}$$

$$\tau = \sqrt{R^2 + (\omega C)^2} \Rightarrow \tau^2 = R^2 + (\omega C)^2$$

$$= -\frac{Em}{\omega C \tau^2}$$

$$\frac{\frac{\omega Em}{R} \times s}{\left(s + \frac{1}{RC}\right)\left(s^2 + \omega^2\right)} = \frac{k_1}{\left(s + \frac{1}{RC}\right)} + \frac{k_2 s + k_3}{s^2 + \omega^2}$$

$$\frac{\omega Em}{R} s = k_1 (s^2 + \omega^2) + (k_2 s + k_3) \left(s + \frac{1}{RC}\right)$$

$$\frac{\omega Em}{R} s = (k_1 + k_2) s^2 + k_2 \omega^2 + \frac{k_2}{RC} s + k_3 s + \frac{k_3}{RC}$$

$$\frac{\omega Em}{R} s = (k_1 + k_2) s^2 + \left(\frac{k_2}{RC} + k_3\right) s + k_1 \omega^2 + \frac{k_3}{RC}$$

$$k_1 + k_2 = 0 \Rightarrow k_1 = -k_2$$

$$k_1 = -\frac{Em}{\omega C \tau^2}$$

$$k_2 = \frac{Em}{\omega C \tau^2}$$

$$\frac{k_2}{RC} + k_3 = \frac{\omega Em}{R}$$

$$\frac{Em}{\omega C \tau^2} + k_3 = \frac{\omega Em}{R}$$

$$k_3 = \frac{\omega Em}{R} - \frac{Em/\omega C \tau^2}{RC}$$

$$= \frac{C \omega Em}{R} - \frac{Em}{\omega C \tau^2 R}$$

$$\begin{aligned}
 k_3 &= \frac{\omega E_m (\omega c^2 \pi^2 R) - Em R}{\omega c^2 \pi^2 R^2} \\
 &= \frac{R [\omega E_m (\omega c^2 \pi^2) - Em]}{\omega c^2 \pi^2 R^2} \\
 &\therefore \frac{i \omega E_m (\omega c^2 \pi^2) - Em}{\omega c^2 \pi^2 R}
 \end{aligned}$$


Sub:  $\pi^2$  on numerator

$$\begin{aligned}
 &= Em \left[ \omega^2 c^2 \left[ R^2 + \frac{1}{\omega^2 c^2} \right] - 1 \right] \\
 &= \frac{Em \left[ \omega^2 c^2 R^2 + 1 - 1 \right]}{\omega^2 c^2 \pi^2 R} \\
 &= \frac{Em \omega^2 c^2 R^2}{\omega^2 c^2 \pi^2 R} \xrightarrow{\cancel{\omega^2 c^2}} \frac{Em \omega R}{\pi^2} \Rightarrow k_3
 \end{aligned}$$

$$\begin{aligned}
 I(s) &= -\frac{Em / \omega c \pi^2}{s + \frac{1}{RC}} + \frac{Em / \omega c \pi^2 s + \omega R Em / \pi^2}{s^2 + \omega^2} \\
 &= \frac{-Em}{\omega c \pi^2} \times \frac{1}{s + \frac{1}{RC}} + \frac{Em}{\omega c \pi^2} \cdot \frac{s}{s^2 + \omega^2} + \frac{\omega R Em}{\pi^2} \frac{\omega}{s^2 + \omega^2}
 \end{aligned}$$

$$i(t) = \frac{-E_m}{\omega C \pi^2} e^{-\frac{1}{R C t}} + \frac{E_m}{\omega C \pi^2} \cos \omega t + \frac{R E_m}{\pi^2} \sin \omega t$$
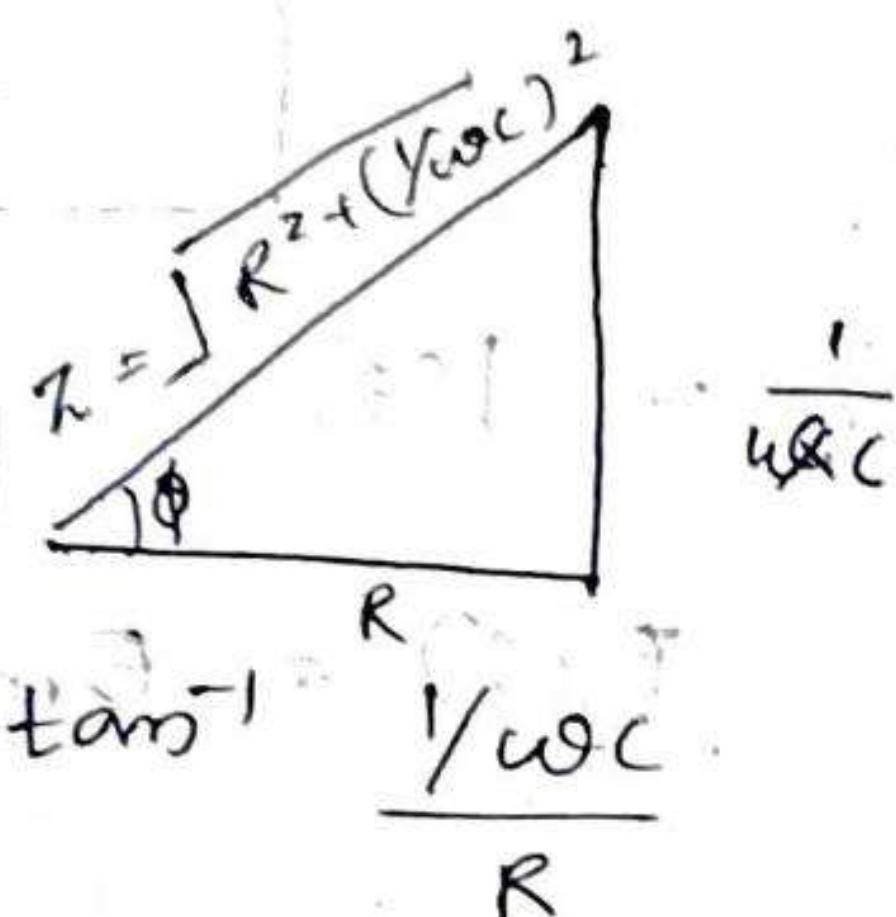
$$= \frac{-E_m}{\omega C \pi^2} e^{-\frac{1}{R C t}} + \frac{E_m}{\pi^2} \left[ R \sin \omega t + \frac{1}{\omega C} \cos \omega t \right]$$



$$\tan \phi = \frac{1/\omega C}{R}$$

$$\phi = \tan^{-1} \frac{1/\omega C}{R}$$

$$\cos \phi = R/\pi \quad R = \pi \cos \phi$$

$$\sin \phi = \frac{1/\omega C}{\pi} = \frac{1}{\omega C} = \pi \sin \phi$$

$$i(t) = \frac{-E_m}{\omega C \pi^2} e^{-\frac{1}{R C t}} + \frac{E_m}{\pi^2} \left[ \pi \cos \phi \sin \omega t + \pi \sin \phi \cos \omega t \right]$$

$$= \frac{-E_m}{\omega C \pi^2} e^{-\frac{1}{R C t}} + \frac{E_m}{\pi} \left[ \sin(\omega t + \phi) \right]$$


transient part

steady state part

RLC circuit excited by AC source.

Consider the RLC circuit - let the ckt be excited by a sinusoidal source  $e(t) = E_m \sin \omega t$  when switch is closed at  $t = 0$ . Let  $i(t)$  be

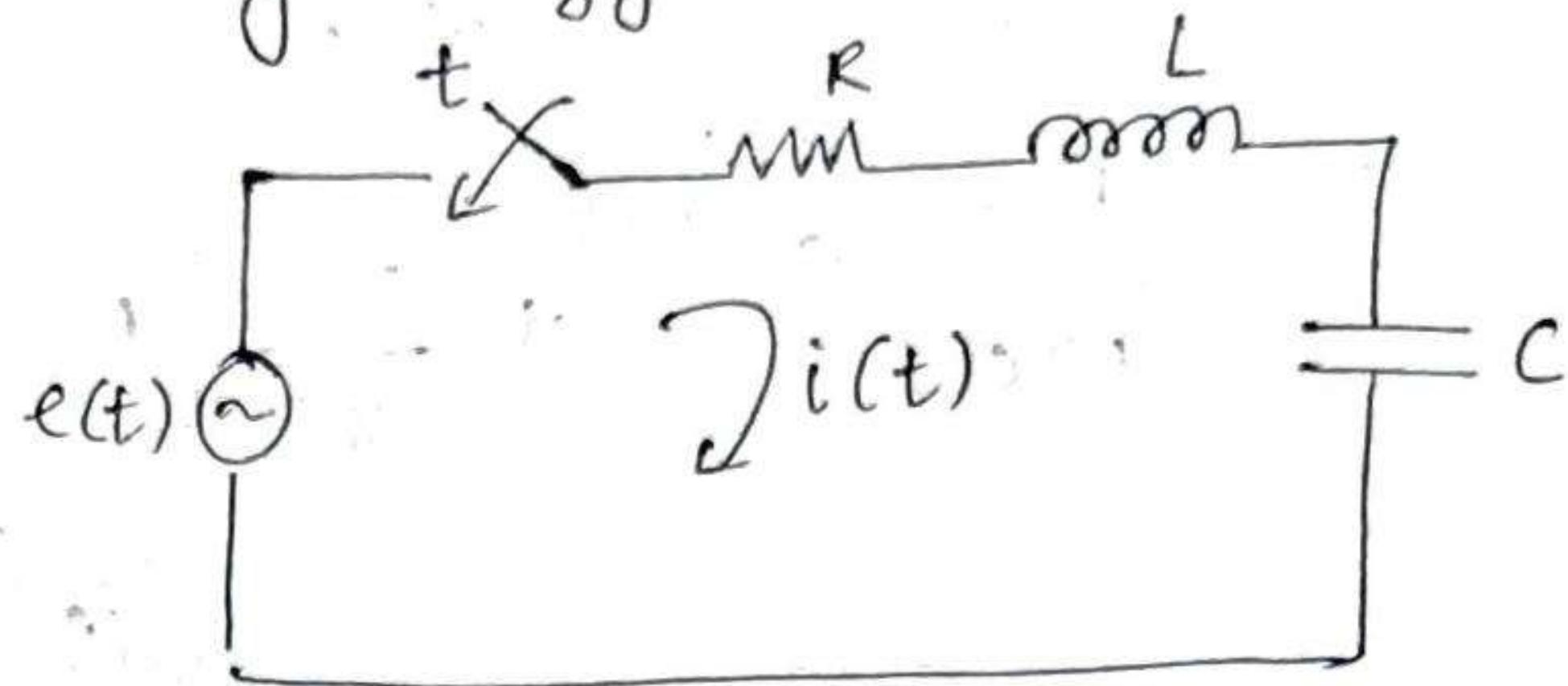
the current through the ckt. Let us assume there is no steady energy in the ckt.



$$L \dot{i}(t) = I(s)$$

$$L [e(t)] = E(s)$$
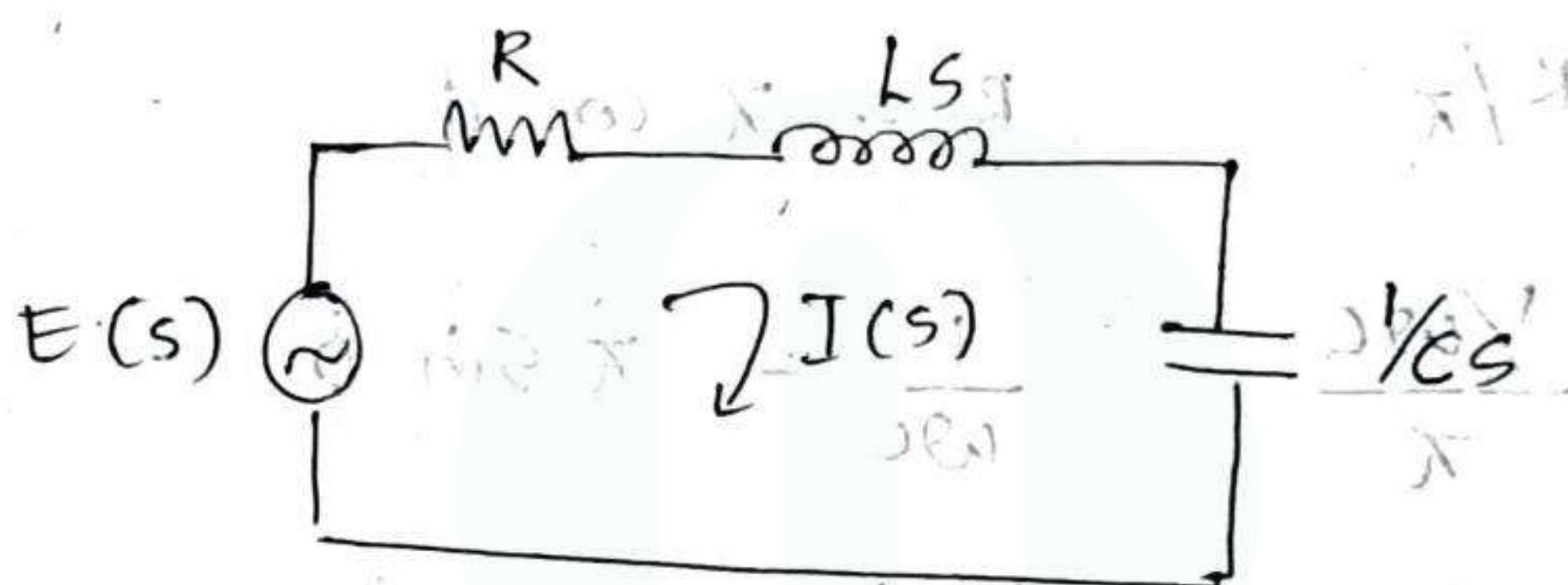
$$E(s) = E_m \frac{\omega}{s^2 + \omega^2}$$



$$I(s) \left[ R + Ls + \frac{1}{Cs} \right] = E(s)_{eq}$$

$$I(s) = \frac{E(s)}{R + Ls + \frac{1}{Cs}}$$

$$\frac{E(\phi + 180^\circ) \text{ cos } \phi}{R + Ls + \frac{1}{Cs}} = \frac{\omega E_m}{s^2 + \omega^2} \left[ \frac{1}{R + Ls + \frac{1}{Cs}} \right]$$

$$\frac{\omega E_m}{s^2 + \omega^2} \left[ \frac{1}{\frac{R}{L}s + \frac{L}{s} + \frac{1}{LC}} \right]$$

$$\frac{\omega E_m s / L}{(s^2 + \omega^2) \left( s^2 + \frac{R}{L}s + \frac{1}{LC} \right)}$$

$$\text{Case I} \Rightarrow \frac{\omega Em s / L}{(s^2 + \omega^2)(s + a)^2}$$

The roots are real and equal

$$\text{Let } (s^2 + \frac{R}{L}s + \frac{1}{LC}) = (s+a)^2$$

$$s = \pm a$$

$$I(s) = \frac{(\omega Em / L) \cdot s}{(s^2 + \omega^2)(s+a)^2}$$

$$= \frac{k_1}{s+a} + \frac{k_2}{(s+a)^2} + \frac{k_3 s + k_4}{s^2 + \omega^2}$$

$$i(t) = \underline{k_1 e^{at}} + k_2 t \bar{e}^{at} + \underline{\text{Im} \sin(\cot \pm \phi)}$$

Case II  $\Rightarrow$  roots are real and unequal

$$\text{Let } (s^2 + \frac{R}{L}s + \frac{1}{LC}) = (s+a)(s+b)$$

$$I(s) = \frac{\omega Em s}{\underline{(s^2 + \omega^2) - (s+a)(s+b)}}$$

$$= \frac{k_1}{(s+a)} + \frac{k_2}{(s+b)} + \frac{k_3 s + k_4}{s^2 + \omega^2}$$

$$= \underline{k_1 \bar{e}^{at}} + k_2 \bar{e}^{bt} + \underline{\text{Im} [\sin(\cot \pm \phi)]}$$

Case III  $\Rightarrow$  The roots are complex conjugate

$$\det \left( s^2 + \frac{R}{L}s + \frac{1}{LC} \right) = s^2 + \frac{Rs}{L} + \frac{1}{LC} + \left( \frac{R}{2L} \right)^2 - \left( \frac{R}{2L} \right)^2 + \omega_d^2$$

$$= (s+a)^2 + \omega_d^2$$

$$a = \left( \frac{R}{2L} \right); \quad \omega_d = \sqrt{\frac{1}{LC} - \left( \frac{R}{2L} \right)^2}$$


$$I(s) = \frac{\omega E_m}{L} \cdot \frac{s}{(s^2 + \omega^2)((s+a)^2 + \omega_d^2)}$$

$$= \frac{k_1 s + k_2}{(s+a)^2 + \omega_d^2} + \frac{k_3 s + k_4}{s^2 + \omega^2}$$


$$i(t) = I_o e^{-at} \sin(\omega_d t + \theta) + I_m \sin(\omega t \pm \phi)$$

20/10/2020

Q. The switch in the circuit is closed at position 1 for a time  $t=0$ . At time  $t=0$ , switch is moved to position 2. Find  $i(t)$  for  $t \geq 0$

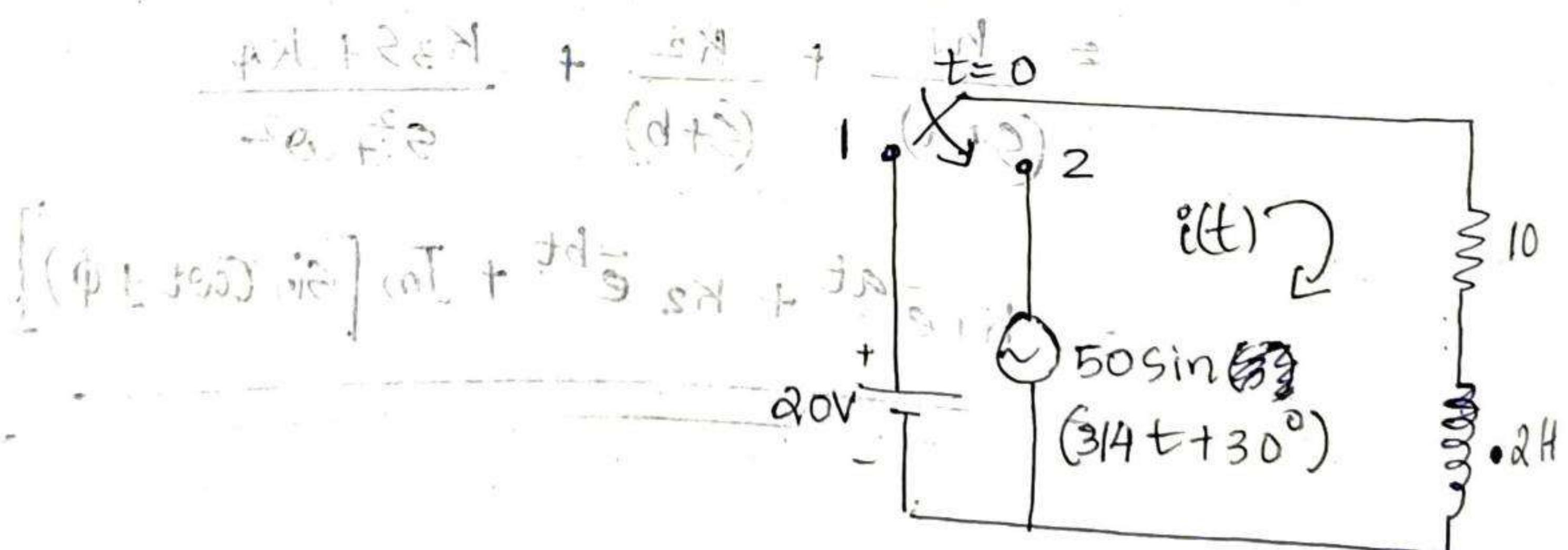


position 1

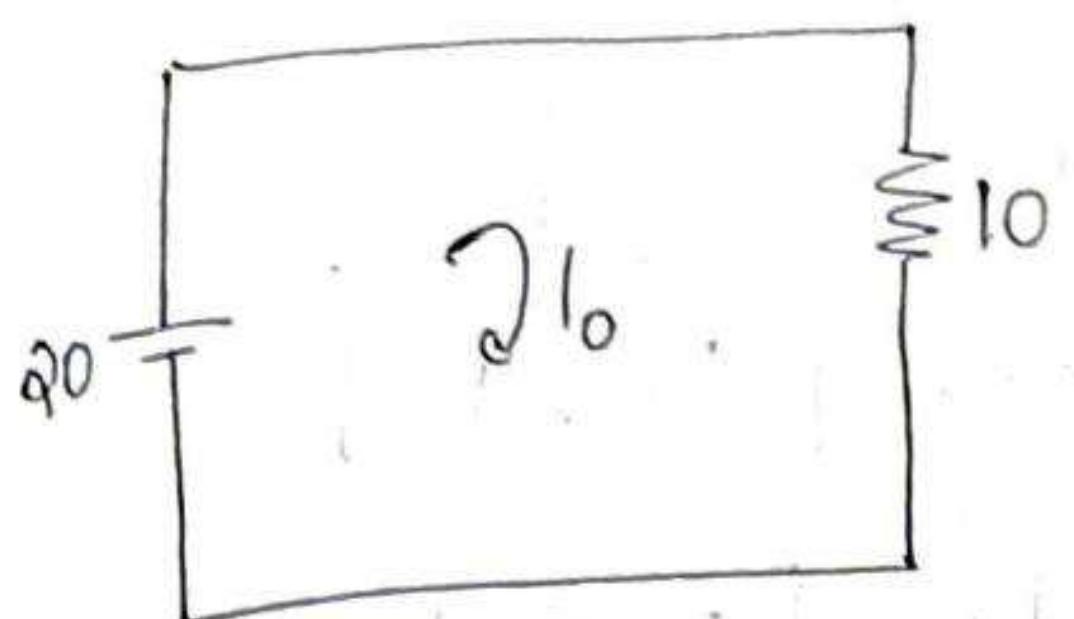

$$\omega_0 = 10 \text{ rad/s}$$

$$I_0 = \frac{\omega_0}{R} = \frac{10}{10} = 1 \text{ A}$$

position 2

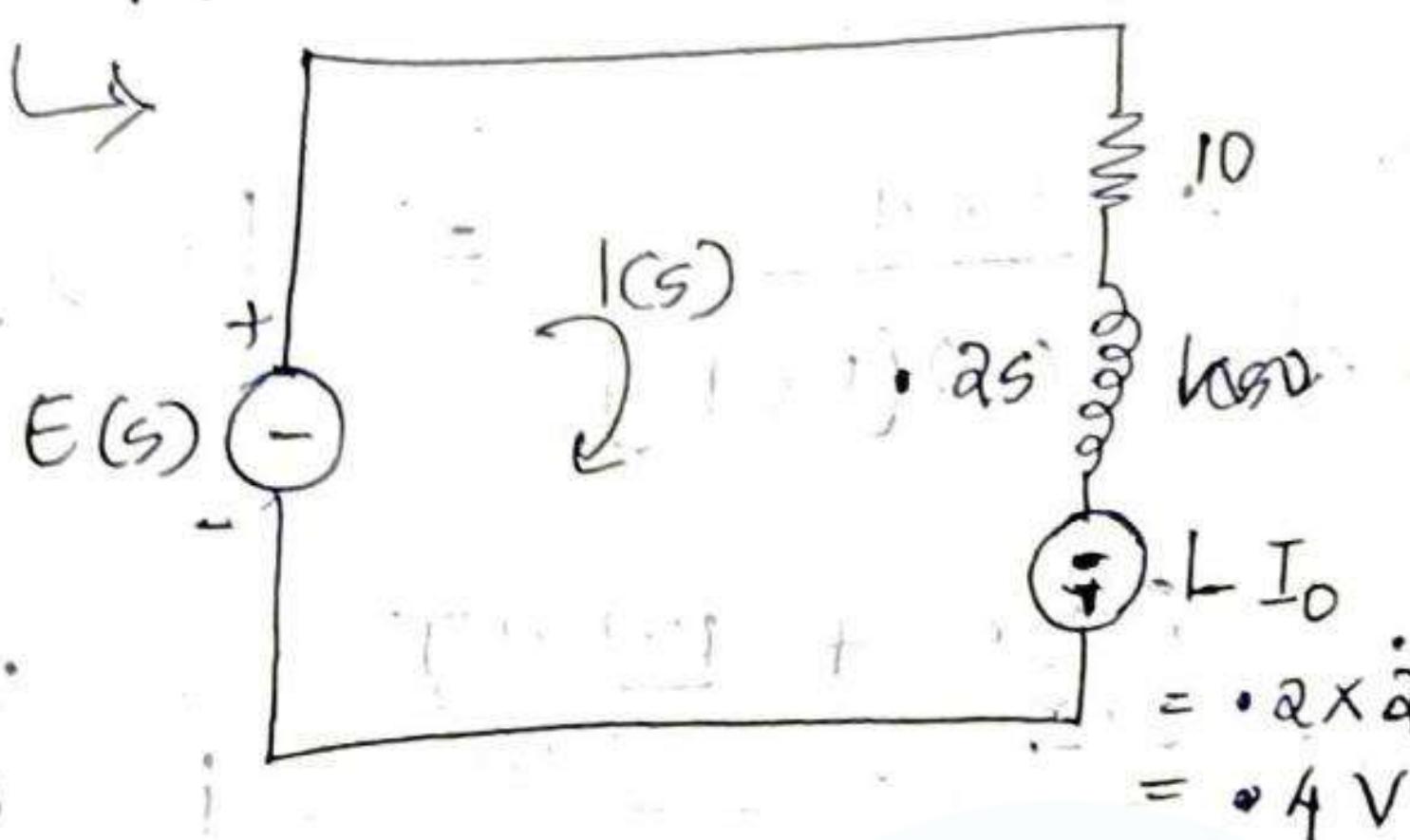

$$= \frac{1}{R} \cdot \omega_0 \cdot I_0 = \frac{1}{10} \cdot 10 \cdot 1 = 1 \text{ A}$$

$$= 1 \times 1 = 1 \text{ A}$$

$$E(t) = 50 \sin(314t + 30^\circ)$$

$$\begin{aligned}
 E(s) &= L \left[ 50 \sin(314t + 30^\circ) \right] \\
 &= 50 \times L \left[ \sin 314t \cos 30 + \cos 314t \sin 30 \right] \\
 &= 50 \times L \left[ \sin 314t \times \frac{\sqrt{3}}{2} + \cos 314t \times \frac{1}{2} \right] \\
 &= 50 \times \frac{\sqrt{3}}{2} L \left[ \sin 314t \right] + 50 \times \frac{1}{2} L \left[ \cos 314t \right] \\
 &= \frac{25\sqrt{3}}{2} \times \frac{314}{s^2 + 314^2} + \frac{25}{2} \times \frac{1}{s^2 + 314^2} \\
 &\approx \frac{13597}{s^2 + 314^2} + \frac{25s}{s^2 + 314^2} \\
 E(s) &= \frac{25s + 13597}{s^2 + 314^2}
 \end{aligned}$$

$$\text{Mesh} \rightarrow E(s) + 0.4 = 10I(s) + 0.2s I(s)$$

$$= I(s) [10 + 0.2s]$$

$$= 0.2 I(s) [10/2 + s]$$

$$\frac{25s + 13597}{s^2 + 314^2} + 0.4 = 0.2 I(s) [50 + s]$$

$$\frac{25s + 13597}{(s^2 + 314^2)0.2 [50 + s]} + \frac{0.4}{0.2 [50 + s]} = I(s)$$

$$I(s) = \frac{\frac{25}{0.2}s + \frac{13597}{0.2}}{(s+50)(s^2 + 314^2)} + \frac{\frac{0.4}{0.2}}{(s+50)}$$

$$I(s) = \left[ \frac{125s + 67985}{(s+50)(s^2 + 314^2)} \right] + \frac{-2}{(s+50)}$$

$$\det \left[ \frac{125s + 67985}{(s+50)(s^2 + 314^2)} + \frac{-2}{(s+50)} \right] = \frac{k_1}{s+50} + \frac{k_2 s + k_3}{s^2 + 314^2}$$

$$k_1 = \left. \frac{125s + 67985}{(s+50)(s^2 + 314^2)} \right|_{s=-50}$$

$$= \frac{125 \times -50 + 67985}{(-50^2 + 314^2)} = \underline{\underline{0.6107}}$$

On cross multiplication

$$125s + 67985 = k_1(s^2 + 314^2) + (k_2s + k_3)(s + 50)$$

$$125s + 67985 = k_1s^2 + k_1314^2 + k_2s^2 + k_2314^2 + 50k_3 + 50k_3$$

$$125s + 67985 = (k_1 + k_2)s^2 + (50k_2 + k_3)s + k_1314^2 + 50k_3$$

$$k_1 + k_2 = 0, \quad (50k_2 + k_3) = 125$$

$$k_1 = -k_2 \quad 50 \times -0.6107 + k_3 = 125$$

$$\underline{k_2 = -0.6107} \quad k_3 = 125 + 30.537$$

$$\underline{k_3 = 155.535}$$

$$I(s) = \frac{0.6107}{s+50} + \frac{-0.6107s + 155.535}{s^2 + 314^2} + \frac{2}{s+50}$$

$$= \frac{2 \cdot 6107}{s+50} - \frac{0.6107s}{s^2 + 314^2} + \frac{155.535}{s^2 + 314^2}$$

$$= 2 \cdot 6107 \times \frac{1}{s+50} - 0.6107 \times \frac{s}{s^2 + 314^2} + \frac{155.535}{314}$$

$$\times \frac{314}{s^2 + 314^2}$$

$$= 2 \cdot 6107 \times \frac{1}{s+50} - 0.6107 \times \frac{s}{s^2 + 314^2} + 0.4953 \times \frac{314}{s^2 + 314^2}$$


Inverse Laplace

$$= 2 \cdot 6107 e^{-50t} - 0.6107 \cos 314t + 0.4953 \sin \frac{314}{50} t$$


$$\underline{\underline{2.6107 e^{-50t}}} + \underline{\underline{0.7863 \sin(314t - 51)}} A$$

parts                          steady part

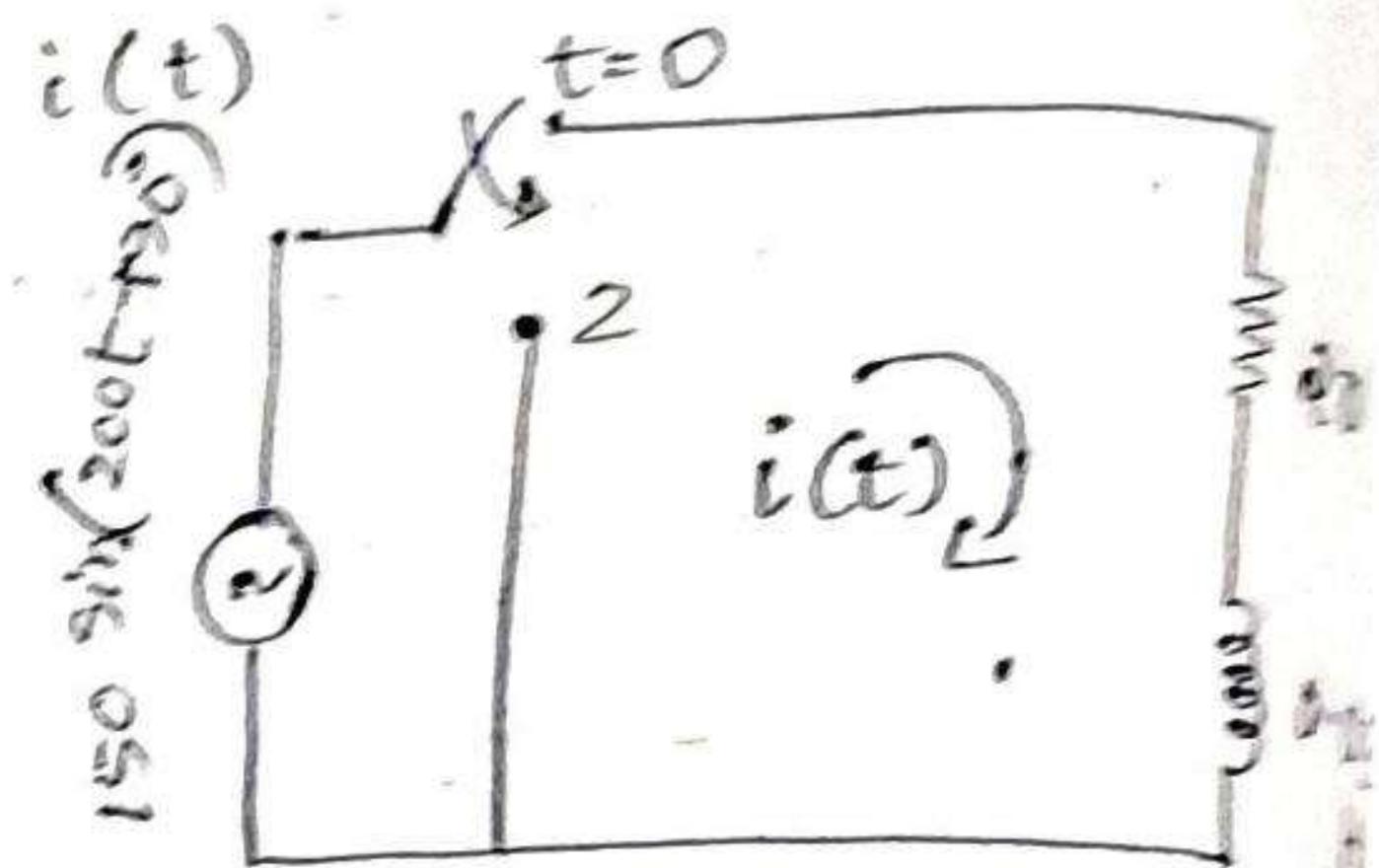Q. In the circuit the switch remains in position 1 until steady state is reached. At time  $t=0$ , switch is changed to position 2. Find  $i(t)$



at position 1

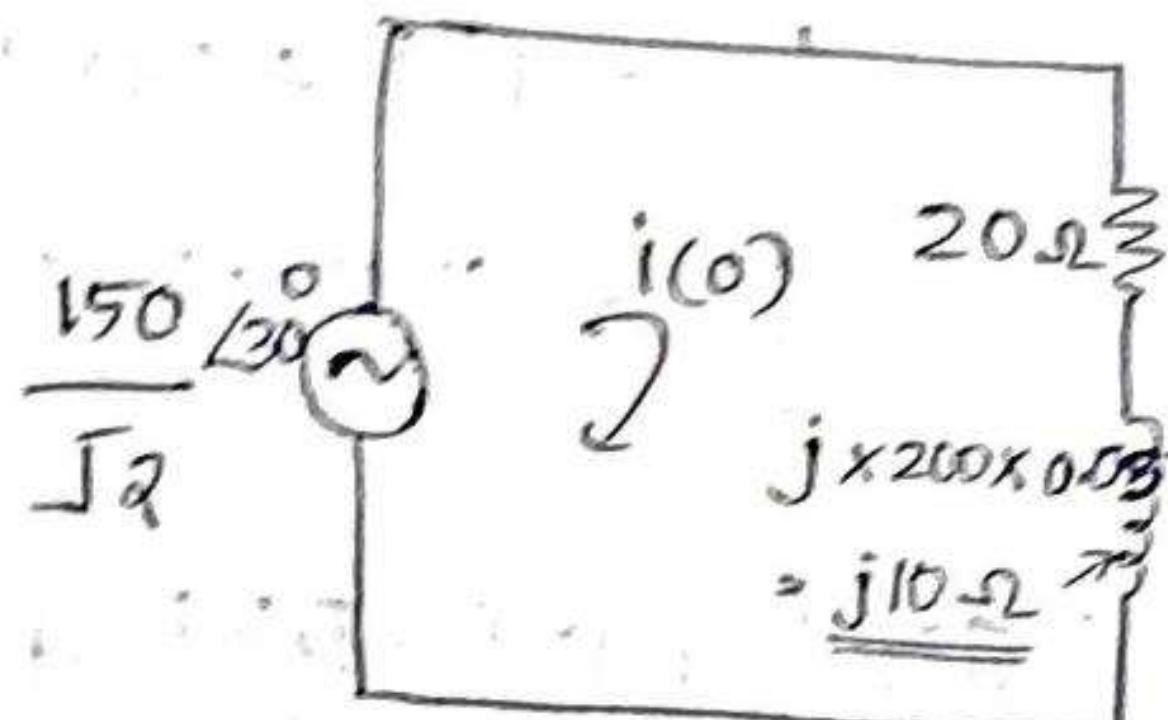

Here circuit is attained steady state, hence we can perform steady state analysis.

$$E_m \sin(\omega t + \phi) = 150 \sin(200t + 30)$$

$$I_0 = \frac{E_m}{\sqrt{R^2}} = \frac{150/\sqrt{2}}{\sqrt{20^2 + 10^2}} = 4.7434 A$$

At position 2;


$$20 I(s) + 0.05 s I(s) = 0.23717$$

$$I(s) \times 0.05 \left( \frac{20}{0.05} + s \right) = 0.23717$$

$$I(s) \times 0.05 (400 + s) = 0.23717$$

$$I(s) = \frac{0.23717}{0.05(400 + s)}$$

$$I(s) = \frac{4.7434}{s + 400}$$

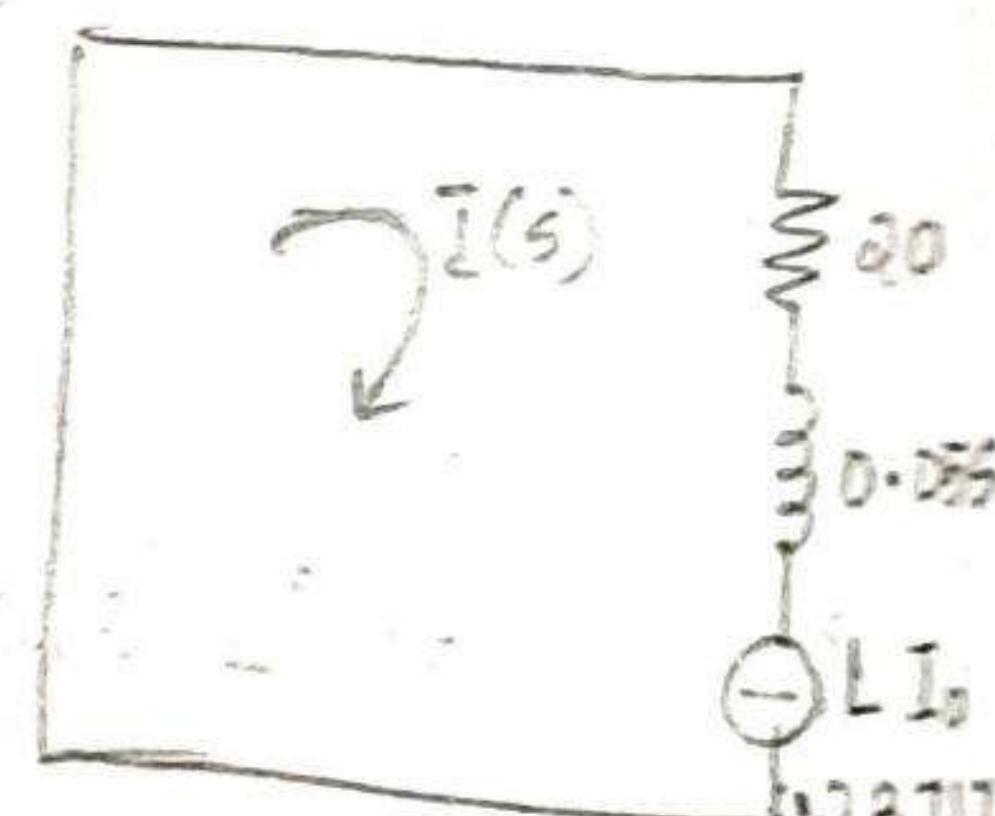

Taking inverse Laplace

$$L^{-1}[I(s)] = -L^{-1}\left[\frac{4 \cdot 7434}{s+400}\right]$$

$$i(t) = 4 \cdot 7434 e^{-400t} A$$

21/10/2020  
Chap 10


Q. In the circuit, the switch is closed at a particular value of  $\alpha'$  so that there is no transient in the RL circuit.

Find the value of  $\alpha'$ .

Ans Given that

$$e(t) = 10 \sin(20t + \alpha)$$

$$\text{let } L[e(t)] = E(s)$$

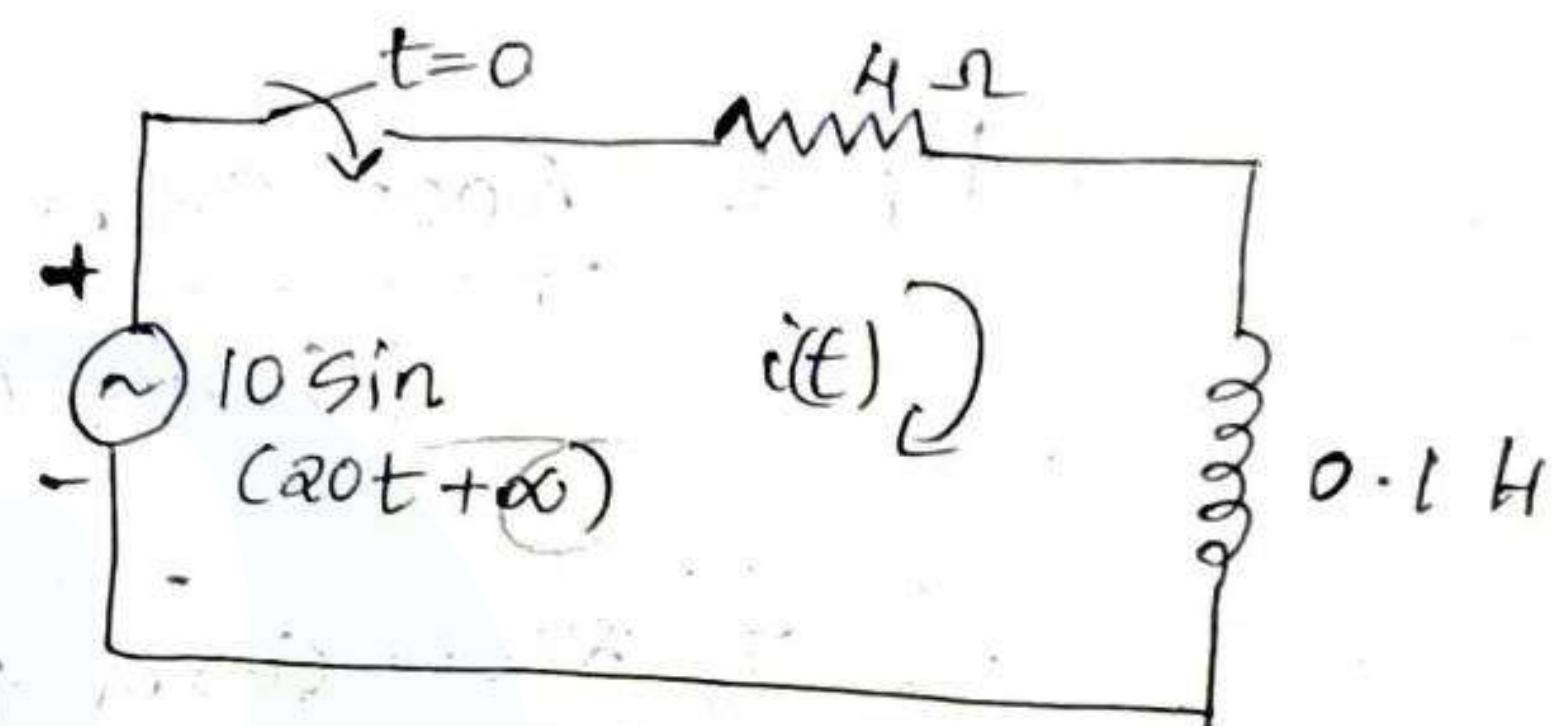

$$E(s) = L[10 \sin(20t + \alpha)]$$

$$= 10 \times L[\sin 20t \cos \alpha + \cos 20t \sin \alpha]$$


$$= 10 \cos \alpha L(\sin 20t) + 10 \sin \alpha L(\cos 20t)$$

$$= 10 \cos \alpha \frac{20}{s^2 + 20^2} + 10 \sin \alpha \frac{s}{s^2 + 20^2}$$

$$= \frac{200 \cos \alpha + 10 \sin \alpha s}{s^2 + 20^2}$$

$$4 I(s) + 0.1s I(s) = E(s)$$
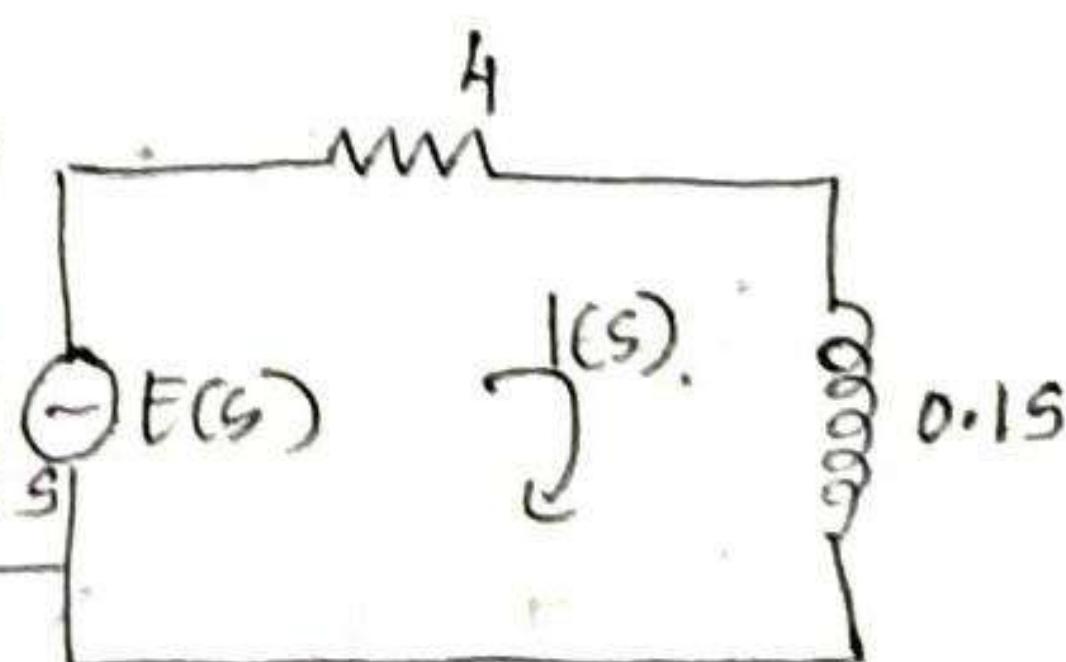
$$I(s) \times 0.1 \left( \frac{4}{0.1} + s \right) = \frac{200 \cos \alpha + 10 \sin \alpha s}{s^2 + 20^2}$$



$$I(s) \times 0.1(s + 40) = \frac{200 \cos \alpha + 10 \sin \alpha s}{s^2 + 20^2}$$

$$I(s) = \frac{200 \cos \alpha + 10 \sin \alpha s}{0.1(s+40)(s^2 + 20^2)}$$

$$I(s) = \frac{2000 \cos \alpha + 100 \sin \alpha s}{(s+40)(s^2 + 20^2)}$$

$$\frac{2000 \cos \alpha + 100 \sin \alpha s}{(s+40)(s^2 + 20^2)} = \frac{k_1}{s+40} + \frac{k_2 s + k_3}{s^2 + 20^2}$$

$$k_1 = \frac{2000 \cos \alpha + 100 \sin \alpha s \times (s+40)}{(s+40)(s^2 + 20^2)} \Big|_{s=40}$$

$$= \frac{2000 \cos \alpha + 100 \sin \alpha \times 40}{-40^2 + 20^2}$$

$$= \frac{2000 \cos \alpha + -4000 \sin \alpha}{-1200}$$

$$[2000 \cos \alpha + 2000 \sin \alpha] \times \frac{1}{-1200} =$$

$$(2000 \cos \alpha) \frac{1}{-1200} + (2000 \sin \alpha) \frac{1}{-1200} =$$

$$= \frac{2000}{-1200} (\cos \alpha - \sin \alpha)$$

$$k_1 = \frac{2000}{-1200} (\cos \alpha - \sin \alpha)$$

$$2000 \cos \alpha + 100 \sin \alpha s = k_1 (s^2 + 20^2) + (k_2 s + k_3)(s+40)$$

$$= k_1 s^2 + k_1 20^2 + k_2 s^2 + k_3 s + 40 k_2 s + 40 k_3$$

$$k_1 + k_2 = 0$$

$$k_1 = -k_2$$

$$k_2 = -\cos \alpha + \sin \alpha$$

$$k_3 + 40k_2 = 100 \sin \alpha.$$

$$k_3 = 100 \sin \alpha - 40(-\cos \alpha + 2 \sin \alpha)$$

$$= 100 \sin \alpha + 40(\cos \alpha - 2 \sin \alpha)$$

$$= 100 \sin \alpha + 40 \cos \alpha - 80 \sin \alpha$$

$$\underline{k_3} = 40 \cos \alpha + 20 \sin \alpha.$$

$$i(s) = \frac{k_1}{s+40} + \frac{k_2 s + k_3}{s^2 + 20^2}$$

$$= \frac{k_1}{s+40} + K_2 \frac{s}{s^2 + 20^2} + \frac{k_3}{20} \frac{20}{s^2 + 20^2}$$

taking inverse Laplace

$$= k_1 e^{-40t} + k_2 \cos 20t + \frac{k_3}{20} \sin 20t$$

(Transient) (Steady State)

For no transient part  $i(t)$

$$k_1 e^{-40t} = 0$$

$$\text{At } t=0 [e^0 = 1, \text{ so it} \neq 0]$$

$$\text{therefore putting } k_1 = 0$$

$$\text{Put } k_1 = \cos \alpha - 2 \sin \alpha = 0$$

$$\cos \alpha = 2 \sin \alpha$$

$$\frac{\sin \alpha}{\cos \alpha} = \frac{1}{2}$$

$$\tan \alpha = 0.5$$

$$\alpha = \tan^{-1}(0.5) = 26.6^\circ$$


$$\text{For no transient in } i(t) \quad \underline{\alpha = 26.6^\circ}$$

- Q. In the RL circuit excited by sinusoidal source; the switch is closed at  $t = 0.001$  second. Find the ratio of max. value to which the current may rise to steady state maximum value.

Given  $E_m \sin \omega t$

$$= 15 \sin 1000t$$

$$\omega = 1000 \text{ rad/s}$$

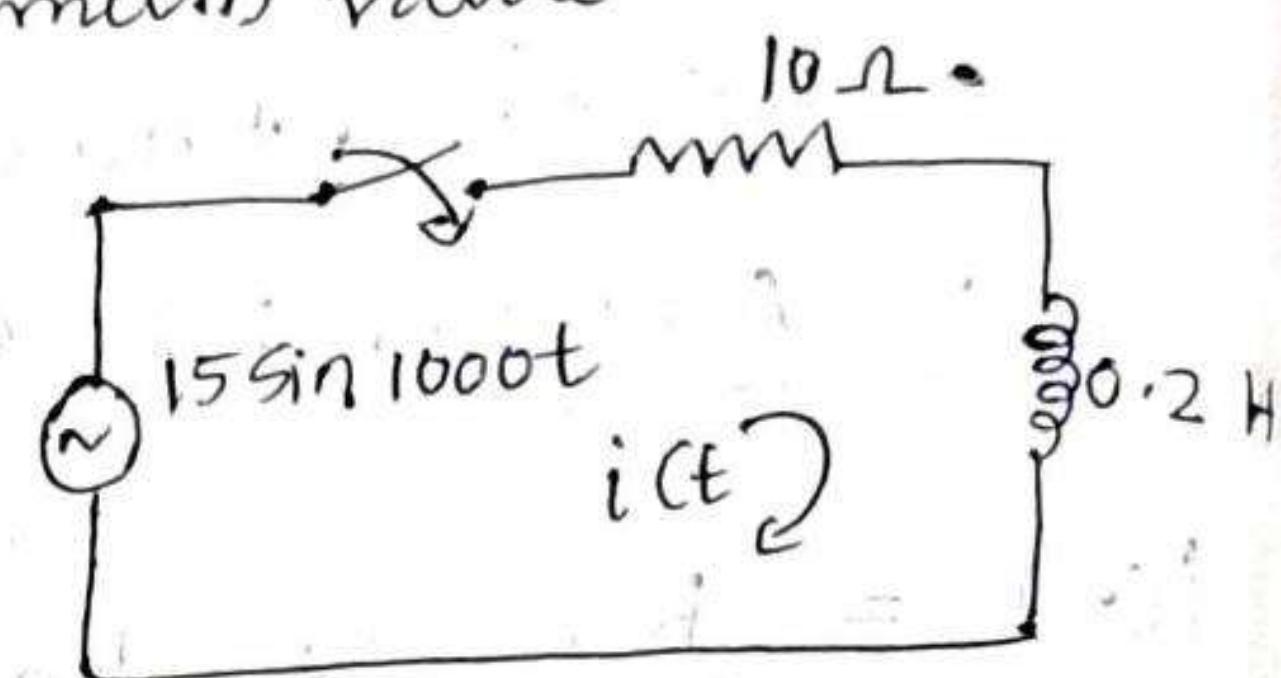

At  $t = 0.001$  second

$$\omega t = 1000 \times 0.001 = 1 \text{ radian}$$

$$\theta = 1 \times \frac{180}{\pi} = 57.3^\circ$$

Let us assume that the excitation source is  $15 \sin(1000t + 57.3^\circ)$  and switch is closed at  $t=0$ .

$$e(t) = 15 \sin(1000t + 57.3^\circ) \text{ V.}$$

$$\text{Let, } L(e(t)) = E(s)$$

$$E(s) = L(e(t)) = L[15 \sin(1000t + 57.3^\circ)]$$

$$= 15 \times L[\sin(1000t + 57.3^\circ)]$$

$$= 15 \times L[\sin 1000t \cos 57.3 + \cos 1000t \sin 57.3]$$

$$= 15 \times L(\sin 1000t) \times 0.5402 + \cos 1000t \times 0.8415$$


$$= 15 \times 0.5402 \times L(\sin 1000t) + 15 \times 0.8415 \times \cos 1000t$$

$$= 8.103 \times \frac{1000}{s^2 + 1000^2} + 12.6225 \times \frac{s}{s^2 + 1000^2}$$

$$= \frac{12.6225s + 8.103}{s^2 + 1000^2}$$

$$10I(s) + 0.2sI(s) = E(s)$$
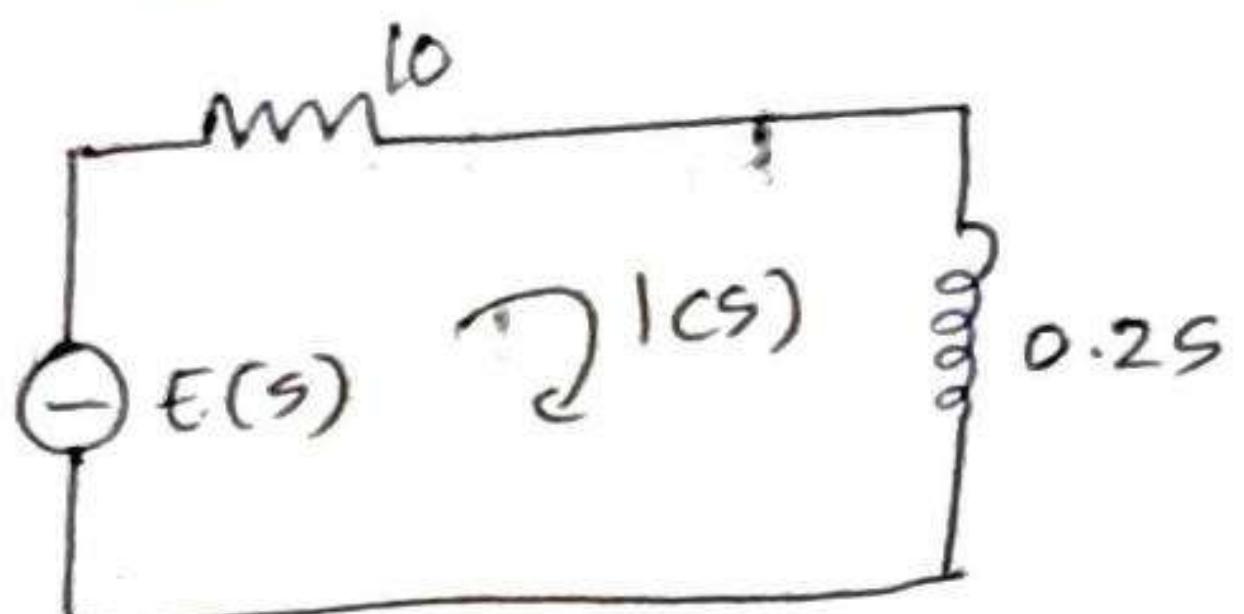
$$I(s) \times 0.2 \left( \frac{10}{0.2} + s \right) = E(s)$$



$$I(s) \times 0.2(s+50) = \frac{12.6225s + 8103}{s^2 + 10^6}$$

$$I(s) = \frac{12.6225s + 8103}{0.2(s+50)(s^2 + 10^6)}$$

$$\frac{12.6225s + 8103}{0.2(s+50)(s^2 + 10^6)} = \frac{63.1125s + 40515}{(s+50)(s^2 + 10^6)}$$

By partial expansion  $I(s) =$

$$\frac{63.1125s + 40515}{(s+50)(s^2 + 10^6)} = \frac{k_1}{(s+50)} + \frac{k_2s + k_3}{s^2 + 10^6}$$

$$k_1 = \left. \frac{63.1125s + 40515}{(s+50)(s^2 + 10^6)} \right|_{s=-50}$$

$$= \frac{63.1125 \times -50 + 40515}{-50^2 + 10^6}$$

$$= \frac{0.0375}{s^2 + 10^6}$$

$$63.1125s + 40515 = k_1(s^2 + 10^6) + (k_2s + k_3)(s+50)$$

$$= k_1s^2 + k_110^6 + k_2s^2 + k_3s + 50k_2s + 50k_3$$

$$= (k_1 + k_2)s^2 + (k_3 + 50k_2)s + 50k_3 + k_110^6$$

$$k_1 + k_2 = 0$$

$$k_2 = -k_1$$

$$\underline{k_2 = -0.037}$$

$$50k_2 + k_3 = 63.1125$$

$$k_3 = 63.1125 - 50 \times -0.037$$


$$\underline{i(s) = 64.9775}$$


$$i(s) = 0.0373 \times \frac{1}{s+50} - 0.0373 \times \frac{s}{s^2 + 10^6} + \frac{64.997}{10^3} \times \frac{10^3}{s^2 + 10^6}$$

$$i(t) = 0.0373 e^{-50t} + 0.0373 \cos 10^3 t + 64.997 \sin 10^3 t$$

22/10/2020

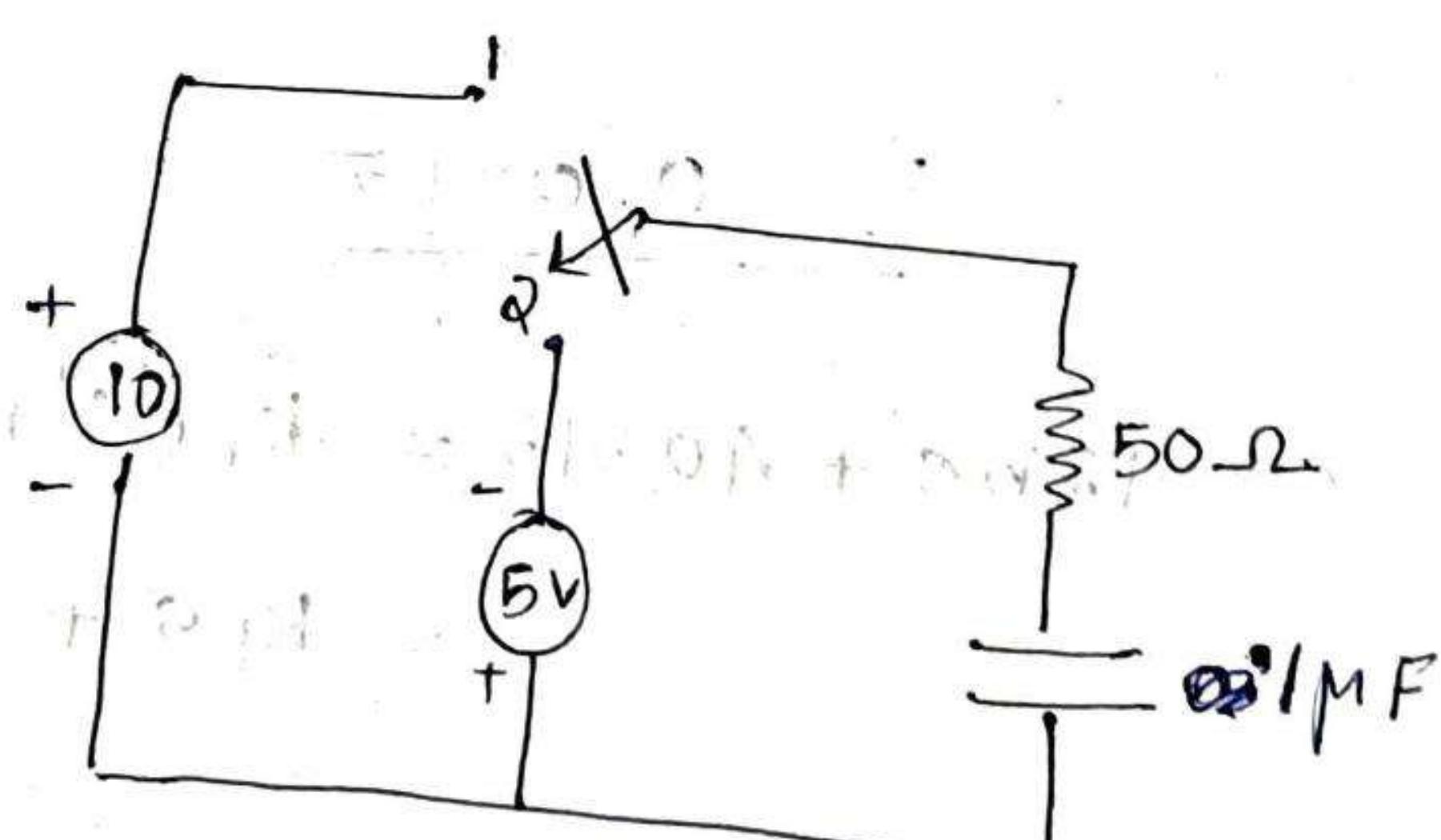- Q. In the circuit, steady state is reached, while the switch is in position 1. At  $t=0$ , the switch is moved in position 2. Determine the energy Q stored in capacitor at  $t=0.1$  ms.



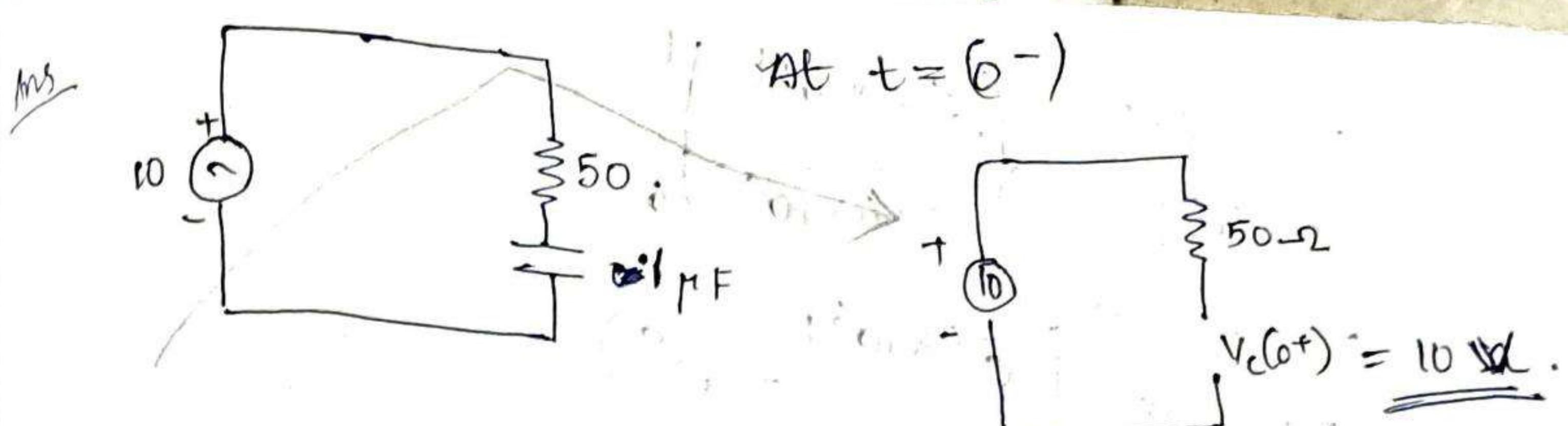

At  $t = 0^+$ .

$$\frac{-10}{s} - \frac{5}{s} = 50I(s) + \frac{10^6}{0.1s} \cdot I(s)$$

$$\frac{-15s}{s} = I(s) \left[ 50 + \frac{10^7}{s} \right]$$

$$I(s) = \frac{-15/s}{\left[ 50 + \frac{10^7}{s} \right]}$$

$$Q = CV = \frac{-15/s}{50s + 10^7} \cdot s = \frac{-15}{50s + 10^7}$$

$$= \frac{-15}{50s + 10^7}$$

$$I(s) = \frac{-15}{50(s + \frac{10^7}{50})} = \frac{-15/50}{s + 2 \times 10^6} = \frac{-0.3}{s + 2 \times 10^6}$$

$$i(t) = -0.3 e^{-2 \times 10^6 t}$$

$$v_C(t) = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{1 \times 10^6} \int -0.3 e^{-2 \times 10^6 t} dt$$

$$= \frac{-0.3}{10^{-6}} \left\{ e^{-2 \times 10^6 t} \right\}_0^t$$

$$+ \frac{0.3}{2 \times 10^{-6}} [e^{-2 \times 10^6 t} - e^0]$$

$$= \frac{0.3}{2} (e^{-2 \times 10^6 t} - 1)$$

$$= \frac{0.3}{2} (e^{-2 \times 10^6 \times 6.1 \times 10^{-3}} - 1)$$

$$= 1.5 (e^{-2 \times 10^6 \times 0.1 \times 10^{-3}} - 1).$$

$$= -1.5.$$


Energy  $Q = C \times V$

$$= 0.1 \times 10^{-6} \times -1.5$$


$$= -1.5 \times 10^{-7}$$

Q. An RC circuit is excited by a sinusoidal source of voltage  $50 \sin 314t$  volts and current in capacitor. Find the voltage  $C = 20 \mu F$ . Take  $R = 100 \Omega$  and

Given that  $e(t) = 50 \sin 314t$  volts

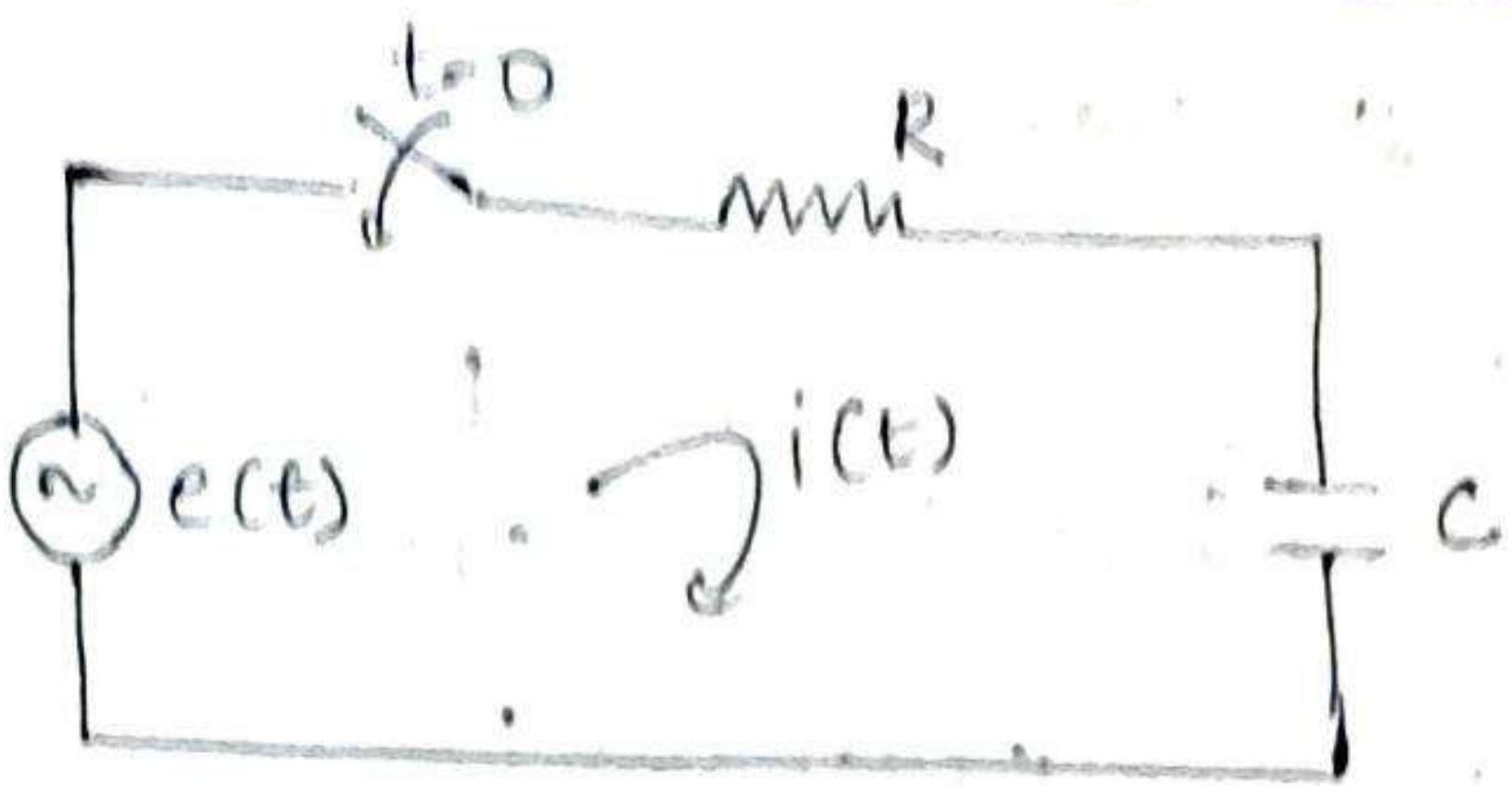
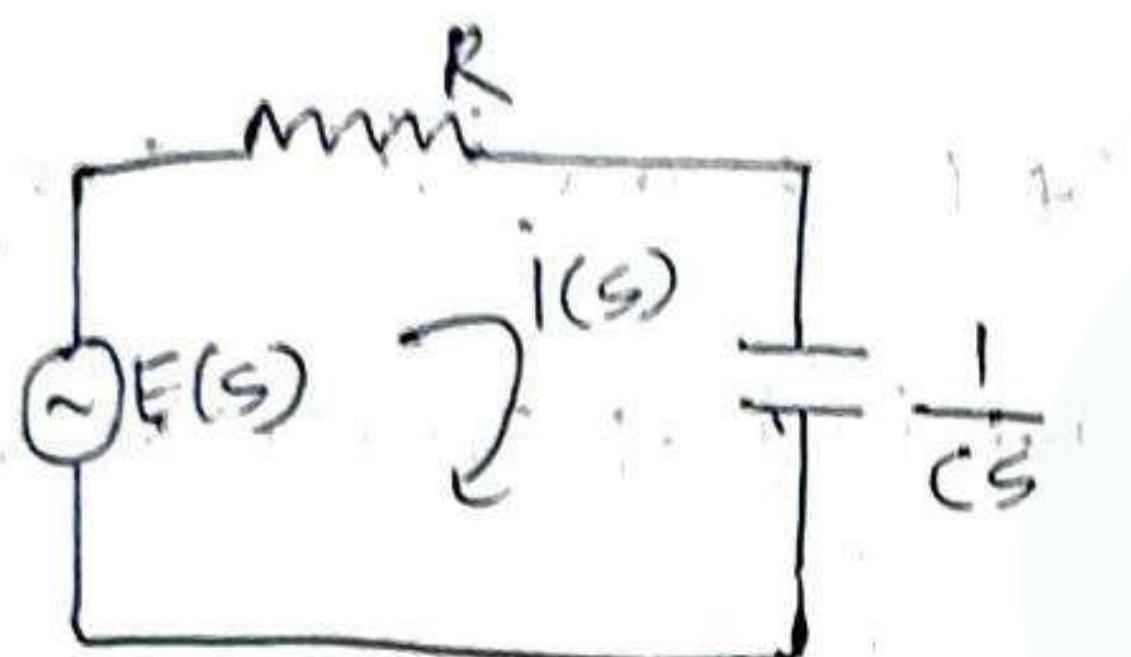
$$\begin{aligned}
 E(s) &= L(e(t)) \\
 &= L[50 \sin 314t] \\
 &= 50 \times L(\sin 314t) \\
 &= 50 \times \frac{314}{s^2 + 314^2} = \underline{\underline{\frac{15700}{s^2 + 314^2}}}
 \end{aligned}$$



$$\begin{aligned}
 I(s) &= \frac{E(s)}{R + \frac{1}{Cs}} \\
 &= \frac{E(s)}{RCS + 1} \cdot \underline{\underline{Cs}}
 \end{aligned}$$

$$\begin{aligned}
 I(s) &= E(s) \times \frac{Cs}{R + \frac{1}{Cs}} \\
 &= \frac{15700}{s^2 + 314^2} \times \frac{s}{R\left(s + \frac{1}{RC}\right)}
 \end{aligned}$$

$$\text{here } RC = 100 \times 20 \times 10^{-4} = 0.002 \text{ s.}$$

$$\begin{aligned}
 I(s) &= \frac{15700}{s^2 + 314^2} \times \frac{s}{100\left(s + \frac{1}{0.002}\right)} \\
 &= \frac{157s}{(s+500)(s^2 + 314^2)}
 \end{aligned}$$

By partial fraction :

$$I(s) = \frac{157s}{(s+500)(s^2 + 314^2)} = \frac{k_1}{s+500} + \frac{k_2 s + k_3}{s^2 + 314^2}$$

$$k_1 = \frac{157s \times (s+500)}{(s+500)(s^2 + 314^2)} \Big|_{s=-500}$$

$$= \frac{157 \times -500}{(-500)^2 + 314^2} = \frac{-0.2252}{\cancel{250000}} = k_1.$$

$$157s = k_1(s^2 + 314^2) + k_2 s + k_3(s+500)$$

$$= k_1 s^2 + k_1 314^2 + k_2 s^2 + k_2 \cancel{s} 500 + k_3 s + 500 k_3$$

$$= (k_1 + k_2)s^2 + (\cancel{k_2} 500 + k_3)s + 500 k_3 + 314^2 k_1$$

$$k_1 + k_2 = 0$$

$$k_2 = -k_1$$

$$\underline{k_2 = 0.2252}$$

$$500 k_2 + k_3 = 157$$

$$k_3 = 157 - 500 \times 0.2252$$

$$\underline{k_3 = 44.4}$$


$$I(s) = \frac{-0.2252}{s+500} + \frac{0.2252s + 44.4}{s^2 + 314^2}$$

$$= \frac{-0.2252}{s+500} + 0.2252 \times \frac{s}{s^2 + 314^2} + \frac{44.4 \times 314}{314} \times \frac{314}{s^2 + 314^2}$$

$$i(t) = -0.2252 e^{-500t} + 0.2252 \cos 314t + \frac{0.141}{314} \sin 314t$$

$$i(t) = -0.2252 e^{-500t} + \left( \sin 314t \times 0.141 + \cos 314t \times 0.225 \right)$$
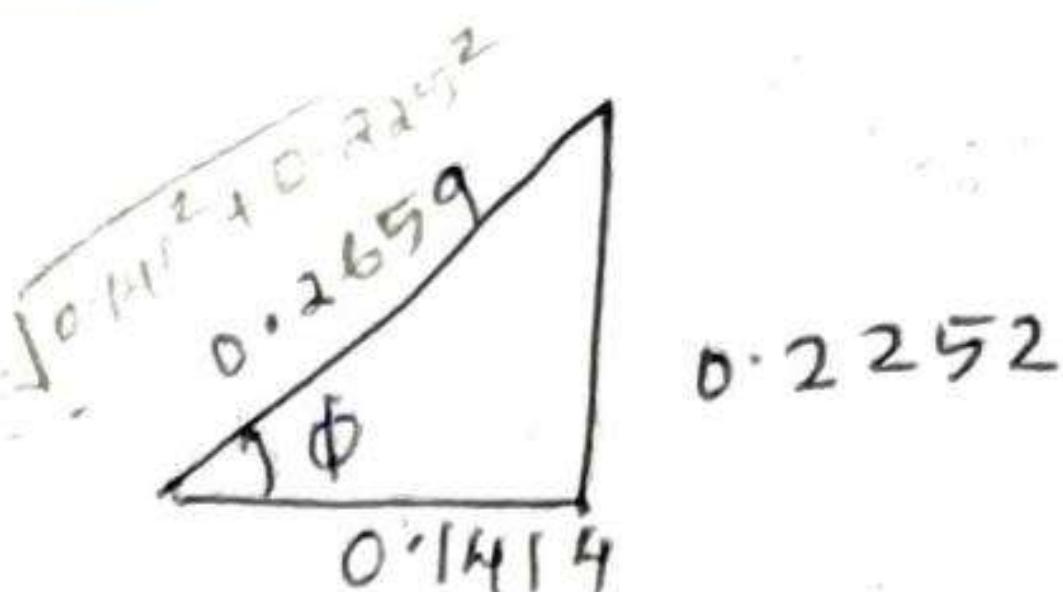
$$\tan \phi = \frac{0.2252}{0.1414} = 1.5926$$



$$\phi = \tan^{-1}(1.5926)$$

$$= 57.9^\circ$$

$$= 58^\circ$$

$$\cos \phi = \frac{0.1414}{0.2659}$$

$$0.1414 = 0.2659 \cos \phi$$

$$\sin \phi = \frac{0.2252}{0.2659}$$

$$0.2252 = \sin \phi \cdot 0.2659$$

$$= 0.2659 \sin 58^\circ$$

$$i(t) = -0.2252 e^{-500t} + \left[ \sin 314t \times 0.2659 \cos 58^\circ + \cos 314t \times 0.2659 \sin 58^\circ \right]$$

$$= -0.2252 e^{-500t} + 0.2659 \left( \sin 314t \cos 58^\circ + \cos 314t \sin 58^\circ \right)$$

$$i(t) = -0.2252 e^{-500t} + 0.2659 \sin(314t + 58^\circ) \text{ Ampere}$$

$$V_C(t) = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{C} \int [0.2252 e^{-500t} + 0.2659 \sin(314t + 58^\circ)] dt$$

$$= \frac{1}{20 \times 10^6} \left[ \frac{-0.2252 e^{-500t}}{-500} - \frac{0.2659 \cos(314t + 58^\circ)}{314} \right]$$

$$= \frac{-0.2252 e^{-500t}}{20 \times 10^6 \times (-500)} + \frac{0.2659}{20 \times 10^6 \times 314} \cos(314t + 58^\circ - 90^\circ)$$

$$= 22.52 e^{-500t} + 42.34 \sin(314t - 32^\circ) V$$