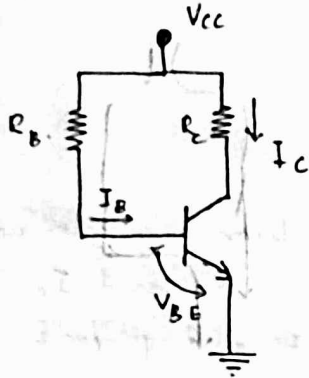


24/11/2021

## Module - 1

### Biasing

#### 1. Fixed bias circuit



Input loop:

Applying KVL for input loop.

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Since  $R_B$  is selected,  $I_B$  is fixed.  
Hence the name fixed bias circuit

Output loop:

Applying KVL for output loop.

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

Q point is given by  $I_C$  and  $V_{CE}$ .


$$V_{CE} = V_C - V_E, \text{ since } V_E = 0$$

$$V_{CE} = V_C$$

$$V_{BE} = V_B - V_E, \text{ since } V_E = 0$$

$$V_{BE} = V_B$$

#### 2. Collector to base bias circuit

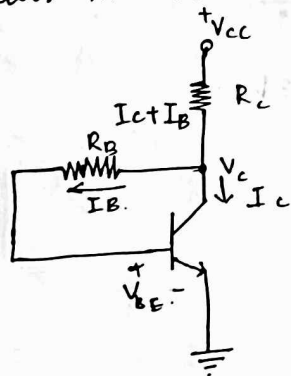

Input loop

Applying KVL.

$$V_{CC} - (I_C + I_B) R_C - I_B R_B - V_{BE} = 0$$

$$V_{CC} - \beta V_{BE} = (\beta I_B + I_B) R_C + I_B R_B$$

$$I_B (\beta + 1) R_C + I_B R_B = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{(1 + \beta) R_C + R_B}$$

$$R_B \ll (1 + \beta) R_C$$

$$I_B = \frac{V_{CC} - V_{BE}}{(1 + \beta) R_C}$$

$$\beta + 1 \approx \beta$$

$$I_B = \frac{V_{CC} - V_{BE}}{\beta R_C}$$

$$\therefore I_c \approx \frac{V_{cc} - V_{BE}}{R_c}$$

Collector current is independent of  $\beta$ .


Output loop

Applying KVL.

$$V_{cc} - (I_c + I_B)R_c - V_{CE} = 0$$

$$V_{CE} = V_{cc} - (I_c + I_B)R_c$$

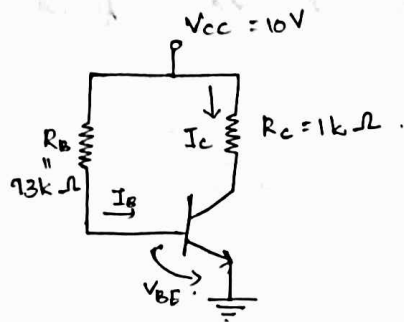Qn 1) Design a fixed bias circuit using a silicon transistor with  $\beta = 50$ ,  $V_{cc} = 10V$ , and dc bias conditions are  $V_{CE} = 5V$  and  $I_c = 5mA$ . Also calculate the operating point when  $\beta = 25$  and  $\beta = 100$ .



Input loop apply KVL.

$$V_{cc} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{cc} - V_{BE}}{R_B}$$

$$\therefore R_B = \frac{V_{cc} - V_{BE}}{I_B}$$

For silicon  $V_{BE} = 0.7V$

$$V_{cc} = 10V$$

$$I_c = 5 \times 10^{-3} A$$

$$\beta = 50$$

$$\therefore I_B = \frac{I_c}{\beta} = \frac{5 \times 10^{-3}}{50} = 10^{-4} A$$

$$R_B = \frac{10 - 0.7}{10^{-4}}$$

$$= 93k\Omega$$

Output loop KVL.

$$V_{cc} - I_c R_c - V_{CE} = 0$$

$$V_{cc} - V_{CE} = I_c R_c$$

$$R_c = \frac{V_{cc} - V_{CE}}{I_c} = \frac{10 - 5}{5 \times 10^{-3}} = \underline{\underline{1k\Omega}}$$

when  $\beta = 25$

Input KVL.  $V_{cc} - I_B R_B - V_{BE} = 0$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$= \frac{10 - 0.7}{93 \times 10^3}$$

$$= 10^{-4} \text{ A} = 100 \text{ } \mu\text{A} = 10^{-4} \text{ A}$$

$$I_C = \beta I_B = 25 \times 10^{-4}$$

$$= \underline{\underline{2.5 \text{ mA}}}$$

Output KVL.

$$V_{CC} - V_{CE} - I_C R_C = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 10 - 2.5 \times 10^{-3} \times 10^3$$

$$= \underline{\underline{7.5 \text{ V}}}$$

when  $\beta = 100$

Input KVL

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{10 - 0.7}{93 \times 10^3} = 10^{-4} \text{ A}$$

$$I_C = \beta I_B = 100 \times 10^{-4} = 0.01 \text{ A}$$

Output KVL.

$$V_{CC} - V_{CE} - I_C R_C = 0$$


$$V_{CE} = V_{CC} - I_C R_C$$

$$= 10 - 0.01 \times 10^3$$

$$= \underline{\underline{0 \text{ V}}}$$

Qn 2)

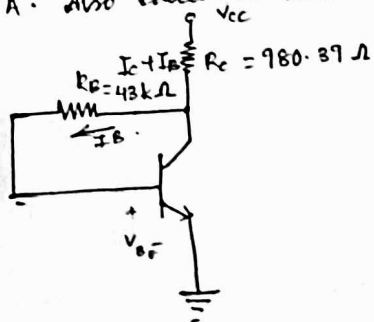Design a collector to base bias circuit using a silicon transistor with  $\beta = 50$ ,  $V_{CC} = 10 \text{ V}$  and dc bias condition  $V_{CE} = 5 \text{ V}$  and  $I_C = 5 \text{ mA}$ . Also calculate the operating point when  $\beta = 25$  and  $\beta = 100$ .



$$\beta = 50$$

$$V_{CC} = 10 \text{ V}$$

$$V_{CE} = 5 \text{ V}$$

$$I_C = 5 \times 10^{-3} \text{ A}$$

$$I_B = \frac{I_C}{\beta} = 10^{-4} \text{ A}$$

KVL for output loop.

$$V_{CC} - (I_C + I_B) R_C - V_{CE} = 0$$

$$\frac{V_{CC} - V_{CE}}{I_C + I_B} = R_C$$

$$R_C = \frac{10 - 5}{10^{-4} + 5 \times 10^{-3}} = \frac{5}{10^{-4} + 5 \times 10^{-3}} = 980.37 \text{ } \Omega$$

Input loop KVL.

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta)R_C}$$

$$10^{-4} = \frac{10 - 0.7}{R_B + 51 \times 980.39}$$

$$10^{-4}(R_B + 50000) = 9.3$$

$$R_B \times 10^{-4} + 5 = 9.3$$

$$R_B = \underline{\underline{43k\Omega}}$$

when  $\beta = 25$ .

Input

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta)R_C}$$

$$I_B = \frac{10 - 0.7}{43000 + 26 \times 980.39}$$
$$= \underline{\underline{1.35 \times 10^{-4} A}}$$

$$I_C = \beta I_B = 25 \times 1.35 \times 10^{-4}$$
$$= \underline{\underline{3.375 \times 10^{-3} A}}$$

Output

$$V_{CE} = V_{CC} - (I_B + I_C)R_C$$
$$= 10 - (1.35 \times 10^{-4} + 3.375 \times 10^{-3}) \times 980.39$$
$$= \underline{\underline{6.54 V}}$$

when  $\beta = 100$

Input


$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta)R_C}$$
$$= \frac{10 - 0.7}{43000 + 101 \times 980.39}$$
$$= \underline{\underline{6.54 \times 10^{-5} A}}$$

$$I_C = \beta I_B$$
$$= 100 \times 6.54 \times 10^{-5}$$
$$= \underline{\underline{6.54 \times 10^{-3} A}}$$


Output

$$V_{CE} = V_{CC} - (I_B + I_C)R_C$$
$$= 10 - (6.54 \times 10^{-5} + 6.54 \times 10^{-3}) \times 980.39$$
$$= \underline{\underline{8.515 V}}$$


### 3) Voltage divider biasing

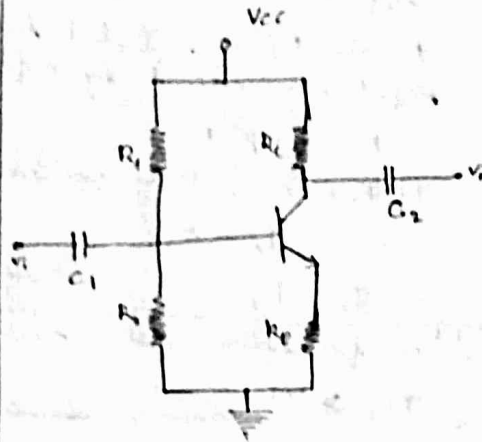

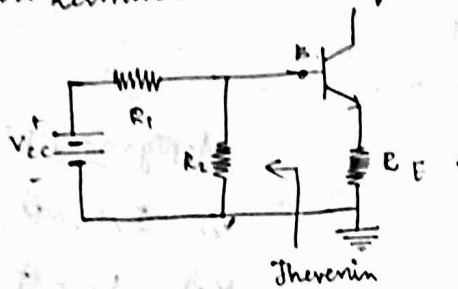Exact Analysis:  
The Thevenin equivalent network for the network to the left of the base terminal can be found.


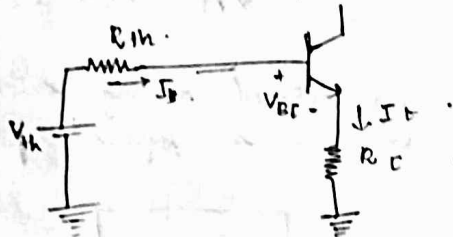
$$V_{th} = V_{th} = V_{cc} \frac{R_2}{R_1 + R_2}$$



$$R_{th} = \frac{R_1 R_2}{R_1 + R_2}$$

#### Exact Analysis

##### Input Loop

Applying KVL

$$V_{th} - I_B R_{th} - V_{BE} - I_C R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (I_C + I_B) R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (\beta I_B + I_B) R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$

$$I_C = \beta I_B$$


##### Output Loop

Applying KVL

$$V_{cc} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{cc} - I_C R_C - I_E R_E$$

1/12/2021

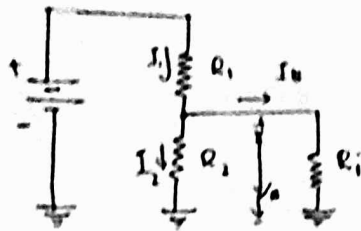

### Approximate Analysis

Resistor  $R_C$  is reflected back to the input base circuit by a factor  $(1+\beta)$

$$R_i = (1+\beta) R_C$$

If  $R_i \gg R_1$ , then we can approx.

- make  $I_B = 0$

$$\therefore I_1 = I_2$$

condition for approximate analysis

$$\beta R_C \geq 10 R_2$$

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$V_E = V_B - V_{BE}$$

$$I_E = \frac{V_E}{R_E}$$

$$I_C \approx I_E$$

Applying KVL for output loop

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$



Qn1) Design a voltage divider biasing circuit using a supply of 20V, a transistor with  $\beta = 80$  and an operating point  $I_C = 10 \text{ mA}$  and  $V_{CE} = 8 \text{ V}$

$$V_{CC} = 20 \text{ V}$$

$$\beta = 80$$

$$I_C = 10 \times 10^{-3} \text{ A}$$

$$V_{CE} = 8 \text{ V}$$

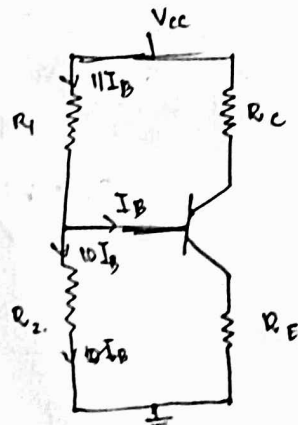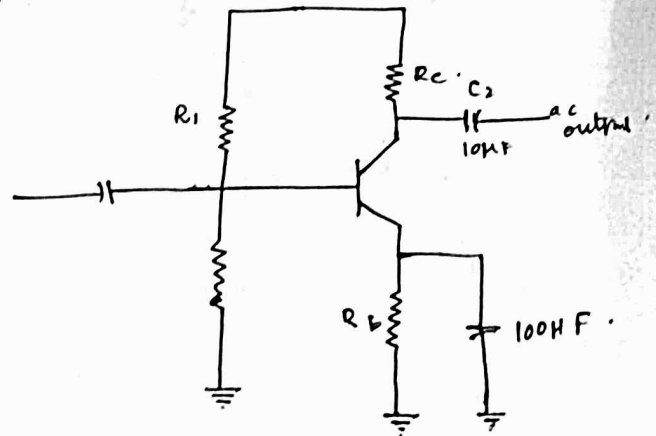

let

$$V_E = \frac{1}{10} V_{CC}$$

$$V_E = 2 \text{ V}$$

$$I_E R_E = 2 V_E$$

$$(I_C + I_B) R_E = V_E$$

$$(1+\beta) I_C R_E = V_E$$

$$81 \times 10^{-3} \times 10 R_E = 2$$

$$R_E = \frac{2}{81 \times 10^{-3} \times 10}$$

$$R_E = 2.489 \Omega$$

Using approximation  $I_E \approx I_C$

$$I_E R_E = 2$$

$$10^{-2} R_E = 2$$

$$R_E = \frac{2}{10^{-2}}$$

$$R_E = 200 \Omega$$

Output KVL

$$V_{CC} - I_C R_C - V_{CE} - V_E = 0$$

$$20 - 10^{-2} R_C - 8 - 2 = 0$$

$$20 - 10 = 10^{-2} R_C$$

$$R_C = \frac{10}{10^{-2}}$$

$$R_C = 10^3 \Omega = 1k\Omega$$

Assume current  $I_B \neq 0$ , current through  $R_2 = 10 I_B$   
 $\therefore$  current through  $R_1 = 11 I_B$

$$V_B = V_E + V_{BE}$$

$$= 2 + 0.7$$

$$= 2.7V$$

$$V_B = 10 I_B R_2$$

$$= 10 \times \frac{I_C}{\beta} R_2$$

$$2.7 = 10 \times \frac{10 \times 10^{-3}}{8} R_2$$

$$2.7 = \frac{10^{-2}}{8} R_2$$

$$R_2 = \frac{2.7 \times 8}{10^{-2}}$$

$$R_2 = 2160 \Omega$$

$$\frac{V_{CC} - V_B}{R_1} = 11 I_B$$

$$R_1 = \frac{20 - 2.7}{11 \times 10^{-3} / 8}$$

$$R_1 = 1258.18 \Omega$$

Qn 1) Determine the operating point for the voltage divider bias circuit by a) Exact analysis  
b) Approximate analysis

$$R_1 = 29k\Omega$$

$$R_2 = 3.9k\Omega$$


$$R_C = 10k\Omega$$

$$R_E = 1.5k\Omega$$

$$\beta = 100$$

$$V_{CC} = 22V$$

$$R_C = 1.5k\Omega$$

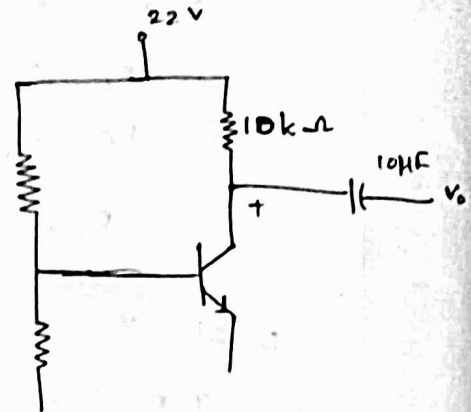

a) Exact Analysis

$$\begin{aligned} E_{Th} &= V_{CC} \frac{R_2}{R_1 + R_2} \\ &= 22 \left[ \frac{3.9 \times 10^3}{29 \times 10^3 + 3.9 \times 10^3} \right] \\ &= 22 \left( \frac{3.9}{3.9 + 29} \right) \\ &= \underline{\underline{2V}} \end{aligned}$$

$$\begin{aligned} R_{Th} &= \frac{R_1 R_2}{R_1 + R_2} \\ &= \frac{29 \times 10^3 \times 3.9 \times 10^3}{(2.9 + 3.9) \times 10^3} \\ &= \underline{\underline{3545.45 \Omega}} \end{aligned}$$

Applying KVL for input loop.

$$E_{Th} - I_B R_{Th} - V_{BE} - R_E I_E = 0$$

$$2 - I_B \times 3545.45 - 0.7 - 1.5 \times 10^3 \times (I_B + I_C) = 0$$

$$\begin{aligned} I_B &= \frac{E_{Th} - V_{BE}}{R_{Th} + (1 + \beta) R_E} \\ &= \frac{2 - 0.7}{3545.45 + 101 \times 1.5 \times 10^3} \\ &= \underline{\underline{8.384 \times 10^{-6} A}} \end{aligned}$$

$$\begin{aligned} I_C &= \beta I_B \\ &= 100 \times 8.384 \times 10^{-6} \\ &= \underline{\underline{8.384 \times 10^{-4} A}} \end{aligned}$$

KVL for output

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$



$$V_{CE} = 22 - 8.8846 \times 10^{-4} \times 10 \times 10^3 - 8.8846 (10^{-6} + 10^{-4}) \times 1.5 \times 10^3$$

$$= \underline{\underline{12.35 \text{ V}}}$$

b) Approximate analysis

$$R_E = 100 \times 1.5 \times 10^3 \Omega$$

$$= 1.5 \times 10^5 \Omega$$

$$10R_2 = 10 \times 3.9 \times 10^3 \Omega$$

$$= 3.9 \times 10^4 \Omega$$

$\therefore R_E \gg 10R_2$ ,  $\therefore$  Approximate analysis can be done.

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$= 22 \left[ \frac{3.9 \times 10^3}{3.9 \times 10^3 + 3.9 \times 10^3} \right]$$

$$= \underline{\underline{2 \text{ V}}}$$

$$V_E = V_B - V_{BE}$$

$$= 2 - 0.7$$

$$= \underline{\underline{1.3 \text{ V}}}$$

$$I_E = \frac{V_E}{R_E}$$

$$= \frac{1.3}{1.5 \times 10^5} = \underline{\underline{8.667 \times 10^{-4} \text{ A}}}$$

$$I_C \approx I_E$$

$$\therefore I_C = 8.667 \times 10^{-4} \text{ A}$$

Output KVL:

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$= 22 - 8.667 \times 10^{-4} (10 \times 10^3 + 1.5 \times 10^3)$$

$$= \underline{\underline{12.03 \text{ V}}}$$

8/12/2021

## Stability factors

$$S(I_{CO}) = \left. \frac{dI_C}{dI_{CO}} \right|_{V_{BE}, \beta \text{ constant}}$$

Stability factor wrt leakage current.

$$S(V_{BE}) = \left. \frac{dI_C}{dV_{BE}} \right|_{I_{CO}, \beta = \text{constant}} \quad \text{SF wrt } V_{BE}$$

$$S(\beta) = \left. \frac{dI_C}{d\beta} \right|_{I_{CO}, V_{BE} = \text{constant}} \quad \text{SF wrt } \beta$$

## General expression

$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

Differentiating wrt  $I_C$

$$1 = \frac{\beta dI_B}{dI_C} + (1 + \beta) \frac{dI_{CO}}{dI_C} \quad \frac{dI_{CO}}{dI_C} = \frac{1}{S}$$

$$1 = \frac{\beta I_B}{I_C} + \frac{1 + \beta}{S}$$

$$1 - \frac{\beta dI_B}{dI_C} = \frac{1 + \beta}{S}$$

$$S = \frac{1 + \beta}{1 - \beta \frac{dI_B}{dI_C}}$$

Voltage divider biasing circuit

$$S(I_{CO})$$

$$V_{TH} - I_B R_{TH} - V_{BE} - I_C R_E = 0$$

$$V_{TH} - I_B R_{TH} - V_{BE} - (I_C + I_B) R_E = 0$$


Diff wrt  $I_C$

$$0 - R_{TH} \frac{dI_B}{dI_C} - 0 - R_E - R_E \frac{dI_B}{dI_C} = 0$$

$$\frac{dI_B}{dI_C} (-R_{TH} - R_E) = R_E$$

$$\frac{dI_B}{dI_C} = \frac{-R_E}{R_{TH} + R_E}$$
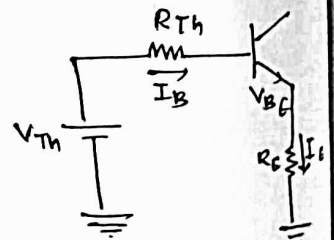
$$\therefore S = \frac{1 + \beta}{1 + \beta \left( \frac{R_E}{R_{TH} + R_E} \right)}$$



$$S(V_{BE})$$

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$V_{TH} - \frac{I_E}{\beta} R_{TH} - V_{BE} - (1+\beta) \frac{I_E}{\beta} R_E = 0$$

Diff wrt  $I_E$

$$0 - \frac{R_{TH}}{\beta} - \frac{dV_{BE}}{dI_E} - \frac{(1+\beta)}{\beta} R_E = 0$$

$$-\frac{R_{TH}}{\beta} - \frac{(1+\beta)}{\beta} R_E = \frac{dV_{BE}}{dI_E}$$



$$\frac{dV_{BE}}{dI_E} = - \frac{(R_{TH} + (1+\beta)R_E)}{\beta}$$

$$\frac{dI_E}{dV_{BE}} = \frac{-\beta}{R_{TH} + (1+\beta)R_E}$$

Qn 1) Design a voltage divider biasing circuit given  $\beta = 50$ ,  $V_{BE} = 0.6$ ,  $V_{CC} = 18V$ ,  $R_C = 4.3k\Omega$ ,  $I_{CQ} = 1.5mA$ ,  $V_{CE} = 10V$ ,  $SF = 8 \leq 4$ .

Exact Analysis

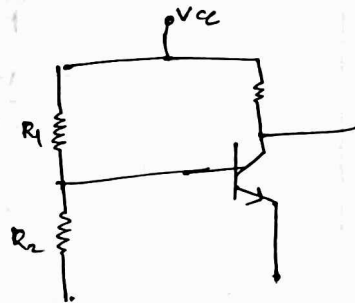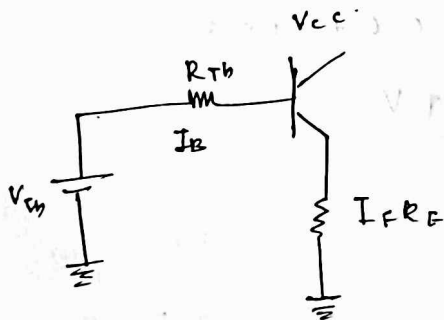Since  $R_C$  is given output loop is taken.



Output loop

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$18 - 1.5 \times 10^{-3} \times 4.3 \times 10^3 - 10 - 1.5 \times 10^{-3} R_E = 0$$

$$R_E = 1033.33 \Omega$$

$$R_E = 1k\Omega$$

$$S_{C_{I_{C0}}} = \frac{1+\beta}{1+\beta \left( \frac{R_E}{R_{Th}+R_E} \right)}$$

$$4 = \frac{1+50}{1+50 \left( \frac{1000}{1000+R_{Th}} \right)}$$

$$4 + (50 \times 4) \frac{1000}{1000+R_{Th}} = 51$$

$$4 + \frac{2 \times 10^5}{1000+R_{Th}} = 47$$

$$1000+R_{Th} = \frac{20 \cdot 2 \times 10^5}{47}$$

$$R_{Th} = \underline{\underline{3255.32 \Omega}} \approx \underline{\underline{3.3 k\Omega}}$$

Input KVL

$$V_{Th} - I_B R_{Th} - V_{BE} - I_E R_E = 0$$

$$V_{Th} = I_B R_{Th} + V_{BE} + I_E R_E$$

$$= \frac{I_C}{\beta} \times 3.3 \times 10^3 + 0.6 + (I_C + I_B) R_E$$

$$= \frac{1.5 \times 10^{-3}}{50} \times 2.3 \times 10^3 + 0.6 + \left( 1.5 \times 10^{-3} + \frac{1.5 \times 10^{-3}}{50} \right) 1000$$

$$= 0.097 + 0.6 + 1.53$$

$$= \underline{\underline{2.229 V}}$$

$$V_{Th} = V_{CC} \frac{R_2}{R_1+R_2}$$

$$\frac{R_2}{R_1+R_2} = V_{Th} / V_{CC}$$

$$= \frac{2.229 V}{12 V} = 0.1238$$

$$R_{Th} = \frac{R_1 R_2}{R_1+R_2}$$

$$R_{Th} = R_1 \times 0.1238$$

$$3.3 \times 10^3 = R_1 \times 0.1238$$

$$R_1 = \underline{\underline{1480.48 \Omega}}$$

$$\frac{R_2}{1480.48 + R_2} = 2.227$$

$$R_2 = 2.227 \times 1480.48 + 2.227 R_2$$

$$R_{TH} = R_1 \times 0.1238$$

$$R_1 = 26648.7214 \Omega$$

$$= \underline{\underline{26.3 k\Omega}}$$

$$R_2 = (0.1238)(R_1 + R_2)$$

$$R_2 = 0.1238 R_1 \times 26.2 \times 10^3 + 0.1238 R_2$$


$$0.8762 R_2 = 3255.94$$

$$R_2 = 8715.95 \Omega$$


$$R_2 = \underline{\underline{2.7 k\Omega}}$$

Bias compensation circuits

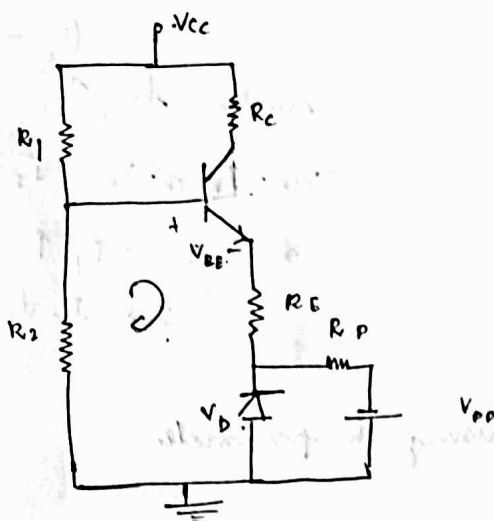1) Diode compensation for variation in  $V_{BE}$




Input

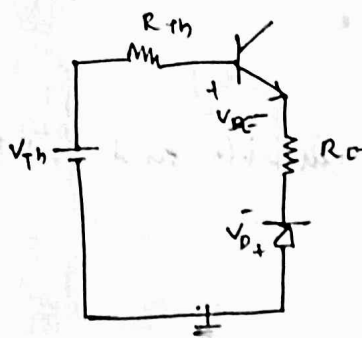

$$V_{TH} - I_B R_{TH} - V_{BE} - I_C R_E + V_D = 0$$

9/12/2021

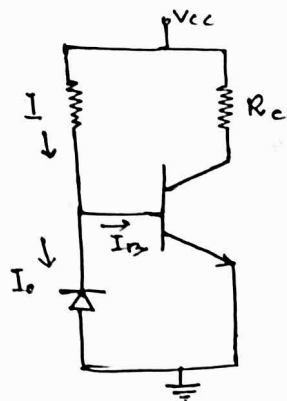2) Diode compensation for instability due to variation in  $I_{CO}$



$I_0$  - leakage current

$$I_B = I - I_0$$

$$I_C = \beta I_B + (1 + \beta) I_{C0}$$

$$1 + \beta \approx \beta$$


$$\therefore I_C = \beta I_B + \beta I_{C0}$$

$$I_C = \beta (I - I_0) + \beta I_{C0}$$

$$I_C = \beta I - \beta I_0 + \beta I_{C0}$$

The diode & transistor is made of same material, the diode is in the reverse biased condition, so there is a leakage current. Any change in leakage current is compensated by diode leakage current thus  $I_C$  remains a constant.

### 3) Thermistor compensation

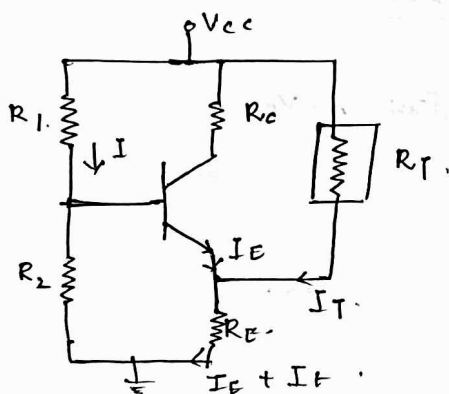

Thermistor has -ve temp coefficient

$$\therefore \text{Temp} \uparrow R_T \downarrow I_T \uparrow$$

$$\therefore (I_E + I_T) \uparrow$$

emitter drop  $\uparrow$

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$\text{when } I_E + I_T \uparrow$$

$$I_B \downarrow I_C \downarrow$$

Transistor modelling using h-parameters

h - hybrid



Let  $V_1$  &  $I_2$  be dependent variables and  $I_1$  &  $V_2$  be independent variables.

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$h_{11}$ ,  $h_{12}$ ,  $h_{21}$ , &  $h_{22}$  are hybrid-parameters.

$$h_{11} = \frac{V_1}{I_1} \bigg|_{V_2 = 0}$$

short circuit input impedance

unit -  $\Omega$ .

$$h_{12} = \frac{V_1}{V_2} \bigg|_{I_1=0}$$


Open circuit reverse voltage gain  
No unit

$$h_{21} = \frac{I_2}{I_1} \bigg|_{V_2=0}$$

Short circuit forward current gain  
No unit

$$h_{22} = \frac{I_2}{V_2} \bigg|_{I_1=0}$$

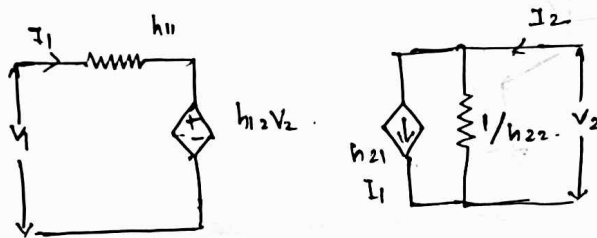Open circuit output admittance  
unit - mho.




$$h_{11} \rightarrow h_i$$

$$h_{12} = h_r$$

$$h_{21} = h_f$$

$$h_{22} = h_o$$

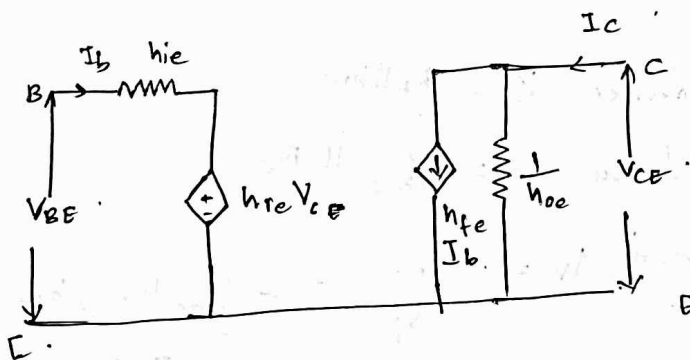
h-parameter model of transistor in CE configuration




13/12/2021

Small signal approximate ac equivalent circuit of CE amplifier

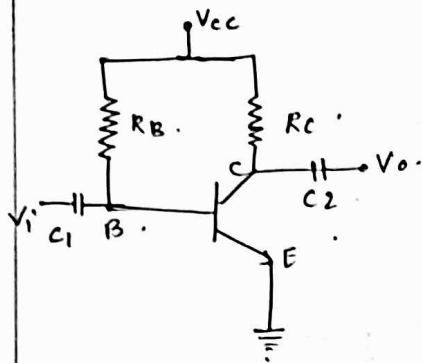In approximate analysis  $h_{re}$  is neglected.



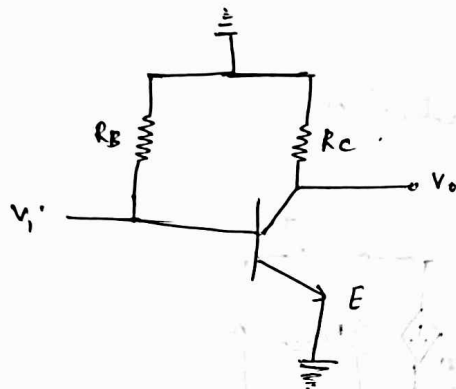
- ground the dc source  $V_{cc}$ .
- short all the capacitors



fixed biasing

$h_{re}$  is neglected

The equivalent is

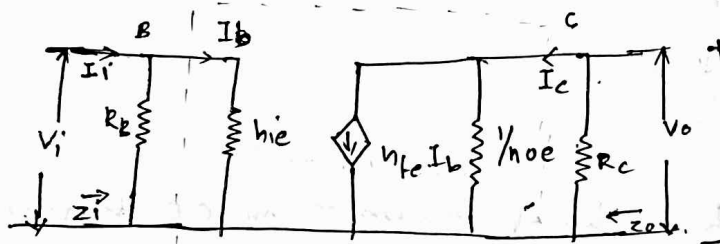

Input impedance  $Z_i = R_B \parallel h_{ie}$

Output Impedance  $Z_o = 1/h_{oe} \parallel R_C$

Voltage gain  $A_v = \frac{V_o}{V_i} = - \frac{(1/h_{oe} \parallel R_C) h_{fe} R_B}{I_b h_{ie}}$

$$= - \frac{h_{fe}}{h_{ie}} (1/h_{oe} \parallel R_C)$$

The negative sign since the current flows in opposite direction



current gain  $A_i$

$$A_i = \frac{I_o}{I_i}, \text{ when } R_B \gg h_{ie}$$

$$A_i = \frac{I_o}{I_i} = \frac{I_b h_{fe}}{I_b} \approx h_{fe}$$



If  $R_B \gg h_{ie}$

$$I_b = I_i \frac{R_B}{R_B + h_{ie}}, \quad \therefore I_i = \frac{I_b (R_B + h_{ie})}{R_B}$$

$$A_i = \frac{I_o}{I_i} = \frac{I_b h_{fe}}{I_b (R_B + h_{ie})} \times R_B$$

$$= \frac{h_{fe} R_B}{R_B + h_{ie}}$$

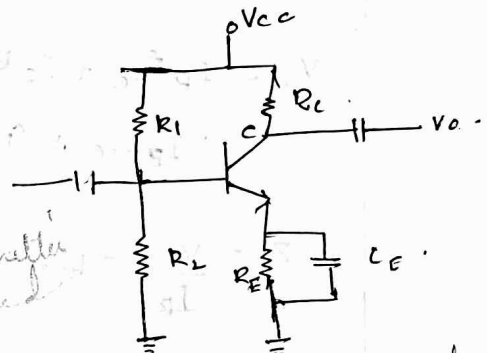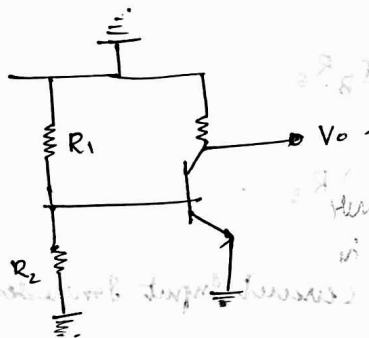
Common emitter amplifier circuit using voltage divider biasing



(Common emitter amplifier)

while doing the ac analysis short all the capacitors & ground all the dc source.

Equivalent is

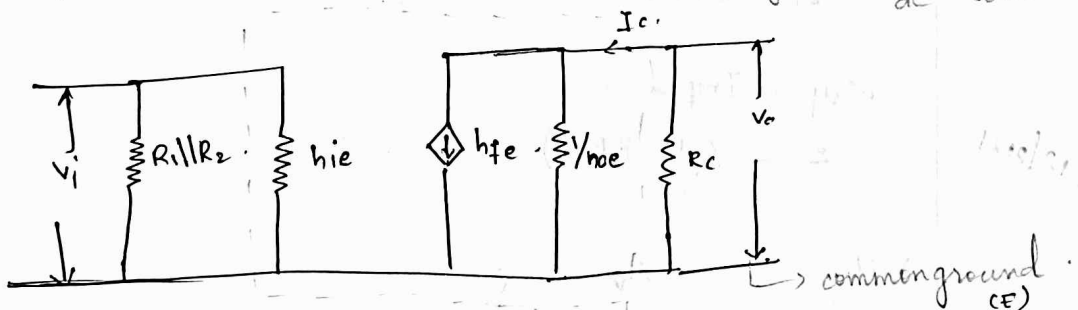

$$Z_i = R_1 || R_2 || h_{ie}$$


$$Z_o = 1/h_{oe} || R_c$$

$$A_v = \frac{-h_{fe} (1/h_{oe} || R_c)}{h_{ie}}$$


$$A_i \approx h_{fe} \text{ or}$$

$$A_i = \frac{h_{fe} (R_1 || R_2)}{(R_1 || R_2) + h_{ie}}$$

when the emitter is unbypassed

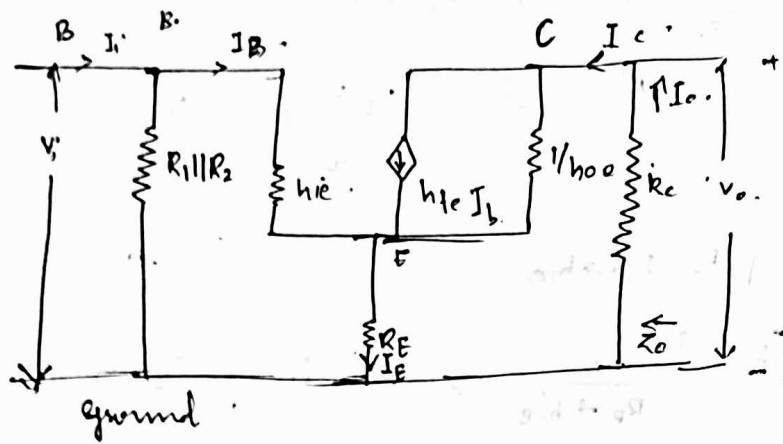

The circuit is

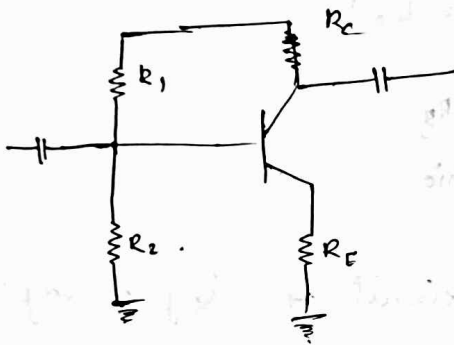

$$V_i = I_B h_{ie} + I_C R_C$$

$$= I_B h_{ie} + (1 + h_{fe}) I_B R_E$$

$$Z_i = \frac{V_i}{I_B} = h_{ie} + (1 + h_{fe}) R_E$$

Transistor Impedance  $Z_i'$  (circuit Input Impedance)

$$Z_i' = (R_1 \parallel R_2) \parallel Z_i$$

Output Impedance

$$Z_o = \left( \frac{1}{h_{oe}} \parallel R_C \right)$$

$$\text{Voltage gain } A_v = \frac{V_o}{V_i}$$

$$V_o = -h_{fe} I_B \left( \frac{1}{h_{oe}} \parallel R_C \right)$$

$$V_i = I_B h_{ie} + (1 + h_{fe}) I_B R_E$$

$$A_v = \frac{-h_{fe} I_B \left( \frac{1}{h_{oe}} \parallel R_C \right)}{I_B h_{ie} + (1 + h_{fe}) I_B R_E}$$

17/12/2021

$$= \frac{-h_{fe} (V_{hce} \parallel R_c)}{h_{ie} + (1+h_{fe}) R_c}$$

in Approximating

$$A_v = \frac{-h_{fe} R_c}{h_{fe} R_E} = \frac{-R_c}{R_E}$$

Current gain

$$A_i = \frac{I_o}{I_i}$$

$$\text{if } R_1 \parallel R_2 \gg h_{ie}$$

$$A_i = \frac{I_c}{I_b} = h_{fe}$$

$$I_b = \frac{I_i \times (R_1 \parallel R_2)}{(R_1 \parallel R_2) + Z_i}$$


$$I_i = \frac{I_b (R_1 \parallel R_2 + Z_i)}{R_1 \parallel R_2}$$

$$A_i = \frac{I_c}{I_b}$$

$$A_i = \frac{h_{fe} I_b (R_1 \parallel R_2)}{I_b (R_1 \parallel R_2 + Z_i)}$$

$$A_i = \frac{h_{fe} (R_1 \parallel R_2)}{(R_1 \parallel R_2) + Z_i}$$

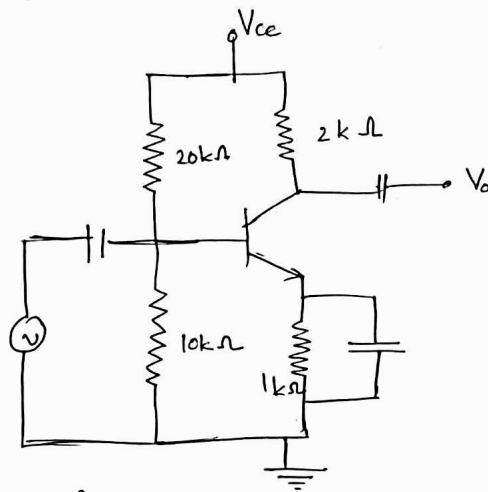Qn 1) calculate the input impedance, output impedance, voltage gain and current gain of the given amplifier circuit.




$$h_{ie} = 1k\Omega$$

$$h_{fe} = 100$$

$$h_{oe} = 25\mu S$$

$Z_i =$

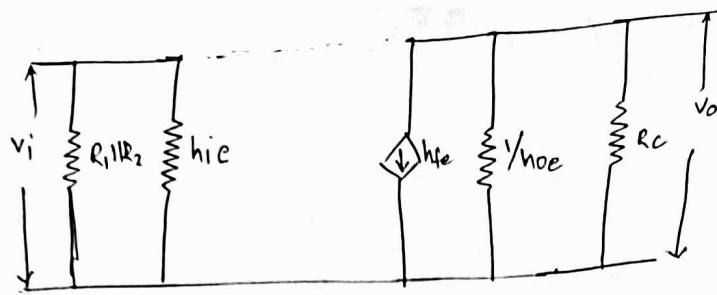

$$R_1 = 20k\Omega$$

$$R_2 = 10k\Omega$$

$$Z_i = R_1 || R_2 || h_{ie}$$

$$= \frac{1}{\frac{1}{20 \times 10^3} + \frac{1}{10 \times 10^3} + \frac{1}{1 \times 10^3}}$$

$$= \frac{1}{\frac{1}{10^3} \left( \frac{1}{20} + \frac{1}{10} + 1 \right)}$$

$$= \frac{1}{\frac{93}{20} \times 10^{-3}}$$

$$869.56 \Omega$$

$$\underline{\underline{869.56 \Omega}}$$

$$Z_o = \frac{1}{h_{oe}} || R_C$$

$$= \frac{1}{25 \times 10^{-6}} || 2 \times 10^3$$


$$= \frac{1}{\frac{1}{25 \times 10^{-6}} + \frac{1}{2 \times 10^3}}$$

$$A_v = \frac{-h_{fe}}{h_{ie}} \left( \frac{1}{h_{oe}} || R_C \right)$$

$$A_i = \frac{h_{fe} (R_1 || R_2)}{(R_1 || R_2) + h_{ie}}$$
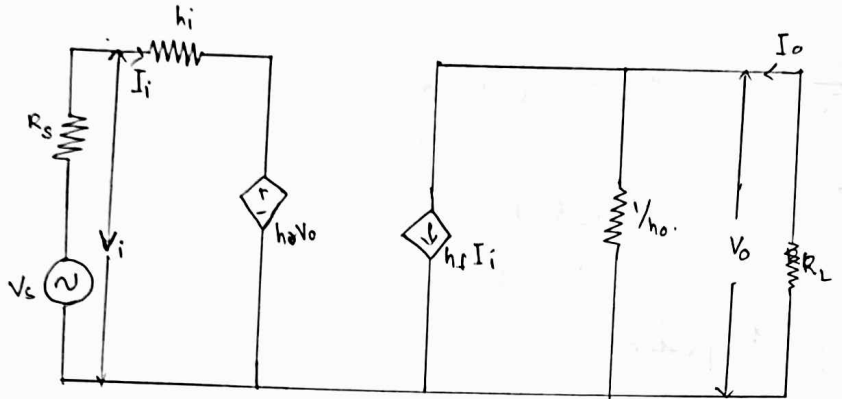
## Exact Equivalent circuit

Small signal analysis of CE amplifier using exact equivalent circuit.



$$V_i = h_i I_i + h_r V_o \quad \text{--- (1)}$$

$$I_o = h_f I_i + h_o V_o \quad \text{--- (2)}$$

Current gain

$$A_i = \frac{I_o}{I_i}$$

$$I_o = h_f I_i + h_o V_o$$

$$V_o = -I_o R_L$$

$$I_o = h_f I_i - h_o R_L I_o$$

$$h_f I_i = I_o (1 + h_o R_L)$$

$$\boxed{\frac{I_o}{I_i} = \frac{h_f}{1 + h_o R_L}}$$

Voltage gain

$$A_v = \frac{V_o}{V_i}$$

$$V_i = h_i I_i + h_r V_o$$

$$I_i = \left( \frac{1 + h_o R_L}{h_f} \right) I_o$$

$$I_i = - \left( \frac{1 + h_o R_L}{h_f} \right) \frac{V_o}{R_L}$$

Approx.

$$V_i = -h_i \frac{V_o}{R_L} \left( \frac{1 + h_o R_L}{h_f} \right) + h_r V_o$$

$$V_i = V_o \left( h_r - \frac{h_i (1 + h_o R_L)}{R_L h_f} \right)$$

$$\frac{V_o}{V_i} =$$

$$V_i = V_o \left( \frac{h_r h_f R_L - h_i (1 + h_o R_L)}{R_L h_f} \right)$$

$$A_v = \frac{V_o}{V_i} = \frac{-h_f R_L}{h_i + (h_i h_o - h_r h_f) R_L}$$

Input Impedance

$$Z_i = \frac{V_i}{I_{i1}}$$

$$V_i = h_i I_i + h_r V_o$$

$$V_o = -I_o R_L$$

$$= \left( -I_i \frac{h_f}{1 + h_o R_L} \right) R_L$$

input

$$V_i = h_i I_i + h_r \left( -I_i R_L \left( \frac{h_f}{1 + h_o R_L} \right) \right)$$

$$V_i = I_i \left( h_i - h_r \left( \frac{R_L h_f}{1 + h_o R_L} \right) \right)$$

$$\frac{V_i}{I_i} = h_i - \frac{h_r h_f R_L}{1 + h_o R_L}$$

$$Z_i = h_i - \frac{h_r h_f R_L}{1 + h_o R_L}$$

Output Impedance

$$Z_o = \frac{V_o}{I_o}$$

$$I_o = h_f I_i + h_o V_o$$

$$I_i = \frac{I_o (1 + h_o R_L)}{h_f}$$

when  $V_s = 0$

$$I_i = - \frac{h_r V_o}{h_i + R_s}$$

$$I_o = -h_f \frac{h_r V_o}{h_i + R_s} + h_o V_o$$

$$I_o = V_o \left( -\frac{h_f h_r}{h_i + R_s} + h_o \right)$$

$$Z_o = \frac{1}{h_o - \left( \frac{h_f h_r}{h_i + R_s} \right)}$$