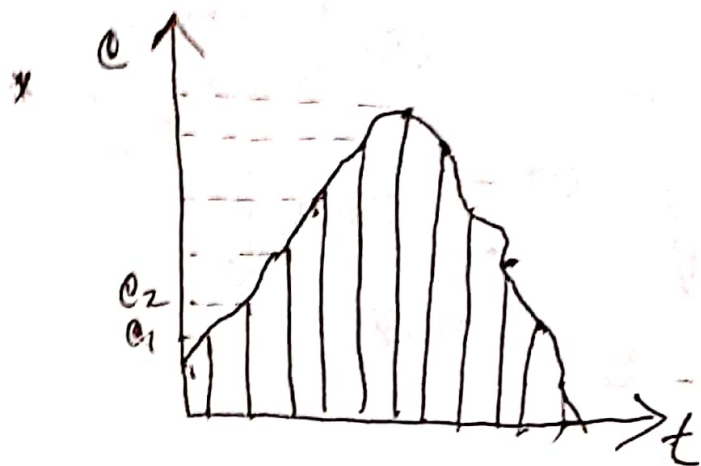



explanation

Average value & rms value



$$E_{av} = \frac{E_1 + E_2 + \dots + E_n}{n}$$
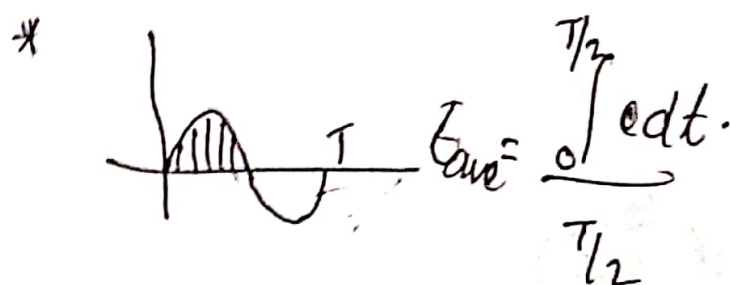
$$E_{av} = \frac{\int_0^t e dt}{T} \quad (\text{for continuous})$$



Average Value = $\frac{\text{Area}}{\text{Base}}$

* $E_{rms} = \sqrt{\frac{e_1^2 + e_2^2 + \dots + e_n^2}{n}} \rightarrow \text{discrete.}$

$$E_{rms} = \sqrt{\frac{\int_0^T e^2 dt}{T}} \rightarrow \text{continuous.}$$

? * $v(t) = V_m \sin \omega t$

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt = 0$$

$$V_{avg} = \frac{1}{\pi} V_m (-\cos \omega t) \Big|_0^\pi$$

$$= \frac{V_m}{\pi} (-2) = \frac{-2V_m}{\pi} + \frac{2V_m}{\pi}$$

$$V_{rms} = \sqrt{\frac{\int_0^{2\pi} V_m^2 \sin^2 \omega t d\omega t}{2\pi}}$$


$$= \sqrt{\frac{\int_0^{2\pi} (1 - \cos 2\omega t) d\omega t}{4\pi}} = \sqrt{\frac{\omega t - \frac{\sin 2\omega t}{2}}{4\pi}} \Big|_0^{2\pi}$$

$$= \frac{V_m}{2} \sqrt{\frac{2\pi - \frac{\sin 4\pi}{2}}{\pi}} = \frac{V_m}{2} \sqrt{\frac{2\pi}{\pi}} = \frac{V_m}{\sqrt{2}}$$

$\cos 2x = 1 - 2\sin^2 x$
 $2\sin^2 x = 1 - \cos 2x$

(rms value is equivalent to dc)

* * Half rectified

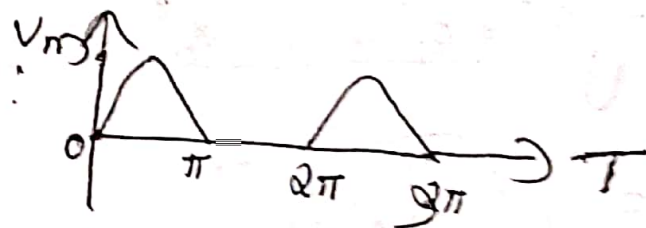

$$V_{ave} = \frac{1}{T} \int_0^T e dt = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \omega t d\omega t$$

$$= \frac{-V_m}{2\pi} [\cos \omega t]_0^{2\pi} = \frac{-V_m}{2\pi} (-2) = \frac{V_m}{\pi}$$

$$V_{rms} = \sqrt{\frac{\int_0^T V_m^2 \sin^2 \omega t d\omega t}{T}} = \sqrt{\frac{\int_0^{2\pi} V_m^2 \sin^2 \omega t d\omega t}{2\pi}}$$

$$\sqrt{\frac{\int_0^{\pi} V_m^2 \sin^2 \omega t d\omega t}{2\pi} + \frac{\int_{\pi}^{2\pi} V_m^2 \sin^2 \omega t d\omega t}{2\pi}}$$

$$\begin{aligned}
 & \frac{1}{\sqrt{2\pi}} \sqrt{\frac{(\cos t - \sin \frac{\omega t}{2})^2}{2} + \frac{(\cos t - \sin \frac{\omega t}{2})^2}{2}} \\
 &= \frac{1}{\sqrt{2\pi}} \sqrt{\frac{\pi + \pi - (0-1)}{2}} = \frac{V_m}{\sqrt{2\pi}} \sqrt{2\pi - 1} \\
 &= \underline{\underline{\frac{V_m}{2}}}
 \end{aligned}$$



* Phases

$$\begin{aligned}
 v(t) &= \\
 &\rightarrow V_m \cos(\omega t + \phi)
 \end{aligned}$$

$$= \operatorname{Re} [V_m e^{j(\omega t + \phi)}] = \operatorname{Re} [V_m e^{j\omega t} e^{j\phi}]$$


$$= \operatorname{Re} [\vec{V} e^{j\omega t}]$$
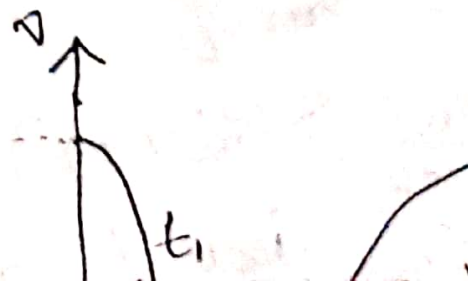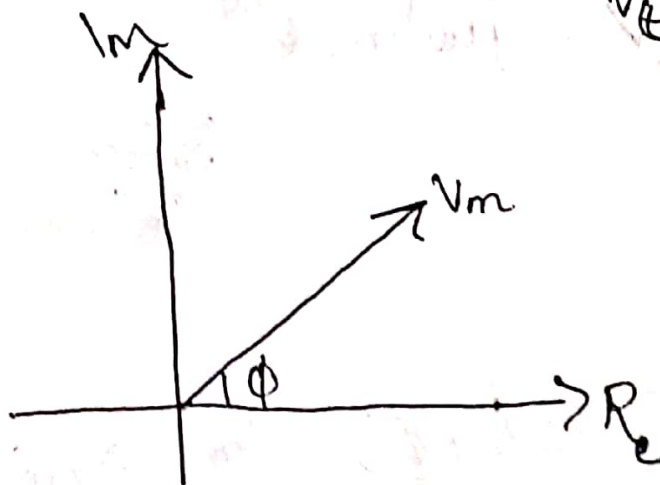
$$\vec{V} = V_m e^{j\phi} \rightarrow \text{phasor representation of } v(t) = V_m \cos(\omega t + \phi)$$



Phasor Relationships of Circuit Elements

* Resistor:

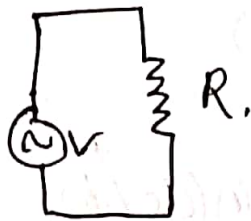

$$V = V_m \cos(\omega t + \phi)$$

$$i = \frac{V}{R} \cos(\omega t + \phi)$$

$$i = i_m \cos(\omega t + \phi)$$


$$i_m = \left(\frac{V}{R}\right)$$

Phasor: $i = I_m \angle \phi$

$$V = R I_m \angle \phi$$

Both the voltage and current are in same phase.

Purely Resistive.

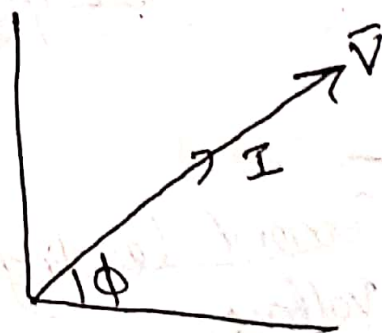

* Purely Inductive circuit



$$i = I_m \cos(\omega t + \phi)$$

$$V = L \frac{di}{dt}$$

$$\frac{di}{dt} = I_m \omega \sin(\omega t + \phi)$$

$$i = +\omega L I_m \cos(\omega t + \phi + 90^\circ)$$
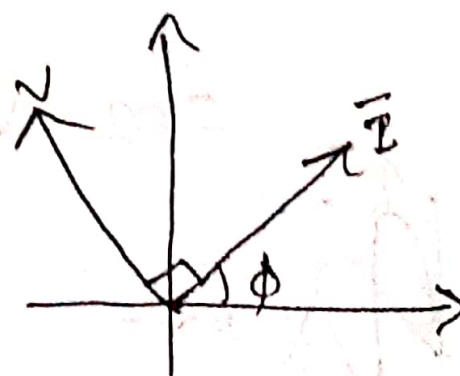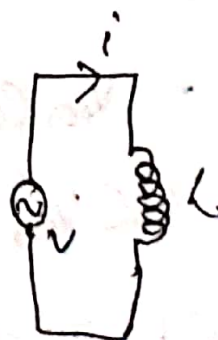
$$V = \omega L I_m \angle (90^\circ + \phi)$$



Current lags behind the Voltage by 90° .

* Purely Capacitive Circuit


$$V = V_m \cos(\omega t + \phi)$$

$$i = C \frac{dV}{dt} = \omega C V_m \sin(\omega t + \phi)$$

$$i = \omega C V_m \sin(\omega t + \phi)$$

$$\omega C V_m \cos(\omega t + \phi + 90^\circ)$$

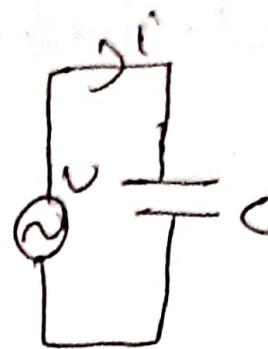
$$V = V_m \angle \phi, i = \omega C V_m \angle (90^\circ + \phi)$$



$$\phi = 90^\circ$$

$$\bar{V} \neq \bar{I}$$

[Current leading the voltage]

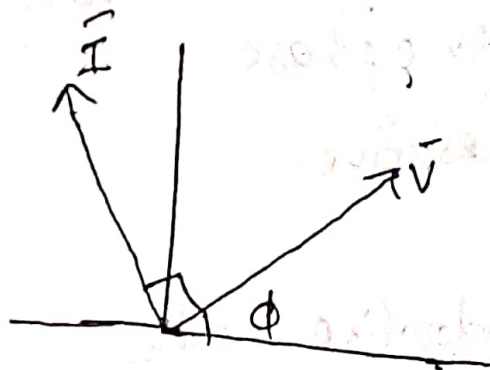

* Inductive


$$P_{\text{inst}} = V i = V_m \cos(\omega t + \phi) \times \omega L I_m \cos(\omega t + \phi + 90^\circ)$$

$$= \omega L V_m^2 \cos(\omega t + \phi) (-\sin(\omega t + \phi))$$

$$= -\omega L V_m^2 \sin 2(\omega t + \phi)$$

$$= -\frac{1}{2} \omega L V_m I_m \sin 2(\omega t + \phi)$$
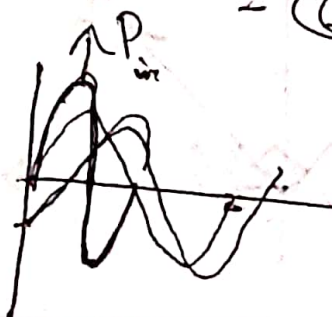
$$= 0 - \frac{V_m I_m}{2} \sin(2\omega t + 2\phi)$$



$$P_{\text{ave}} = 0$$

* Capacitive: $P_{inst} = i_m V_m$
 $= V_m (\cos(\omega t + \phi))$
 $= -\frac{V_m I_m}{2} \sin 2\omega t, \quad \omega = \omega t + \phi$

Angular Frequency of Power = 2ω .

$\frac{V}{I} = \frac{1}{j\omega C} = \frac{-j}{\omega C}$ 1. $\frac{V}{I} = R$ Resistive
 2. $\frac{V}{I} = j\omega L$ Inductive
 3. $\frac{V}{I} = \frac{-j}{\omega C}$ Capacitive

* Impedance Z

Ratio of Resistance offered: $Z = \frac{V}{I}$

$$Z = R$$

$$= j\omega L$$

$$= \frac{-j}{\omega C}$$

→ if $\omega = 0$, dc circuit, $Z = 0$: purely inductive.
 $Z = \infty$: purely capacitive.


Purely Inductive: $\omega = 0, Z = 0$
 $\omega = \infty, Z = \infty$

Purely Capacitive: $\omega = 0, Z = \infty$
 $\omega = \infty, Z = 0$

Admittance: $(\frac{1}{Z})$, $Y = \frac{1}{Z} = G + jB$ Conductance $G = \frac{1}{R}$
Susceptance $B = \frac{1}{X}$

* $Z = R \pm jX \rightarrow$ reactance

11/20/19

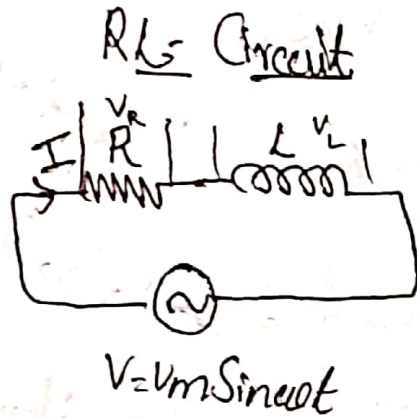


$$V_L = I X_L$$

$$V_R = IR$$

X_L - reactance offered by inductance

$$X_L = \omega L$$

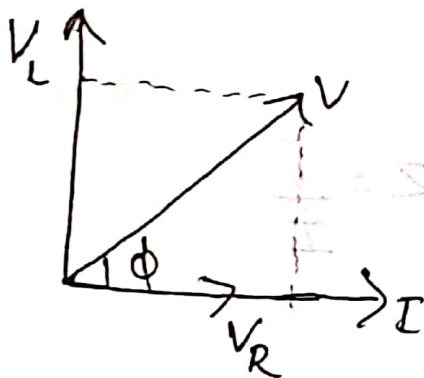

$$I = I_m \sin(\omega t - \phi)$$

$$V = \sqrt{V_R^2 + V_L^2}$$

$$V = I \sqrt{R^2 + (\omega L)^2}$$


$$\Rightarrow I = \frac{V}{\sqrt{R^2 + (\omega L)^2}}$$

$$\phi = \tan^{-1}\left(\frac{V_L}{V_R}\right) = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$* |Z| = \sqrt{R^2 + (\omega L)^2}$$

$$Z = R + j\omega L$$
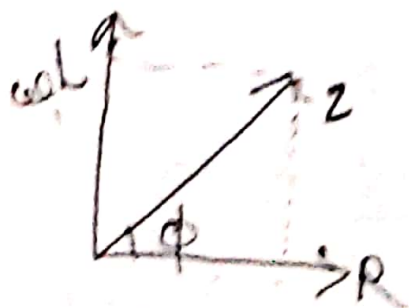
$$Z \angle \phi ; \sqrt{R^2 + (\omega L)^2} \angle \tan^{-1}\left(\frac{\omega L}{R}\right)$$



$$V = \sqrt{V_R^2 + V_L^2}$$

$$V = I \sqrt{R^2 + \left(\frac{1}{C\omega}\right)^2}$$

$$|Z| = \sqrt{R^2 + \left(\frac{1}{C\omega}\right)^2}$$


$$Z = R - \frac{j}{C\omega}$$

$$\phi = \tan^{-1}\left(\frac{1}{C\omega R}\right)$$

Power, $P = V_R I$
 $= VI \cos \phi$

$\cos \phi = \text{power factor of circ.}$

RC Circuit

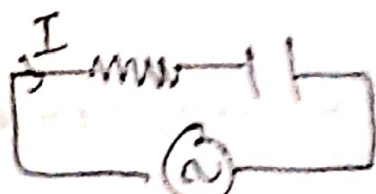



$$V_t = V_m \sin \omega t$$

$$V_R = IR$$

$$V_L = I X_C$$

$$X_C = \frac{1}{C\omega}$$

$$I = I_m \sin(\omega t + \phi)$$

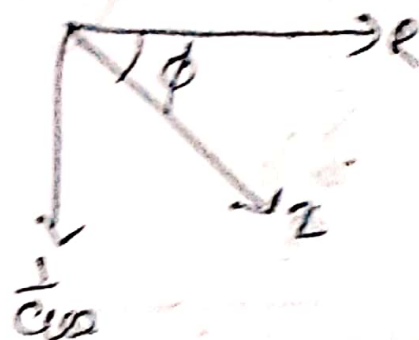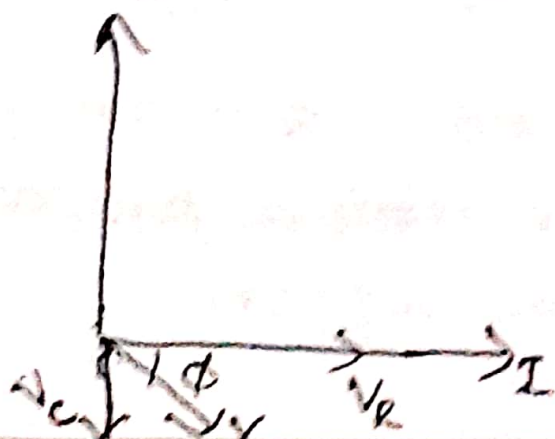


$$P = V_R I$$


$$= VI \cos \phi$$

Power factor is leading
 Bcoz current is leading

* RLC Circuit

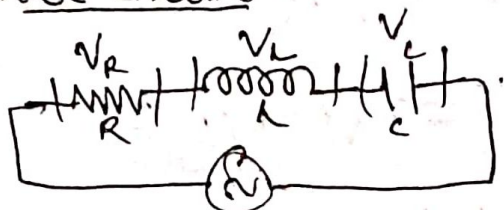

$$V = V_m \sin \omega t$$

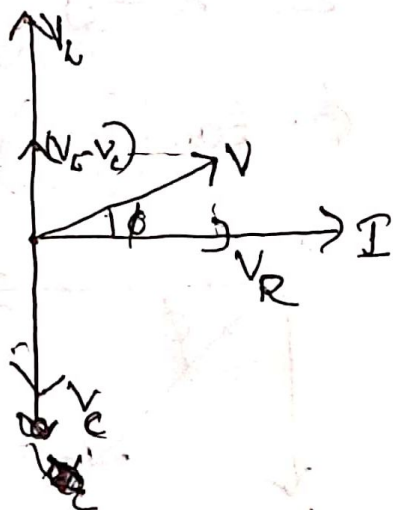

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$= I \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$\phi = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{R} \right)$$

$$Z = |Z| \angle \phi, Z = R + j(\omega L - \frac{1}{\omega C})$$

A resistor of $R = 50 \Omega$ $L = 0.1 H$

are connected in series across a $200V$ $50 Hz$ supply. Find the impedance, power factor, current, active power and reactive power

$$Z = 12 \angle \phi$$

$$\bar{I} = \frac{V_m \sin(\omega t + \phi)}{Z}$$

$$= \frac{V \angle 0^\circ}{12 \angle \phi} = \frac{V}{12} \angle -\phi$$

$$\bar{I} = I_m \sin(\omega t - \phi)$$

* if $X_L > X_C$, current lags the voltage (V) by ϕ

* $X_C > X_L$, current leads the voltage by ϕ

* $P = VI \cos \phi$ - Active power

(Watts) Resistance


* $P = VI \sin \phi$ - Reactive power

(V.A) Reactance

* $P = VI$ is Apparent power

(S) Volt Amp.

$$S = \sqrt{P^2 + Q^2}$$

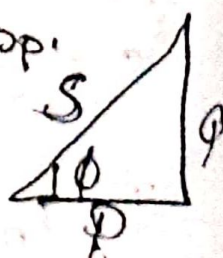

P - active