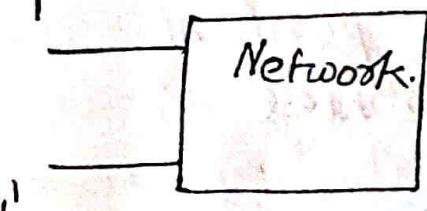


Module 5Two port network

Any n/w may be represented by a rectangular box.




A pair of terminals at which a signal may enter or leave a n/w is called a port.

A port is defined as any pair of terminals into which energy is supplied or from which energy is withdrawn.

N/ws are classified into single port and two port networks.

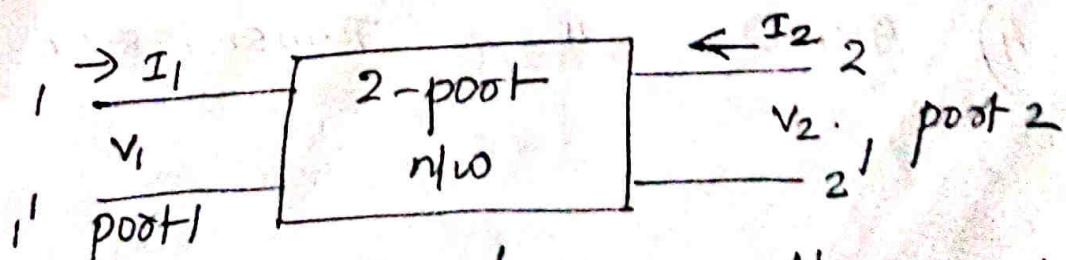A single port n/w has a pair of terminals to which the source is connected ie If the n/w consists of only one port then the n/w is called one port n/w. and if the n/w consists of two port, then it is a two port n/w.



The port 1 is normally connected to the driving source or input and is called

port 2-2' connected to load is called output port.

This building blocks are common in electronic systems, communications systems, transmission & distribution sys.

Each and every two port NW are represented by 4 variables where V_1 and I_1 are the S/p port voltage and current and V_2 & I_2 are the O/p port voltage & current. Two of the 4 variables are independent and another two are dependent.

There are 4 sets of parameters commonly used in the analysis of these networks. The parameters are.

1) Z parameter (open circuit impedance parameters)

2) Y " (short circuit admittance parameters)

3) h " (Hybrid ")

4) ABCD " (Transmission ")

Driving point functions :


- Driving point impedance
- " admittance.

For a 2 port n/w, driving point impedance is defined as the ratio of transform voltage of a port to the transform current at the same port. Denoted as $Z(s)$.

$$Z(s) = \frac{V(s)}{I(s)}$$

Driving point admittance is defined as the ratio of transform ~~voltage~~ ^{current} of a port to the transform ~~voltage~~ voltage at the same port. Denoted as $Y(s)$
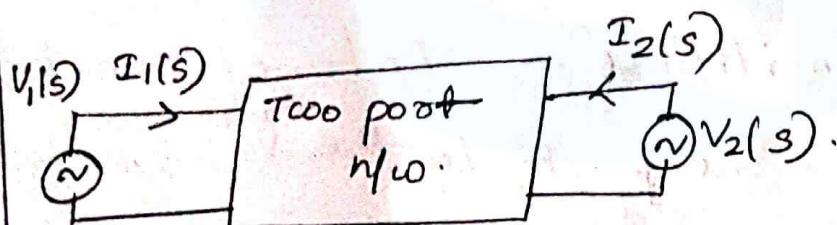
$$Y(s) = \frac{I(s)}{V(s)} = \frac{1}{Z(s)}$$



The driving point impedance at port 1

$$Z_{11}(s) = \frac{V_1(s)}{I_1(s)}$$

$$\text{At port 2, } Z_{22}(s) = \frac{V_2(s)}{I_2(s)}$$

Defining point admittance at post 1

$$Y(s) = Y_{11}(s) = \frac{I_1(s)}{V_1(s)}$$

$$\text{at post 2, } Y_{22}(s) = \frac{I_2(s)}{V_2(s)}$$

Transfer function:

= Ratio of transform n/w response to
transform n/w excitation.

Transfer impedance — Ratio of transform
voltage at one post to the transform
current at another post.

$$Z_{12}(s) = \frac{V_1(s)}{I_2(s)}$$

$$Z_{21}(s) = \frac{V_2(s)}{I_1(s)}$$

Transfer admittance — Ratio of transform
current at one post to the ^{transform} voltage at
another post. $Y(s)$

$$Y_{12}(s) = \frac{I_1(s)}{V_2(s)}$$

$$Y_{21}(s) = \frac{I_2(s)}{V_1(s)}$$

Voltage Transfer ratio = Ratio of transform voltage at one port to the transform voltage at another port.

$$G_{12}(s) = \frac{V_1(s)}{V_2(s)}$$

$$G_{21}(s) = \frac{V_2(s)}{V_1(s)}$$


Current Transfer ratio — ratio of transform current at one port to transform current at another port.

$$\alpha_{12}(s) = \frac{I_1(s)}{I_2(s)}$$

$$\alpha_{21}(s) = \frac{I_2(s)}{I_1(s)}$$

Impedance Parameters.

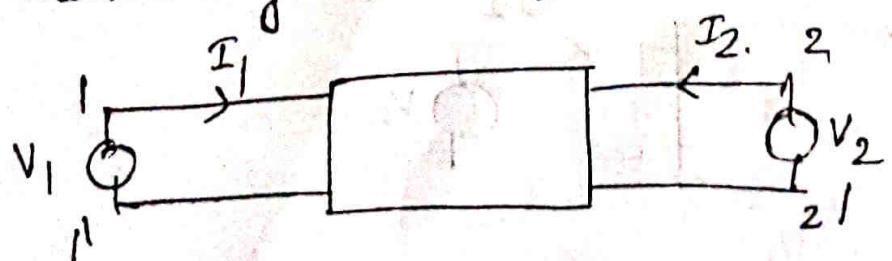4 variables are specified for a 2 port network. If any two are specified, the other two can be determined. The 4 variables are related by the eqns.



Expressing V_1, V_2 in terms of currents I_1, I_2 . $V_1, V_2 \rightarrow$ dependent variables, $I_1, I_2 \rightarrow$ indep.

V_1 is the response produced by 2 currents I_1 & I_2

$$V_1 = I_1 z_{11} + I_2 z_{12}$$


$$V_2 = I_1 z_{21} + I_2 z_{22}$$

$z_{11}, z_{12}, z_{21}, z_{22}$ are called impedance parameters. Unit is Ω . $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$

To find z parameters.

Open circuit port 1 or port 2.

If port 2 is open circled, $I_2 = 0$.

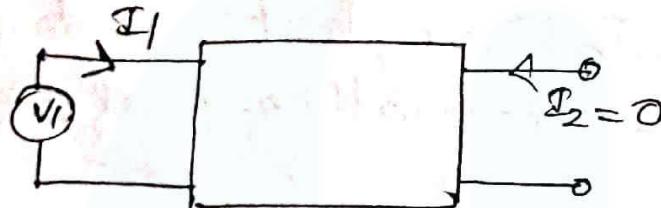

$$V_1 = I_1 z_{11} \Rightarrow z_{11} = \frac{V_1}{I_1} \quad \text{Open circuit I/p impedance}$$

$$V_2 = I_1 z_{21} \Rightarrow z_{21} = \frac{V_2}{I_1} \quad \text{Open circuit transfer impedance.}$$

→ Open circuit transfer impedance.

If port 1 is short-circuited, $I_1 = 0$



$$z_{12} = \frac{V_1}{I_2}, \quad z_{22} = \frac{V_2}{I_2}$$


= OC transfer \Rightarrow Open circuit O/p z .

KtuQbank
Since these eqns are involve os at one port, these parameters are called Open Ckt Impedance parameters or Z parameters.

Z_{11}, Z_{22} = Driving point Impedance,

Z_{12}, Z_{21} = oc transfer impedance.

Admittance Parameters.

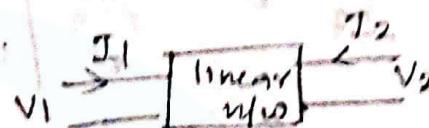

The equations relating the four variables can be written as,

dependent variables

$I_1 = Y_{11}V_1 + Y_{12}V_2$
$I_2 = Y_{21}V_1 + Y_{22}V_2$


Unit is Ω^{-1} .

To find Y parameters.

Impose condition like short circuiting

either point 1 or 2.


Port 2 is shorted i.e. $V_2=0$.

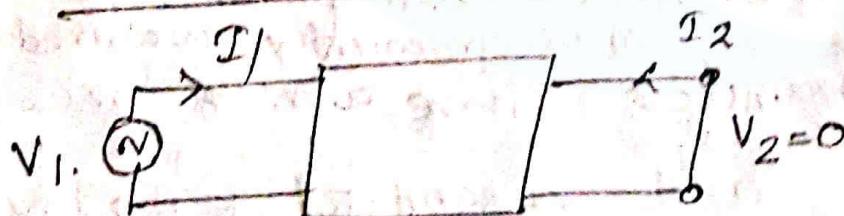

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = 18 \text{ si/p admittance}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = 8 \text{ si transfer admittance}$$

If port 1 is shorted, $V_1 = 0$.

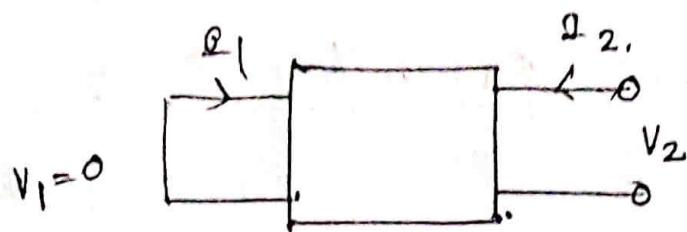

$$Y_{12} = \frac{I_1}{V_2} \Big| V_1=0 = 8c \text{ transfer admittance}$$

$$Y_{22} = \frac{I_2}{V_2} \Big| V_1=0 = 8c \text{ o/p admittance.}$$

Also called 8c Admittance parameters, as it involves a SC at one port.

$$Y_{11}, Y_{22} = 8c \text{ Driving point admittance}$$

$$Y_{12}, Y_{21} = II \text{ transfer }$$

Hybrid Parameters. (h)

Here the voltage of one port and current of other port are taken as the independent variables.

- used in the analysis of transistor networks; ie because these parameters can be conveniently measured.
- the parameters have a mixture of units as Ω and A . So the name hybrid.

If the voltage at 1-1' and I at 2-2' are taken as dependent variables.


$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

To find h parameters.

Impose both short ckt and open ckt condition.

If port 2 is short ckted, $V_2 = 0$

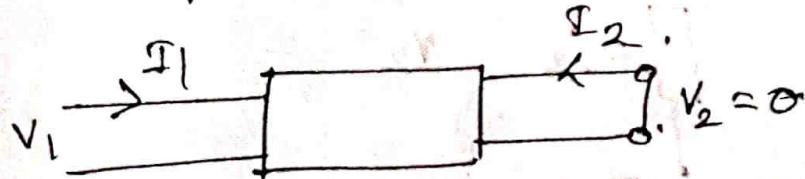


$$V_1 = h_{11} I_1, \quad h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \rightarrow \text{sc s/p Z}$$

$$I_2 = h_{21} I_1, \quad h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} \rightarrow \text{sc}$$

forward
current
ratio.

If port 1 is open ckted, $I_1 = 0$

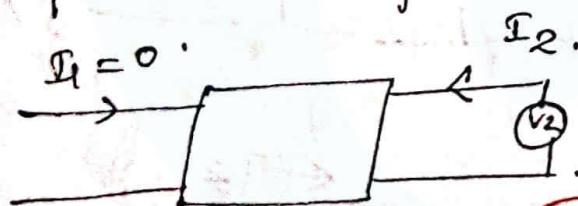

$$V_1 = h_{12} V_2, \quad h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \rightarrow \text{oc reverse voltage ratio.}$$




$$I_2 = h_{22} V_2, \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} \rightarrow \text{oc o/p}$$

mho \leftarrow admittance

h_{12}, h_{21} = voltage transfer ratio
— current transfer ratio

$h_{12}, h_{21} \rightarrow \text{dimensionless.}$

Equivalent GfL

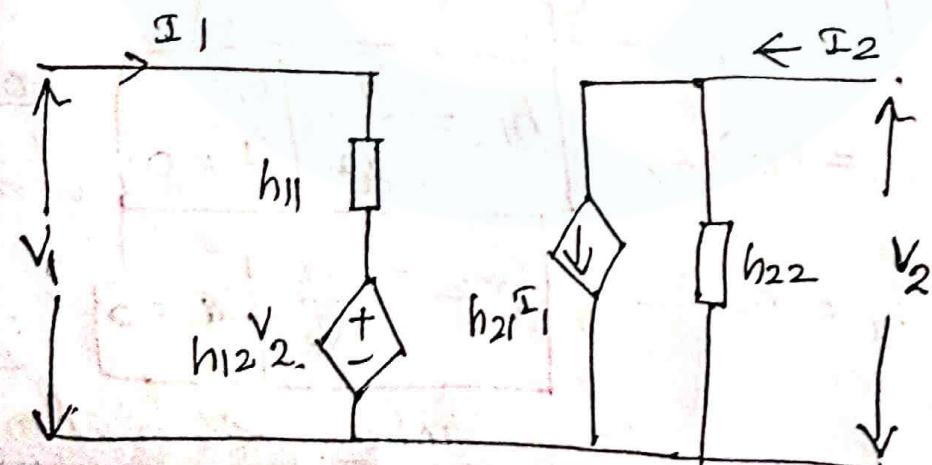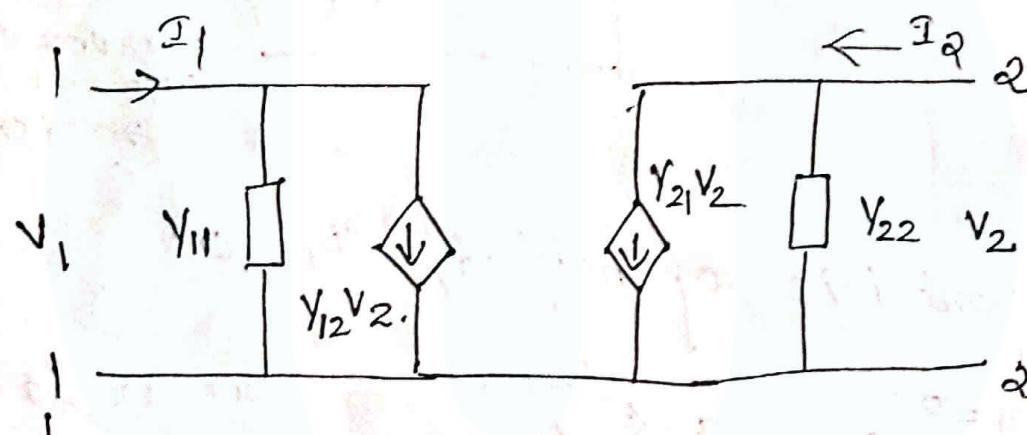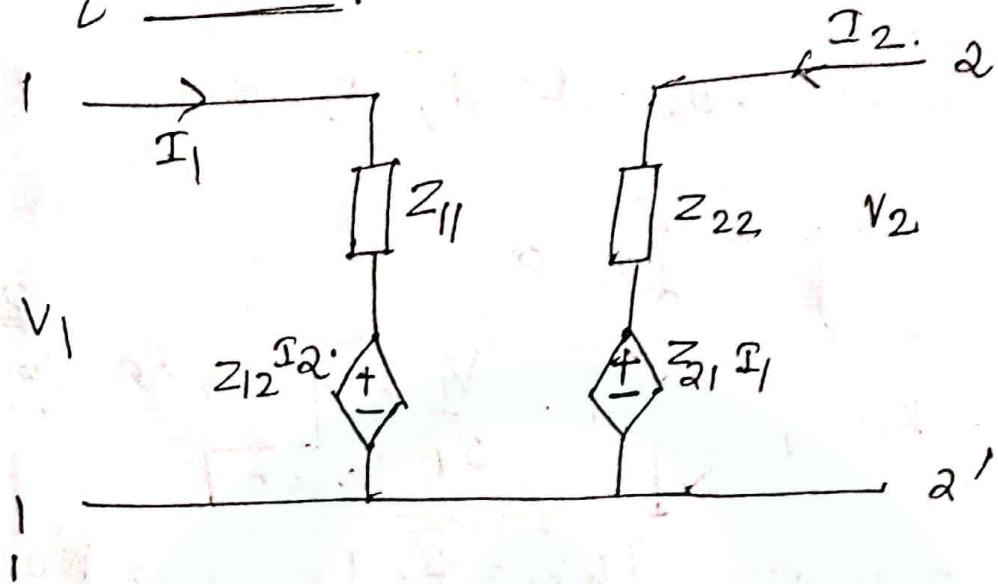

Transmission Parameters. (ABCD) (Chain) (Generator)

- commonly used in transmission line at receiving end.

- V_1, I_1 at port 1-1 as sending end are expressed in terms of V_2, I_2 - receiving end.

- cascade networks.

Expresses voltage & current at one port in terms of voltage & current at point 2. They are defined by

$$V_1 = AV_2 - BI_2, \quad I_1 = CV_2 - DI_2$$

A, B, C, D are transmission parameters.

Negative sign for I_2 is that I_2 is in a dir oppo to that of conventional current direction.

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

To find ABCD.

Both short circuit & open circuit on port 2.

Open circuiting port 2, applying v_1 at 1-1, $I_2=0$



$$V_1 = AV_2$$

$$A = \frac{V_1}{V_2} \mid I_2=0$$

= OC reverse:

voltage ratio

(voltage transfer ratio)

= OC transfer

admittance.

$$C = \frac{I_1}{V_2} \mid I_2=0$$

Short circuiting port 2, $V_2=0$ applying v_1 at 1-1.



$$B = \left| \frac{V_1}{I_2} \right|_{V_2=0} = 8c \text{ transfer impedance}$$

$$D = \left| -\frac{I_1}{I_2} \right|_{V_2=0} = 8c \text{ reverse current ratio.}$$

= current transfer ratio.

Dimensionless - A & D.

C - OC admittance parameter - Y

B - 8c impedance " - Ω

Condition for Reciprocity & Symmetry.

A 2port n/w is said to be reciprocal, if the ratio of the transform n/w response to the transform n/w excitation is constant to an interchange of the positions of the excitation and the response in the n/w.

A 2port n/w is said to be symmetric, if the ports can be interchanged without changing the port voltages & currents.

\mathbf{Z}

$$z_{12} = z_{21}$$

$$z_{11} = z_{22}$$

 \mathbf{Y}

$$y_{12} = y_{21}$$

$$y_{11} = y_{22}$$

 \mathbf{h}

$$h_{12} = h_{21}$$


$$h_{11} h_{22} - h_{12} h_{21} = 1$$

 \mathbf{ABCD}

$$AD - BC = 1$$


$$A = D$$

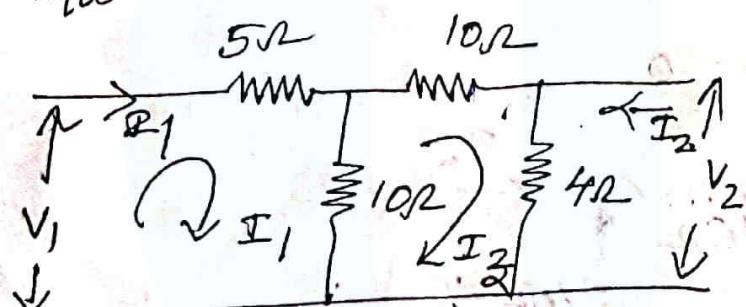- ① Find the \mathbf{Z} parameter of the following network.



Opening port 2.

$$Z_{11} = \frac{V_1}{I_1} \quad | \quad I_2 = 0$$

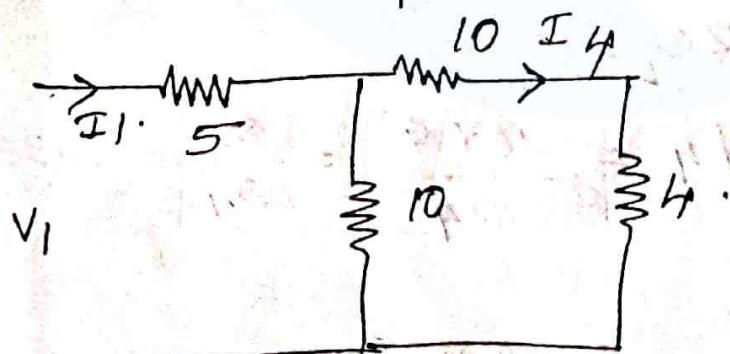

$$V_1 = I_1 Z_{eq}$$

$$\begin{aligned} Z_{eq} &= 14 / (10 + 5) \\ &= \frac{14 \times 10}{24} + 5 \\ &= \underline{\underline{10.8}} \end{aligned}$$

$$\frac{V_1}{I_1} = Z_{11} = \underline{\underline{10.8\Omega}}$$

$$Z_{21} = \frac{V_2}{I_1} \left| \begin{array}{l} I_2 = 0 \\ V_1 = I_1 Z_{11} + \frac{1}{2} Z_{12} \end{array} \right. . \quad \left| \begin{array}{l} V_2 = I_1 Z_{21} + I_2 Z_{22} \\ \dots \end{array} \right.$$

$$V_2 = V_{4\Omega \text{ in}} = 4 \times I_4$$


$$I_4 = \frac{I_1 \times 10}{10 + 10 + 4}$$

$$= I_1 \times \frac{10}{24}$$

$$V_2 = I_1 \times \frac{10}{24} \times 4 = \frac{10}{6} I_1$$

$$\frac{V_2}{I_1} = Z_{21} = \frac{10}{6} = \frac{5}{3} \Omega = \underline{1.67 \Omega}$$

O.C port 1, $I_1 = 0$

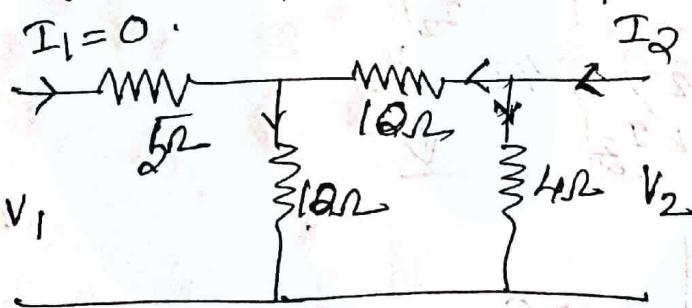

$$V_2 = I_2 Z_{eq}$$

$$Z_{eq} \Rightarrow 20//4 = \frac{20 \times 4}{24} = \frac{80}{24} = 3.33 \Omega$$

$$Z_{22} = \frac{V_2}{I_2}$$

$$V_1 = I_1 \times 5 + I_1 \times 10 \Omega$$

$$= 10 \times I_{10}$$

$$Z_{22} = \frac{V_2}{I_2}$$

$$I_{10} = \frac{I_2 \times 4}{10 + 10 + 4}$$

$$V_1 = 10 \times \frac{I_2 \times 4}{10 + 10 + 4} = \frac{40}{24} I_2$$

$$\frac{V_1}{I_2} = \frac{40}{24} = \underline{1.67 \Omega}$$

Relationship b/n Parameter

① Σ in terms of γ

γ parameter eqns are

$$I_1 = \gamma_{11}V_1 + \gamma_{12}V_2 \quad \text{--- (b)}$$

$$I_2 = \gamma_{21}V_1 + \gamma_{22}V_2.$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \gamma_{11} & \gamma_{12} \\ \gamma_{21} & \gamma_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$V_1 = I_1 z_{11} + I_2 z_{12}$$

$$V_2 = I_1 z_{21} + I_2 z_{22}$$


--- (a)

Solving for V_1 & V_2 , using Cramer's rule.

$$V_1 = \frac{\begin{vmatrix} I_1 & \gamma_{12} \\ I_2 & \gamma_{22} \end{vmatrix}}{\begin{vmatrix} \gamma_{11} & \gamma_{12} \\ \gamma_{21} & \gamma_{22} \end{vmatrix}} = \frac{\gamma_{22} I_1 - \gamma_{12} I_2}{\gamma_{11} \gamma_{22} - \gamma_{21} \gamma_{12}}$$

$$= \frac{\gamma_{22}}{\Delta \gamma} I_1 - \frac{\gamma_{12}}{\Delta \gamma} I_2 \quad \left| \begin{array}{l} \cancel{\gamma_{11} \gamma_{22} - \gamma_{21} \gamma_{12}} \\ \cancel{\gamma_{11} \gamma_{22} - \gamma_{21} \gamma_{12}} \end{array} \right.$$
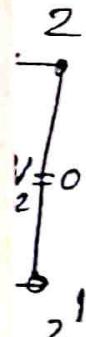
$$V_2 = \frac{\gamma_{11}}{\Delta \gamma} I_2 - \frac{\gamma_{21}}{\Delta \gamma} I_1$$



Comparing these eqns with eqn (a).

$$z_{11} = \frac{\gamma_{22}}{\Delta \gamma}, z_{12} = -\frac{\gamma_{12}}{\Delta \gamma}$$

$$z_{21} = -\frac{\gamma_{21}}{\Delta \gamma}, z_{22} = \frac{\gamma_{11}}{\Delta \gamma}$$

$$\Delta \gamma = \underline{\underline{\gamma_{11} \gamma_{22} - \gamma_{12} \gamma_{21}}}$$

② Forms of ABCD.

$$I_1 = CV_2 - DI_2, \quad V_1 = AV_2 - BI_2.$$

$$V_2 = \frac{I_1 + DI_2}{C} = \frac{1}{C} I_1 + \frac{D}{C} I_2.$$

$$V_1 = A\left(\frac{1}{C} I_1 + \frac{D}{C} I_2\right) - BI_2.$$

$$= \frac{A}{C} I_1 + \frac{AD}{C} I_2 - BI_2.$$

$$= \frac{A}{C} I_1 + \frac{AD - BC}{C} I_2.$$

Comparing with std eqn of Z parameters,

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$$\boxed{\begin{aligned} z_{11} &= \frac{A}{C}, & z_{12} &= \frac{AD - BC}{C} \\ z_{21} &= \frac{1}{C}, & z_{22} &= \frac{D}{C}. \end{aligned}}$$

③ Forms of h parameters.

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2. \quad \text{--- (2)}$$

$$\Rightarrow V_2 = \frac{I_2 - h_{21} I_1}{h_{22}} = \frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1.$$

$$= -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2.$$

$$V_1 = h_{11} I_1 + h_{12} \left[-\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \right]$$

$$\begin{aligned}
 &= b_{11} I_1 + b_{12} \frac{(b_{21})}{b_{22}} I_1 + \frac{b_{12}}{b_{22}} I_2 \\
 &= \frac{b_{11}b_{22} - b_{12}b_{21}}{b_{22}} I_1 + \frac{b_{12}}{b_{22}} I_2 \\
 &= \frac{\Delta b}{b_{22}} I_1 + \frac{b_{12}}{b_{22}} I_2.
 \end{aligned}$$

Comparing with std eqns.

$$\boxed{
 \begin{aligned}
 z_{11} &= \frac{\Delta b}{b_{22}}, & z_{12} &= \frac{b_{12}}{b_{22}} \\
 z_{21} &= -\frac{b_{21}}{b_{22}}, & z_{22} &= \frac{1}{b_{22}}
 \end{aligned}
 }$$

④ Yparameters of Interns of Z parameter

$$Y = \frac{1}{Z}$$


$$[I] = [Y] [V] \Leftrightarrow [Y] [I] [Z]$$

$$[Y] = [Z]^{-1}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}^{-1}$$

$$Y_{11} = \frac{z_{22}}{z_{11}z_{22} - z_{12}z_{21}}, \quad Y_{12} = -\frac{z_{12}}{\Delta Z}$$
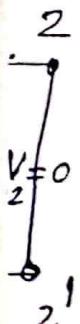
$$Y_{21} = -\frac{z_{21}}{\Delta Z}, \quad Y_{22} = \frac{z_{11}}{\Delta Z}$$



$$\frac{V_2}{Z}$$

5) Interrme of ABCD

$$V_1 = AV_2 - BI_2$$

$$\Rightarrow I_2 = \frac{AV_2 - V_1}{B} = \left(-\frac{1}{B}\right)V_1 + \frac{A}{B}V_2.$$

$$I_1 = CV_2 - DI_2$$

$$= CV_2 - D\left[\left(-\frac{1}{B}\right)V_1 + \frac{A}{B}V_2\right]$$

$$= CV_2 + \frac{D}{B}V_1 - \frac{AD}{B}V_2.$$

$$= \frac{BC - AD}{B}V_2 + \frac{D}{B}V_1$$

$$I_1 = \frac{D}{B}V_1 - \frac{(AD - BC)}{B}V_2.$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

Comparing,

$$Y_{11} = \frac{D}{B}, \quad Y_{12} = \frac{AD - BC}{B}$$

$$Y_{21} = -\frac{1}{B}, \quad Y_{22} = \frac{A}{B}$$

6) Interrme of h parameter.

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$\Rightarrow I_1 = \frac{V_1 - h_{12}V_2}{h_{11}} = \frac{1}{h_{11}}V_1 - \frac{h_{12}}{h_{11}}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$= h_{21}\left[\frac{1}{h_{11}}V_1 - \frac{h_{12}}{h_{11}}V_2\right] + h_{22}V_2$$

$$\begin{aligned}
 &= \frac{h_{21}}{h_{11}} v_1 - \frac{h_{21}h_{12}}{h_{11}} v_2 + h_{22} v_2 \\
 &= \frac{h_{21}}{h_{11}} v_1 - \frac{h_{21}h_{12}}{h_{11}} v_2 + h_{11}h_{22} v_2 \\
 &= \frac{h_{21}}{h_{11}} v_1 + v_2 \left[\frac{h_{11}h_{22} - h_{12}h_{21}}{h_{11}} \right]
 \end{aligned}$$

Comparing ,

$$\begin{cases}
 Y_{11} = \frac{1}{Y_{11}}, \quad Y_{12} = -\frac{h_{12}}{h_{11}} \\
 Y_{21} = \frac{h_{21}}{h_{11}}, \quad Y_{22} = \frac{h_{11}h_{22} - h_{12}h_{21}}{h_{11}}
 \end{cases}$$

ABCD parameters - in terms of Z parameter

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

∴

$$\begin{cases}
 V_2 = A V_1 + B I_2 \\
 I_1 = C V_2 + D I_2
 \end{cases} \quad | A$$

$$\begin{aligned}
 I_1 &= \frac{V_2 - Z_{22} I_2}{Z_{21}} \\
 &= \frac{1}{Z_{21}} V_2 - \frac{Z_{22}}{Z_{21}} I_2
 \end{aligned}$$

$$V_1 = Z_{11} \left[\frac{1}{Z_{21}} V_2 - \frac{Z_{22}}{Z_{21}} I_2 \right] + Z_{12} I_2.$$

$$= \left(\frac{Z_{11}}{Z_{21}} \right) V_2 - I_2 \left[\frac{Z_{22} Z_{11} - Z_{12} Z_{21}}{Z_{21}} \right].$$

Comparing with eqns (A),

$$A = \frac{z_{11}}{z_{21}}, \quad B = \frac{z_{22}z_{11} - z_{12}z_{21}}{z_{21}}$$

$$C = \frac{1}{z_{21}}, \quad D = \frac{z_{22}}{z_{21}}$$

In terms of Y parameters.

$$\begin{array}{l|l} I_2 = Y_{21}V_1 + Y_{22}V_2 & V_1 = AV_2 - BI_2 \\ I_1 = Y_{11}V_1 + Y_{12}V_2 & I_1 = CV_2 - DI_2 \end{array}$$

$$\Rightarrow V_1 = \frac{I_2 - Y_{22}V_2}{Y_{21}}$$

$$= \frac{1}{Y_{21}} I_2 - \frac{Y_{22}}{Y_{21}} V_2 = V_2 \left(-\frac{Y_{22}}{Y_{21}} \right) - I_2 \left(\frac{1}{Y_{21}} \right)$$

$$I_1 = Y_{11} \left[\frac{1}{Y_{21}} I_2 - \frac{Y_{22}}{Y_{21}} V_2 \right] + Y_{12}V_2.$$

$$= \frac{Y_{11}}{Y_{21}} I_2 - \frac{Y_{11} Y_{22}}{Y_{21}} V_2 + Y_{12}V_2$$

$$= I_2 \frac{Y_{11}}{Y_{21}} - V_2 \left[\frac{Y_{11} Y_{22}}{Y_{21}} - \frac{Y_{12} Y_{21}}{Y_{21}} \right]$$

Comparing with the eqns,

$$A = -\frac{Y_{22}}{Y_{21}}, \quad B = -\frac{1}{Y_{21}}$$

$$C = -\left(\frac{Y_{11} Y_{22}}{Y_{21}} - \frac{Y_{12} Y_{21}}{Y_{21}} \right)$$

$$D = -\frac{Y_{11}}{\underline{Y_{21}}}.$$

Integers of h parameters.

$$I_2 = h_{21} I_1 + h_{22} V_2.$$

$$I_1 = \frac{I_2 - h_{22} V_2}{h_{21}} = \frac{1}{h_{21}} I_2 - \frac{h_{22}}{h_{21}} V_2$$

$$V_1 = h_{11} I_1 + h_{12} V_2 = h_{11} \left[\frac{1}{h_{21}} I_2 - \frac{h_{22}}{h_{21}} V_2 \right] + h_{12} V_2.$$

$$= \frac{h_{11}}{h_{21}} I_2 - \frac{h_{11} h_{22}}{h_{21}} V_2 + h_{12} V_2.$$

$$= \frac{h_{11} I_2 - h_{11} h_{22} V_2 + h_{12} h_{21} V_2}{h_{21}}$$

$$= I_2 \left[\frac{h_{11}}{h_{21}} \right] - V_2 \left[\frac{h_{11} h_{22}}{h_{21}} + \frac{h_{12} h_{21}}{h_{21}} \right]$$

$$V_1 = A V_2 - B I_2, \quad I_1 = C V_2 - D I_2.$$

$$V_1 = V_2 \left[-\frac{(h_{11} h_{22} - h_{12} h_{21})}{h_{21}} \right] + \left(-\frac{h_{11}}{h_{21}} \right) - I_2.$$

$$A = -\frac{(h_{11} h_{22} - h_{12} h_{21})}{h_{21}}, \quad B = -\frac{h_{11}}{h_{21}}$$

$$C = -\frac{\underline{h_{22}}}{\underline{h_{21}}} , \quad D = -\frac{1}{\underline{h_{21}}} ,$$

② Find the Y parameter.

h parameter in terms of z parameters.

$$V_1 = I_1 Z_{11} + I_2 Z_{12} \quad V_1 = h_{11} I_1 + h_{12} V_2$$

$$V_2 = I_1 Z_{21} + I_2 Z_{22} \quad I_2 = h_{21} I_1 + h_{22} V_2$$

$$\begin{aligned} I_2 &= \frac{V_2 - I_1 Z_{21}}{Z_{22}} \\ &= \frac{1}{Z_{22}} V_2 - \frac{Z_{21}}{Z_{22}} I_1 \end{aligned}$$

K.

$$V_1 = Z_{11} I_1 + Z_{12} \left[\frac{V_2}{Z_{22}} - \frac{Z_{21}}{Z_{22}} I_1 \right]$$

$$V_1 = I_1 \left[Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22}} \right] + V_2 \frac{Z_{12}}{Z_{22}}$$

$$I_2 = \frac{1}{Z_{22}} V_2 - \frac{Z_{21}}{Z_{22}} I_1$$

$$h_{11} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}}, \quad h_{12} = \frac{Z_{12}}{Z_{22}} = 0$$

$$h_{21} = -\frac{Z_{21}}{Z_{22}}, \quad h_{22} = 1/Z_{22}$$

In terms of γ parameters.

$$I_1 = \gamma_{11} V_1 + \gamma_{12} V_2$$

$$\Rightarrow V_1 = \frac{I_1 - \gamma_{12} V_2}{\gamma_{11}} \quad \text{--- (1)}$$

$$I_2 = \gamma_{21} V_1 + \gamma_{22} V_2$$

$$= \gamma_{21} \left[\frac{I_1 - \gamma_{12} V_2}{\gamma_{11}} \right] + \gamma_{22} V_2$$

$$= I_1 \cdot \frac{\gamma_{21}}{\gamma_{11}} - \frac{\gamma_{21} \gamma_{12}}{\gamma_{11}} V_2 + \gamma_{22} V_2$$

Comparing,

$$h_{11} = \frac{1}{\gamma_{11}}, \quad h_{12} = -\frac{\gamma_{12}}{\gamma_{11}}$$

$$h_{21} = \frac{\gamma_{21}}{\gamma_{11}}, \quad h_{22} = \frac{\gamma_{11} \gamma_{22} - \gamma_{12} \gamma_{21}}{\gamma_{11}} + 1$$

Integrating ABCD.

$$I_1 = CV_2 - DI_2 \Rightarrow I_2 = \frac{CV_2 - I_1}{D}$$

$$V_1 = AV_2 - BI_2 \Rightarrow V_1 = AV_2 - B \left[\frac{CV_2 - I_1}{D} \right]$$

$$= AV_2 - \frac{BCV_2}{D} + I_1 \frac{B}{D}$$

$$= V_2 \left(\frac{AD - BC}{D} \right) + I_1 \cdot \frac{B}{D}$$

Comparing,

$$h_{11} = \frac{B}{D}, \quad h_{12} = \frac{AD - BC}{D},$$

$$h_{21} = -\frac{1}{D}, \quad h_{22} = \frac{C}{D}.$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = \text{sc transfer impedance}$$

$$D = \left. -\frac{I_1}{I_2} \right|_{V_2=0} = \text{sc reverse current ratio.}$$

= current transfer ratio.

Dimensionless - A & D

C - sc admittance parameter - ω


B - sc impedance " - ωR

Condition for Reciprocity & Symmetry.

A 2port n/w is said to be reciprocal, if the ratio of the feedfrom n/w response to the transform n/w excitation is constant to an interchange of the position of the excitation and the response in the n/w.

A 2port n/w is said to be symmetric, if the ports can be interchanged without changing the port voltages & currents.

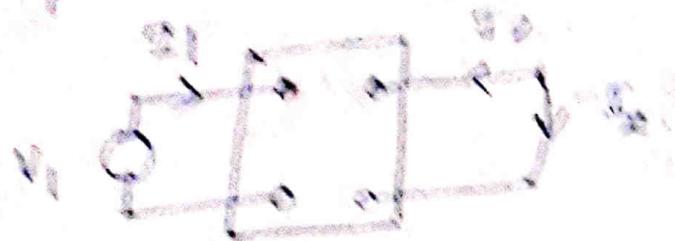Requirements to parameter can be separated. Here two port nodes can be separated as:



s_2 is assumed to be
in positive direction
of I_2 around.

$$\begin{aligned} V_1 &= Z_{11} S_1 + Z_{12} I_2 \quad \rightarrow \quad V_1 = Z_{11} S_1 - Z_{12} I_2 \\ V_2 &= Z_{21} S_1 + Z_{22} S_3 \quad \rightarrow \quad 0 = Z_{21} S_1 - Z_{22} S_3 \end{aligned}$$

(V_2 is zero as o/p is shorted)

$$\rightarrow I_2 = \frac{Z_{11} S_1 - V_1}{Z_{12}} \quad , \quad Z_{21} S_1 = Z_{22} S_3 \\ S_1 = \frac{Z_{22} S_3}{Z_{21}}$$


$$= -V_1 + Z_{11} \frac{Z_{22} S_3}{Z_{21}} \quad , \quad -V_1 \frac{Z_{21} + Z_{11} Z_{22} S_3}{Z_{21} Z_{12}}$$

$$I_2 Z_{21} Z_{12} = -V_1 Z_{21} + I_2 Z_{11} Z_{22}$$

$$I_2 [Z_{12} Z_{21} - Z_{11} Z_{22}] = -V_1 Z_{21}$$

$$I_2 = \frac{V_1 Z_{21}}{Z_{11} Z_{22} - Z_{12} Z_{21}}$$

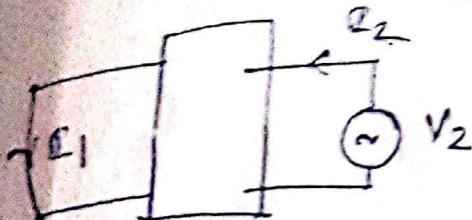Interchange the o/p & i/p voltage
of currents,



Governing eqns are

$$0 = I_1 Z_{11} + I_2 Z_{12}$$

$$V_2 = -Z_{21} I_1 + Z_{22} I_2.$$

Solving, $I_1 = \frac{V_2 Z_{12}}{Z_{11} Z_{22} - Z_{12} Z_{21}}$

Assuming $V_1 = V_2$, and comparing I_1 , $\underline{I_2}$
 $\underline{Z_{12} = Z_{21}}$.

Symmetry

Applying voltage V at o/p post and keeping the o/p post open.

$$V_1 = I_1 Z_{11}, \quad Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

Applying voltage V at o/p post and keeping open circuit at i/p post

$$V_2 = I_2 Z_{22}, \quad \underline{Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}}$$

Symmetry is when $\frac{V}{I_1} = \frac{V}{I_2}$ leads to

the condition,

$$\underline{\underline{Z_{11} = Z_{22}}}$$

In Y parameter

$$\boxed{\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned}}$$

Shorting o/p, $V_2 = 0$

$$I_1 = Y_{11}V_1, \quad I_2 = -Y_{21}V_1, \quad \text{-ve sign}$$

Indicates the diode is outward of
the node.

$$Y_{21} = -\frac{I_2}{V_1}, \quad \text{--- (a)}$$

(With interchanging of response
excitation)

$V_1 = 0$, I_1 is flowing, outward.

$$-I_1 = Y_{12}V_2, \quad Y_{12} = -\frac{I_1}{V_2}. \quad \text{--- (b)}$$

If $V_1 = V_2$, LHS of eqns (a) & (b)
will be identical, provided the ckt is
reciprocal.

$Y_{21} = Y_{12}$, the ckt will be
reciprocal.

For symmetrical h/ω, $Y_{11} = Y_{22}$,
This is possible if $Y_{11} = Y_{22}$,

Y parameter will be symmetric

If the s/p & o/p ports can be interchanged
without changing the voltage or current
at each port.

In ABCD parameter

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Shunting the o/p port and V_1 at s/p port,

$$V_2 = 0$$

$$V_1 = -BI_2, \quad \frac{I_2}{V_1} = -\frac{1}{B}. \quad \text{--- (1)}$$

With interchange of excitation & response,
the voltage source V_2 is at the s/p port
 I_1 is the sc current at the s/p port.

$$0 = AV_2 - BI_2, \quad I_1 = CV_2 - DI_2 -$$

$$\Rightarrow I_2 = \frac{A}{B} V_2, \quad I_1 = CV_2 - \frac{ADV_2}{B}. \\ = V_2 \left(\frac{BC - AD}{B} \right).$$

$$\Rightarrow \frac{I_1}{V_2} = \frac{BC - AD}{B} = \frac{(AD - BC)}{B} \quad \text{--- (2)}$$

When $V_1 = V_2$, LHS of eqns will be identical, provided $AD - BC = 1$.

Condition for reciprocity is,

$$\boxed{AD - BC = 1}$$

$$\text{For symmetry, } Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{AV_2 - BI_2}{CV_2 - DI_2}$$

$$= \frac{A}{C} \mid I_2 = 0.$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_p=0} = \cancel{\frac{D}{C}} \underline{\underline{\frac{D}{C}}}$$

$$\begin{cases} I_1 = 0 = CV_2 - DI_2, \\ I_p \end{cases}, V_2 = \frac{DI_2}{C}, \frac{V_2}{I_2} = \frac{D}{C}] .$$

For z parameter, $Z_{11} = Z_{22}$ to be symmetrical.

$$\therefore \boxed{Z_{11} = Z_{22}}, \boxed{\frac{A}{C} = \frac{D}{C}}, \boxed{A = D}$$

In h parameter.

$$\boxed{V_1 = h_{11} I_1 + h_{12} V_2}$$

$$\text{with } V_2 = 0, V_1 = h_{11} I_1, h_{11} = \frac{V_1}{I_1} \quad \text{--- (1)}$$

$$\boxed{I_2 = h_{21} I_1 + h_{22} V_2}$$

$$V_2 = 0, \Rightarrow -I_2 = h_{21} I_1. \quad \text{--- (2)}$$

$$\frac{(2)}{(1)} \Rightarrow \frac{h_{21}}{h_{11}} = -\frac{I_2}{V_1}$$

Interchanging the excitation & response
 V_2 is applied at op post, s/p terminals
 are shorted, I_1 is reversed

$$0 = -h_{11} I_1 + h_{12} V_2.$$

$$\Rightarrow \frac{I_1}{V_2} = \frac{h_{12}}{h_{11}}.$$

Assume $V_1 = V_2$,

LHS will be same, provided $b_{21} = -b_{12}$
 This is the condition for reciprocity.

For symmetry

O/p is shorted, $I_2 = 0$

$$Z_{11} = \frac{V_1}{I_1} = \frac{h_{11} I_1 + h_{12} V_2}{I_1} = h_{11} + h_{12} \frac{V_2}{I_1}.$$

$$I_2 = h_{21} I_1 + h_{22} V_2. \quad = h_{11} - h_{12} \frac{h_{21}}{h_{22}}$$

$$\Rightarrow \frac{V_2}{I_1} = -\frac{h_{21}}{h_{22}}$$

$$\boxed{Z_{11} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} = \frac{\Delta h}{h_{22}} = Z_{11}}$$

Taking $\Phi_1 = 0$,

$$Z_{22} = \frac{V_2}{I_2} = \frac{V_2}{h_{22} V_2} = \frac{1}{h_{22}}.$$

$$I_2 = h_{21} \Phi_1 + h_{22} V_2$$

$$I_2 = h_{22} V_2$$

If $\Delta h = 1$, $Z_{11} = Z_{22}$, this leads
 to condition of symmetry.

$$\text{i.e. } \underline{h_{11} h_{22} - h_{12} h_{21} = 1}.$$