

MODULE-IV

THREE PHASE NETWORKS AND RESONANCE

Series Resonance

Principle of resonance is used in the application of radio receiver. If we consider a series RLC ckt, what current can lag behind or lead. It depends on the value of X_L or X_C . If we consider inductive reactance the current lags behind the supply voltage. If we consider the capacitive reactance the current leads the supply voltage.


$X_L > X_C$: inductive ckt

$X_C > X_L$: capacitive ckt

A ckt containing reactance is said to be in resonance if the vltg across the ckt is in phase with the current through it.

At resonance, ckt is purely resistive & the net reactance is zero ($X_L = X_C$)

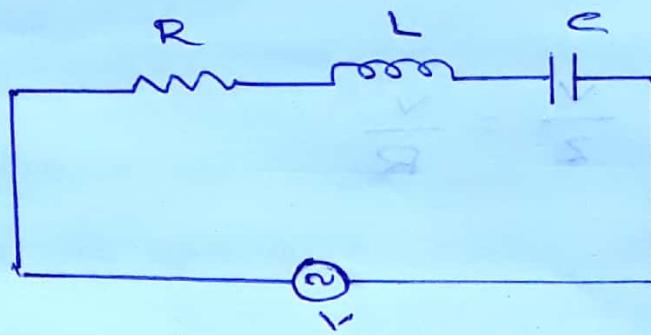The frequency at which the resonance occurs is called the resonant frequency.



$$\bar{Z} = R + jX_L - jX_C$$

$$= R + j\omega L - \frac{j}{\omega C}$$

$$= R + j(\omega L - \frac{1}{\omega C})$$

At resonance, Z is purely resistive.

Therefore condition for resonance is

$$\omega L - \frac{1}{\omega C} = 0$$

$$\omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Power Factor

$$\cos \phi = \frac{R}{Z} = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

But at resonance $\omega L = \frac{1}{\omega C}$

$$\cos \phi = \frac{R}{Z} = 1$$

Current

$$I_0 = \frac{V}{Z} = \frac{V}{R}$$

Voltage

At resonance

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\omega_0 L I_0 = \frac{I_0}{(\frac{1}{\omega_0 C} + R)}$$


$$V_{L_0} = V_{C_0}$$

Properties Of Resonance of RLC Series Ckt

- The applied vltg and the resulting current are inphase which also mean that the pf of RLC series ckt is unity.
- The net reactance is zero at resonance and the impedance does have the resistive part only.
- The current in the ckt is maximum.
- At resonance, the ckt has got minimum impedance and maximum admittance.
- Frequency of resonance is $f_0 = \frac{1}{2\pi\sqrt{LC}}$


Behaviour of R, L, C with change in frequency

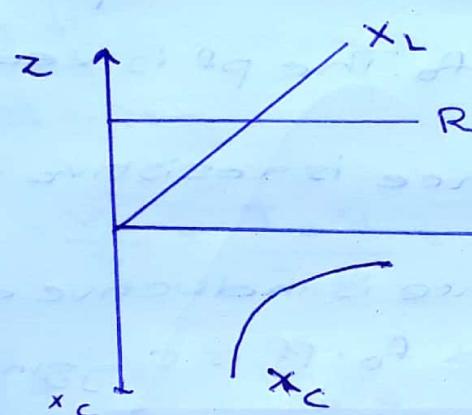
- Resistance remain constant with the change in frequencies.
- Inductive reactance X_L is directly proportional to f .
- Capacitive reactance X_C is inversely proportional to f .



Impedance v/s Frequency

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

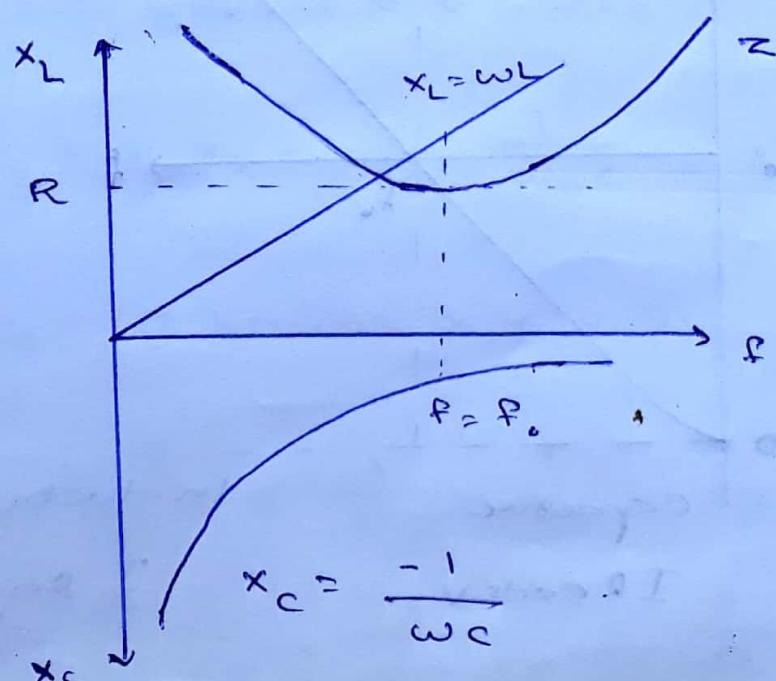

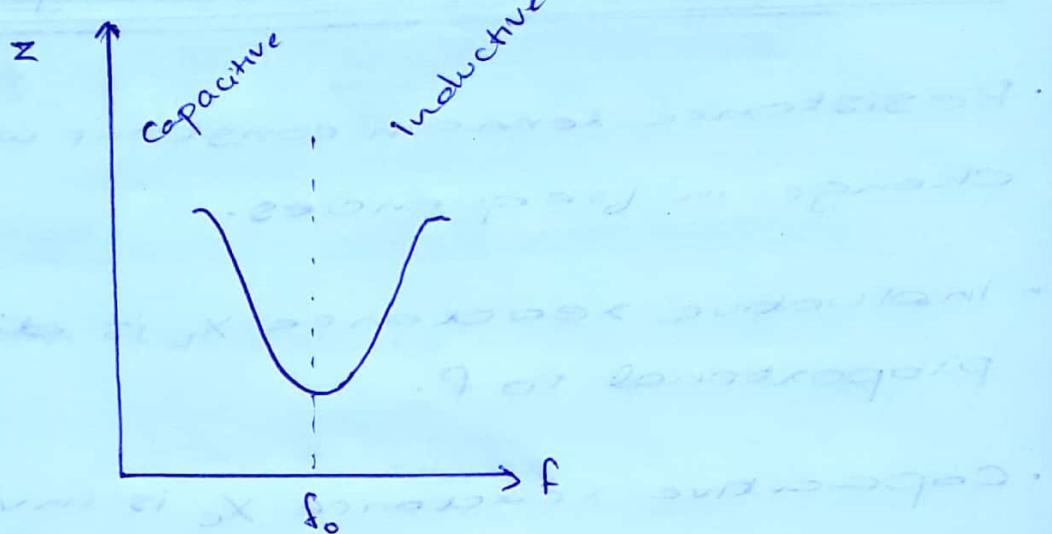


When $f < f_0$, impedance is capacitive and decreases up to f_0 . The pf is lagging.

At $f = f_0$ impedance is resistive. Pf is unity.

When $f > f_0$, impedance is inductive and goes on increasing beyond f_0 . Pf is leading.

Phase Angle v/s Frequency.

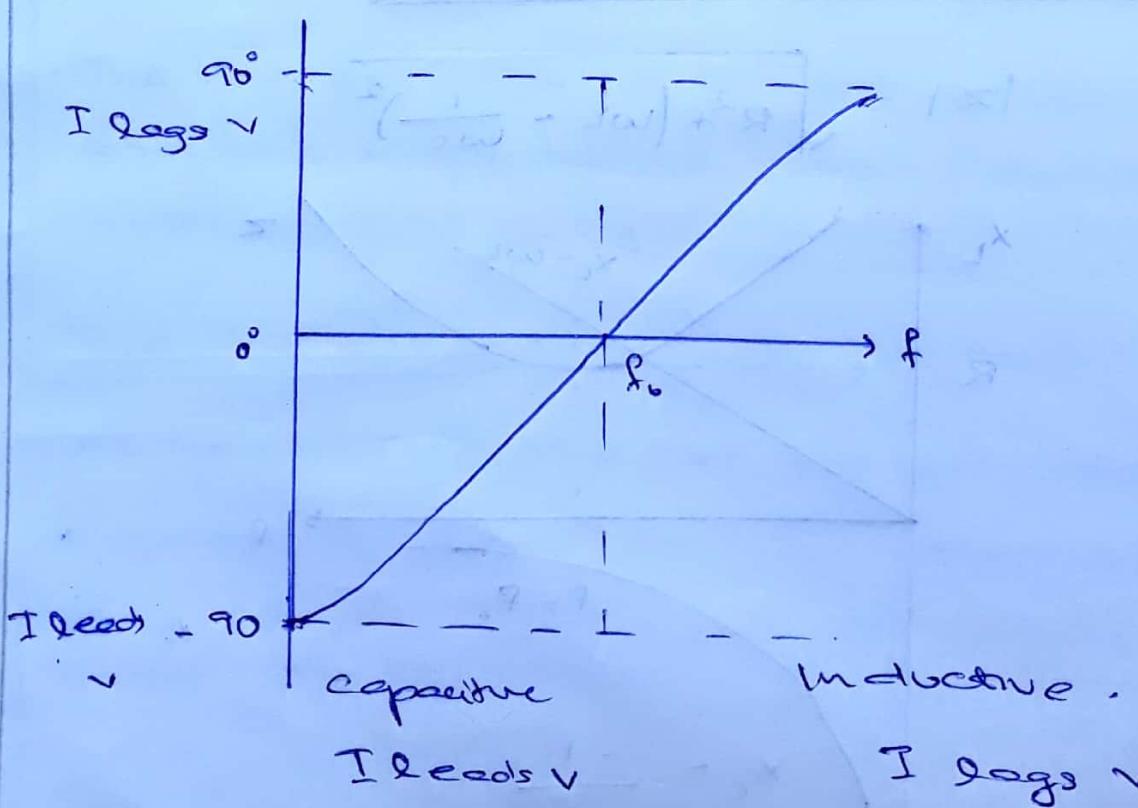

The phase angle decreases as the frequency approaches the resonant value, and is 0° at resonance.

The phase angle approaches 90° as the frequency goes higher.

Q Factor of Series Resonating Ckt.

It is defined as the ratio of voltage across the inductor or capacitor to the applied voltage.

$$Q = \frac{V_L}{V} = \frac{I_0 X_L}{I_0 R} = \frac{X_L}{R} = \frac{\omega_0 L}{R}$$

$$\text{also } Q = \frac{V_C}{V} = \frac{I_0 X_C}{I_0 R} = \frac{X_C}{R} = \frac{1}{\omega_0 C R}$$

$$V_L = I_0 X_L = \frac{V}{R} X_L = \frac{V}{R} \omega_0 L = \frac{\omega_0 L}{R} V$$

$$V_L = Q \text{ factor} \times V \text{ volts.}$$

$$\text{and } V_C = I_0 X_C = \frac{V}{R} \cdot \frac{1}{\omega_0 C} = \frac{1}{\omega_0 C R} V$$


$$V_C = Q \text{ factor} \times V \text{ volts.}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{1}{\omega_0 C R} = \frac{1}{\frac{1}{\sqrt{LC}} \cdot CR} = \frac{1}{R} \sqrt{\frac{C}{L}}$$

Bandwidth Of An RLC Ckt.

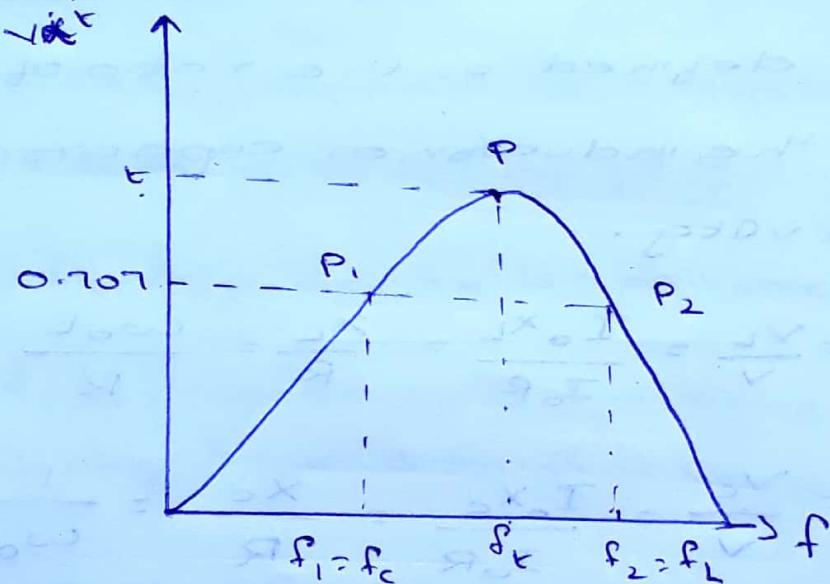The bandwidth of any system is the range of frequencies for which the current or output voltage is equal to 70.7% of its value at the resonant frequency. It is denoted by BW.



$$BW = f_2 - f_1$$

The frequency band within the limits of lower and upper half power frequency is called the band width of the resonant ckt.

At half power frequencies.

$$X = \pm (X_L - X_C) = R$$

{ +ve indicate predominance of X_L or X_C .

$$\therefore R = \pm (\omega L - \frac{1}{\omega C}) = \pm X$$

Let ω_1 be frequency when the net ckt reactance be -ve and ω_2 be frequency when the net ckt reactance is +ve.

$$(\omega_2 L - \frac{1}{\omega_2 C}) = R \quad \text{--- (1)}$$

$$(\omega_1 L - \frac{1}{\omega_1 C}) = -R \quad \text{--- (2)}$$

Adding (1) and (2)

$$(\omega_2 + \omega_1)L - \frac{1}{C} \left(\frac{1}{\omega_2} + \frac{1}{\omega_1} \right) = 0$$

$$(\omega_2 + \omega_1)L = \frac{1}{C} \left(\frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right)$$

$$\omega_1 \omega_2 = \frac{1}{LC} \quad \text{--- (3)}$$

Subtracting (1) - (2)

$$(\omega_2 - \omega_1)L + \frac{1}{C} \left(\frac{1}{\omega_1} - \frac{1}{\omega_2} \right) = 2R$$

$$(\omega_2 - \omega_1)L + \frac{1}{C} \left(\frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right) = 2R \quad \text{--- (4)}$$

Divide (4) by L

$$\omega_2 - \omega_1 + \frac{1}{LC} \left(\frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right) = \frac{2R}{L}$$

$$(\omega_2 - \omega_1) + \frac{1}{LC} \frac{\omega_2 - \omega_1}{\omega_1 \omega_2} = \frac{2R}{L}$$

$$2(\omega_2 - \omega_1) = \frac{2R}{L}$$

$$\text{Bandwidth } (\omega_2 - \omega_1) = \frac{R}{L} \quad \text{--- (5)}$$

$$Q \text{ factor} = \frac{\omega_0 L}{R}$$

$$\frac{\omega_0}{Q \cdot R} = \frac{R}{L} \left(\frac{1}{\omega_0} - \frac{1}{\omega} \right)$$

Comparing with (5)

$$\frac{\omega_0}{Q} = \omega_2 - \omega_1$$

$$Q = \frac{\omega_0}{\omega_2 - \omega_1}$$

$$= \frac{f_0}{f_2 - f_1}$$

i.e.,

$$Q = \frac{f_0}{\text{Bandwidth}} \quad \text{--- (6)}$$

Expression of Half Power Frequencies

In RLC Series Resonating Ckt & Relationship

B/w f_1 , f_2 and f_0 .

From Eqn (3)

$$\omega_1, \omega_2 = \frac{1}{LC} \quad \text{--- (6)}$$

Also at resonance $\omega_0 = \frac{1}{\sqrt{LC}}$ --- (7)

Comparing (6) and (7)

$$\omega_0^2 = \omega_1 \omega_2$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

The resonant frequency is the geometric mean of the two half power frequencies.

From ③

$$\omega_1 \omega_2 = \frac{1}{LC}$$

$$\omega_{0.2} - \omega_{0.1} = \frac{R}{L}$$

$$\frac{1}{\omega_1 LC} - \omega_1 = \frac{R}{L}$$

$$\frac{1 - \omega_1^2 LC}{\omega_1 LC} = \frac{R}{L}$$

$$1 - \omega_1^2 LC = \omega_1 RC$$

$$\omega_1^2 LC + \omega_1 RC - 1 = 0$$

$$\omega_1 = \frac{-RC \pm \sqrt{R^2 C^2 - 4LC}}{2LC}$$

Taking +ve sign of radical,

$$\omega_1 = \frac{-R}{2LC} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Similarly substituting the value of ω_1 from eqn ③ in ⑤ and on simplification will yields.

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Frequency at which V_C & V_L are maximum.

$$V_C = IX_C$$

$$V_C = \frac{V}{\sqrt{R^2 + \left(\omega_L - \frac{1}{\omega_C}\right)^2}} \times \frac{1}{\omega_C}$$

$$V_C^2 = \frac{V^2}{\omega_C^2 [R^2 + \left(\omega_L - \frac{1}{\omega_C}\right)^2]}$$

$$= \frac{V^2}{\omega_C^2 R^2 + (\omega_C^2 L - 1)^2}$$

On differentiating;

$$\frac{dV_C^2}{d\omega} = 0 = \frac{-V^2 [2\omega_0 C^2 R^2 + 2(\omega_0^2 LC - 1)2\omega_0 C]}{[\omega_0^2 C^2 R^2 + (\omega_0^2 LC - 1)^2]^2}$$

$$2\omega_0 C^2 R^2 + 2(\omega_0^2 LC - 1)2\omega_0 LC = 0 \quad [\because V \neq 0]$$

$$2\omega_0 C^2 R^2 + 4\omega_0^3 L^2 C^2 - 4\omega_0 LC = 0$$

$$2\omega_0 C (CR^2 + 2\omega_0^2 L^2 C - 2L) = 0$$

$$\therefore 2\omega_0^2 L^2 C + CR^2 - 2L = 0$$

$$\omega_0^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

The above expression of frequency at which the voltage across the capacitor is maximum.

To find the frequency at which V_L is maximum.

$$V_L = I X_L$$

$$= \frac{\sqrt{\omega L}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$V_L^2 = \frac{\sqrt{\omega^2 L^2}}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$= \frac{\sqrt{\omega^4 L^2 C^2}}{\omega^2 C^2 R^2 + (\omega^2 L C - 1)^2}$$

By differentiating V_L^2 with respect to ω
and setting $\frac{dV_L^2}{d\omega} = 0$.

$$2\omega^2 LC - \omega^2 C^2 R^2 - 2 = 0$$

$$\omega^2 (2LC - CR^2) = 2$$

$$\omega^2 = \frac{2}{2LC - CR^2}$$

$$\frac{2}{2LC - CR^2} = \frac{1}{LC - \frac{C^2 R^2}{2}}$$

$$\omega = \sqrt{\frac{1}{LC - \frac{C^2 R^2}{2}}}$$

$$f_0 = \frac{1}{2\pi \sqrt{LC - \frac{C^2 R^2}{2}}}$$

Problems

1. A series RLC circuit has $R = 2\Omega$, $L = 2.0mH$, $C = 10\mu F$. Calculate i) Q factor of the ckt.
ii) bandwidth iii) resonant frequency and
iv) half power frequency $f_{1/2}$ and f_2 .

$$R = 2\Omega$$

$$L = 2.0mH$$

$$C = 10\mu F$$

$$i) Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{2} \sqrt{\frac{2 \times 10^3}{10 \times 10^{-6}}} = 7.07$$

$$iii) \omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{2 \times 10^3 \times 10 \times 10^{-6}}} = 1125.39 \text{ Hz}$$

$$ii) B_{WI} = \frac{f_0}{Q}$$

$$= \frac{1125.39}{7.07} = 159.23 \text{ Hz}$$

$$iv) f_1 = \frac{-R \pm \sqrt{R^2 + 4LC}}{4\pi L}$$

$$= -2 \pm \frac{\sqrt{4 + 4 \left(\frac{2 \times 10^3}{10 \times 10^{-6}} \right)}}{4 \times \pi \times 2 \times 10^{-3}}$$

$$= 1048.62 \text{ Hz}$$

$$f_2 = \frac{R + \sqrt{R^2 + 4LC}}{2\pi L}$$

$$= 2 + \frac{\sqrt{4 + 4(2 \times 10^{-3} \times 10^{-5})}}{4\pi \times 2 \times 10^{-3}}$$

$$= 1208.4 \text{ Hz}$$

OR

f_1 and f_2 can be determined by using

$$f_2 = f_a + \frac{\text{Bandwidth}}{2}$$

$$f_1 = f_a - \frac{\text{Bandwidth}}{2}$$

2. Obtain the values of R , L , C in a series

RLC circuit that resonates at 1.5 kHz and consumes 50 W from a 50V AC source operating at the resonant frequency.

Calculate the inductance and capacitance of the circuit. The BW is 0.75 kHz.

\Rightarrow

$$\text{BW} = f_2 - f_1$$

For a series circuit of resonance.

$$V_R = V_{\text{supply}} = 50V$$

$$P_{loss} = \frac{V^2}{R} = \frac{50^2}{R}$$

$$50 = \frac{50^2}{R}$$

$$\underline{\underline{R = 50 \Omega}}.$$

$$Q = \frac{f_0}{BW} = \frac{1.5}{0.75} = 2$$

$$Q = \frac{L\omega_0}{R} = \frac{2\pi f_0 L}{R}$$

$$2 = \frac{2\pi \times 1.5 \times 10^3 L}{80}$$

$$\frac{2 \times 50}{2\pi \times 1.5 \times 10^3} = L$$

$$\underline{\underline{L = 0.0106 H}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$1.5 \times 10^3 \times 2\pi = \frac{1}{\sqrt{L \cdot C}}$$

$$\sqrt{C} = \frac{1}{1.5 \times 10^3 \times 2\pi \times \sqrt{0.0106}}$$

$$C = 1.061 \times 10^{-6} F$$

3. A series resonating circuit has $R = 1\text{ k}\Omega$, half power frequencies of 10 and 90 kHz. Determine the band width and the resonant frequency. Calculate the inductance and capacitance of the circuit.

$$\Rightarrow BW = f_2 - f_1 = 90 - 10 = 80 \text{ kHz}$$

$$f_0 = \sqrt{f_1 f_2} = \sqrt{90 \times 10} = \sqrt{900} = 30 \text{ kHz}$$

$$Q = \frac{f_0}{BW} = \frac{30}{80} = \underline{\underline{\frac{3}{8}}}$$

$$Q = \frac{2\pi f_0 L}{R}$$

$$\frac{3}{8} = \frac{2\pi \times 30 \times 10^3 \times L}{1000}$$

$$2.25 \text{ mH} = L$$

At series resonance.

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$30 \times 10^3 = \frac{1}{2\pi \sqrt{2 \times 10^{-3} C}}$$

$$\sqrt{C} = \frac{30 \times 10^3 \times 2\pi \sqrt{2} \times (\bar{\rho})^3}{1}$$

$$C = \underline{0.014 \text{ MF}}$$

4. A voltage $V(t) = 10 \sin \omega t$ is applied to a series RLC circuit. At resonant frequency of the circuit the maximum voltage across the capacitor is found to be 500V. Moreover the bandwidth is known to 400 rad/s and the impedance at resonance is 100Ω. Find the resonant frequency. Also find the values of L and C of the circuit.

→ The applied voltage to the circuit is.

$$V_{\text{max}} = 10 \text{ V}$$

$$V_{\text{rms}} = \frac{10}{\sqrt{2}} = \underline{\underline{7.07 \text{ V}}}$$

$$V_C = 500 \text{ V}$$

$$\Phi = \frac{V_C}{V_{\text{rms}}} = \frac{500}{7.07} = 70.7$$

$$B.W. = \omega_2 - \omega_1 = 400 \text{ rad/s.}$$

$$\text{At resonance } Z = R = 100 \Omega.$$

$$\Phi = \frac{\omega_0}{B.W.} = \frac{\omega_0}{\omega_2 - \omega_1}$$

$$\omega_0 = Q(\omega_2 - \omega_1)$$

$$= 28280 \text{ rad/s}$$

$$f_0 = \frac{28280}{2\pi} = 4499 \text{ Hz}$$

$$B.W = \omega_2 - \omega_1 = \frac{R}{L}$$

$$L = \frac{R}{\omega_2 - \omega_1}$$

$$L = \frac{100}{400} = 0.25 \text{ H}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$C = \frac{1}{(2\pi f_0)^2 L} = \frac{1}{(2\pi \times 4499)^2 \times 0.25}$$

$$C = 5 \text{ nF}$$

5. A constant voltage at a frequency of 1 MHz is applied to an inductor in series with a variable capacitor. When the capacitor is set to 500 pF, the current has its maximum value while it is reduced to one-half when the capacitance is 600 pF. Find R, L and Q factor of the inductor.

⇒

$$f_0 = 1 \text{ MHz}$$

$$C_1 = 500 \text{ pF}$$

$$C_2 = 600 \text{ pF}$$

$$C = 500 \text{ pF}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{L \times 500 \times 10^{-12}}}$$

$$10^6 = \frac{1}{2\pi\sqrt{L \times 500 \times 10^{-12}}}$$

$$L = 0.05 \text{ mH}$$

$$X_L = 2\pi f_0 L = 2\pi \times 10^6 \times 0.05 \times 10^{-3} = 314.16 \Omega$$

When capacitance is 600 pF, the current reduces to one half of the current at resonance.

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi \times 10^6 \times 600 \times 10^{-12}} = 265.26 \Omega$$

$$I = \frac{1}{2} I_0$$

$$\therefore \frac{V}{2} = \frac{1}{2} \frac{V}{R}$$

$$Z = 2R$$

$$\sqrt{R^2 + (X_L - X_C)^2} = 2R$$

$$R^2 + (314.16 - 265.26)^2 = 4R^2$$

$$3R^2 = 2391.21$$

$$\therefore R = \underline{\underline{28.23\Omega}}$$

$$Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}}$$

or $\frac{x_L}{R}$

$$= \frac{1}{28.23} \sqrt{\frac{0.05 \times 10^{-3}}{500 \times 10^{-12}}}$$

$$= \underline{\underline{11.2}}$$

Parallel Resonance.

Consider a parallel circuit consisting of a coil and capacitor as shown in fig. The impedance of two branches are:

$$\bar{Z}_1 = R + jx_L$$


$$\bar{Z}_2 = -jx_C$$

$$\bar{Y}_1 = \frac{1}{\bar{Z}_1} = \frac{1}{R + jx_L}$$

$$= \frac{R - jx_L}{R^2 + x_L^2}$$

$$\bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{-jx_C} = \frac{jx_C}{x_C^2}$$

$$= \frac{j}{x_C}$$

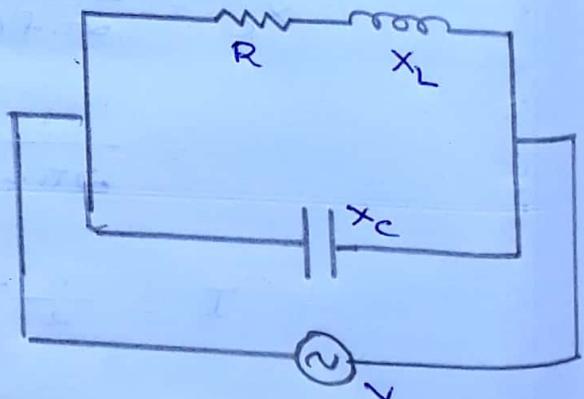

Admittance of the circuit, \bar{Y} .

$$\bar{Y} = \bar{Y}_1 + \bar{Y}_2$$

$$= \frac{R - jX_L}{R^2 + X_L^2} + j\frac{1}{X_C}$$

$$= \frac{R}{R^2 + X_L^2} - j\left(\frac{X_L}{R^2 + X_L^2} - \frac{1}{X_C}\right)$$

At resonance circuit is purely resistive. i.e. the condition for resonance is

$$\frac{X_L}{R^2 + X_L^2} = \frac{1}{X_C}$$

$$X_L X_C = R^2 + X_L^2$$

$$\omega_0 L \frac{1}{c \omega_0} = R^2 + \omega_0^2 L^2$$

$$\omega_0^2 L^2 = \frac{L}{c} - R^2$$

$$\omega_0^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

f_0 is called the resonant frequency of the ckt.


If R is very small as compared to L then

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Dynamic Impedance of Parallel Circuit.

At resonance, the circuit is purely resistive.

∴ Dynamic impedance at resonance.

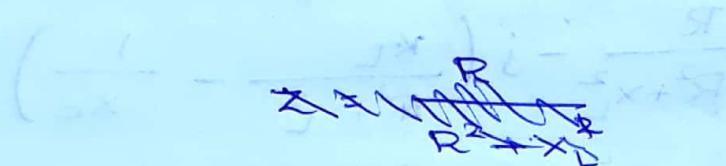

$$Z = \frac{R^2 + X_L^2}{R}$$

At resonance.

$$R^2 + X_L^2 = X_L X_C$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{cR}}$$



$$\therefore Z = \frac{R}{CR}$$

Properties of Resonance of Parallel LRC Ckt.

- * Power factor is unity.
- * Current at resonance [$\sqrt{1/(LC)}$] is minimum.
- * Net impedance at resonance of parallel circuit is maximum at equal to $(1/\sqrt{LC})\Omega$.
- * The admittance is minimum.
- * The resonant frequency of this ckt $f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$

Variation of Capacitive and Inductive Susceptance

Impedance And Current With Frequency.

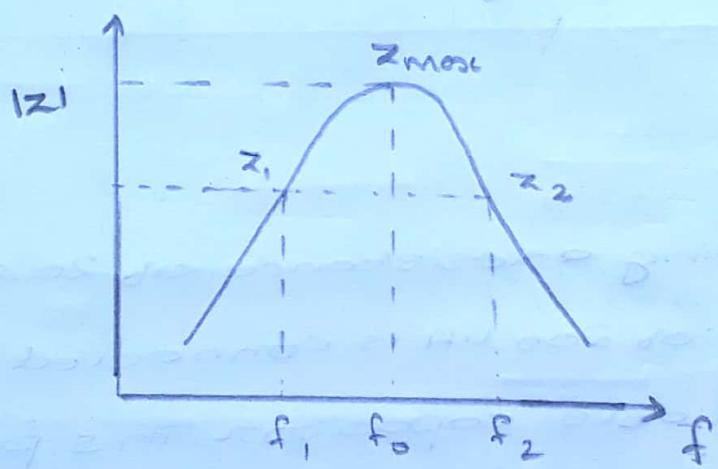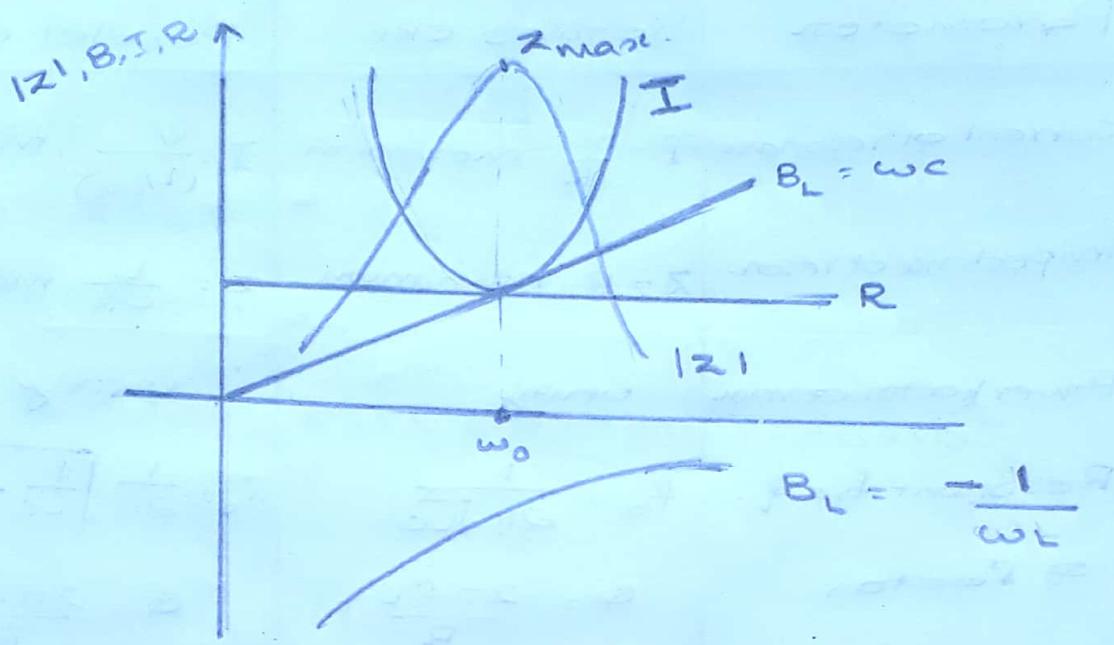

Q factor of Parallel Resonating circuit (I magnification at resonance)

$$Q = \frac{I_m}{I} = \frac{\sqrt{1/x_C}}{\sqrt{1/z}} = \frac{z}{x_C} = \frac{L}{CR} \times \omega_0 C$$

$$Q = \frac{L \omega_0}{R}$$

Ckt also known as: λ selector ckt

antiresonant ckt

tuned ckt.

Comparison of Series & Parallel Resonant Ckt.

Parameter	Series Ckt	Parallel ckt.
Current at resonance	$I = \frac{V}{R}$, maximum	$I = \frac{V}{(L/C)}$, minimum.
Impedance at reson.	$Z = R$, minimum	$Z = \frac{L}{CR}$, maximum.
Power factor at reson.	unity	unity
Resonant freq.	$f_0 = \frac{1}{2\pi\sqrt{LC}}$	$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$
Q factor	$Q = \frac{2\pi f L}{R}$	$Q = \frac{2\pi f L}{R}$
It magnifies	Volt across L & C	Current across L & C

Problems

1. A coil having a resistance of 20Ω and an inductance of 200 mH is connected in parallel with a variable capacitor. This parallel combination is connected in series with a resistance of 8000Ω . A voltage of 230 V at a frequency of 10^6 Hz is applied across the circuit. Calculate the value of capacitance at resonance b) Q factor of the circuit. c) dynamic impedance of the circuit. d) total circuit current.

$$\Rightarrow Q = 20 \Omega$$

$$L = 200 \text{ mH}$$

$$f = 10^6 \text{ Hz}$$

$$V = 230 \text{ V}$$

$$R_s = 8000 \Omega$$

$$X_L = L\omega = 2\pi f L = 2\pi \times 10^6 \times 200 \times 10^{-6} \\ = 1256.6 \Omega$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$10^6 = \frac{1}{2\pi} \sqrt{\frac{1}{200 \times 10^{-6} \times C} - \frac{20^2}{(200 \times 10^6)^2}}$$

$$C = 126.65 \times 10^{-12} \text{ F} = 126.65 \text{ pF}$$


$$Q \text{ factor } Q_0 = \frac{2\pi f L}{R}$$

$$= \frac{2\pi \times 10^6 \times 200 \times 10^{-6}}{20}$$

$$= 62.83.$$

$$\text{Dynamic impedance } Z = \frac{L}{CR}$$
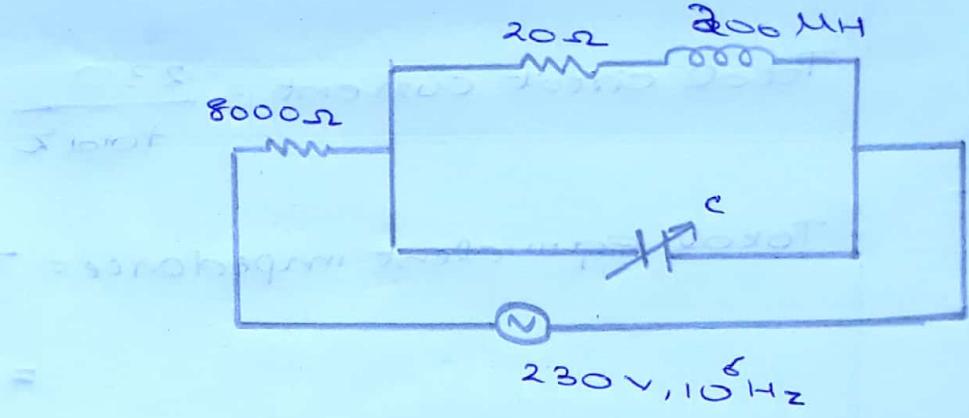
$$= \frac{200 \times 10^{-6}}{126.65 \times 10^{-12} \times 20} = 78958 \Omega$$



$$\text{Total circuit current} = \frac{230}{\text{total } Z}$$


$$\begin{aligned}\text{Total equivalent impedance} &= 78958 + 8000 \\ &= 86958 \Omega\end{aligned}$$

$$\therefore \text{Total circuit current} = \frac{230}{86958} = 2.645 \times 10^{-3} \text{ A} = \underline{\underline{2.65 \text{ mA}}}$$

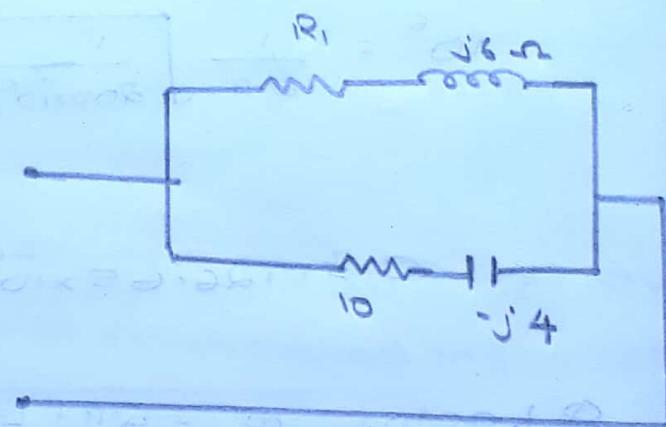2. Find the value of R_1 such that the circuit given in figure is resonant.

$$\Rightarrow Y = \frac{1}{R_1+j6} + \frac{1}{10-j4}$$

$$= \frac{R_1-j6}{R_1^2+36} + \frac{10+j4}{10^2+16}$$



$$= \frac{R_1}{R_1^2+36} + \frac{10}{10^2+16} + j \left(\frac{4}{10^2+16} - \frac{6}{R_1^2+36} \right)$$

During resonance Imaginary part of $Y = 0$.

$$\frac{4}{10^2+16} = -\frac{6}{R_1^2+36}$$

$$R_1^2 + 36 = \frac{116}{4} \times 6$$

$R_1 = 11.75\Omega$