

\* ~~220V~~

A balanced 3 phase load consists of 3 coils having resistance of  $5\ \Omega$  and inductance of  $0.01\text{ H}$ . It is connected to a  $415\text{ V}, 50\text{ Hz}$  3 phase ac supply. Determine Phase voltage, phase current, power factor, active power when loads are connected in (i) star (ii) Delta

→

(i) Star


$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

$$V_L = 415\text{ V}$$

$$V_{ph} = 239.60\text{ V}$$
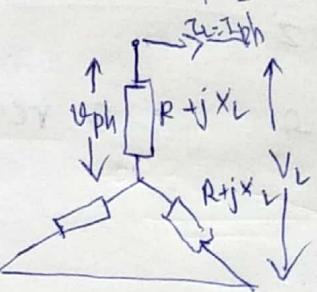
$$\begin{aligned} R &= 5\ \Omega \\ L &= 0.01\text{ H} \\ f &= 50\text{ Hz} \end{aligned}$$



$$\text{Impedance, } |Z| = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{R^2 + 4\pi^2 f^2 L^2}$$

$$= \sqrt{25 + 9.869} = \underline{\underline{5.904}}$$

$$Z = R + jX_L$$

$$Z = 5 + j3.14$$

$$Z = \frac{V_{ph}}{I_{ph}}$$

$$5 + j3.14$$

$$\underline{\underline{5.904}} = \frac{239.60}{I_{ph}}$$

$$\therefore I_{ph} = \underline{\underline{40.58 \angle -32.12^\circ\text{ A}}}$$

$$\cos \phi = \frac{R}{Z} = \frac{5}{5.904} = 0.846$$


$$\phi = \cos^{-1}(0.846) = \underline{\underline{32.22}}$$

$$\text{ACTIVE POWER} = VI \cos \phi$$

$$= \underline{\underline{8.225\text{ KW}}}$$

High  
After susti. recic.  
met P. q
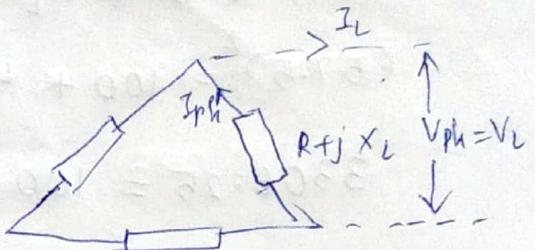
$$\begin{aligned} \text{Active power} &= \sqrt{3} V_L I_L \cos \phi \\ &= \sqrt{3} \times 415 \times 40.58 \times 0.846 \\ &= \underline{\underline{24.67 \text{ KW}}} \end{aligned}$$



$$V_{ph} = V_L = 415 \text{ V}$$

$$I_{ph} = \frac{I_L}{\sqrt{3}}$$

$$Z = R + j X_L$$

$$Z = 5 + j 3.14$$

$$Z = \frac{V_{ph}}{I_{ph}} \quad \therefore I_{ph} = \frac{83}{14.58} \angle -32.12^\circ \text{ A}$$

$$I_L = \frac{143.76}{70.28} \angle -32.12^\circ \text{ A}$$

$$\cos \phi = \frac{R}{Z} \quad \therefore \cos \phi = \underline{\underline{0.846}}$$

$$\begin{aligned} \text{Active power} &= \sqrt{3} V_L I_L \cos \phi \\ &= \underline{\underline{24.67 \text{ KW}}} = \frac{87.42 \text{ KW}}{112.73 \text{ KW}} \end{aligned}$$

- \* A  $10 \Omega$  resistor and  $300\text{mH}$  inductor are connected in series across  $230 \text{ V}$  sinusoidal voltage. Circuit current is  $4 \text{ A}$ . Calculate supply frequency and phase angle b/w current and voltage.

$$\rightarrow R = 10 \Omega$$

$$L = 30 \text{ mH}$$

$$I = 4 \text{ A}$$

$$V = 230 \text{ V}$$

$$Z = \frac{V}{I} = \frac{230}{4} = 57.5$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$(57.5)^2 = 100 + 4\pi^2 f^2 \times 9 \times 10^{-6} \times 10^2 \times 10^2$$

$$3306.25 = 100 + 355.30 \times 10^2 f^2$$

$$f^2 = \frac{3206.25 \times 10^2}{355.30}$$

$$f^2 = 9.02 \times 10^4$$

$$f = \sqrt{9.02 \times 10^4} = \frac{300 \text{ Hz}}{\cancel{10^2}} = \underline{\underline{30 \text{ Hz}}}$$

$$\cos \phi = \frac{R}{Z} = \frac{10}{57.5} = \underline{\underline{79.98}}$$

$$\therefore \phi = \underline{\underline{79.98^\circ}}$$

\* A series circuit containing capacitance  $2\mu F$  and a resistor of  $500\Omega$ . An ac source is connected which draws a current of  $50 \angle 0$  mA. The angular frequency of A.C. source is  $400\pi$

- Draw circuit and find source voltage
- Find voltage across capacitor and resistor
- Draw voltage phasor diagram

$$C = 2 \times 10^{-6} F$$

$$R = 500\Omega$$

$$I = 50 \angle 0 \text{ mA}$$

$$W = 1400 \pi$$

$$Z = R - jX_C$$

$$X_C = \frac{1}{C\omega} = \frac{1}{2 \times 10^6 \times 400\pi} = 397.88$$

$$Z = 500 - j397.88$$

$$|Z| = 638.99$$

$$Z = 638.99 \angle -38.5^\circ$$

$$Z = \frac{V}{I}$$


$$V = XI$$

$$= \underline{31.94 \angle -38.51^\circ V}$$

voltage across resistor,  $V_R = I \times R$   
 $= 25 V$

voltage across capacitor  $\Rightarrow V_C = I \times X_C$   
 $= \underline{19.894 V}$

UDSF GECT

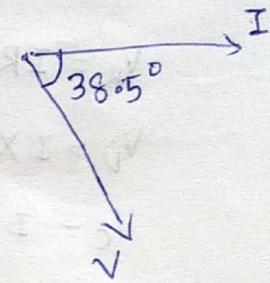

- \* A 3 phase core wire, 400 V system feeds 3 loads  $10-j8 \Omega$  connected in star. calculate  $I_L$  in each phase.

→ STAR:

$$V_L = \sqrt{3} V_{ph}$$

$$V_L = 400 V$$

$$V_{ph} = 230.94 V$$

$$Z = 10 - j8 \Omega$$

$$Z_{ph} = 10 - j8$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}}$$

$$I_{ph} = \frac{230.94}{12.806 \angle -38.6^\circ}$$

$$I_{ph} = 18.033 \angle 38.6^\circ$$


$$I_L = 18.033 \angle 38.6^\circ$$

$$I_R = 18.033 \angle 38.6^\circ$$

$$I_Y = 18.033 \angle -\cancel{158.6}^\circ$$

$$I_B = 18.033 \angle -\cancel{278.6}^\circ$$

LCR circuit

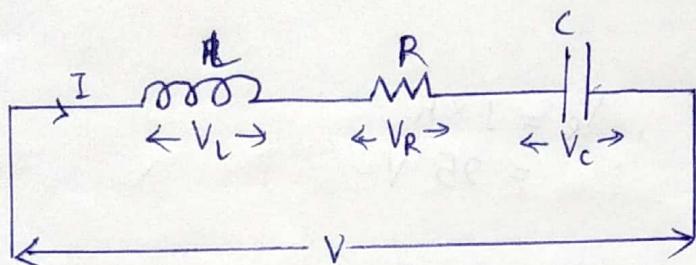

$$V_R = IR$$

$$V_L = IX_L$$

$$V_C = IX_C$$

$$V = \vec{V}_R + \vec{V}_L + \vec{V}_C$$

$$= \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$


$$\angle Z = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

$$Z = R + j(X_L - X_C)$$

$$\cos \phi = \frac{R}{Z}$$

$$P = VI \cos \phi$$

$$Q = VI \sin \phi$$

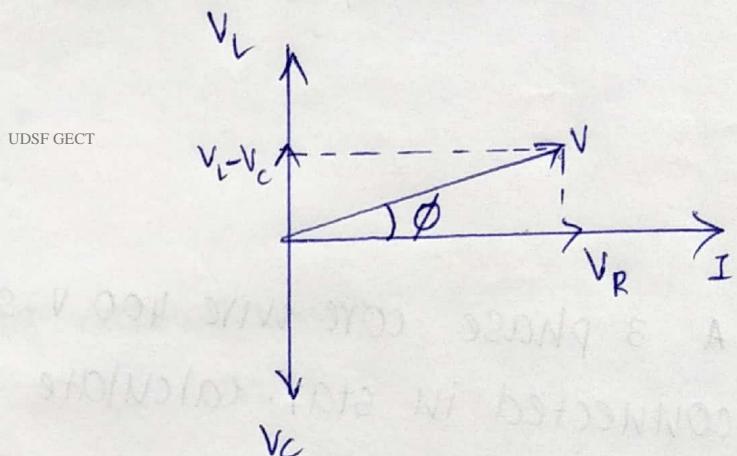

3 100  $\Omega$  non-inductive resistors are connected in (a) star and (b) delta across a 400 V, 50 Hz 3 phase supply. Calculate power taken from supply in each case. If one of resistor is open circuited, what will be the value of total power taken from mains in each of 2 cases?

$$V_L = 400 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$R = 100 \Omega ; 3 \text{ resistors}$$

(a) Star

$$V_{ph} = \frac{V_L}{\sqrt{3}} , I_{ph} = I_L$$

UDSF GECT

$$x = 0 \therefore Z = R = 100 \Omega$$

$$V_{ph} = \frac{400}{\sqrt{3}} = 230.94 \text{ V}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \underline{\underline{2.30 \text{ A}}}$$

$$I_L = I_{ph}$$

$$\underline{\underline{I_L = 2.30 \text{ A}}}$$

$$\begin{aligned} P &= \sqrt{3} V_L I_L \cos \phi \\ &= \sqrt{3} \times 400 \times 2.30 \times 1 \\ &= \underline{\underline{1593.486 \text{ kW}}} \end{aligned}$$

(b) Delta

$$V_{ph} = V_L = 400 \text{ V}$$

$$I_{ph} = \frac{I_L}{\sqrt{3}}$$

POWER CONSUMED IN STAR CONNECTED SYSTEM

$$V_{ph} = \frac{V_L}{\sqrt{3}}$$

$$I_{ph} = I_L$$

POWER CONSUMED,

$$P_{star} = 3 \times \frac{V_L}{\sqrt{3}} \times I_L \times \cos \phi$$

$$P_{star} = \sqrt{3} V_L I_L \cos \phi$$

- \* A balanced star connected load of  $8 + j6 \Omega$  is connected to a 3 phase 230 V supply. Find line currents, phase currents, active power, reactive power, total Volt amperes, PF

$$V_L = 230 \text{ V}$$

$$Z_{ph} = 8 + j6 \Omega$$

star connection

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{230}{\sqrt{3}} = 132.79$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{132.79}{\sqrt{64+36} \angle 36.8^\circ} = \frac{13.279 \angle -36.8^\circ}{\sqrt{100} \angle -j7.95^\circ} = \frac{13.279 \angle -36.8^\circ}{10 \angle -j7.95^\circ}$$

$$I_L = I_{ph} = 13.279 \angle -36.8^\circ \text{ A}$$

$$\text{POWER FACTOR} = \cos \phi = \underline{0.8007}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$P = \sqrt{3} \times 230 \times 13.279 \times \frac{-36.8}{180^\circ} \times 0.8007$$

$$\underline{P = 4.235 \text{ KW}}$$

reactive power,

$$Q = \sqrt{3} V_L I_L \sin \phi$$

$$\underline{Q = 3.171 \text{ KVAR}}$$

$$V_L = 230 \text{ V}$$
$$I_L = 13.279 \text{ A}$$
$$P =$$

$$\text{total VA} = \sqrt{3} V_L I_L \quad (\text{apparent})$$

$$= \sqrt{3} \times 230 \times 13.279$$

$$\underline{\underline{= 5.289 \text{ KVA}}}$$

$I_R, I_Y, I_B$

$$I_R = 13.279 < -36.8^\circ$$

phase diff. of  $120^\circ$

$$I_Y = 13.279 < -156.8^\circ$$

$$I_B = 13.279 < -276.8^\circ$$

$I_R = I_Y = I_B = \text{Phase currents}$

- \* A 400 V, 50 Hz 3 phase supply is applied across 3 terminals of a delta connected 3 phase load. The resistance and reactance of each phase is  $6\Omega$  and  $8\Omega$ . calculate  $I_L, I_{ph}, P, Q$ , apparent power

$$f = 50 \text{ Hz}$$

$$I_L = \sqrt{3} I_{ph}$$

$$V_L = 400 \text{ V}$$

$$V_L = V_{ph} = 400 \text{ V}$$

$$R = 6\Omega \quad X = 8\Omega$$

$$I_L = \frac{V_L}{R} = \frac{400}{6} \rightarrow 66.67 A$$

$$I_X = \sqrt{3} I_{ph}$$

$$I_{ph} = 38.48 A$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}}$$

$$Z_{ph} = 6 + j8$$

$$I_{ph} = \frac{400}{10 \angle 53.13} = \underline{40 \angle -53.13}$$

$$I_L = \sqrt{3} I_{ph}$$

$$I_L = 69.28 \angle -53.13$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 69.28 \times \cos(53.13)$$

$$= \underline{\underline{28.79 \text{ KW}}}$$

$$Q = \sqrt{3} V_L I_L \sin \phi$$

$$= \sqrt{3} \times 400 \times 69.28 \times \sin(53.13)$$

$$= \underline{\underline{38.398 \text{ KVAR}}}$$

$$\text{apparent power, } S = \sqrt{3} V_L I_L$$

$$= \sqrt{3} \times 400 \times 69.28$$

$$= \underline{\underline{47.998 \text{ KVA}}}$$

POWER factor = 0.6

3 impedances  $Z_1 = 8 + j6 \Omega$ ,  $Z_2 = 4 + j3 \Omega$  and  $Z_3 = 18 - j9 \Omega$  are connected in series across ac supply. If voltage drop across  $Z_1$  is  $40 + j30 V$ , calculate  
 (i) current in circuit (ii) voltage drop across  $Z_2, Z_3$   
 (iii) total supply voltage (iv) total power consumed  
 (v) power factor (vi) draw phasor diagram.

$$Z_1 = 8 + j6 \Omega$$

$$Z_2 = 4 + j3 \Omega$$

$$Z_3 = 18 - j9 \Omega$$

$$\text{Voltage drop across } Z_1 = 40 + j30 V$$

$$I_1 = \frac{|V|}{|Z_1|} = \frac{\sqrt{40^2 + 30^2}}{\sqrt{8^2 + 6^2}} = \frac{50}{10} = 5 A$$

Since series connection, current will be same

$$\therefore \text{Total current in circuit} = 5 A$$

$$\begin{aligned} V_{21} &= I \times Z_1 \\ &= 5(8 + j6) V = 40 + j30 V \end{aligned}$$

$$\begin{aligned} V_{22} &= I \times Z_2 \\ &= 5(4 + j3) V = 20 + j15 V \end{aligned}$$

$$\begin{aligned} V_{23} &= I \times Z_3 \\ &= 5(18 - j9) V = 90 - j45 V \end{aligned}$$

$$\begin{aligned} \text{Total voltage} &= V_{21} + V_{22} + V_{23} \\ &= 5(8 + 4 + 18) + j5(3 + 6 - 9) \\ &= 5 \times (30 + 0j) = 150 + 0j V \end{aligned}$$

(iv) Power,  $P = VI \cos\phi$   ~~$= 150 \times 5 = 750 \text{ W}$~~   $\Rightarrow \underline{750 \text{ W}}$

(v) Power Factor,  $\cos\phi = \frac{R}{Z} = \frac{30}{30} = 1$

$$\phi = \cos^{-1}(1) = 0$$

(vi) Phasor




polar form

$$V_1 = 40 + j 30 = 50 \angle 36.8698^\circ$$

$$V_2 = 20 + j 15 = 25 \angle 36.8698^\circ$$

$$V_3 = 90 - j 45 = 100.62 \angle -26.565^\circ$$

$$V = 150 \angle 0^\circ$$

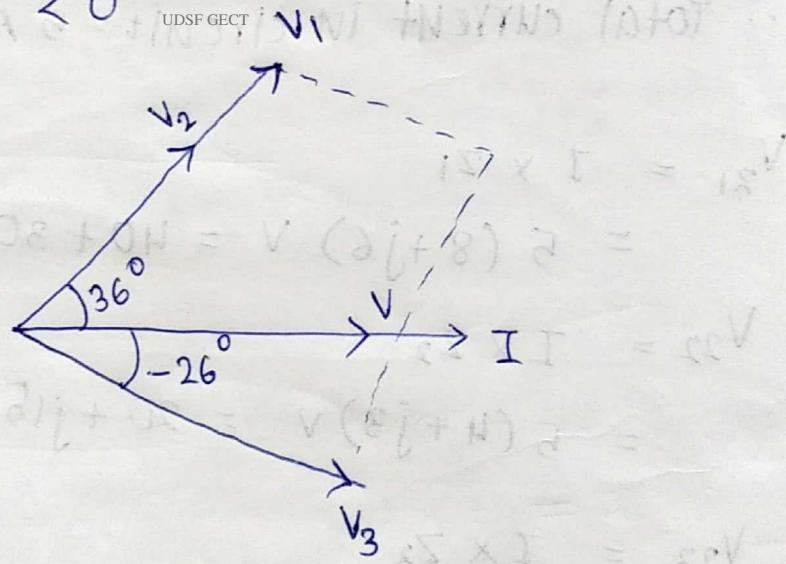

- \* A circuit consists of resistor of value  $50 \Omega$  and an inductor of  $1 \text{ mH}$ . Under steady state condition, what is the value of energy stored in inductor if applied voltage is  $150 \text{ V dc}$ ?

$$R = 50 \Omega$$

$$L = 1 \text{ mH}$$

$$V = 150 \text{ V}$$

$$E = \frac{1}{2} L I^2$$



$$I = \frac{V}{R} = \frac{150}{50} = 3 \text{ A}$$

$$E = \frac{1}{2} L I^2$$
$$= \frac{1}{2} \times 10^{-3} \times 9$$
$$E = 4.5 \times 10^{-3} \text{ J}$$

UDSF GECT

under steady state  
condition,  
→ inductor act as  
short circuit  
→ capacitor act as  
open circuit  
→ LR circuit act  
as resistive

# Series LCR circuit

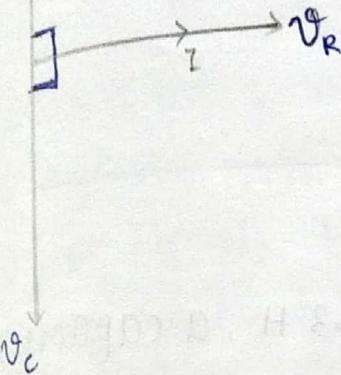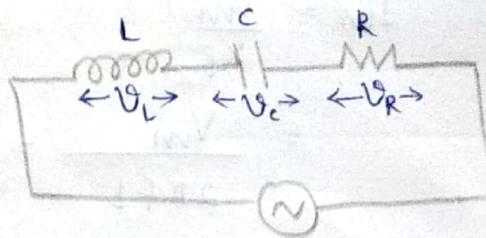

$$V = IR + jIX_L - jIX_C$$

$$V = I[R + j(X_L - X_C)]$$

$$Z = R + j(X_L - X_C) \text{ ; Impedance}$$

magnitude of  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

$$\cos \phi = \frac{R}{Z} \text{ ; power factor}$$

A 50 Hz, 230 V is applied to a 0.673 H inductor. Write the time equation for applied voltage and current through inductor assuming that when  $t=0, V=0$  and is going +ve.

$$V_{rms} = 230 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$L = 0.673 \text{ H}$$

$$V = V_{rms} \sin \omega t$$

$$V = 325.269 \sin \omega t = 325.269 \sin 314t$$

$$I = I_m \sin(\omega t - \pi/2)$$

$$V_m = V_{rms} \times \sqrt{2}$$

$$I_m = \frac{V_m}{X_L} = \frac{V_m}{\frac{2\pi f L}{2\pi \times 50 \times 0.673}} = \frac{325 \cdot 269}{211 \cdot 4291}$$

$$I_m = 1.5384 \text{ A}$$

$$I = 1.538 \sin(\omega t - \pi/2) \text{ A}$$

$$I = 1.538 \sin(314t - \pi/2) \text{ A}$$

\* A resistor of  $10\ \Omega$ , an inductor of  $0.3 \text{ H}$ , a capacitor of  $C$  are connected in series across  $230 \text{ V}, 50 \text{ Hz}$  main supply. ( $C = 100 \mu\text{F}$ ) calculate

- Impedance
- current
- $V_R, V_L, V_C$
- Power in Watts
- Power factor

UDSF GECT

$$\rightarrow i) X_L = 2\pi f L = 94.24$$

$$X_C = \frac{1}{2\pi f C} = \cancel{3.18} \quad 31.847$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{100 + 3892.886} = \underline{\underline{63.149}} \text{ } \Omega$$

$$ii) I_{rms} = \frac{V_{rms}}{Z} = \underline{\underline{3.64}} \text{ A}$$

$$iii) V_R = IR = 3.64 \times 10 = 36.4 \text{ V}$$

$$V_L = IX_L = 343.03 \text{ V}$$

$$V_C = IX_C = 115.923 \text{ V}$$

$$\text{High Power factor} \cos \phi = \frac{R}{Z} = \frac{10}{63.149} = 0.158$$

$$P = V_{\text{rms}} I_{\text{rms}} \cos \phi$$

$$P = 132.277 \text{ W}$$

A circuit takes a current of 3A at a power factor of 0.6 lagging when connected to 150V, 50Hz.

Another circuit takes a current of 5A at a P.F. of 0.8 lagging when connected to same supply. If these 2 circuits are connected in series to 230V, 50Hz supply, calculate current drawn from circuit

1st circuit : RL

2nd circuit : RC

Impedance of 1st circuit :

$$\text{case 1: } Z \cos \phi = 0.6 \\ \phi = -53.13^\circ$$

$$I_1 = 3 \text{ A} \\ = 3, \angle -53.13^\circ \text{ A}$$

$$I_2 = 5 \text{ A} \\ = 5 \angle 36.86^\circ \text{ A}$$

$$Z_1 = \frac{V}{I_1} = \frac{150}{3 \angle -53.13^\circ} = 50 \angle 53^\circ$$

$$Z_2 = \frac{V}{I_2} = \frac{150}{5 \angle 36.86^\circ} = 30 \angle -36.86^\circ$$

1st circuit :

2nd circuit :

$$Z_1 = 30.09 + j 39.93, \star 24.003 - 17.99j = Z_2$$

$$\therefore Z = Z_1 + Z_2 = 54.093 + j 21.94$$

$$I = \frac{V}{Z} = \frac{230}{\sqrt{(54.093)^2 + (21.94)^2}}$$

$$Z = |Z| < \theta$$

$$Z = 58.37 < 22.166$$

$$I = \frac{V}{Z} = 3.94 A$$

\* A series circuit with R and L draws a current of 1A when connected across 10V, 50 Hz supply. Assuming the resistance to be 5Ω, find inductance. What is the power factor? Draw phasor diagram.

→

$$I = 1 A$$

$$R = 5 \Omega$$

$$V = 10 V$$

$$f = 50 \text{ Hz}$$

UDSF GECT

$$Z = \frac{V}{I} = 10$$

$$\cos \phi = \frac{R}{Z} = \frac{5}{10} = \underline{\underline{0.5}}$$

$$V_R = IR \\ = 5 V$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$Z^2 = R^2 + (2\pi f L)^2$$


$$100 = 25 + 4\pi^2 \times 2500 \times L^2$$

$$75 = 4\pi^2 \times 2500 \times L^2$$

$$L^2 = 0.0007599$$

$$\therefore L = 0.0275$$

$$\therefore L = 2.7 \times 10^{-2} H$$

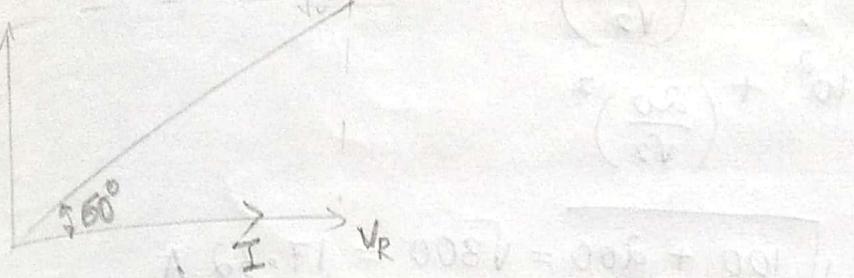

The apparent power drawn by an A.C. circuit is 10KVA and active power is 8kW. What is the reactive power? What is the power factor?

$$\text{power factor} = \frac{\text{active power}}{\text{apparent power}}$$

$$S = P + jQ$$

$$S = \sqrt{P^2 + Q^2}$$

$$S = 10 \text{ KVA}$$

$$P = 8 \text{ kVA}$$

$$10 \times 10^3 = \sqrt{(8 \times 10^3)^2 + Q^2}$$

$$10^8 = 64 \times 10^6 + Q^2$$

$$Q^2 = 10^8 - 0.64 \times 10^8$$

$$Q^2 = 0.36 \times 10^8$$

$$Q = \underline{\underline{0.6 \times 10^4}} = \underline{\underline{6 \text{ KVAR}}}$$

$$\text{power factor} = \frac{8}{10} = \underline{\underline{0.8}}$$

- \* Find the rms value of resultant current in a wire carrying simultaneous a dc 10A and sinusoidal ac of peak value 20A.

$$I_{dc} = 10 \text{ A}$$

$$I_m = 20 \text{ A}$$

$$i = I_{dc} + I_m \sin \omega t$$

$$i = 10 + 20 \sin \omega t$$

$$I_{rms}^2 = I_{dc}^2 + \left(\frac{Im}{V_2}\right)^2$$

$$= 10^2 + \left(\frac{20}{\sqrt{2}}\right)^2$$

$$I_{rms} = \sqrt{100 + 200} = \sqrt{300} = \underline{\underline{17.32 \text{ A}}}$$

\* The waveform of voltage and current of a circuit are given by  $E = 120 \sin(314t)$  and  $I = 10 \sin(314t + \pi/6)$ . calculate value of resistance and capacitance which are connected in series. Also draw waveform of  $V$ ,  $I$ , phasor diag. calculate power consumed by circuit

$\rightarrow$

$$E_m = 120 \text{ V}$$

$$\omega = 314$$

$$\phi = \pi/6$$

$$I_m = 10 \text{ A}$$

$$V_{rms} = \frac{120}{\sqrt{2}} \quad I_{rms} = \frac{10}{\sqrt{2}}$$

$$Z = \frac{V_{rms}}{I_{rms}} = \frac{120}{10} = \underline{\underline{12}} \quad Z\phi = 30^\circ$$

$$2\pi f = 314$$

$$f = 50 \text{ Hz}$$

$$Z = |Z| \angle \phi$$

$$Z = 12 \angle 30^\circ$$

$$Z = R + jX$$

$$Z = 6\sqrt{3} + 6j$$

$$R = 6\sqrt{3} = \underline{\underline{10.39 \Omega}}$$

$$X = 6$$


$$\frac{1}{2\pi f C} = 6$$

$$C = \frac{1}{2\pi f \times 6} = 5.3 \times 10^{-4} \text{ F} = \underline{\underline{530 \mu\text{F}}}$$

~~$$P = \cancel{V_{rms}^2 R}$$~~

$$P = V_{rms} \times I_{rms} \times \cos\phi$$
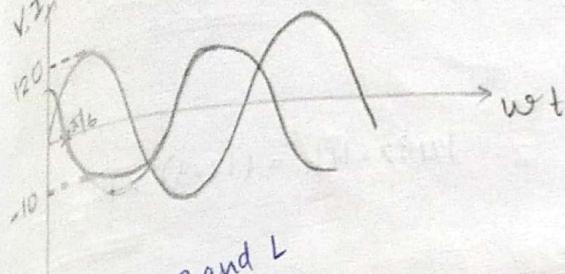
$$P = \frac{120}{\sqrt{2}} \times \frac{10}{\sqrt{2}} \times \frac{\sqrt{3}}{2} = \underline{\underline{519.61 \text{ W}}}$$



(coils) A and B are connected in series across 200V, 50 Hz AC supply. The power input to circuit ~~28~~ kW and 1.5 kVAR. If resistance of coil A is  $4\Omega$ , reactance is  $8\Omega$ , calculate resistance and reactance of coil B. Also calculate active power consumed by coil A and B, total impedance of circuit

$$V = 200 \text{ V}$$


$$f = 50 \text{ Hz}$$

$$R_A = 4 \Omega$$

$$X_A = 8 \Omega$$

$$P = 2.2 \text{ kW}$$

$$Q = 1.5 \text{ kVAR}$$

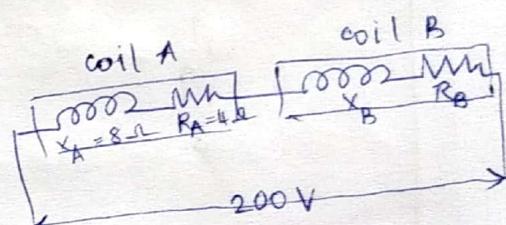

$$\begin{matrix} 4.84 \\ 2.25 \end{matrix}$$

$$S = P + jQ$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{(2.2)^2 + (1.5)^2} = 2.66 \text{ kVAR}$$

$$S = VI$$

$$I = \frac{2.66 \times 10^3}{200} = \underline{\underline{13.3 \text{ A}}}$$

~~$$V_A = IR_A = 13.3 \times 4 = 53.2 \text{ V}$$~~

~~$$V_B = 146.8$$~~

$$X_B = \frac{V_B}{I} = \underline{\underline{11.03 \Omega}}$$

$$P_A = I^2 R_A = (13.3)^2 \times 4 = 707.56 \text{ W}$$

$$P_T = P_A + P_B$$

$$P_B = 1492.44$$

$$R_B = 8.43 \Omega$$

Total impedance,  $Z = \frac{V}{I}$

$$Z = \sqrt{R^2 + X^2}$$

$$Z = \sqrt{R_A^2 + R_B^2 + X_A^2 + X_B^2}$$

$$\frac{V}{I} = \sqrt{R_A^2 + R_B^2 + X_A^2 + X_B^2}$$

$$\frac{200}{13.3} = \sqrt{16 + 71.0649 + 64 + X_B^2}$$

$$15.03 = \sqrt{151.0649 + X_B^2}$$

$$X_B = 15.03 - 12.290$$

$$X_B = 2.74$$

$$Z = \frac{V}{I} = \sqrt{(R_A + R_B)^2 + (X_A + X_B)^2}$$

$$15.03 = \sqrt{(12.43)^2 + (8 + X_B)^2}$$

solving,

$$X_B = 0.46 \Omega$$

$$P_A = I^2 R_A = 707.56 \text{ W}$$

$$P_B = I^2 R_B = 1491.18 \text{ W}$$

Total Impedance =  $\underline{\underline{?}}$

$$1492.44 = (13.3)^2 \times R$$