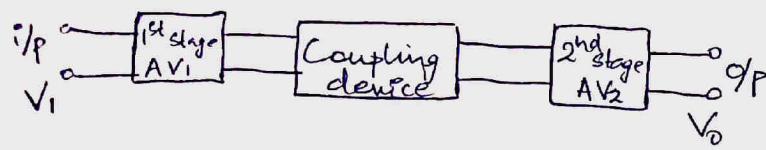


# MODULE-3

## MULTISTAGE AMPLIFIERS



$AV_1 \rightarrow$  gain of 1<sup>st</sup> stage  
 $AV_2 \rightarrow$  gain of 2<sup>nd</sup> stage

- In practical applications, situations may occur where single-stage amplifier becomes insufficient, so multistage amplifiers are used.
- Here output of 1<sup>st</sup> stage is coupled to the input of next stage using a coupling device (may be capacitor or transformer).
- The process of joining two amplifier stages using a coupling device is known as cascading.
- Overall gain = product of voltage gains of first & second stage.

$$\Rightarrow AV = AV_1 \times AV_2$$


→ Purpose of coupling device :-

- \* To transfer the AC from the output of one stage to the input of next stage.
- \* To block the DC to pass from the output of one stage to the input of next stage.

Types of coupling in multistage amplifier :-


- Transformer coupling - here transformer acts as coupling device
  - RC coupling - resistors and capacitors used.
  - Direct coupling - o/p of 1<sup>st</sup> directly connected to i/p of 2<sup>nd</sup>.
- (Coupling - how we connect  
of 1<sup>st</sup> to i/p  
of 2<sup>nd</sup> stage  
and so on...)
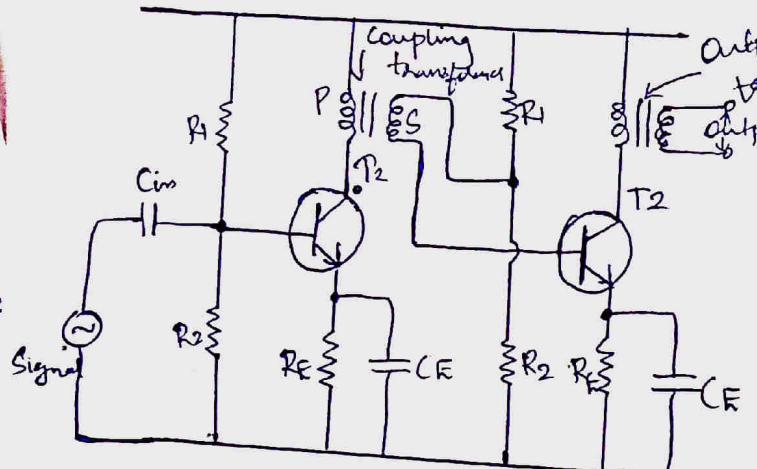
## KtuQbank transformer coupling Amplifiers




- 2 transistors are there.
- Resistor is not present here at collector side
- No capacitor also - to pass the signal from 1st to 2<sup>nd</sup> stage of transistors.
- Instead coupling transformer is placed there.

- Near output side also both collector resistor & capacitor is absent & the output is taken through output transformer
- Transformer allows only ac to pass & blocks dc.
- It contains current carrying coils, 1° winding P & 2° winding S.
- In b/w 2 windings iron core is kept (II), when current passes through 1° coil, due to the changes there current induces in 2° coil by mutual induction.
- Mainly instead of capacitor, transformer is used (both blocks and it brings signal from 1<sup>st</sup> to 2<sup>nd</sup> stage dc)
- $R_1$  &  $R_2$  → used for biasing purpose
- $R_E$  → for stabilization
- $C_E$  → acts as bypass capacitor

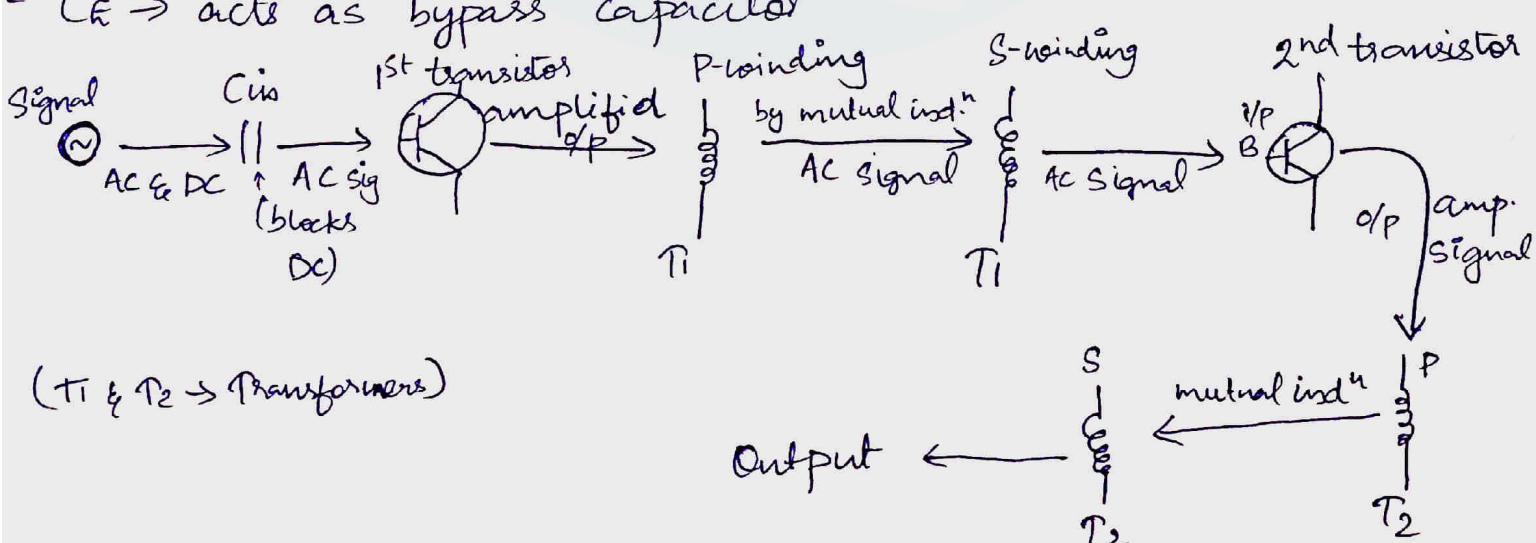

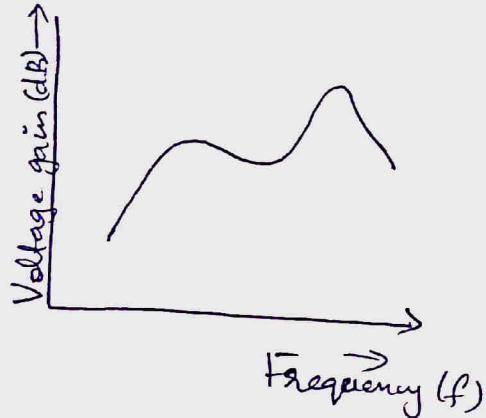→ **F**req**uency response curve of transformer coupled amplifier:**



- Voltage gain is not constant
- freqs. are amplified in different ways.
- This freq. response curve is not good
- If RC coupled, its mid-freq. range is constant.

→ Advantages of transformer coupled amplifier :-

- Excellent impedance matching is provided - so max power transfer occurs.  
(transferring power from one stage to next one)
- Since collector & resistance is absent, the gains achieved is higher (∴ there is no voltage drop).
- There will be no power loss in collector and base resistors
- Efficient in operation


→ Disadvantages :-

- Poor frequency response (not const. voltage gain)
- Freq. distortion is higher
- Transformers tend to produce hum noise.
- Transformers are bulky & costly.

→ Applications :-


- Mostly used for impedance matching purposes.
- Used for power amplification
- Used in applications where max. power transfer is needed  
(for voltage amplification - RC coupled amplifiers are used)

## KtuQbank Directly Coupled Amplifier

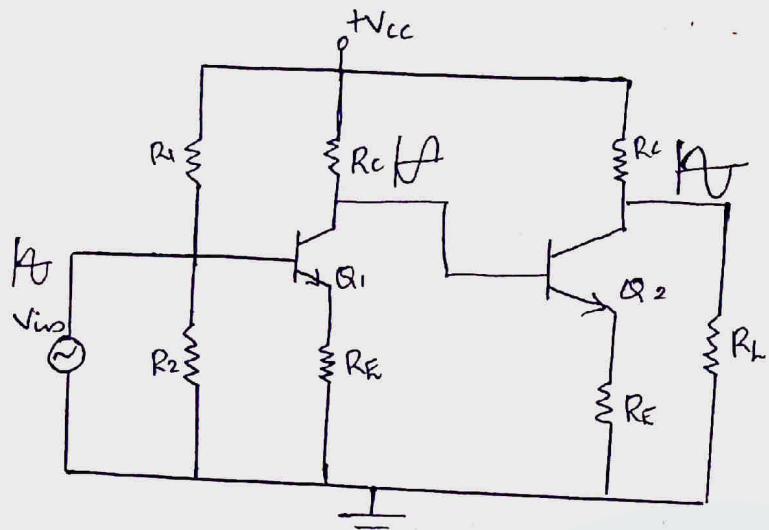

- capacitors are not at all used
- It is used to amplify low freq signals.  
 $f < 10\text{Hz}$
- ind., cap, transformers are not used b/c its electrical size is very large when used at low freq range.

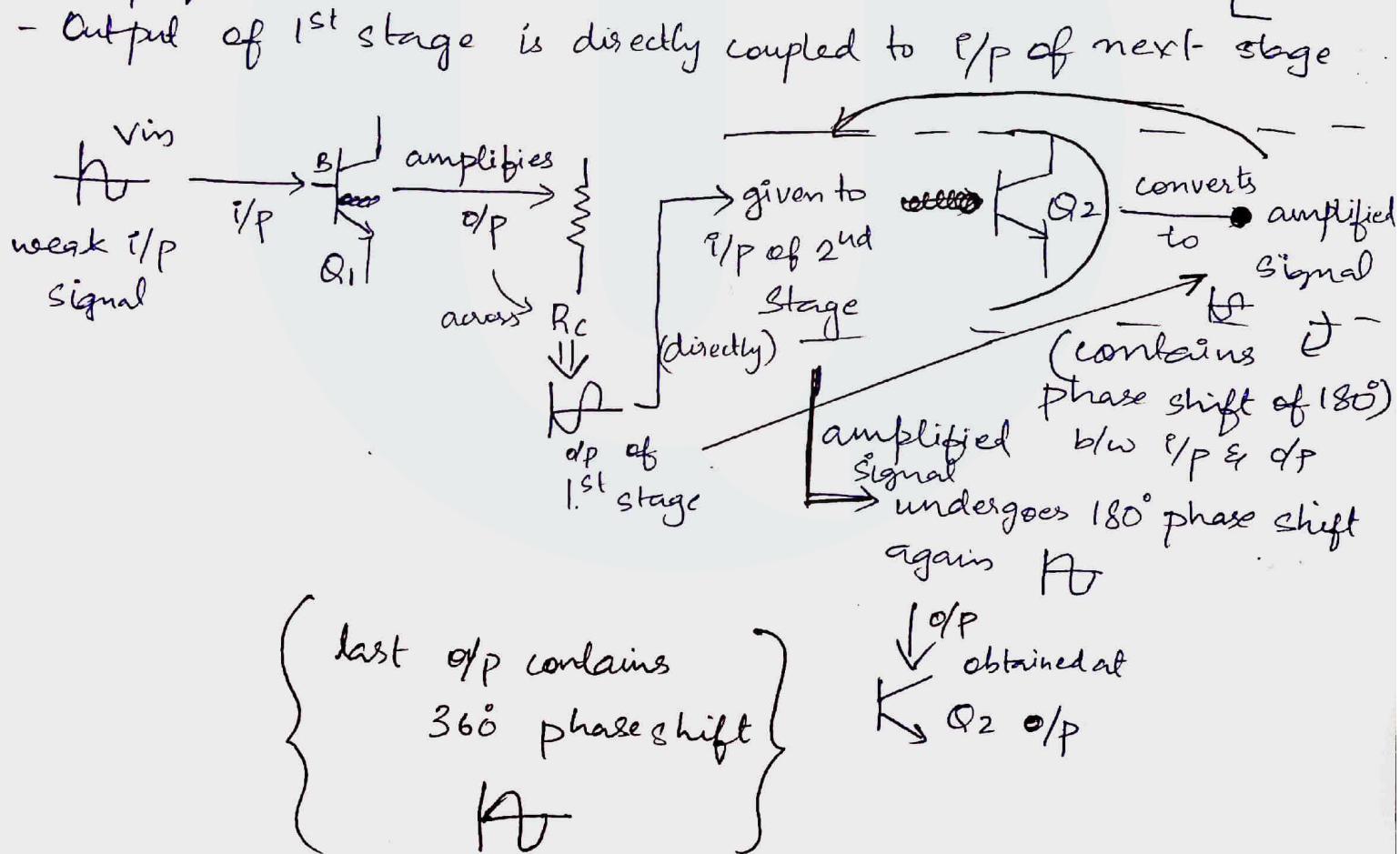- At first stage, voltage divider biasing is used (includes  $R_1, R_E, R_2$ )
- VD biasing is necessary to keep the <sup>(operating pt)</sup> exactly at the centre of load-line so that transistor  $Q_1$  will work as an amplifier.
- Output of 1<sup>st</sup> stage is directly coupled to i/p of next stage



### Applications :

- Headphones, loud speakers.


Ktu Q bank

- Excellent freq. response
- Low cost
- Simple circuit & min resistors are used
- Amplify very low freq. signals (both ac & dc)

Disadvantages :-


- Not suitable for high freq. Signals
- No coupling capacitors (dc from 1st enters 2nd stage) both ac & dc
- Output changes with temp.

### ③ RC Coupled Amplifier

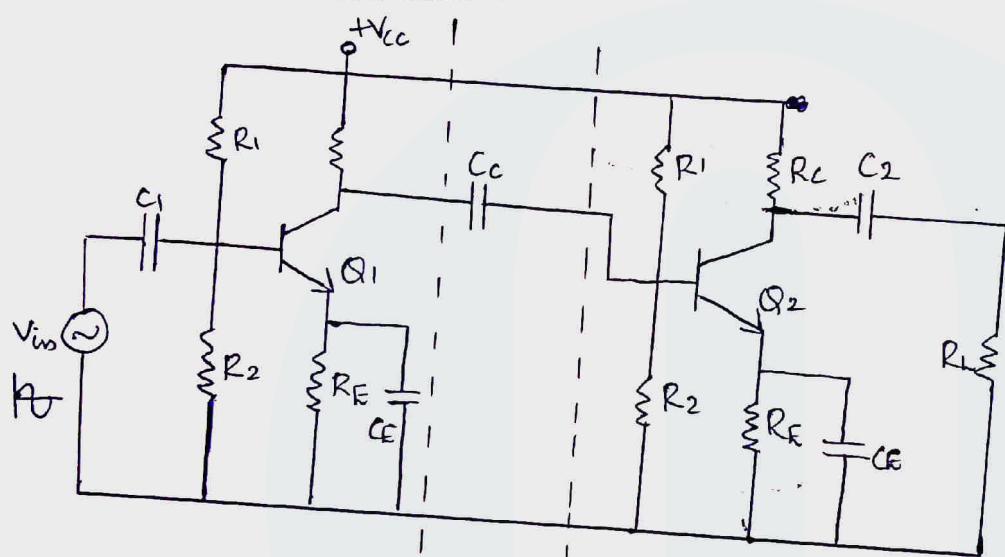

- $R_1, R_2, R_E \rightarrow$  voltage divider biasing
- $Q_1 \& Q_2 \rightarrow$  2 stages
- $C_c \rightarrow$  coupling cap. which couples o/p of 1<sup>st</sup> to i/p of 2<sup>nd</sup>.

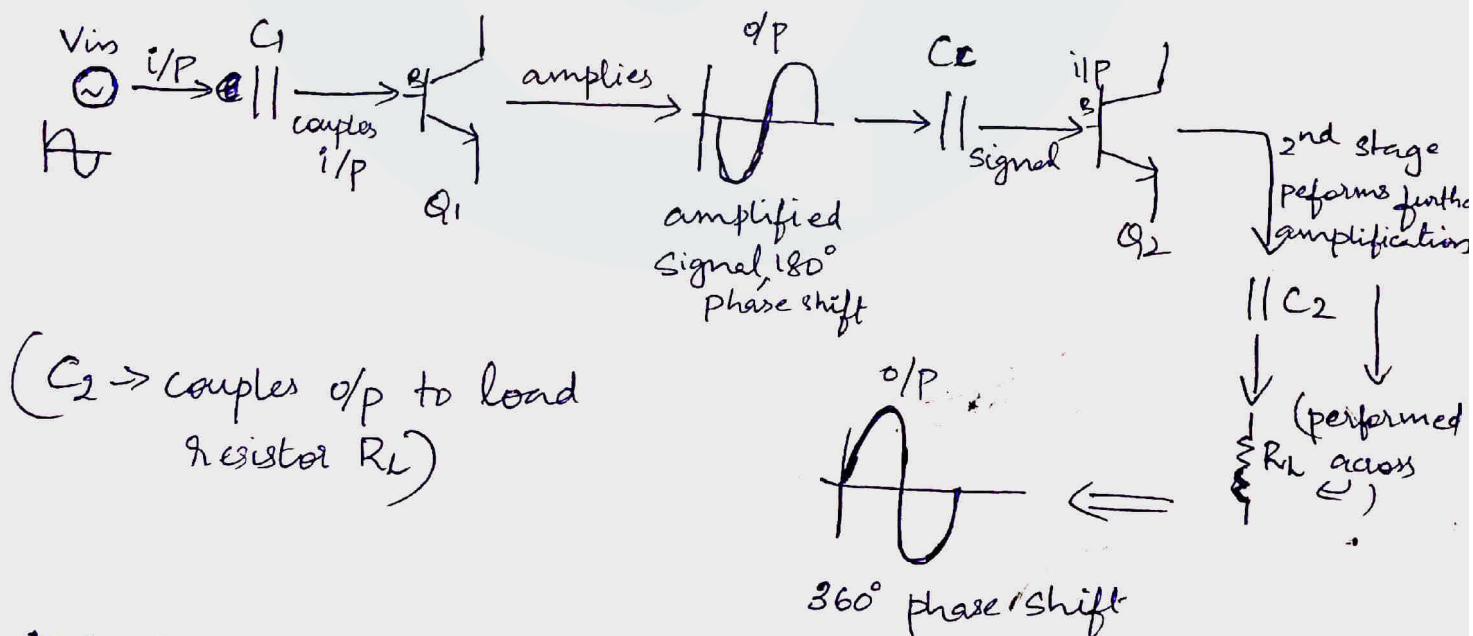-  $R_C$  &  $C_C$  present  $\rightarrow$  RC Coupled Amplifier



Application:

- used for voltage amplification


## KtuQbank Advantages:

- Simple Network
- Cost effective
- req. less space & weight
- mostly used in audio freq. range
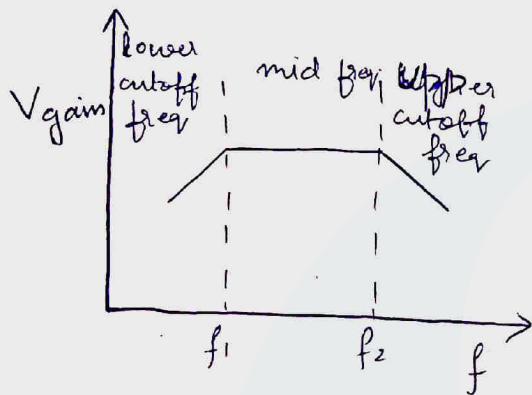
## Disadvantages:

- Not used for impedance matching network
- Not having great gain
- Noise is high

→ Frequency response curve of RC coupled amplifier :-



- Voltage gain drops at low freq (< 50Hz) and high freq (> 20kHz)
- Voltage gain remains const. at mid freq. range

$$X_C = \frac{1}{2\pi f C}$$

\*- If  $f \downarrow$ ,  $X_C \uparrow$ : So only small part of signal passes from 1st to 2nd stage.


- Emitter bypass capacitor cannot shunt emitter resistor effectively b/c of this large reactance at low freq.

- Thus voltage gain drops

\*- If  $f \uparrow$ ,  $X_C \downarrow$ , so reactance of coupling capacitor will be very small, so it becomes like a short circuit.

- This low reactance affects the transistor i.e. voltage gain drops.

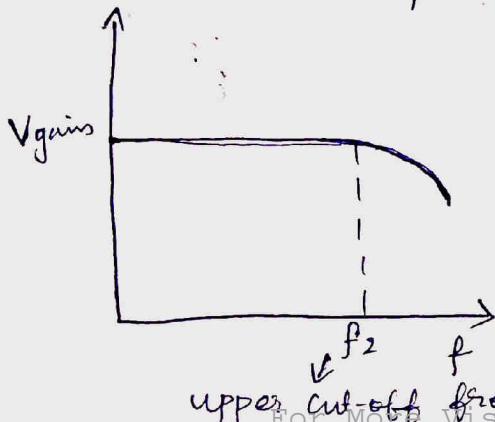→ Frequency response curve of Direct coupled amplifier :-



- no voltage drop at low freq (b/c coupling or bypass capacitors are absent), so constant
- After  $f_2$ , voltage gain reduces due to inter-electrode cap. & wiring cap. (stray cap)
- Inter electrode cap causes undesirable effect on the fun' of electrical comp. & circuits.

## POWER AMPLIFIERS (Large Signal Amplifier)

- Used when high power requirements are there  
eg: Audio amplifier, Antenna.
- Some BJTs have certain limitations, so power BJTs can be used  $\Rightarrow$  so power amplifiers are (less power dissipation) used. not wastage
- Parameters include distortion (linear)
- Depending on the rating of current & voltage, power BJT or Power Mosfet can be checked.
- Conventional BJT & JFET has limitations such as:
  - \* current handling capacity is not more than 0.8A.
  - \* cannot handle voltage more than 100V.
  - \* temp. " capacity is upto 150°C only.
- So power amplifiers are used.
- It is <sup>also</sup> called as Large signal amplifier b/c conventional BJT & JFET uses only less current or voltage, so Q<sub>pt</sub> or operating pt. varies only in a small range of current or voltage. But in power amplifiers large amount is used so large signals are used or considered and there is the analysis of large signal; hence the name large signal amplifier.


→ It can be classified into :-

- \* Class A power amplifiers
- \* Class B "
- \* Class AB "
- \* Class C "


→ Classification is based on :-

- Angle of conduction
- Efficiency
- Position of operating pt
- Distortion
- Application

## KtuQbank A power amplifier

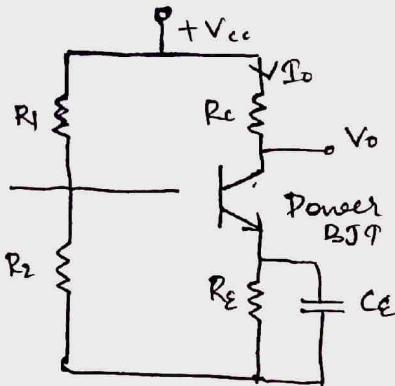


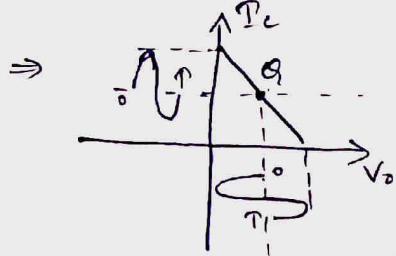- ~~high~~<sup>low</sup> distortion
- Q pt. will be always in active regions
- conduction angle is from  $0 - 2\pi$  (360°) for the signal (no clipping occurs)
- low efficient (65%)
- simple circuit



- It is used in 1st step amplification of outdoor communication circuits/systems
- eff. will not exceed 50%.

## → Class AB power amplifier

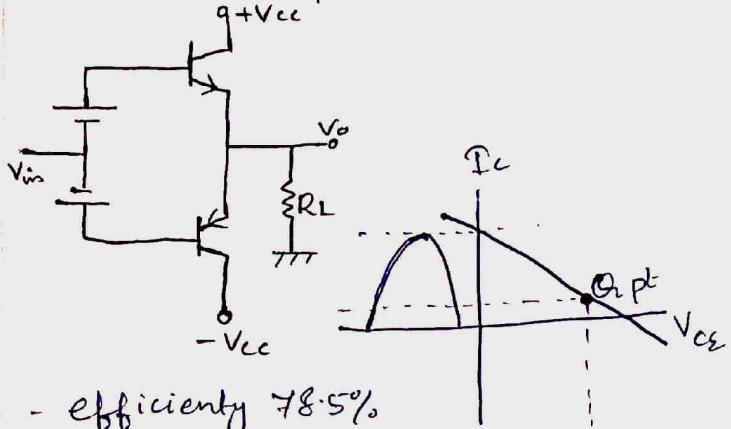


- efficiency 78.5%
- Q pt is near to & just below the active regions
- conduction angle is >180° but <360°
- distortions are less but a cross over dist. will be present which can be solved by changing the ckt. i.e. Voltage is supplied for both transistors.

→ This amplifier ckt is called complementary-symmetry power amplifier circuit b/c the transistors used are comp. in nature.

→ radio-freq. amplifiers uses this

## → Class C power amplifier

### → Class B power amplifier

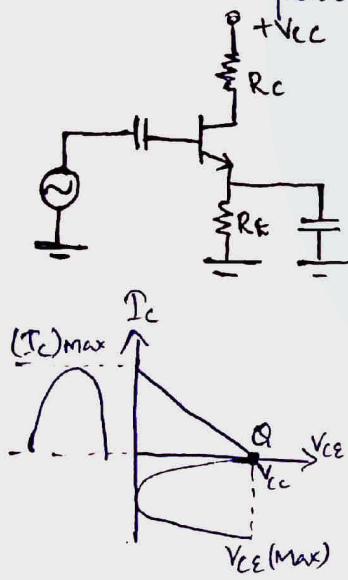


- conduction angle is 0 - 180° (for half i/p cycle only)
- efficiency is about 78.5%
- Q pt. will be in cut-off region
- disadvantages of class A is solved here.

- distortions are more when compared to class A
- used in audio amplifiers.

→ Q pt is placed below the cutoff region

- conduction angle is very low ( $\approx 60^\circ$ )
- efficiency is high, 95% ( $< 180^\circ$ )
- maximum distortions
- audio power amplifiers used this class C.
- used in communication systems

Ktu Q bank  
Class A power amplifier

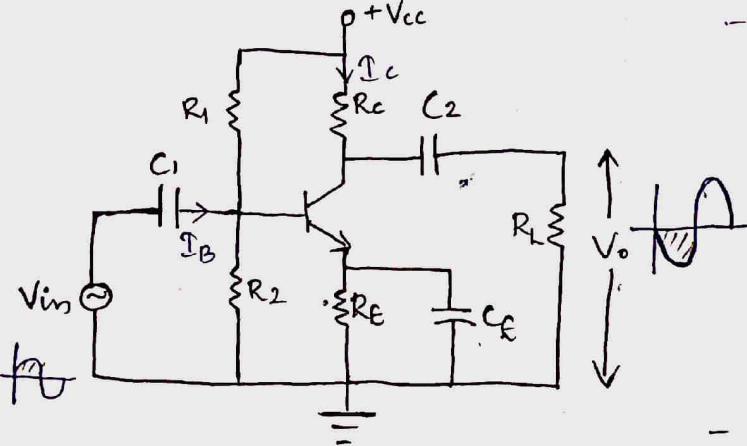

- ckt diagram is similar to single stage CE amplifier only diff is power transistor is used here instead normal transistor and RE is directly coupled to the transistor i.e. directly coupled trans.

- only one transistor is used here in amplifier stage (single ended)

- This amplifier is also called as <sup>power</sup> single ended - class A <sub>amplifier</sub>.

-  $R_1, R_2, R_E \rightarrow$  forms voltage divider biasing ckt

-  $C_1$  &  $C_2 \rightarrow$  coupling capacitors  $C_1 \rightarrow$  couples i/p to base of trans.

-  $C_E \rightarrow$  bypass cap.  $C_2 \rightarrow$  connects o/p to  $R_L$ .

- bypasses all emitter current to the ground hence voltage drop across  $R_E$  will be less, voltage gain  $\uparrow$ s.

- output current will flow for the entire cycle of i/p signal. &  $180^\circ$  phase shift b/w i/p & o/p signal & amplified o/p is obt.

### Working:

- During the first half cycle,  $I_B$  flows through the base terminal of transistor,  $V_{CC}$  supplies collector current  $I_C$ .

$$I_C = \beta \cdot I_B \quad \beta \rightarrow \text{current gain}; \text{ as } I_B \uparrow s, I_C \uparrow$$

$$\text{o/p voltage } V_{CE} = V_{CC} - I_C(R_C + R_E).$$

when  ~~$I_B$~~   $I_C \uparrow s$  &  $V_{CC}$  remains const  $\Rightarrow V_{CE} \downarrow s$ .

due to  $V_{CE} \downarrow$ , we get a negative half cycle in the o/p


- During -ve half cycle, reverse happens.

$$I_B \downarrow s, I_C \downarrow s \Rightarrow V_{CE} \uparrow s$$


i.e. we get a +ve half cycle in the o/p



Ktu Q bank  
load - line variations

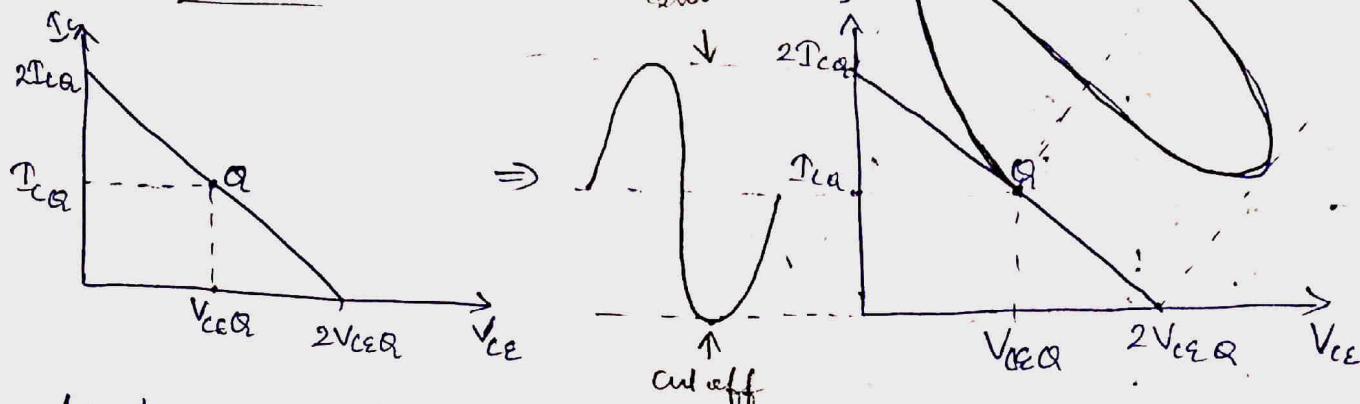


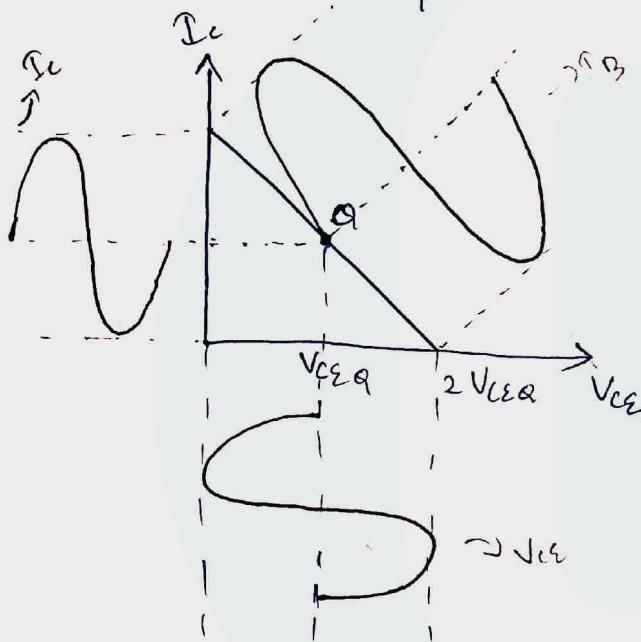- As base current  $I_B$  rises from  $Q$  pt. in the +ve & -ve half cycle, the output current  $I_c$  also changes from  $Q$  pt  $I_{cQ}$  to  $2I_{cQ}$  & it attains max pt. at 0.



- Output voltage varies from  $V_{ceQ}$  to zero during the half cycle & from  $V_{ceQ}$  to  $2V_{ceQ}$  during -ve half cycle.


→ Class B push pull power amplifier

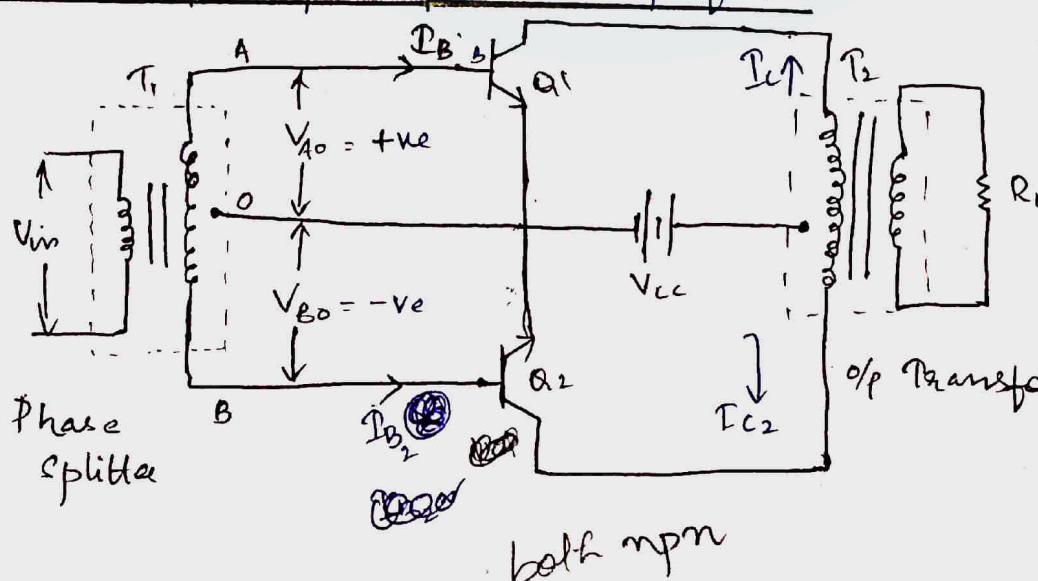

- During the half cycle :  
 $I_B$  flows  
 $I_{B2} \times$   
 $I_c$  flows
- -ve half cycle  
 $I_B \times$   
 $I_B \checkmark$   
 $I_{c2} \checkmark$

Ktu Q bank Here the transistor biasing & the input signal will flow in such a way that the output current is available only for the half input. (cond<sup>n</sup> angle  $\rightarrow 0-180^\circ$ )

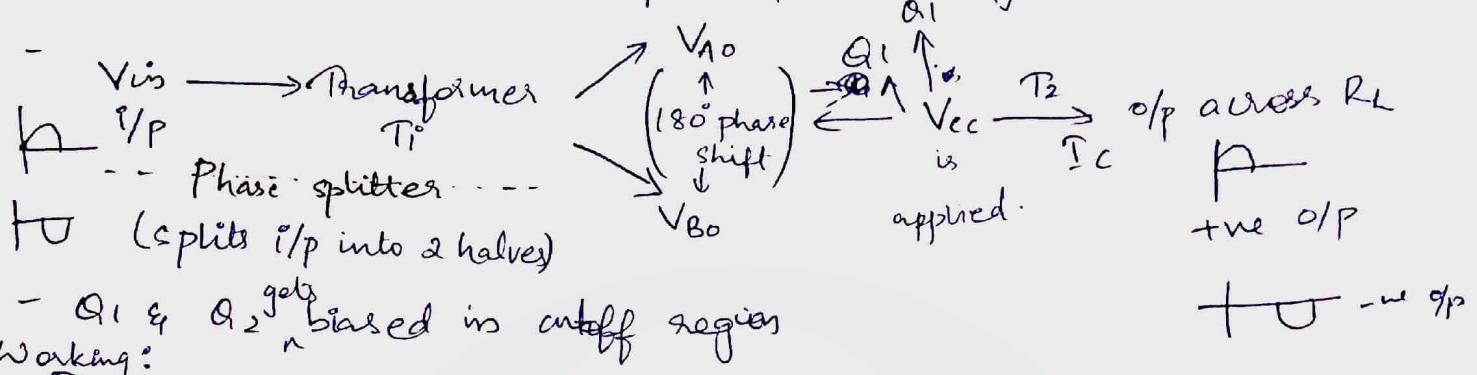- So 2 transistors are used to get the entire output (full range). and this is called as push pull arrangement of transistors



- Q<sub>1</sub> & Q<sub>2</sub> get biased in cutoff region

Working:

- During the half cycle of i/p signal, V<sub>A0</sub> will be +ve & V<sub>B0</sub> will be -ve. the voltage is given to base-emitter junction of transistor Q<sub>1</sub>, so it undergoes forward biasing. -ve voltage to Q<sub>2</sub> undergoes reverse biasing.
- Since Q<sub>1</sub> is forward biased, it acts as a closed switch & Q<sub>2</sub> reverse biased, acts as open switch.
- So I<sub>B</sub> flows through Q<sub>1</sub> & I<sub>B2</sub> will not flow through Q<sub>2</sub>.
- As I<sub>B</sub> flows through Q<sub>1</sub>, I<sub>C</sub> also flows through it and the 1<sup>o</sup> winding of transformer is coupled to 2<sup>o</sup> winding and we will get a positive half cycle across R<sub>L</sub>. P → P
- During -ve half cycle, reverse happens.
  - I<sub>B2</sub> flows Q<sub>2</sub> & I<sub>C2</sub> also flows through it.
  - Thus we get -ve half cycle as output across R<sub>L</sub> H → H

⇒ During : the half cycle

Q<sub>1</sub> is on  
Q<sub>2</sub> is off  
⇒ +ve o/p

-ve half cycle


Q<sub>1</sub> is off  
Q<sub>2</sub> is on  
⇒ -ve o/p

KtuQbank during +ve & -ve half cycle, one transistor is pushed in to conduction & other one is pulled out of it which is referred to as push-pull method and called as push-pull amplifier.

→ Advantages of Class B amplifier:-

- Efficiency = 78.5%
- Eliminates harmonic distortions at o/p
- It has maximum o/p

### • Class AB power amplifier

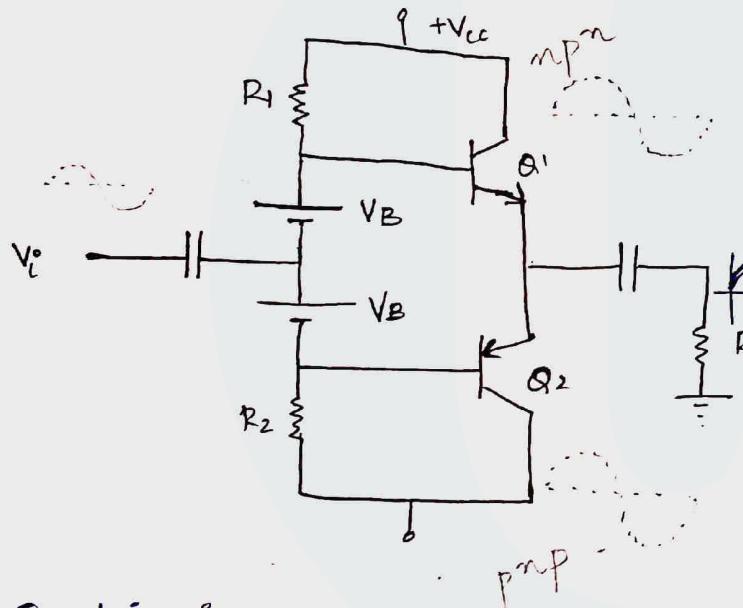

- Q1 & Q2 are complementary to each other

- 2 VB voltages are used to avoid cross-over dist.


(when one signal is moved from one trans to another one, dist occurs in its o/p wave shape)

Working :-


- During +ve half cycle, Q1 conducts & Q2 is cutoff and vice versa
- In -ve half cycle, Q2 conducts & Q1 cutoff.

will be less

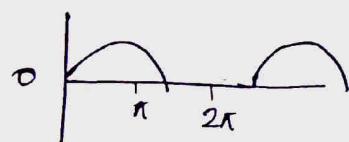→ o/p half cycle ( $\pi$ ) but less full cycle ( $2\pi$ )  
→ cond'g angle  $>\pi, <2\pi$




o/p wave form

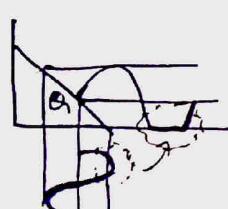


→ Q pt is placed b/w active & cutoff regions

- efficiency 50-60%

## KtuQbank C power amplifier

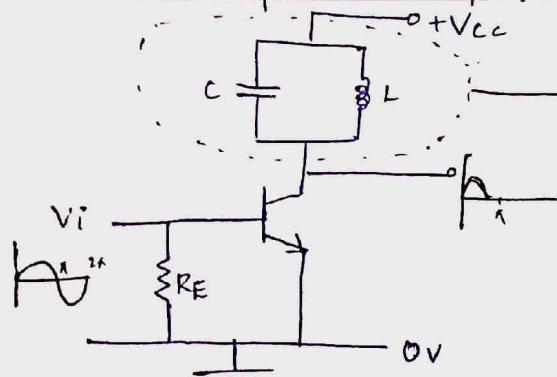

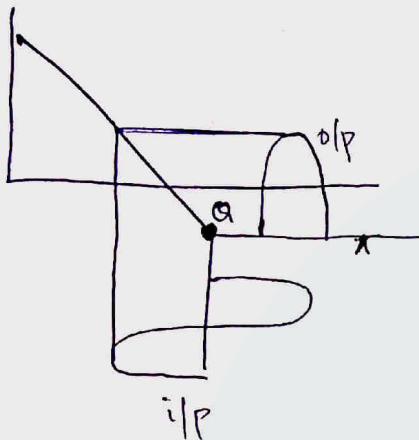- used for high frequency purposes
- tanked portion (comb' of C & L in parallel)
- due to this tanked circuit, it is called as tuned power amplifier




- Q is below cutoff region
- disadvantage: dist. angle  $< 120^\circ$  (b/w  $60^\circ$  &  $120^\circ$ )
- Operated in high freq. region
- used for analog applications (not digital)
- efficiency  $> 90\%$
- heavy distortion, not suitable for audio amp.

## → Feedback:

- process of giving O/P back to I/P signal
- either full O/P or a part of signal is given

Two types -

- Positive feedback

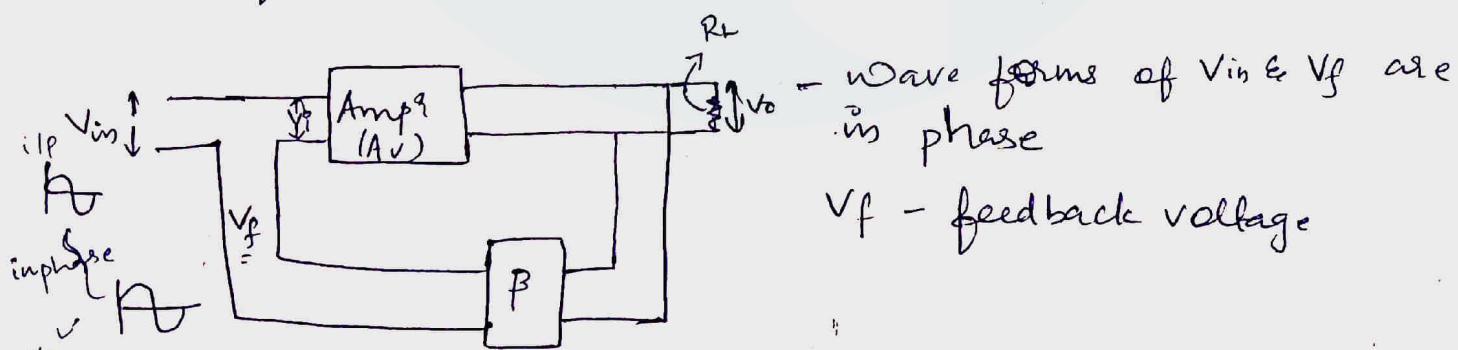


- here a part of O/P voltage which is applied back to I/P
- Both signals I/P signal & part of O/P given to I/P gets added since they are in phase.

Ktu Q bank will be greater for the feedback ( $V_{in} + V_f$ ) is given to  
 → the feedback = regenerative feedback amplifier


$$V_i = V_{in} + V_f$$

### • Negative feedback

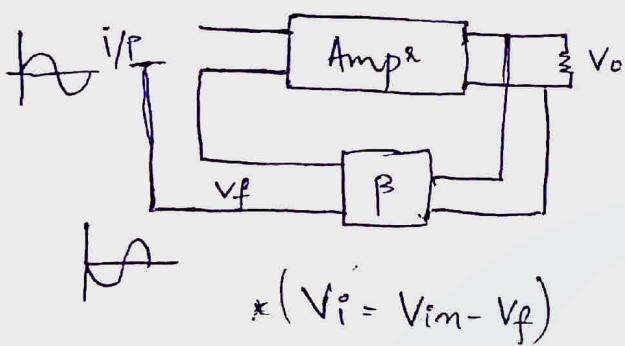


- a part of o/p is given to i/p but less b/c both are out of phase i.e o/p & i/p signal are out of phase
- ⇒  $V_i \downarrow$  since both gets subtracted
- -ve feedback = degenerative feedback

→ Gain (without feedback) :

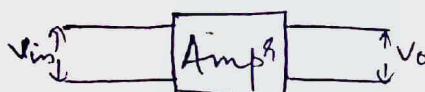

$$A_V = \frac{V_o}{V_{in}} = \frac{\text{o/p voltage}}{\text{i/p voltage}}$$

→ Gain (with feedback) :

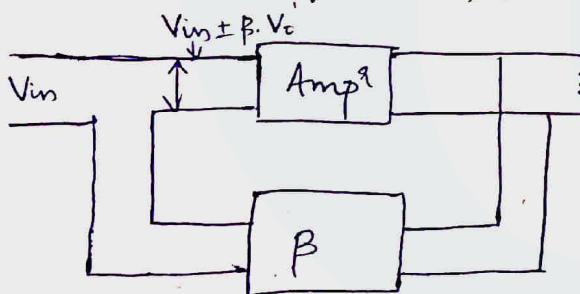

- $\beta$  - feedback factor
- output voltage with feedback  $V_o'$

$$- V_i \text{ given} = V_{in} \pm \beta \cdot V_o'$$

$$\rightarrow A_V = \frac{V_o'}{V_{in} \pm \beta \cdot V_o'}$$

$$A_{vf} = \frac{V_o'}{V_{in} + \beta \cdot V_o'}$$

- the fb:

$$A_V = \frac{V_o'}{V_{in} - \beta \cdot V_o'}$$

- ve fb.

Gain (for the fb)

$$A_V = \frac{V_o'}{V_{in} + \beta \cdot V_o'}$$

$$\Rightarrow A_{vf} = \frac{A_V}{1 - \beta \cdot A_V}$$

$\Rightarrow A_{vf} > A_V$

for -ve f.b :

$$A_{vf} = \frac{A_V}{1 + \beta \cdot A_V}$$

$$\Rightarrow A_{vf} < A_V$$

- +ve feedback where voltage gain  $A_s$  is used in oscillator ckt.
  - -ve " " "  $\downarrow s$  " amplifier ckt.

~~vin~~

\* BARKHAUSEN'S CRITERION (applicable for oscillators) (the fb is used)

$$A_{vp} = \frac{Av}{1 - \beta Av}$$

$\Delta v_f = \sqrt{\text{gain with } f_b}$

$A_v = v$  gain without  $P_b$ /open loop gain

- \* If  $\beta A V$  becomes 1,


$$Avf = \frac{Av}{2} \Rightarrow Avf = \infty$$

$$A_{vf} = \frac{V_o}{V_{in}} \rightarrow V_{in} = 0$$

i.e. the oscillators do not require input signal

- \* - So necessary cond<sup>n</sup> for producing oscillations is that input signal should not be given.

$$\textcircled{1} \quad \beta A v = 1$$

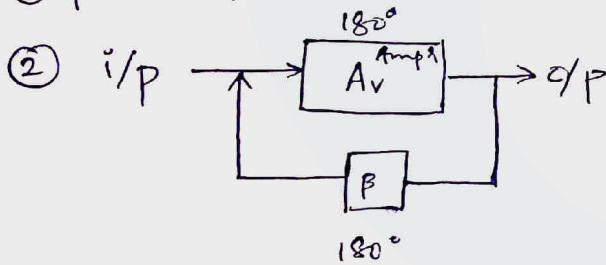


- 1<sup>st</sup> i/p is given  $\Rightarrow 180^\circ$  phase shifted o/p
  - 2<sup>nd</sup> part of this o/p again phase shift given as i/p. (feedback signal)  $^{180^\circ}$
  - both i/p & fd signal are in phase

- closed loop gains


$$\angle B \cdot A V = 0^\circ \text{ or } 360^\circ$$

## RC Oscillatore

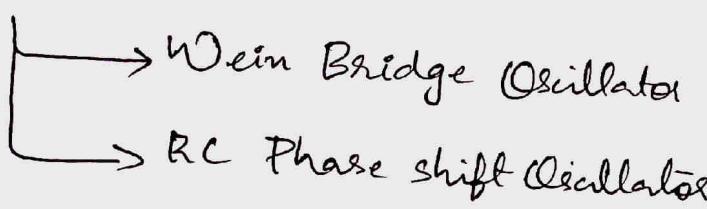


- Tuned LC oscillators
  - Hartley oscillator
  - Colpitts "
  - Tuned collector &

# Wein Bridge Oscillator

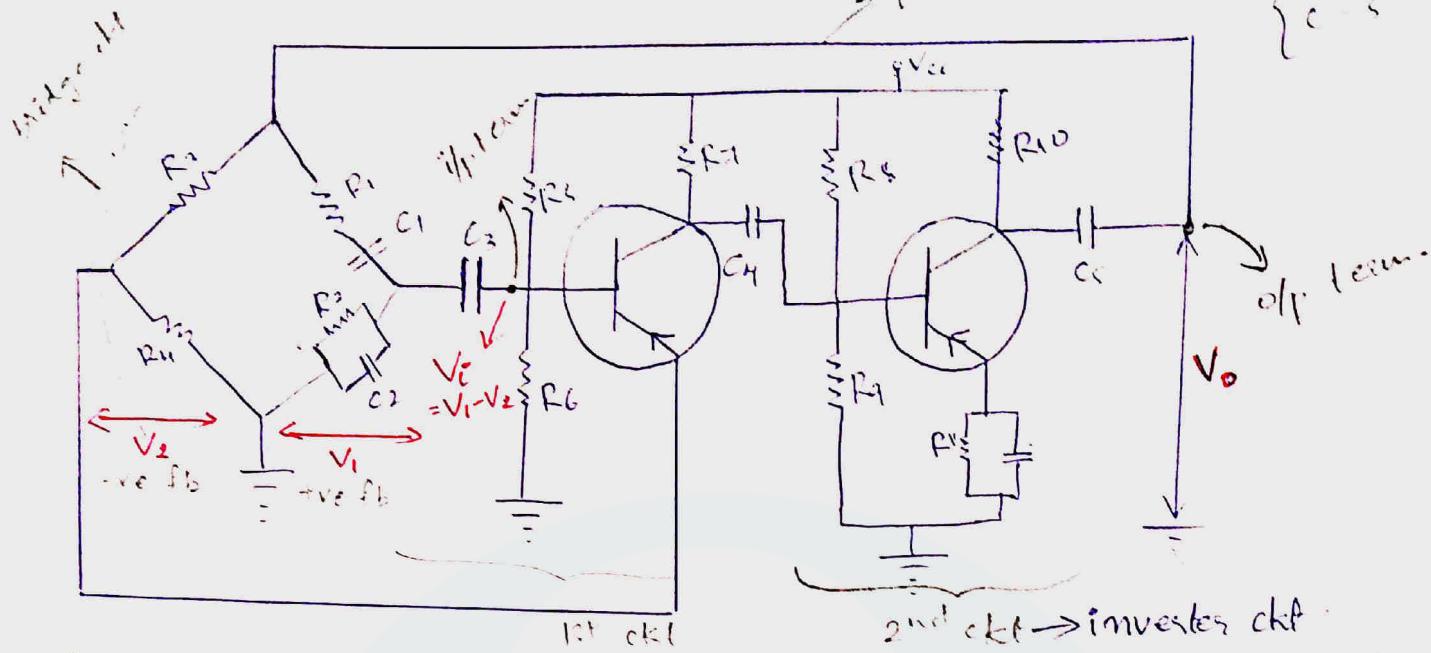

- 2 common emitter transistors are present - pnp. & connected in voltage divider biasing arrangement.
- from the o/p <sup>of 1<sup>st</sup></sup> transistor it connected to next <sup>transistor</sup> by a coupling capacitor  $C_4$
- $C_5$  - coupling cap., kept at o/p of 2<sup>nd</sup> transistor, and through this transistor is feedbacked to a bridge ckt
- $C_3$  - connects bridge ckt to base of 1<sup>st</sup> transistor
- we must get a phase shift of  $360^\circ$  so 2 transistors are kept and 2<sup>nd</sup> portion of ckt is called inverter ckt (makes  $180^\circ$  phase shift again as we need  $360^\circ$ )
- 1<sup>st</sup> ckt acts as a oscillator & an amplifier
- oscillations from oscillator are damped so to make it undamped a feedback network is provided which connects to bridge ckt i.e used for stabilization.
- oscillator  $\rightarrow$  dc to ac converter
- for an amplifier to act. as an oscillator it should follow 3 criteria :-
  - negative fb
  - $A_{v,p} = 1$
  - $L_p A_v = 360^\circ \text{ or } 0^\circ$
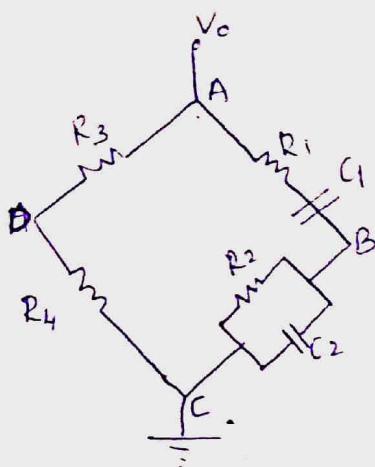
## Mathematical Analysis for Wien Bridge Oscillator :-



For Balanced bridge,

$$\frac{R_3}{R_4} = \frac{R_{AB}}{R_{AC}}$$

$$\frac{R_3}{R_4} = \frac{\frac{R_1 + j\omega C_1}{R_2 j\omega C_2}}{R_2 + j\omega C_2} = \frac{\left[ R_1 + \frac{1}{j\omega C_1} \right]}{\left[ R_2 + \frac{1}{j\omega C_2} \right]}$$

$$\text{Suppose } R_1 = R_2 = R \\ C_1 = C_2 = C$$

$$\Rightarrow \frac{R_3}{R_4} = \frac{\left[ R + \frac{1}{j\omega C} \right] \left[ R + \frac{1}{j\omega C} \right]}{\left[ \frac{R}{j\omega C} \right]}$$

$$\Rightarrow \frac{R_3}{R_4} = \frac{j\omega C}{R} \left[ R^2 + \frac{1}{j^2 \omega^2 C^2} + \frac{2R}{j\omega C} \right]$$

$$\frac{R_3}{R_4} = \frac{j\omega C}{R} \left[ R^2 - \frac{1}{\omega^2 C^2} \right] + 2$$

Compare real parts on both sides,

$$\Rightarrow \frac{R_3}{R_4} = 2 \Rightarrow R_3 = 2R_4 \quad \text{--- (1)}$$

Compare img. parts,

$$0 = \frac{\omega C}{R} \left[ R^2 - \frac{1}{\omega^2 C^2} \right]$$


$$R^2 - \frac{1}{\omega^2 C^2} = 0 \rightarrow R = \frac{1}{\omega C} \Rightarrow \omega = \frac{1}{RC}$$

$$\text{also } \omega = 2\pi f \Rightarrow 2\pi f = \frac{1}{RC}$$

$$\therefore f = \boxed{\frac{1}{2\pi RC}}$$

## KtuQbank

### RC Phase Shift Oscillator

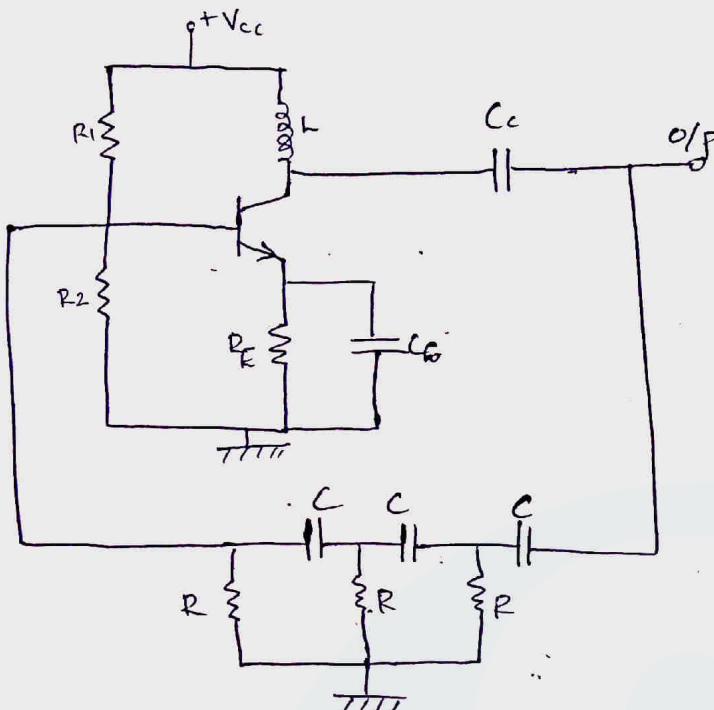

- Also called as an sine waves oscillators (prod. sine waves)
- used for producing audio-freq. signals (20Hz - 20kHz)
- (for high freq. LC osc used)
- upper part  $\rightarrow$  amplifier
- lower "  $\rightarrow$  RC components (3)
- Resonance freq,

$$f = \frac{1}{2\pi\sqrt{RC}}$$


- we know  $A_{VP} = 1$   
also gain  $A_V = 29$

$$\Rightarrow \beta = \frac{1}{29}$$

Working :-


- each RC produces  $60^\circ$  phase shift, total  $180^\circ$
  - CE amplifier also prod:  $180^\circ$
- }  $360^\circ$  phase shift  
cond<sup>n</sup> for the fb  
oscillator

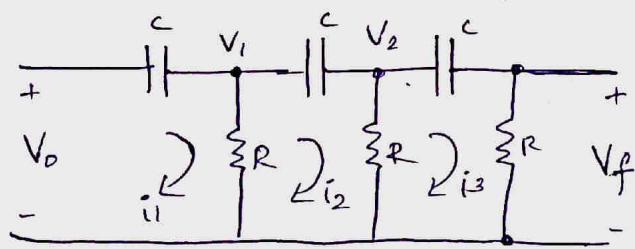Frequency of RC phase shift oscillator :-




$$V_f = i_3 \cdot R$$

$$\Rightarrow i_3 = \frac{V_f}{R}$$

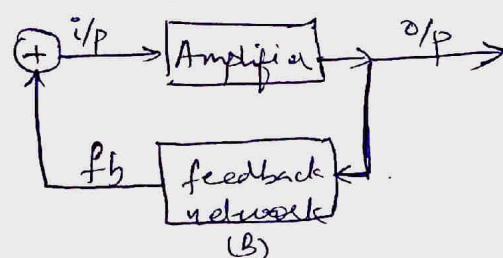

KtuQbank  
Node 2, apply KVL,

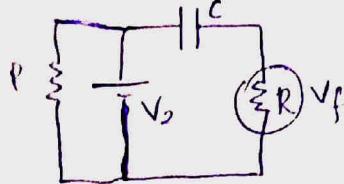


$$\Rightarrow V_2 = V_C + V_f$$

$$V_2 = V_f + i_2 \times X_C$$

$$V_2 = V_f + \frac{V_f}{j\omega C} - V_f + \frac{V_f}{j\omega RC}$$

$$\left\{ V_2 = V_f \left( 1 + \frac{1}{j\omega RC} \right) \right\} - ①$$

② At Node 2, apply KCL,

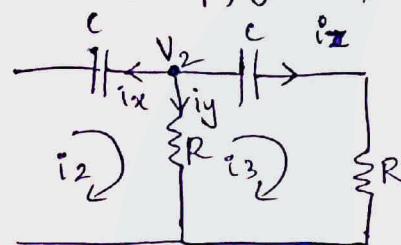

$$i_x + i_y + i_2 = 0 \quad i_x = -i_2$$

$$-i_2 + i_y + i_3 = 0 \quad i_z = i_3$$

$$i_2 = i_y + i_3$$

$$i_2 = \frac{V_2}{R} + \frac{V_f}{R}$$

Sub ① here,

$$i_2 = \frac{V_f}{R} \left( 1 + \frac{1}{j\omega RC} \right) + \frac{V_f}{R}$$

$$\left\{ i_2 = \frac{V_f}{R} \left( 2 + \frac{1}{j\omega RC} \right) \right\} - ②$$

③ At Node 1, apply KVL

$$V_1 = V_C + V_2$$

$$V_C = i_2 \cdot X_C$$

$$V_f = V_2$$

$$V_C = i_2 \times \frac{1}{j\omega C}$$

$$V_1 = V_2 + \frac{i_2}{j\omega C}$$

Subs. ① here,

$$\Rightarrow V_1 = V_f \left( 1 + \frac{1}{j\omega RC} \right) + \frac{1}{j\omega C} \left( \frac{V_f (2 + \frac{1}{j\omega RC})}{R} \right)$$

$$\left\{ V_1 = \frac{V_f}{j\omega RC} \left( 3 + j\omega RC + \frac{1}{j\omega RC} \right) \right\} - ③$$

④ Apply KCL at node 1,



$$\left\{ \begin{array}{l} i_1 + i_2 + i_Z = 0 \\ i_Z = -i_1 \quad i_Z = i_2 \end{array} \right.$$

$$\Rightarrow i_1 = i_2$$

$$i_1 = \frac{V_1}{R} + i_2$$

Subs. ② and ③ here,

$$i_1 = \frac{V_f}{j\omega RC} \left( 3 + j\omega RC + \frac{1}{j\omega RC} \right) + \frac{\frac{V_f}{R} \left( 2 + \frac{1}{j\omega RC} \right)}{j\omega RC}$$

$$\frac{V_f}{R} \left( 2 + \frac{1}{j\omega RC} \right)$$

$$\Rightarrow i_1 = \frac{V_f}{R} \left[ \frac{3}{j\omega RC} + 1 + \frac{1}{j^2 \omega^2 C^2} + 2 + \frac{1}{j\omega RC} \right]$$

$$\left\{ i_1 = \frac{V_f}{R} \left[ 3 + \frac{4}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right] \right\} - ④$$

⑤ At node V0:

$$V_0 = V_C + V_1$$

$$V_C = i_1 \times X_C$$

$$\text{Sub } V_0 = \frac{i_1}{j\omega C} + V_1$$

③ & ④

$$V_0 = \frac{V_f}{j\omega RC} \left[ 3 + \frac{4}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right] + \frac{V_f}{j\omega RC} \left[ 3 + j\omega RC + \frac{1}{j\omega RC} \right]$$

10

$$V_o = \frac{V_f}{j\omega RC} \left( \frac{6 + j\omega RC + 5}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right)$$

$$\frac{V_f}{V_o} = j\omega RC \times \left( \frac{1}{\frac{6 + j\omega RC + 5}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2}} \right) = \frac{j\omega RC}{j\omega RC} \left( \frac{1}{\frac{6}{j\omega RC} + 1 + \frac{5}{j^2 \omega^2 R^2 C^2} - \frac{1}{j^2 \omega^2 R^2 C^2}} \right)$$

equating Imag. parts,

$$\Rightarrow 0 = \frac{6}{j\omega RC} - \frac{1}{j\omega^3 R^3 C^3}$$

$$\Rightarrow 6 = \frac{1}{\omega^2 R^2 C^2} \Rightarrow \omega^2 = \frac{1}{R^2 C^2 6}$$

$$\Rightarrow \omega = \frac{1}{RC\sqrt{6}} \quad \omega = 2\pi f$$

$$\Rightarrow f = \frac{1}{2\pi RC\sqrt{6}}$$

→ LC Tuned Oscillator:

- oscillator connected with inductor & collector capacitor
- if L & C are connected || el, it is called as tank circuit.
- used for high freq applications ( $> 500\text{MHz}$ )
- It is of 3 types:-

① Tuned collector oscillator


- If the tank circuit  $\overset{\text{L & C are || el}}{\text{is connected to collector side of voltage divider bias ckt}},$  then it is called as a tuned collector oscillator

② Hartley oscillator


- If is the feedback network, considering 3 components,  $Z_1$  &  $Z_2$  are inductors &  $Z_3$  is a capacitor, then it is a Hartley oscillator

③ Colpitts oscillator

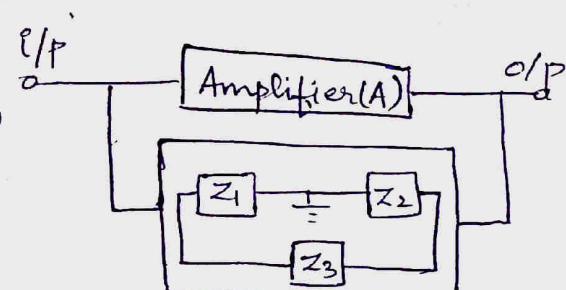
- if  $Z_1$  &  $Z_2$  are capacitors &  $Z_3$  is an inductor, then Colpitts



feedback network

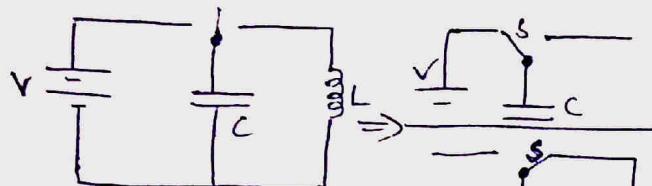

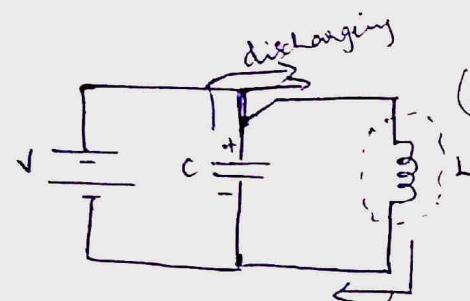during this pos<sup>n</sup> the capacitor gets fully charged




- presently cap. is full charged but when a potential diff. arises b/w two 2 plates of capacitor, charge will be stored in the form of an electrostatic field.

But now when S is connected to h side, capacitor starts discharging to inductor. So when current passes

through inductor, charge is stored as a magnetic field - also voltage of capacitor ↓s, current through inductor ↑s, magnetic field strength ↑s.

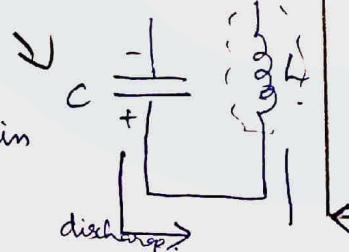Now when cap. gets fully discharged, maximum current flows through inductor, no current from capacitor. Again then current of inductor reduces, mag. field ↓s, variations can be observed in inductor i.e. a collapse happens in emf of magnetic field. The emf generated due to collapse is called back emf.



- Now the back emf which is formed in the inductor, starts flowing towards capacitor, this current flow again starts charging capacitor

- Thus capacitor again attains max. charged condition.


- The mag. field in inductor when current reaches capacitor changes to electrostatic field.

- Now when max, capacitor again starts discharging (goes on) but is opposite dir.

- Inductor gets a magnetic field again

- This goes on....


- We get an ideal output wave form as:

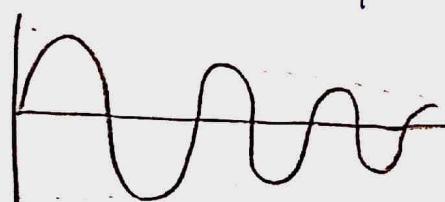

{ if an ideal inductor & capacitor was used, we get a perfect sine wave as output waveform

- Not perfect sine wave due to losses in h & C and thus after each cycle, the amplitude of the oscillations starts decreasing -

## Kelvin-Batley Oscillator

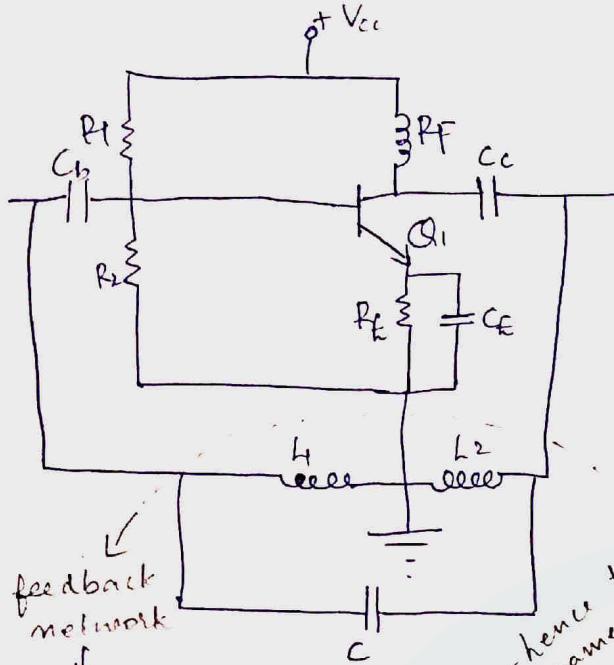

- $L_1$  &  $L_2$  in series)  $\parallel$  el with  $C$ .
- Autotransformers can be used in case of ~~inductors~~ inductors.

- used in radio receivers.
- $R_f \rightarrow$  Radio freq. coil, used to give the  $V_{cc}$  (that we apply) to collector side smoothly.
- $C_b \rightarrow$  coupling cap at base  $\Rightarrow$  allows ac to pass, dc to block.
- $R_f \rightarrow$  used for thermal stability

hence the name Hartley  $C_f \rightarrow$  bypass capacitor, it prevents the bypassing through  $R_f$  which results in large voltage drop across it & affects the oscillations <sup>(variations)</sup> of the o/p.

### Working:-

- When supply is given, capacitor  $C$  starts charging.
- When it gets fully charged, it starts discharging the charge stored in the form of electrostatic field to inductor  $L_2$  where charge is stored in the form of magnetic field.
- Now when  $C$  is fully discharged, <sup>there will be</sup> no current flow to  $L_2$  which is current value in  $L_2 \Rightarrow$  its magnetic field strength  $\rightarrow$  results in a collapse of mag. field. This variation induces an emf i.e back emf.
- This back emf again starts charging capacitor, mag. field in  $L_2$  gets converted to electro <sup>static</sup> field again  $\Rightarrow$  ~~no~~ oscillations are produced across  $L_2$ . These oscillations & o/p are in phase.
- These osc. from  $L_2$  transferred to  $L_1$  but undergoes a phase shift of  $180^\circ$  (due to the earthing provided b/w  $L_1$  &  $L_2$ )
- This is given to the transistor where a phase shift of  $180^\circ$  again happens. (total  $360^\circ$  phase shift)
  - i.e cond<sup>n</sup> for an amplifier to work as an oscillator is satisfied in o/p

$$f = \frac{1}{2\pi L_{eq}C}$$

$$L_{eq} = L_1 + L_2 + 2M$$

## Applications :-

- used to produce a sine wave of desired freq.
- mostly used as a local oscillator in radio receivers
- used as R.F oscillator.


## Advantages :-

- Instead of using large transformer, a single coil can be used as an auto-transformer.
- Freq. can be varied by employing either a variable capacitor or a variable inductor.
- Less number of components are sufficient.
- The amplitude of o/p remains constant over a fixed freq. range.

## Disadvantages :-

- It cannot be a low freq. oscillator
- Harmonic distortions are present.

## ② Colpitts Oscillator

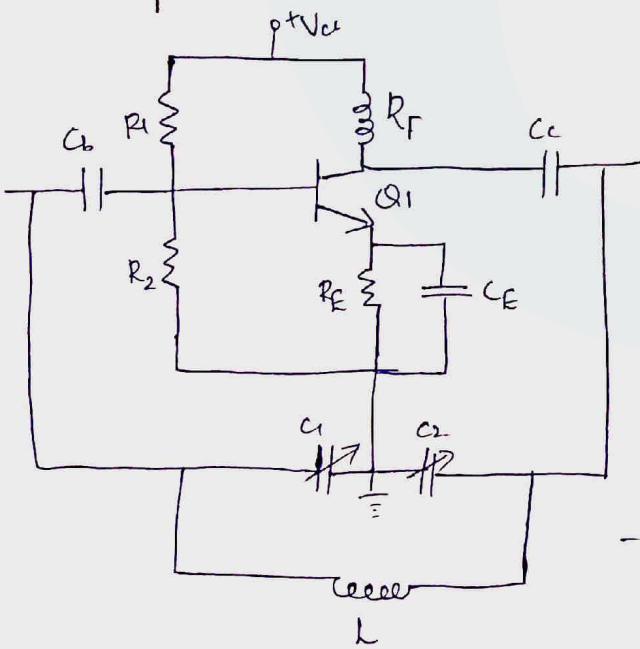

- diff. from Hartley oscillator is that  $C_1$  &  $C_2$  are placed here instead of inductors  $L$  instead of  $C$ .
- Colpitts oscillator removes or clears the 2 disadvantages of Hartley

## Working :-

- when supply is given,  $C_1$  &  $C_2$  gets charged  $\Rightarrow$  when fully charged  $\Rightarrow$

gets discharged to inductor  $\Rightarrow$  gets stored in the form of mag field  $\Rightarrow$  when mag field reaches max.  $\Rightarrow$  its strength starts  $\downarrow$   $\Rightarrow$  collapse  $\Rightarrow$  emf generated  $\Rightarrow$  earthing + transistor  $\Rightarrow$  works as an (back emf)  $180^\circ$   $12$   $180^\circ$   $\rightarrow$  phase shift oscillator

$$C_P = \frac{1}{C_1} + \frac{1}{C_2}$$

$$2\pi \sqrt{LC_P}$$

Advantages :-

- generate sinusoidal signals of very high freq.
- withstand high & low temp.
- frequency stability is high
- freq. can be varied by using both variable capacitors
- less no. of components are sufficient
- Amplitude of o/p remains const. over a fixed freq. range.


Applications:-

- can be used as high freq. sinewave generator
- " temp. sensor with some associated circuitry
- used as local oscillator in radio receivers.
- " R.F. oscillator
- used in mobile applications.

### → Crystal Oscillator

- when Hartley & Colpitts oscillators are used for a long time, its freq. stability of oscillator gets affected & results in some variations (power supply var./load var./temp var.), so in order to avoid this Crystal oscillator is used.
- crystal - hexagonal in shape 
- ~~It has~~ a property called piezoelectric property - if a mechanical stress is given to any one side/phase, a potential diff is developed across its opposite side
- If crystal is used as an oscillator, inverse piezoelectric effect is produced.

Ktu Q bank  
inverse piezoelectric effect: If we apply a potential diff., mechanical stress is developed on the opposite side which produces vibrations  $\Rightarrow$  changes into oscillations.

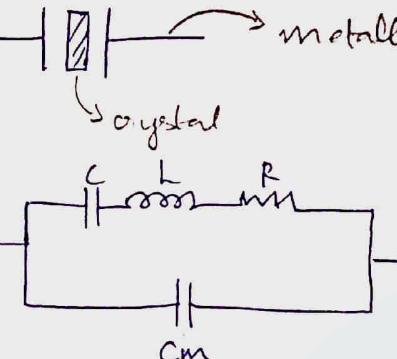- Crystals are Rochelle salt, Tourmaline, Quartz (mostly used)
-  similar to capacitor
  - $\rightarrow$  naturally available
  - inexpensive
  - mech. strength

- When ac voltage is applied across crystal, it starts vibrating i.e. at supply freq. that we apply, oscillator vibrates.
- If supply freq. = <sup>natural</sup> freq. of crystal or if they matches  $\Rightarrow$  it reaches its resonance condition i.e. max. vibration is obtained in the crystal  $\Rightarrow$  oscillations are produced.


Two cond<sup>n</sup>  $\rightarrow$  - crystal vibrates - series resonant freq.  $f_s$   
 - do not vibrate - parallel resonant freq. cond<sup>n</sup>,  $f_p$

$$\left\{ f_p = \frac{1}{2\pi \sqrt{L \left( \frac{C_m + C}{C_m} \right)}} \right\}, \left\{ f_s = \frac{1}{2\pi \sqrt{L C}} \right\}$$

(impedance  $\uparrow$ , feedback  $\downarrow$ )

- When crystal is used as an oscillator, it is used in both low impd. & high impd. mode
  - $\downarrow$  Series res.
  - $\downarrow$  Parallel res.


→ Series Resonant Mode :-

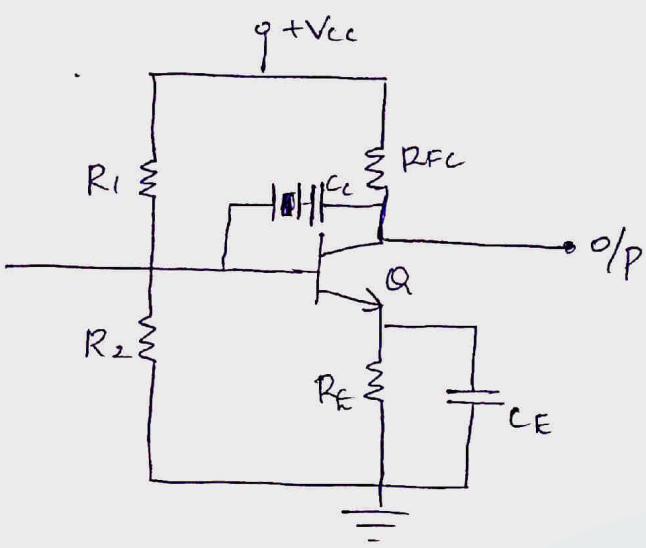

- $R_E$  for thermal stability
- $C_E$  - bypass cap.
- crystal is connected to  $C_C$  (comp. cap) & feedback is given (conn. in series)
- Series resonant freq. is obtained.

$$\left\{ f_S = \frac{1}{2\pi L_C} \right\}$$

→ Parallel Resonant Mode :-

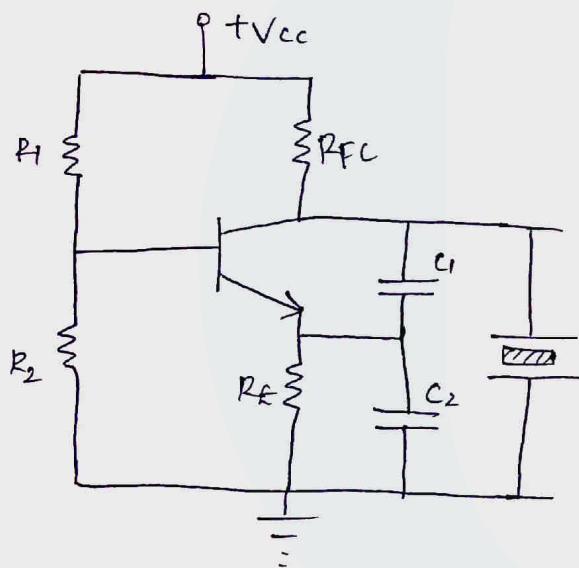

- here capacitive voltage divider  $C_1$  &  $C_2$  are used instead of  $C_E$
- crystal is connected // el to these
- thus //el resonant freq mode

$$\left\{ f_P = \frac{1}{2\pi\sqrt{L\left(\frac{C_m \cdot C}{C_m + C}\right)}} \right\}$$


• When compared to other oscillators, crystal oscillator will not affect frequency stability.

- Operating range : 40 kHz - 100 MHz

- Applications : Communication system

Tracking system

Video Gaming

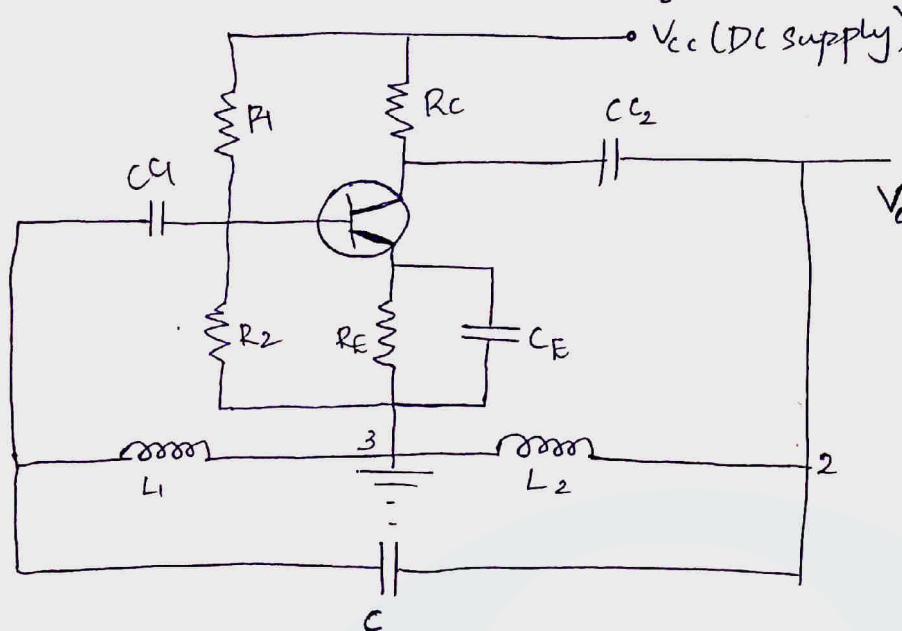Hartley Oscillator (Frequency derivation)

-  $R_1, R_2 \& R_E$  provides necessary DC biasing to the transistor

- $Z_1 \& Z_2 \rightarrow$  ind. reactance
- $Z_3 \rightarrow$  cap. reactance

$$Z_1 = j\omega L_1 + j\omega M$$

$$Z_2 = j\omega L_2 + j\omega M$$

$$Z_3 = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

$$\left\{ h_{ie} [Z_1 + Z_2 + Z_3] + Z_1 Z_2 (1 + h_{fe}) + Z_1 Z_3 = 0 \right\} - \text{Generalised eqn of oscillator}$$

$$\begin{aligned} \text{Subs. } &\Rightarrow h_{ie} \left[ j\omega h + j\omega M + j\omega L_2 + j\omega M - \frac{j}{\omega C} \right] + (j\omega L_1 + j\omega M)(j\omega L_2 + j\omega M) \times \\ &\quad (1 + h_{fe}) \\ &\quad + (j\omega L_1 + j\omega M) \left( -\frac{j}{\omega C} \right) = 0 \end{aligned}$$

$$\begin{aligned} &\Rightarrow \omega_j h_{ie} \left[ L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right] - \omega^2 (L_1 + M)(L_2 + M)(1 + h_{fe}) \\ &\quad + \left( \frac{L_1 + M}{C} \right) = 0 \end{aligned}$$

To find freq, equate imaginary part = 0

$$\omega_j h_{ie} \left[ L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right] = 0$$

$$\Rightarrow L_1 + L_2 + 2M = \frac{1}{\omega^2 C}$$


$$\omega = 2\pi f$$

$$\omega = \frac{1}{\sqrt{(L_1 + L_2 + 2M) \times C}}$$

(equate  
 $L_1 + L_2 + 2M = L$ )

$$\Rightarrow f = \frac{1}{2\pi\sqrt{(L_1 + L_2 + 2M)C}} \Rightarrow f = \frac{1}{2\pi\sqrt{LC}} //$$

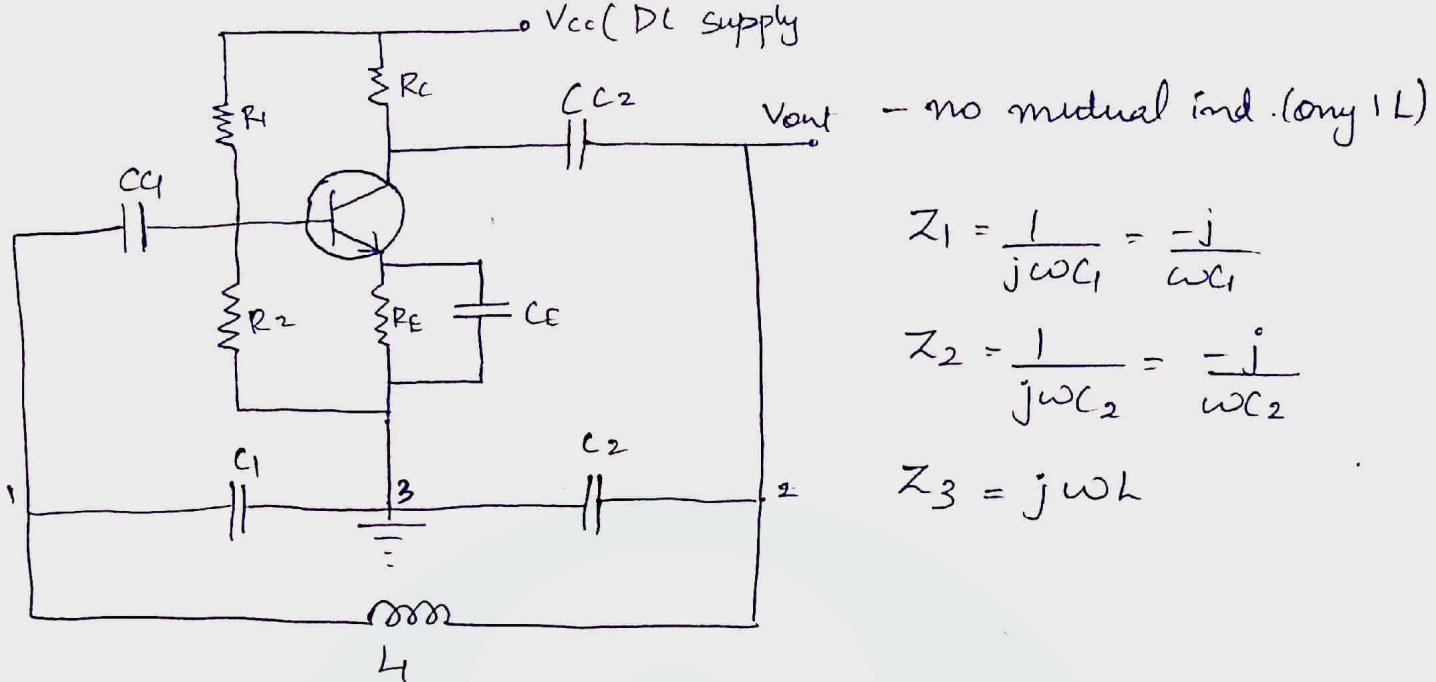Ktu Q bank  
Colpitts Oscillator (Frequency derivation)



$$Z_1 = \frac{1}{j\omega C_1} = \frac{-j}{\omega C_1}$$

$$Z_2 = \frac{1}{j\omega C_2} = \frac{-j}{\omega C_2}$$

$$Z_3 = j\omega L$$

$$h_{ie} [Z_1 + Z_2 + Z_3] + Z_1 Z_2 (1 + h_{fe}) + Z_1 Z_3 = 0$$

$$\Rightarrow h_{ie} \left[ \frac{-j}{\omega C_1} - \frac{j}{\omega C_2} + j\omega L \right] + (1 + h_{fe}) \left( \frac{-j}{\omega C_1} \right) \left( \frac{-j}{\omega C_2} \right) + \left( \frac{-j}{\omega C_1} \right) \left( j\omega L \right) = 0$$

$$\Rightarrow \frac{h_{ie} \cdot j}{\omega} \left[ \frac{-1}{C_1} - \frac{1}{C_2} + \omega^2 L \right] + (1 + h_{fe}) \left( \frac{-1}{\omega^2 C_1 C_2} \right) + \frac{L}{C_1} = 0$$

eq. imaginary part = 0

$$\text{i.e. } \frac{h_{ie}}{\omega} \left[ \frac{-1}{C_1} - \frac{1}{C_2} + \omega^2 L \right] = 0$$

$$\Rightarrow \omega^2 L = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\Rightarrow \omega = \sqrt{\frac{1}{L} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)}$$

$$\omega = 2\pi f \Rightarrow f = \frac{1}{2\pi} \sqrt{\frac{1}{L} \left( \frac{1}{C_1} + \frac{1}{C_2} \right)}$$

— x —